



Sheet (1) - Solution

1. (a) What are the connections to a basic OP-AMP?

solution :

Inverting input, noninverting input, output, positive and negative supply voltages

(b) Compare a practical OP-AMP to an ideal OP-AMP and describe some of the characteristics of a practical OP-AMP?

Solution

Practical op-amp: High open-loop gain, high input impedance, low output impedance, and high CMRR.

Ideal op-amp: Infinite open-loop gain, infinite input impedance, zero output impedance, and infinite CMRR.

A practical op-amp has very high input impedance, very low output impedance, and very high voltage gain.

(c) List the amplifier stages in a typical OP-AMP?

solution :

Differential amplifier, voltage amplifier, and push-pull amplifier

(d) What does a differential amplifier amplify?

solution :

The difference between its two input voltages

(e) Distinguish between differential and single – ended inputs?

solution :

Differential input is between two input terminals. Single-ended input is from one input terminal to ground (with other input grounded).

(f) For a given value of open loop gain, does a higher CMRR result in a higher or lower Common Mode Gain?

solution :

A higher CMRR results in a lower common-mode gain.

(g) Two – IC OP-AMP are available to you their characteristics are listed below. Choose the one you think is more desirable.

OP-AMP 1 : $Z_{in} = 5M\Omega$, $Z_{out} = 100\Omega$, $A_{OL}=100,000$.

OP-AMP 2 : $Z_{in} = 10M\Omega$, $Z_{out} = 75\Omega$, $A_{OL}=150,000$.

solution :

Op amp 2 is more desirable because it has a higher input impedance, a lower output impedance, and a higher open-loop gain.

2. Identify the type of input mode for each OP-AMP in the Figure 1.

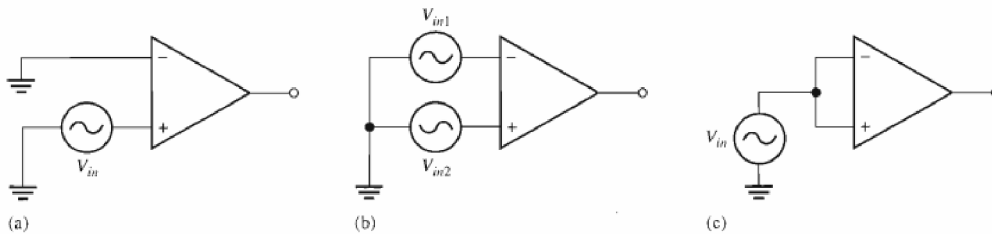


Figure (1)

solution :

- (a) Single-ended input
- (b) Differential input
- (c) Common-mode

3. The open loop gain of a certain OP-AMP is 175,000. Its common Mode gain is 0.18. Determine CMRR in Decibel.

solution :

$$CMRR(dB) = 20 \log\left(\frac{A_{ol}}{A_{cm}}\right) = 20 \log\left(\frac{175,000}{0.18}\right) = 120 \text{ dB}$$

4. Determine the bias current I_{Bias} , given that the input currents to an OP-AMP are $8.3\mu A$ and $7.9 \mu A$ and then calculate the input offset current.

solution :

$$I_{BIAS} = \frac{8.3 \mu A + 7.9 \mu A}{2} = 8.1 \mu A$$

Input bias current is the average of the two input currents. Input offset current is the difference between the two input currents.

$$I_{OS} = |8.3 \mu A - 7.9 \mu A| = 400 \text{ nA}$$

5. How long does it take the output voltage to go from -10V to +10V, if the slew rate is $0.5V/\mu s$.

solution :

$$\Delta t = \frac{\Delta V_{out}}{\text{slew rate}} = \frac{20 \text{ V}}{0.5 \text{ V}/\mu s} = 40 \mu s$$