



Sheet (3)

1. A certain low-pass filter has critical frequency of 800Hz. What is its bandwidth?

$$BW = f_c = \mathbf{800 \text{ Hz}}$$

2. A single pole high-pass filter has a frequency-selective circuit with $R=2.2\text{K}\Omega$ and $C=0.0015\mu\text{F}$. What is the critical frequency?

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(2.2 \text{ k}\Omega)(0.0015 \mu\text{F})} = \mathbf{48.2 \text{ Hz}}$$

3. What is the roll-off rate of the filter described in problem 3?

The roll-off is **20 dB/decade** because this is a single-pole filter

4. What is the Bandwidth of a band-pass filter whose critical frequencies are 3.2 KHz and 3.9 KHz? What is the Q of this filter?

$$BW = f_{ch} - f_{cl} = 3.9 \text{ kHz} - 3.2 \text{ kHz} = 0.7 \text{ kHz} = \mathbf{700 \text{ Hz}}$$
$$f_0 = \sqrt{f_{cl} f_{ch}} = \sqrt{(3.2 \text{ kHz})(3.9 \text{ kHz})} = 3.53 \text{ kHz}$$
$$Q = \frac{f_0}{BW} = \frac{3.53 \text{ kHz}}{700 \text{ Hz}} = \mathbf{5.04}$$

5. What is the center frequency of a filter with a Q of 15 and a bandwidth of 1 KHz?

$$Q = \frac{f_0}{BW}$$
$$f_0 = Q(BW) = 15(1 \text{ kHz}) = \mathbf{15 \text{ kHz}}$$

6. What is the damping factor in each active filter shown in figure (1)? Which filter optimized for a Butterworth response characteristic?

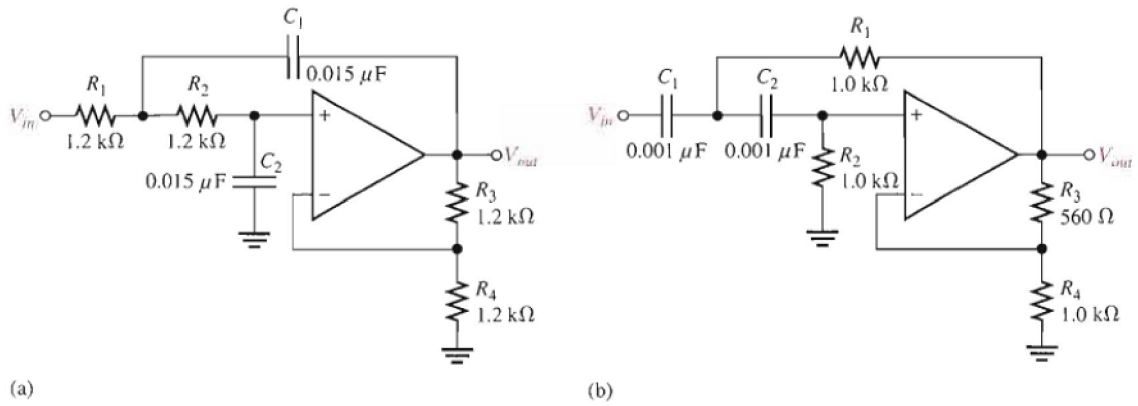


Figure (1)

(a) 2nd order, 1 stage

$$DF = 2 - \frac{R_3}{R_4} = 2 - \frac{1.2 \text{ k}\Omega}{1.2 \text{ k}\Omega} = 2 - 1 = 1 \quad \text{Not Butterworth}$$

(b) 2nd order, 1 stage

$$DF = 2 - \frac{R_3}{R_4} = 2 - \frac{560 \Omega}{1.0 \text{ k}\Omega} = 2 - 0.56 = 1.44 \quad \text{Approximately Butterworth}$$

7. For the filter in figure (1-a) that do not have a Butterworth response, specify the necessary changes to convert it to Butterworth response.

From Table 15-1 in the textbook, the damping factor must be 1.414; therefore

$$\frac{R_3}{R_4} = 0.586$$

$$R_3 = 0.586R_4 = 0.586(1.2 \text{ k}\Omega) = 703 \Omega$$

Nearest standard value: 720 Ω

8. For the figure (2) shown:

- (a) Is the four-pole filter approximately optimized for a Butterworth response? What is the roll-off rate?

High Pass

1st stage:

$$DF = 2 - \frac{R_3}{R_4} = 2 - \frac{1.0 \text{ k}\Omega}{6.8 \text{ k}\Omega} = 1.85$$

2nd stage:

$$DF = 2 - \frac{R_7}{R_8} = 2 - \frac{6.8 \text{ k}\Omega}{5.6 \text{ k}\Omega} = 0.786$$

From Table 15-1 in the textbook:

1st stage $DF = 1.848$ and 2nd stage $DF = 0.765$

Therefore, this filter is **approximately Butterworth**.

Roll-off rate = **80 dB/decade**

- (b) Without changing the response curve, adjust the component values in the filter to make it an equal-value filter. Select $C=0.22\mu\text{F}$ for both stages.

$$R = R_1 = R_2 = R_5 = R_6 \text{ and } C = C_1 = C_2 = C_3 = C_4$$

Let $C = 0.22 \mu\text{F}$ (for both stages).

$$f_c = \frac{1}{2\pi\sqrt{R^2 C^2}} = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_c C} = \frac{1}{2\pi(190 \text{ Hz})(0.22 \mu\text{F})} = 3.81 \text{ k}\Omega$$

Choose $R = 3.9 \text{ k}\Omega$ (for both stages)


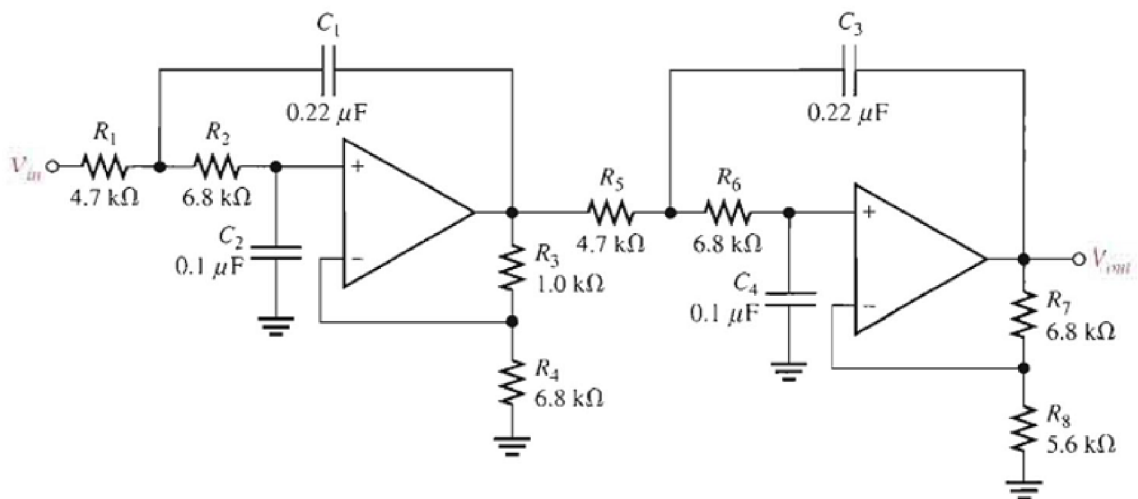


Figure (2)

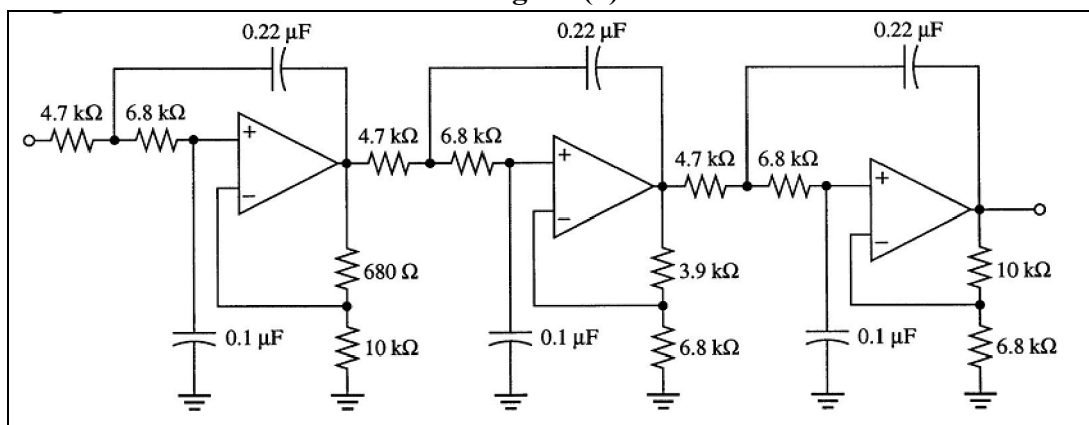

9. For the filter shown in figure (3):
- How would you increase the critical frequency?
 - How would you increase the gain?

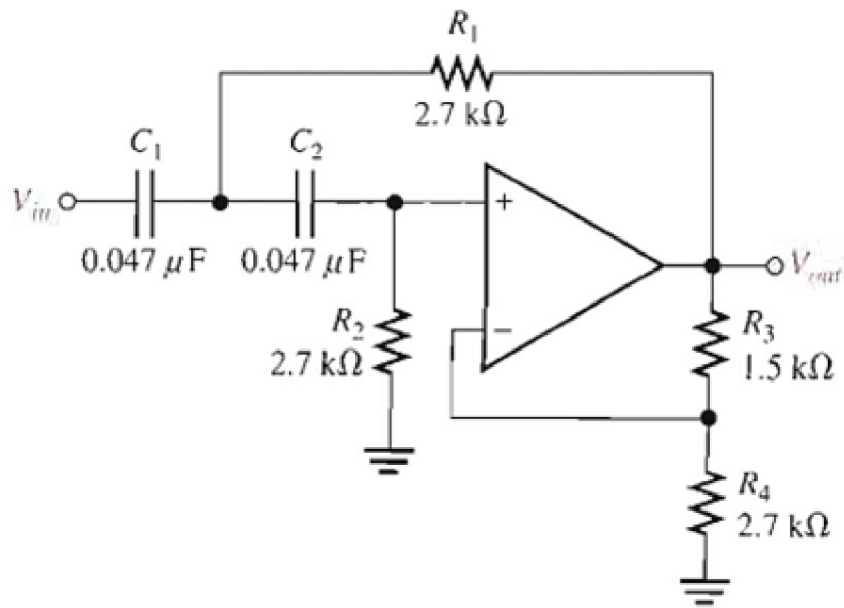


Figure (3)

- Decrease R_1 and R_2 or C_1 and C_2 .
- Increase R_3 or decrease R_4 .

10. Optimize the state variable filter in figure (4) for $Q=50$. What bandwidth is achieved?

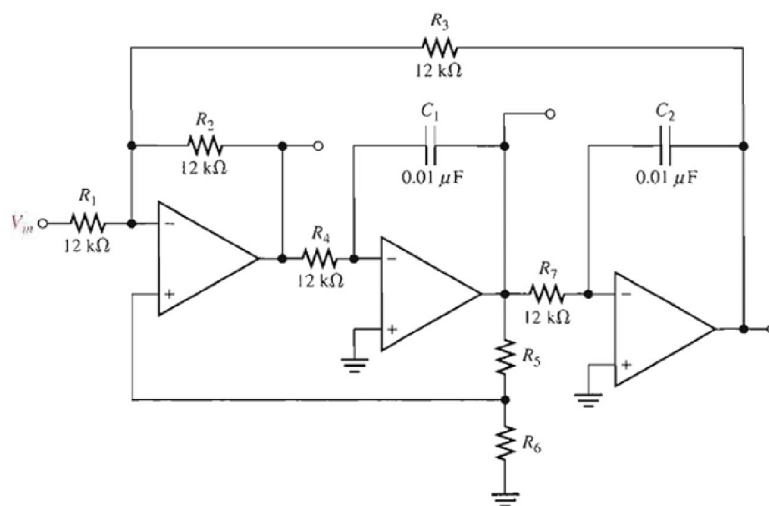


Figure (4)

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right)$$

Select $R_6 = 1 \text{ k}\Omega$.

$$Q = \frac{R_5}{3R_6} + \frac{1}{3} = \frac{R_5 + R_6}{3R_6}$$


$$3R_6Q = R_5 + R_6$$

$$R_5 = 3R_6Q - R_6 = 3(1.0 \text{ k}\Omega)(50) - 10 \text{ k}\Omega = 150 \text{ k}\Omega - 10 \text{ k}\Omega = 140 \text{ k}\Omega$$

$$f_0 = \frac{1}{2\pi(12 \text{ k}\Omega)(0.01 \mu\text{F})} = 1.33 \text{ kHz}$$

$$BW = \frac{f_0}{Q} = \frac{1.33 \text{ kHz}}{50} = 26.6 \text{ Hz}$$

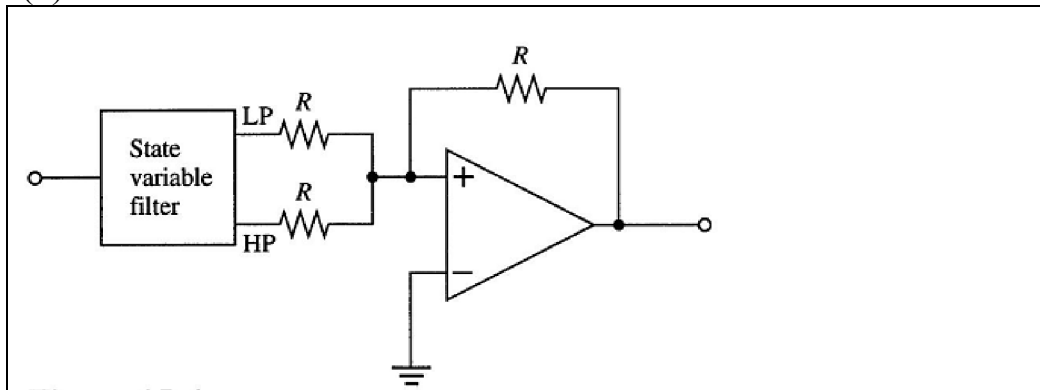11. Show how to make a notch filter using the basic circuit in figure (4).



12. Modify the band-stop filter in problem 11 for a center frequency of 120Hz.




$$f_0 = f_c = \frac{1}{2\pi RC}$$

Let C remain $0.01 \mu\text{F}$.

$$R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi(120 \text{ Hz})(0.01 \mu\text{F})} = 133 \text{ k}\Omega$$

Change R in the integrators from $12 \text{ k}\Omega$ to $133 \text{ k}\Omega$.

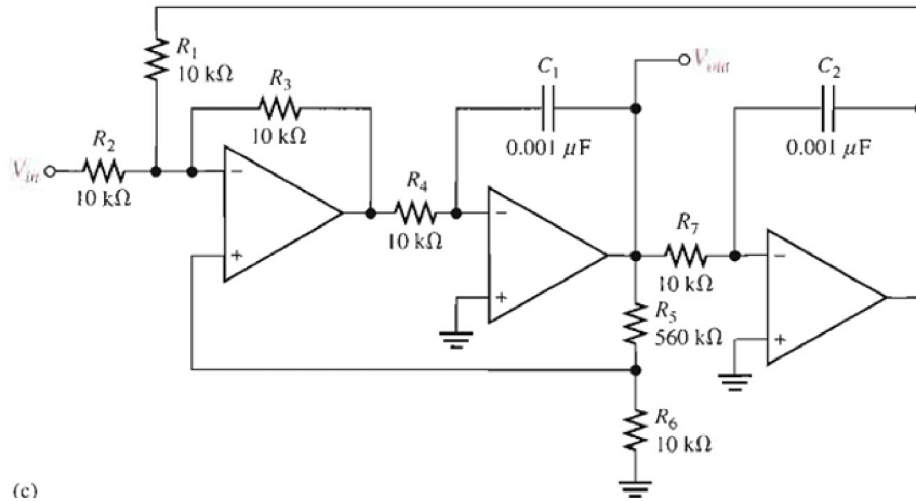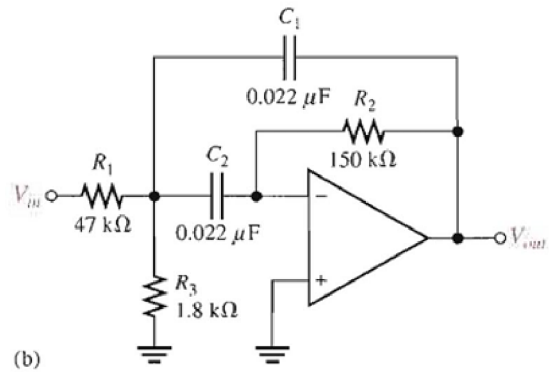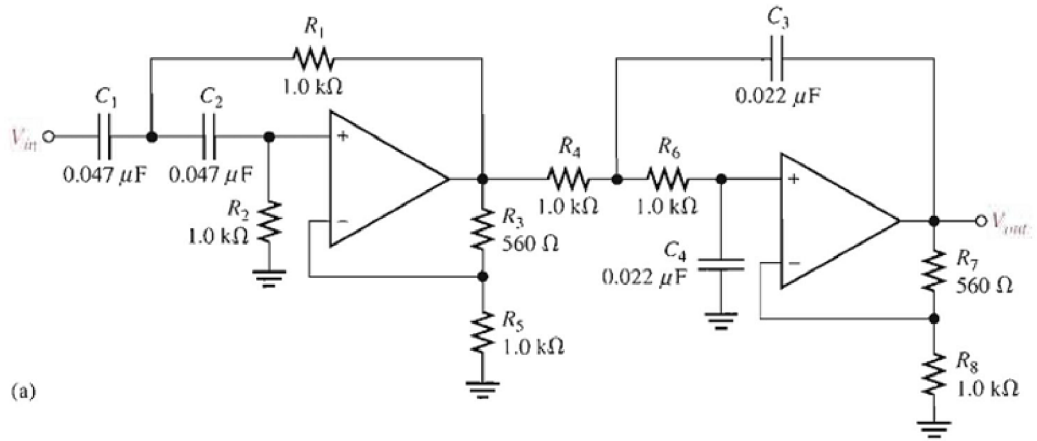13. Determine the center frequency and bandwidth for each filter in figure (5).



(a) 1st stage:

$$f_{c1} = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.0 \text{ k}\Omega)(0.047 \text{ }\mu\text{F})} = 3.39 \text{ kHz}$$

2nd stage:

$$f_{c2} = \frac{1}{2\pi RC} = \frac{1}{2\pi(1.0 \text{ k}\Omega)(0.022 \text{ }\mu\text{F})} = 7.23 \text{ kHz}$$

$$f_0 = \sqrt{f_{c1}f_{c2}} = \sqrt{(3.39 \text{ kHz})(7.23 \text{ kHz})} = 4.95 \text{ kHz}$$

$$BW = 7.23 \text{ kHz} - 3.39 \text{ Hz} = 3.84 \text{ kHz}$$

$$(b) f_0 = \frac{1}{2\pi C} \sqrt{\frac{R_1 + R_2}{R_1 R_2 R_3}} = \frac{1}{2\pi(0.022 \text{ }\mu\text{F})} \sqrt{\frac{47 \text{ k}\Omega + 1.8 \text{ k}\Omega}{(47 \text{ k}\Omega)(1.8 \text{ k}\Omega)(150 \text{ k}\Omega)}} = 449 \text{ Hz}$$

$$Q = \pi f_0 C R_3 = \pi(449 \text{ Hz})(0.022 \text{ }\mu\text{F})(150 \text{ k}\Omega) = 4.66$$

$$BW = \frac{f_0}{Q} = \frac{449 \text{ Hz}}{4.66} = 96.4 \text{ Hz}$$

(c) For each integrator:

$$f_c = \frac{1}{2\pi RC} = \frac{1}{2\pi(10 \text{ k}\Omega)(0.001 \text{ }\mu\text{F})} = 15.9 \text{ kHz}$$

$$f_0 = f_c = 15.9 \text{ kHz}$$

$$Q = \frac{1}{3} \left(\frac{R_5}{R_6} + 1 \right) = \frac{1}{3} \left(\frac{560 \text{ k}\Omega}{10 \text{ k}\Omega} + 1 \right) = \frac{1}{3} (56 + 1) = 19$$

$$BW = \frac{f_0}{Q} = \frac{15.9 \text{ kHz}}{19} = 838 \text{ Hz}$$

Good Luck