



Sheet (5) - solution

1. Why is the phase shift through the RC feedback circuit in a phase shift oscillator 180° ?

The three RC circuits contribute a total of 180° , and the inverting amplifier contributes 180° for a total of 360° around the loop.

2. What is the basic difference between the Colpitts and the Hartley oscillators?

Colpitts uses a capacitive voltage divider in the feedback circuit; Hartley uses an inductive voltage divider.

3. What is the advantage of a FET amplifier in a colpitts or Hartley oscillator?

The higher FET input impedance has less loading effect on the resonant feedback circuit.

4. How can you distinguish a Colpitts oscillator from a Clapp oscillator?

A Clapp has an additional capacitor in series with the inductor in the feedback circuit.

5. What value of R_f is required in Figure 1? What is f_r ?

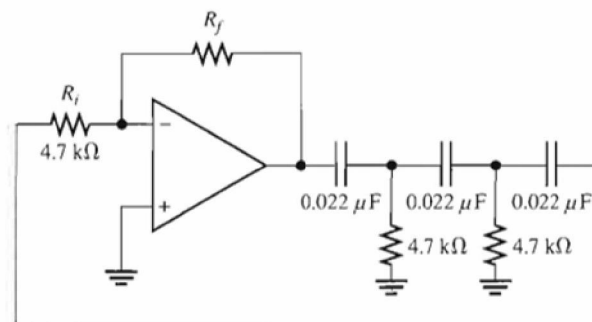


Figure 1

$$B = \frac{1}{29}$$

$$A_{cl} = \frac{1}{B} = 29$$

$$A_{cl} = \frac{R_f}{R_i}$$

$$R_f = A_{cl}R_i = 29(4.7 \text{ k}\Omega) = 136 \text{ k}\Omega$$

$$f_r = \frac{1}{2\pi\sqrt{6((4.7 \text{ k}\Omega)(0.02 \mu\text{F}))}} = 691 \text{ Hz}$$

6. Calculate the frequency of oscillation for each circuit in figure 2 and identify the type of oscillator. Assume $Q > 10$ in each case.

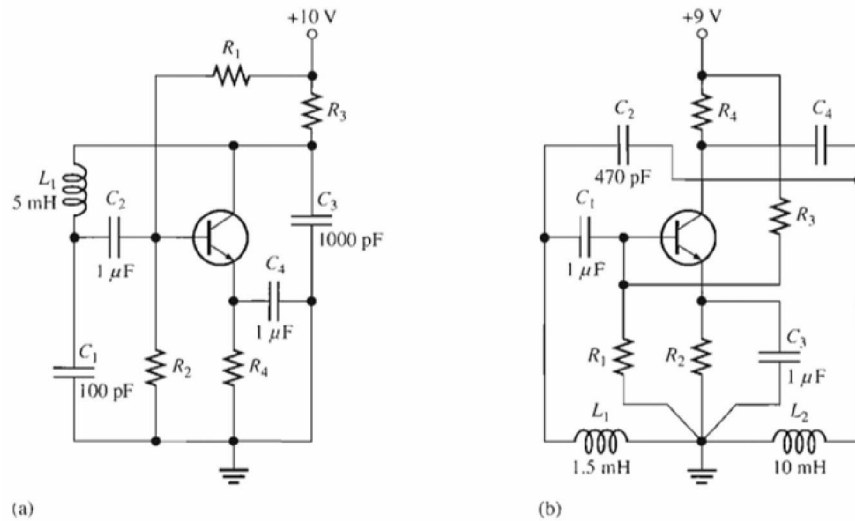


Figure 2

(a) *Colpitts*: C_1 and C_3 are the feedback capacitors.

$$f_r = \frac{1}{2\pi\sqrt{L_1 C_T}}$$

$$C_T = \frac{C_1 C_3}{C_1 + C_3} = \frac{(100 \mu\text{F})(1000 \text{ pF})}{1100 \text{ pF}} = 90.9 \text{ pF}$$

$$f_r = \frac{1}{2\pi\sqrt{(5 \text{ mH})(90.9 \text{ pF})}} = \mathbf{236 \text{ kHz}}$$

(b) *Hartley*:

$$f_r = \frac{1}{2\pi\sqrt{L_T C_2}}$$

$$L_T = L_1 + L_2 = 1.5 \text{ mH} + 10 \text{ mH} = 11.5 \text{ mH}$$

$$f_r = \frac{1}{2\pi\sqrt{(11.5 \text{ mH})(470 \text{ pF})}} = \mathbf{68.5 \text{ kHz}}$$

7. Determine the gain of amplifier stage must be in figure 3 in order to have sustained oscillation.

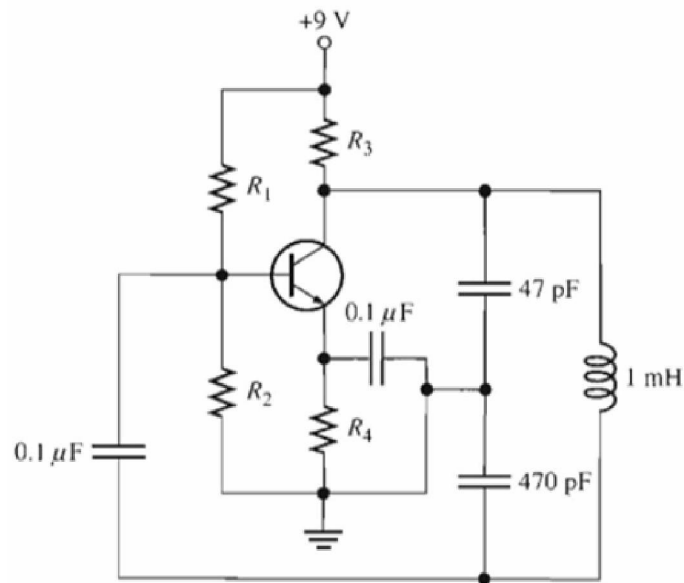


Figure 3

$$B = \frac{47 \text{ pF}}{470 \text{ pF}} = 0.1$$

The condition for sustained oscillation is

$$A_v = \frac{1}{B} = \frac{1}{0.1} = 10$$

Good Luck