



## Sheet (5) - solution

### Oscillators – part 2

1. Why is the phase shift through the RC feedback circuit in a phase shift oscillator  $180^\circ$ ?
2. What is the basic difference between the Colpitts and the Hartley oscillators?
3. What is the advantage of a FET amplifier in a colpitts or Hartley oscillator?
4. How can you distinguish a Colpitts oscillator from a Clapp oscillator?
5. What value of  $R_f$  is required in Figure 1? What is  $f_r$ ?


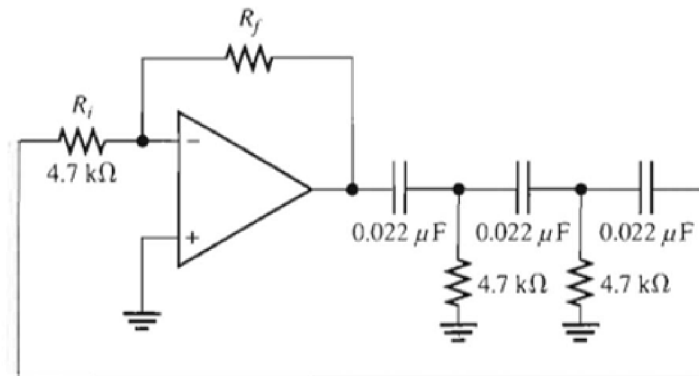



Figure 1

6. Calculate the frequency of oscillation for each circuit in figure 2 and identify the type of oscillator. Assume  $Q > 10$  in each case.

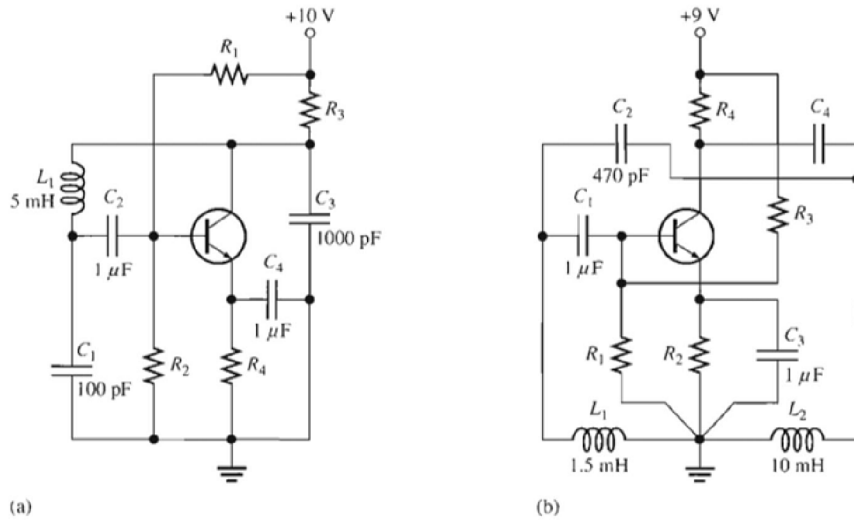

**Figure 2**

7. Determine the gain of amplifier stage must be in figure 3 in order to have sustained oscillation.

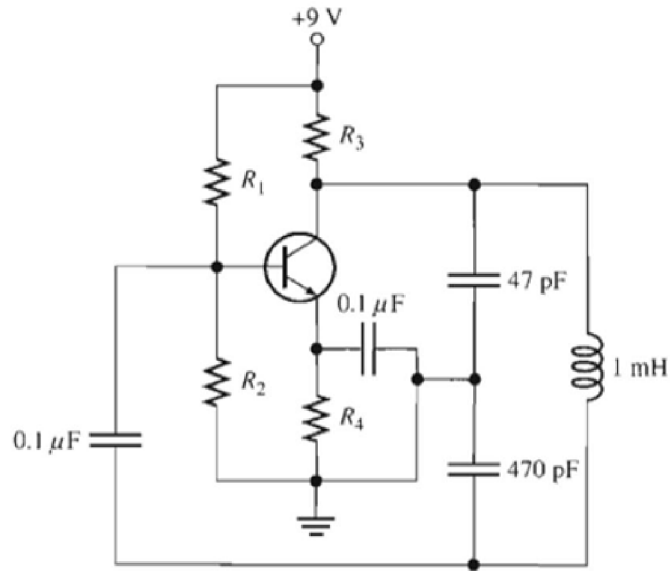

**Figure 3**

*Good Luck*