



Sheet (6)-solution

Oscillators – part 3

1. What is a VCO, and basically, what does it do?

A voltage-controlled oscillator exhibits a frequency that can be varied with a dc control voltage.

2. Upon what principle does a relaxation oscillator operate?

The basis of a relaxation oscillator is the charging and discharging of a capacitor.

3. What type of signal does the circuit in figure 1 produce? Determine the frequency of the output.

Triangular waveform.

$$f = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right) = \frac{1}{4(22 \text{ k}\Omega)(0.022 \text{ }\mu\text{F})} \left(\frac{56 \text{ k}\Omega}{18 \text{ k}\Omega} \right) = 1.61 \text{ kHz}$$

4. Show how to change the frequency of oscillation in figure 1 to 10 KHz.

Change f to 10 kHz by changing R_1 :

$$f = \frac{1}{4R_1C} \left(\frac{R_2}{R_3} \right)$$

$$R = \frac{1}{4fC} \left(\frac{R_2}{R_3} \right) = \frac{1}{4(10 \text{ kHz})(0.022 \text{ }\mu\text{F})} \left(\frac{56 \text{ k}\Omega}{18 \text{ k}\Omega} \right) = 3.54 \text{ k}\Omega$$

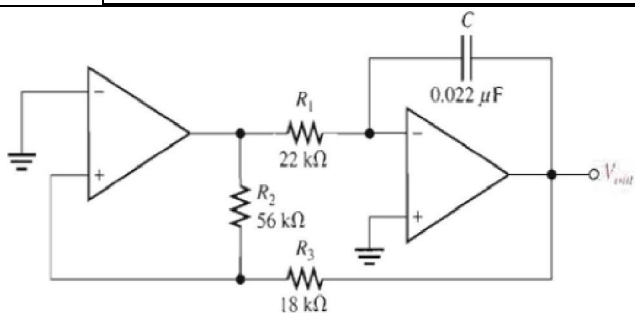


Figure 1

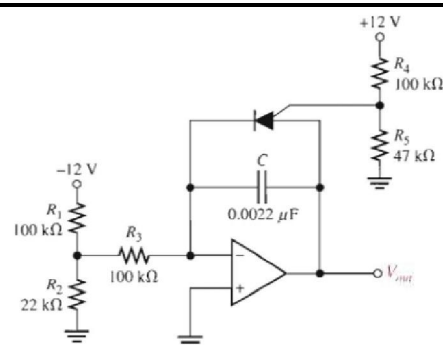


Figure 2

5. Determine the amplitude and frequency of the output voltage in figure 2. Use 1V as the forward PUT voltage.

$$T = \frac{V_p - V_F}{\left(\frac{|V_{IN}|}{RC}\right)}$$

$$V_p = \left(\frac{R_5}{R_4 + R_5}\right)12 \text{ V} = \left(\frac{47 \text{ k}\Omega}{147 \text{ k}\Omega}\right)12 \text{ V} = 3.84 \text{ V}$$


PUT triggers at about $+3.84 \text{ V} + 0.7 \text{ V} = 4.54 \text{ V}$
 Amplitude = $+4.54 \text{ V} - 1 \text{ V} = 3.54 \text{ V}$

$$V_{IN} = \left(\frac{R_2}{R_1 + R_2}\right)(-12 \text{ V}) = \left(\frac{22 \text{ k}\Omega}{122 \text{ k}\Omega}\right)(-12 \text{ V}) = -2.16 \text{ V}$$

$$T = \frac{4.54 \text{ V} - 1 \text{ V}}{\left(\frac{2.16 \text{ V}}{(100 \text{ k}\Omega)(0.002 \mu\text{F})}\right)} = 328 \mu\text{s}$$

$$f = \frac{1}{T} = \frac{1}{328 \mu\text{s}} = 3.05 \text{ kHz}$$

See Figure 16-1.

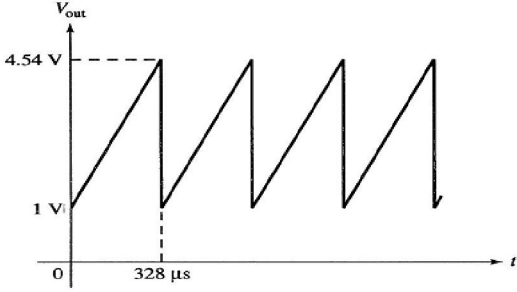

6. Modify the sawtooth generator in figure 2 so that its peak-to-peak is 4V.

$$V_G = 5 \text{ V. Assume } V_{AK} = 1 \text{ V.}$$

$$V_G = \left(\frac{R_5}{R_4 + R_5}\right)12 \text{ V}$$

Change R_4 to get $V_G = 5 \text{ V}$.
 $5 \text{ V}(R_4 + 47 \text{ k}\Omega) = (47 \text{ k}\Omega)12 \text{ V}$
 $R_4(5 \text{ V}) = (47 \text{ k}\Omega)12 \text{ V} - (47 \text{ k}\Omega)5 \text{ V}$
 $R_4 = \frac{(12 \text{ V} - 5 \text{ V})47 \text{ k}\Omega}{5 \text{ V}} = 65.8 \text{ k}\Omega$

7. A certain Sawtooth generator has the following parameters values: $V_{IN}=3\text{V}$, $R=4.7\text{K}\Omega$, $C=0.001\mu\text{F}$.determine its peak-to-peak output voltage if the period is $10\mu\text{s}$.

$$T = \frac{V_p - V_F}{\left(\frac{V_{IN}}{RC}\right)}$$

$$V_p = \left(\frac{V_{IN}}{RC}\right)T + V_F = \left(\frac{3 \text{ V}}{(4.7 \text{ k}\Omega)(0.001 \mu\text{F})}\right)10 \mu\text{s} + 1 \text{ V} = 7.38 \text{ V}$$

$$V_{pp(out)} = V_p - V_F = 7.38 \text{ V} - 1 \text{ V} = 6.38 \text{ V}$$