



Sheet (2)

1. A non-inverting amplifier has R_i of $1\text{K}\Omega$ and R_f of $100\text{K}\Omega$. Determine V_f and B if $V_{out} = 5\text{V}$.
2. For the non-inverting amplifier shown in figure (1). Determine $A_{cl(NI)}$, V_{out} , and V_f .

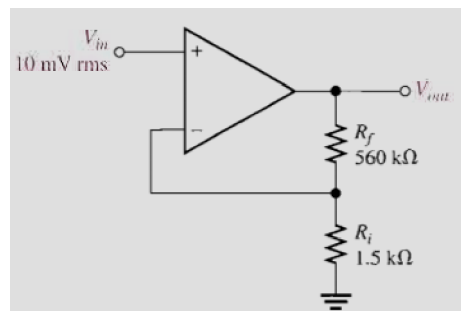


Figure (1)

3. Calculate the closed loop gain for non-inverting amplifier has $R_i=4.7\text{K}\Omega$, $R_f=47\text{K}\Omega$, and $A_{OL}=150,000$.
4. For an inverting amplifier with closed loop gain of -300 , and R_1 of $10\text{K}\Omega$, calculate the value required to R_f to satisfy this gain.
5. Determine the approximate values for I_{in} , I_f , V_{out} , A_{cl} in figure (2).

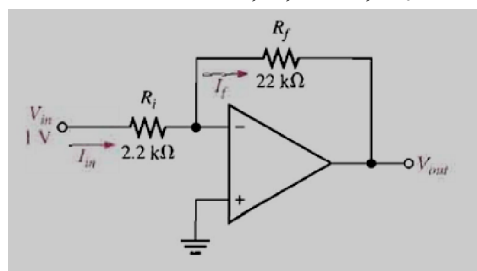


Figure (2)

6. Determine the input and output impedances for the following amplifiers of fig.3

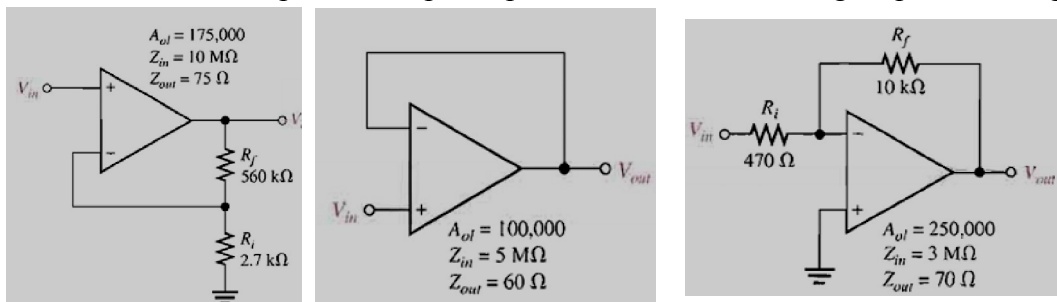


Figure (3)



7. A voltage follower is driven by a voltage source resistance of 75Ω .
 - (a) What value of compensating resistor is required for bias current and where should the resistor be placed?
 - (b) If the two input currents after compensation are $42\mu\text{A}$ and $40\mu\text{A}$. What is the output error voltage?
8. A particular voltage follower has an input offset voltage of 2nV . What is the output error voltage?
9. What is the input offset voltage of an op-amp if a dc voltage of 35mV is measured when the input voltage is zero? The opamp's open loop gain is specified to be $200,000$.
10. The midrange open-loop gain of a certain op-amp is 120dB . Negative feedback reduces this gain by 50dB . What is the closed-loop gain?
11. The upper critical frequency of an op-amp's open loop response is 200Hz .
If the midrange gain is $175,000$, what is the ideal gain at 200Hz ? What is the actual gain? What is the op-amp's open-loop bandwidth?
12. An RC lag circuit has a critical frequency of 8.5 KHz . Determine the phase shift for each frequency and plot a graph of its phase angle versus frequency.
(i) 100Hz (ii) 400Hz (iii) 850Hz (IV) 8.5 KHz (v) 25 KHz .
13. An RC lag circuit has a critical frequency of 5 KHz . If the resistance value is $1\text{K}\Omega$. What is X_c when $f=3\text{KHz}$.
14. Determine the attenuation of an RC lag circuit with $f_c=12\text{ KHz}$ for 1 KHz and 100 KHz .
15. A certain amplifier has an open-loop gain in midrange of $180,000$ and an open-loop critical frequency of 1500Hz . If the attenuation of the path is 0.015 , what is the closed-loop bandwidth?
16. Given that $f_{c(ol)}=750\text{Hz}$, $A_{ol}=89\text{dB}$, and $f_{c(cl)}=5.5\text{KHz}$, determine the closed loop gain in decibels.
17. Which of the amplifiers shown in figure (4) has the smaller Bandwidth?

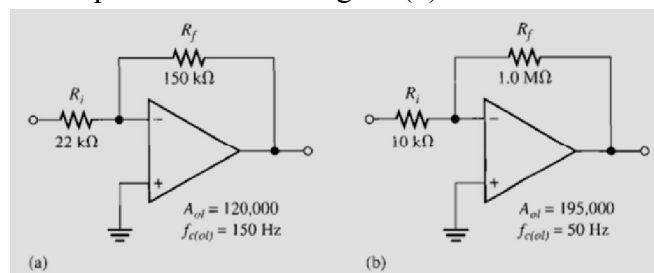


Figure (4)

Good Luck

Dr. Rokaia Mounir