



## Sheet1

- 1] Starting from the transmission line model, derive an equation for the attenuation constant and phase constant of transmission line in terms of R, L, C, G.

From lecture 1 , pozar pp.50

- 2] Use the telegrapher equation, and general solution of wave equation to derive an equation for the characteristic impedance of transmission line.

From lecture 1 , pozar pp.50-51

- 3] The current on a transmission line is given as  $i(t) = 1.2 \cos(1.51 \times 10^{10}t - 80.3z)$  A. Determine (a) the frequency, (b) the wavelength, (c) the phase velocity, and (d) The phasor representation of this current.

$$i(t) = 1.2 \cos(1.51 \times 10^{10}t - 80.3z)$$

a)  $\omega = 2\pi f = 1.51 \times 10^{10} \Rightarrow f = 2.4 \text{ GHz}$

b)  $k = 80.3 \text{ m}^{-1} = 2\pi/\lambda \rightarrow \lambda = 0.0782 \text{ m}$

c)  $v_p = \omega/k = 1.88 \times 10^8 \text{ m/sec} \Rightarrow \epsilon_r = \sqrt{c/v_p} = 2.55$

d)  $I = 1.2 \angle -80.3z \text{ (rad)}$

- 4] A transmission line has the following per unit length parameters:  $L=0.2\mu\text{H/m}$ ,  $C=300\text{pF/m}$ ,  $R=5\Omega/\text{m}$  and  $G=0.01\text{S/m}$ . Calculate the propagation constant and the characteristic impedance of this line at 500MHz. Recalculate these quantities in the absence of loss ( $R=G=0$ ).

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)} = \sqrt{(5+j628)(0.01+j0.94)} = \sqrt{(628/89.54^\circ)(.94/89.39^\circ)}$$

$$= 24.3/89.465^\circ = 0.23 + j24.3 = \alpha + j\beta \text{ np/m, rad/m } \checkmark$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{628/89.54^\circ}{.94/89.39^\circ}} = 25.8/0.08^\circ = 25.8 + j0.03 \Omega \checkmark$$

- 5] RD-402U semi-rigid coaxial cable has an inner conductor diameter of 0.91 mm, and a dielectric diameter (equal to the inner diameter of the outer conductor) of 3.02 mm. Both conductors are copper and the dielectric material is Teflon. Compute the R, L, G, and C parameters of this line at 1 GHz, and use these results to find the characteristic impedance and attenuation of the line at 1 GHz.

Given: Teflon relative permittivity=2.08, copper conductivity  $\sigma=5.813 \times 10^7$  s/m, surface resistivity  $R_s = (\omega\mu/2\sigma)^{1/2}$

From Table 2.1:

$$L = \frac{\mu_0}{2\pi} \ln \frac{b}{a} = 2.40 \times 10^{-7} \text{ H/m}$$

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln b/a} = 9.64 \times 10^{-11} \text{ Fd/m}$$

$$R = \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right) = 3.76 \text{ } \Omega/\text{m}$$

$$G = \frac{2\pi\omega\epsilon_0\epsilon_r \tan\delta}{\ln b/a} = 2.42 \times 10^{-4} \text{ S/m}$$

For small loss,  $Z_0 = \sqrt{L/C} = 49.9 \text{ } \Omega \checkmark$

From (2.85a),  $\alpha \approx \frac{1}{2} \left( \frac{R}{Z_0} + GZ_0 \right) = 0.044 \text{ np/m} = 0.38 \text{ dB/m} \checkmark$

### REPORT

- 6] The characteristic impedance of a certain lossless transmission line is 72  $\Omega$ . If

$L = 0.5 \mu\text{H} / \text{m}$ , Find C,  $v_{ph}$  and  $\beta$  If  $f = 80\text{MHz}$ .

hint

$$\text{characteristic impedance } z_0 = \sqrt{\frac{L}{C}} = 72 = \sqrt{\frac{0.5 \times 10^{-6}}{C}}$$

$$V_{ph} = \frac{1}{\sqrt{LC}}$$

$$\beta = \omega\sqrt{LC}$$

*Good Luck*

*Dr. Gehan Sami*