



Sheet 2 - solution

- 1] A lossless transmission line is terminated with a 100Ω load. If the SWR on the line is 1.5, find the two possible values for the characteristic impedance of the line.

$$|\Gamma| = \frac{S-1}{S+1} = \frac{0.5}{2.5} = 0.2$$

$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{100 - Z_0}{100 + Z_0} \right| \quad (Z_0 \text{ real})$$

So either,

$$\frac{100 - Z_0}{100 + Z_0} = 0.2 \Rightarrow Z_0 = Z_L \frac{1 - \Gamma}{1 + \Gamma} = 100 \left(\frac{.8}{1.2} \right) = 66.7 \Omega \quad \checkmark$$

or

$$\frac{100 - Z_0}{100 + Z_0} = -0.2 \Rightarrow Z_0 = Z_L \frac{1 - \Gamma}{1 + \Gamma} = 100 \left(\frac{1.2}{.8} \right) = 150 \Omega \quad \checkmark$$

- 2] Let Z_{sc} be the input impedance of a length of coaxial line when one end is short-circuited and let Z_{oc} be the input impedance of the line when one end is open-circuited. Derive an expression for the characteristic impedance of the cable in terms of Z_{sc} and Z_{oc} .

$$Z_{sc} = jZ_0 \tan \beta l \quad , \quad Z_{oc} = -jZ_0 \cot \beta l$$

$$Z_{sc} \cdot Z_{oc} = Z_0^2 \Rightarrow Z_0 = \sqrt{Z_{sc} Z_{oc}}$$

- 3] A 100Ω transmission line has an effective dielectric constant of 1.65. Find the shortest open-circuited length of this line that appears at its input as a capacitor of 5 pF at 2.5 GHz. Repeat for an inductance of 5 nH.

C: $Z_{oc} = -j/\omega C = -j12.73 \Omega = -jZ_0 \cot \beta l \quad C = 5 \text{ pF}$

$$\tan \beta l = 100/12.73 \Rightarrow \beta l = 82.74^\circ \quad \checkmark$$

$$\lambda_0 = 0.12 \text{ m}, \quad \beta = 2\pi\sqrt{\epsilon_e}/\lambda_0 = 3854^\circ/\text{m} \Rightarrow l = \underline{2.147 \text{ cm}} \quad \checkmark$$

L: $Z_{oc} = j\omega L = +j78.5 \Omega = -jZ_0 \cot \beta l \quad L = 5 \text{ nH}$

$$\tan \beta l = -100/78.5 \Rightarrow \beta l = 128.1^\circ \quad \checkmark \Rightarrow l = \underline{3.324 \text{ cm}} \quad \checkmark$$

These results were verified with Serenade.

- 4] A radio transmitter is connected to an antenna having an impedance $80 + j40 \Omega$ with a 50Ω coaxial cable. If the 50Ω transmitter can deliver 30 W when connected to a 50Ω load, how much power is delivered to the antenna?

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j40}{130 + j40} = \frac{50 \angle 53^\circ}{136 \angle 17^\circ} = 0.367 \angle 36^\circ \checkmark$$

$$P_{\text{LOAD}} = P_{\text{INC}} - P_{\text{REF}} = P_{\text{INC}} (1 - |\Gamma|^2) = 30 [1 - (0.367)^2] = 25.9 \text{ W} \checkmark$$

- 5] The transmission line circuit shown below has $V_g = 15 \text{ V rms}$, $Z_g = 75 \Omega$, $Z_0 = 75 \Omega$, $Z_L = 60 - j40 \Omega$, and $\ell = 0.7\lambda$. Compute the power delivered to the load using three different techniques:

(a) find Γ and compute

$$P_L = \left(\frac{V_g}{2} \right)^2 \frac{1}{Z_0} (1 - |\Gamma|^2);$$

$V_g = 15 \text{ V RMS}, Z_g = 75 \Omega, Z_0 = 75 \Omega, Z_L = 60 - j40 \Omega, \ell = 0.7\lambda.$

a) $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-15 - j40}{135 - j40} = \frac{42.7 \angle -110.6^\circ}{140.8 \angle -16.5^\circ} = 0.303 \angle -94^\circ = -0.021 - j0.302$

$$P_L = \left(\frac{V_g}{2} \right)^2 \frac{1}{Z_0} (1 - |\Gamma|^2) = 0.681 \text{ W} \checkmark$$

This method is actually based on $P_L = P_{\text{inc}} (1 - |\Gamma|^2)$. It is the simplest method, but only applies to lossless lines.

(b) find Z_{in} and compute

$$P_L = \left| \frac{V_g}{Z_g + Z_{\text{in}}} \right|^2 \text{Re}(Z_{\text{in}}); \text{ and}$$

b) $Z_{\text{in}} = Z_0 \frac{Z_L + jZ_0 \tan \beta \ell}{Z_0 + jZ_L \tan \beta \ell} = 75 \frac{60 + j190.8}{198.1 + j184.7} = 75 \frac{200 \angle 72.5^\circ}{270.8 \angle 43^\circ}$

$$= 55.4 \angle 29.5^\circ = 48.2 + j27.3 \Omega$$

$$P_L = \left| \frac{V_g}{Z_g + Z_{\text{in}}} \right|^2 \text{Re}(Z_{\text{in}}) = \left| \frac{15}{123.2 + j27.3} \right|^2 (48.2) = 0.681 \text{ W} \checkmark$$

This method computes $P_L = P_{\text{in}} = |I_{\text{in}}|^2 R_{\text{in}}$, and also applies only to lossless lines.


(c) find V_L and compute

$$P_L = \left| \frac{V_L}{Z_L} \right|^2 \operatorname{Re}(Z_L).$$

$$\begin{aligned} V(z) &= V^+(e^{-j\beta z} + \Gamma e^{j\beta z}) \\ V_L = V(0) &= V^+(1 + \Gamma) & V^+ &= \frac{V_g}{2} = 7.5 \text{ v} \\ &= 7.5(1 - 0.021 - j0.302) \\ &= 7.68 \angle -17^\circ \end{aligned}$$

$$P_L = \left| \frac{V_L}{Z_L} \right|^2 \operatorname{Re}(Z_L) = \left(\frac{7.68}{72.1} \right)^2 (60) = 0.681 \text{ w } \checkmark$$

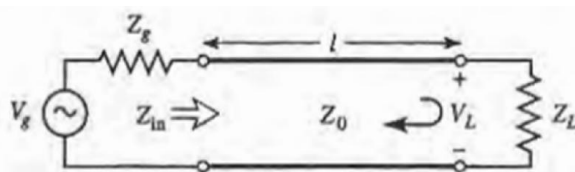(d) Discuss the rationale for each of these methods. Which of these methods can be used if the line is not lossless?




This method computes $P_L = |I_L|^2 R_L$, and applies to lossy as well as lossless lines. Note the concept that $V^+ = V_g/2$ requires a good understanding of the transmission line equations, and only applies here because $Z_g = Z_0$.

6 For a purely reactive load impedance of the form $Z_L = jX$, show that the reflection coefficient magnitude $|\Gamma|$ is always unity. Assume the characteristic impedance Z_0 is real.

$$\begin{aligned} Z_L &= jX \\ \Gamma &= \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX - Z_0}{jX + Z_0} \\ |\Gamma|^2 &= \Gamma \Gamma^* = \frac{(jX - Z_0)(-jX - Z_0)}{(jX + Z_0)(-jX + Z_0)} = \frac{X^2 - jZ_0X + jZ_0X + Z_0^2}{X^2 + Z_0^2} = 1 \checkmark \end{aligned}$$

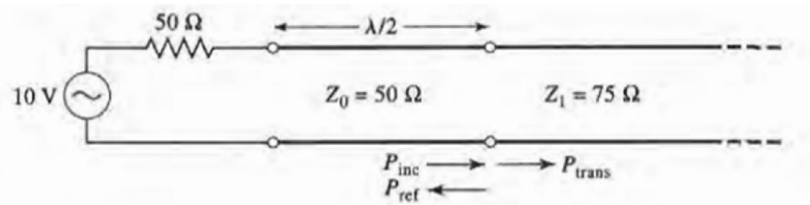7 Consider the transmission line circuit shown below. Compute the incident power, the reflected power, and the power transmitted into the infinite 75Ω line. Show that power conservation is satisfied.



$$\text{POWER DELIVERED BY SOURCE} = \frac{1}{2} \frac{(10)^2}{50+75} = 0.400 \text{ W} \checkmark$$

$$\text{POWER DISSIPATED IN } 50\Omega \text{ LOAD} = \frac{1}{2} (50) \left(\frac{10}{50+75} \right)^2 = 0.160 \text{ W} \checkmark$$

$$\text{POWER TRANSMITTED DOWN LINE} = \frac{1}{2} (75) \left(\frac{10}{50+75} \right)^2 = 0.240 \text{ W} \checkmark$$

$$\text{INCIDENT POWER} = \frac{1}{2} (50) \left(\frac{10}{50+50} \right)^2 = 0.250 \text{ W} \checkmark$$


$$\text{REFLECTED POWER} = P_{\text{INC}} |\Gamma|^2 = .250 \left| \frac{75-50}{75+50} \right|^2 = 0.010 \text{ W} \checkmark$$

$$P_{\text{INC}} - P_{\text{REF}} = .250 - .010 = 0.240 = P_{\text{TRANS}} \checkmark$$

$$P_{\text{DISS}} + P_{\text{TRANS}} = .160 + .240 = 0.400 = P_{\text{SOURCE}} \checkmark$$

8 A generator is connected to a transmission line as shown below. Find the voltage as a function of z along the transmission line. Plot the magnitude of this voltage for

$$-l \leq z \leq 0$$

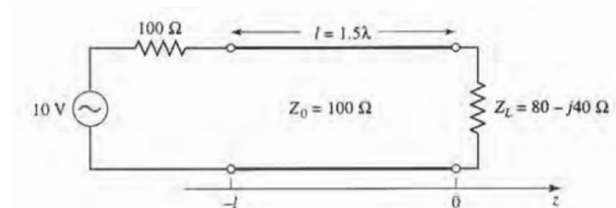

$$\Gamma = \frac{-20-j40}{180-j40} = \frac{44.7 \angle -116.6^\circ}{184.4 \angle -12.5^\circ} = 0.24 \angle -104^\circ = -0.058 - j 0.233 \checkmark$$

$$V_L = 10 \frac{80-j40}{180-j40} = 10 \frac{89.4 \angle -26^\circ}{184 \angle -12.5^\circ} = 4.86 \angle -13.5^\circ$$

$$V(z) = V^+ [e^{-j\beta z} + \Gamma e^{j\beta z}] \quad V^+ = 10 \frac{100}{100+100} = 5 \text{ V } \checkmark$$


So $V(z) = 5 [e^{-j\beta z} + \Gamma e^{j\beta z}]$

$$V_{\text{MAX}} = 5(1+|\Gamma|) = 5(1.24) = 6.2 \text{ at } z = -0.355\lambda$$

$$V_{\text{MIN}} = 5(1-|\Gamma|) = 5(0.76) = 3.8 \text{ at } z = -0.105\lambda$$

These results repeat every $\lambda/2$.

$|V(z)|$ is plotted below

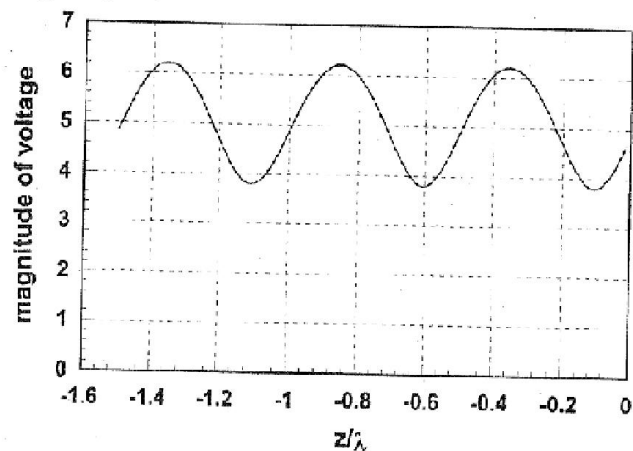

Good Luck

Dr. Gehan Sami