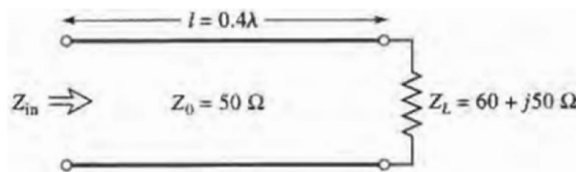




## Sheet 3 - Solution

1] Use the Smith chart to find the following quantities for the transmission line circuit below:


- (a) The SWR on the line.
- (b) The reflection coefficient at the load.
- (c) The load admittance.
- (d) The input impedance of the line.
- (e) The distance from the load to the first voltage minimum.
- (f) The distance from the load to the first voltage maximum.



$$Z_0 = 50 \Omega, Z_L = 60 + j50 \Omega, l = 0.4 \lambda$$

From Smith chart, ( $Z_L = 1.2 + j1.0$ )

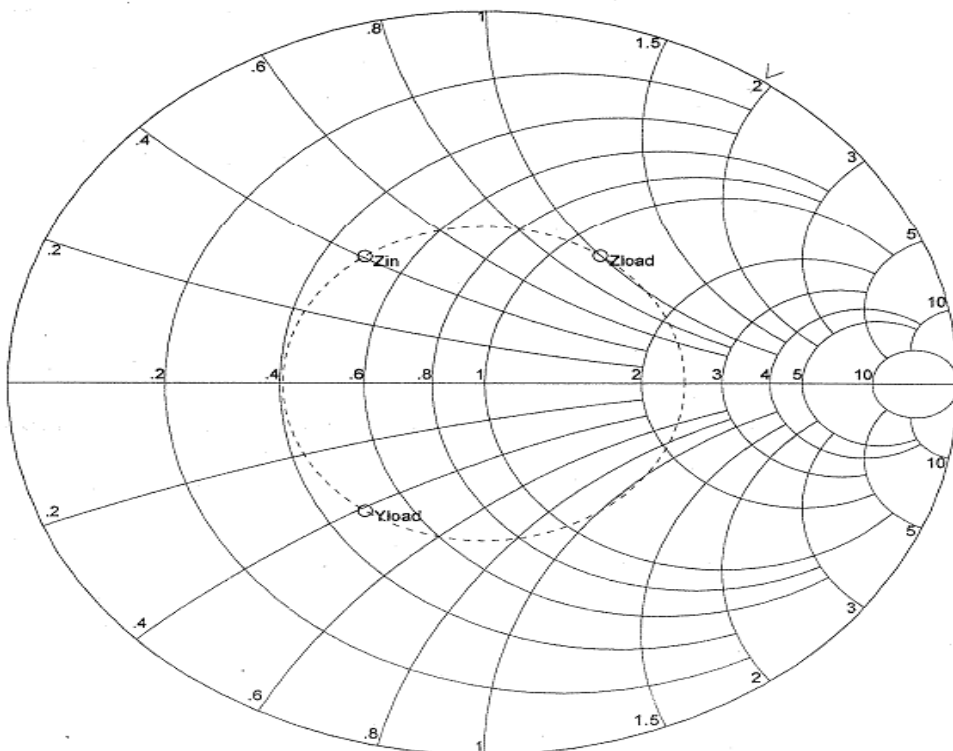- a)  $SWR = 2.46$  ✓
- b)  $\Gamma = 0.422 \angle 54^\circ$  ✓
- c)  $Y_L = (0.492 - j.410) / 50 = 9.84 - j 8.2 \text{ mS}$  ✓
- d)  $Z_{in} = 24.5 + j 20.3 \Omega$
- e)  $l_{min} = 0.325 \lambda$
- f)  $l_{max} = 0.075 \lambda$



2 Repeat problem (1) for  $Z_L = 40 - j30\Omega$ .

**(REPORT)**

$$Z_0 = 50\Omega, Z_L = 40 - j30\Omega, l = 0.4\lambda$$

From Smith chart, ( $Z_L = 0.80 - j0.60$ )

a)  $SWR = 2.00$


b)  $\Gamma = 0.333 / 270^\circ$

c)  $Y_L = (0.800 + j0.600) / 50 = 16.0 + j12.0 \text{ mS } \checkmark$

d)  $Z_{in} = 93.2 - j21.6 \Omega$

e)  $l_{MIN} = 0.125\lambda$

f)  $l_{MAX} = 0.375\lambda$

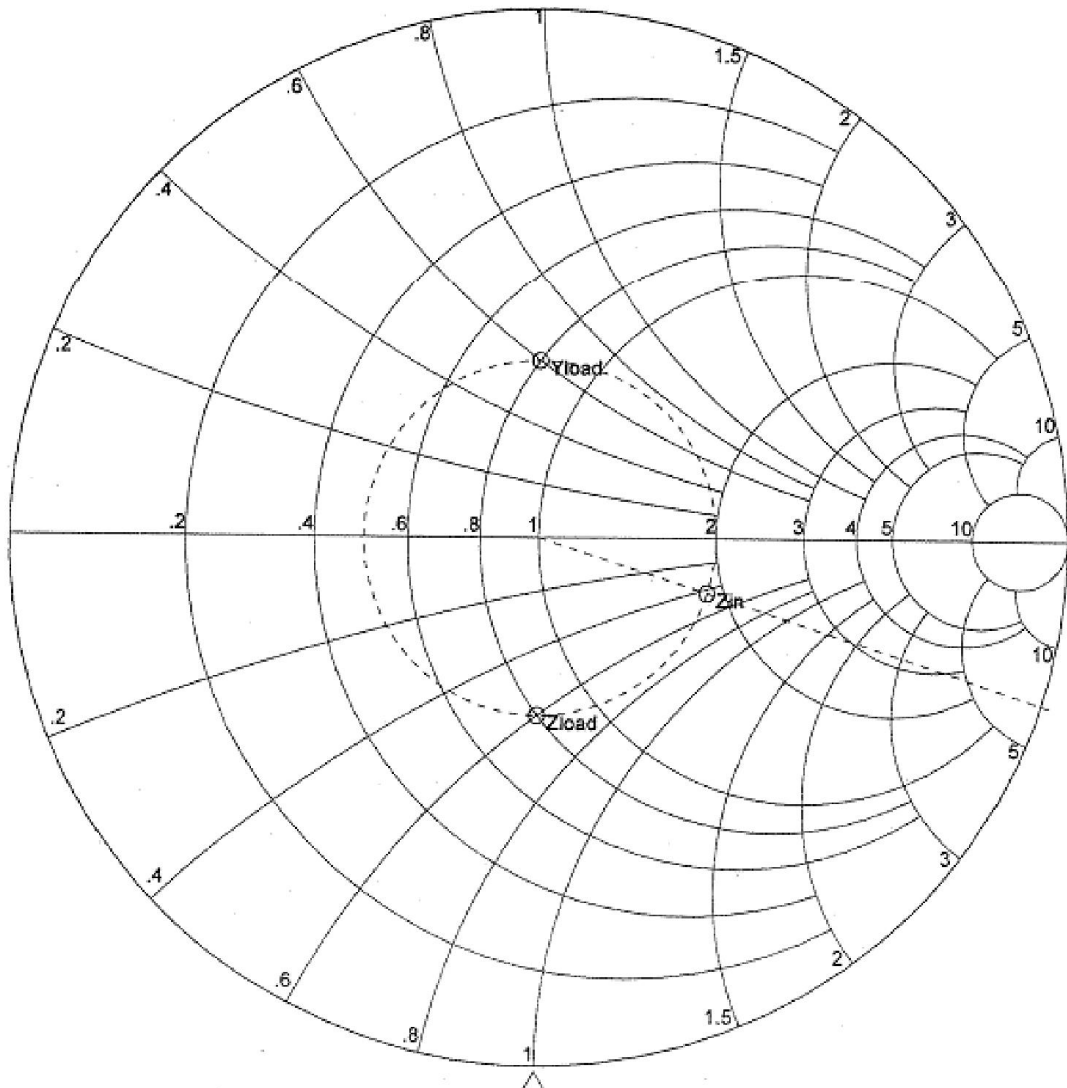

3 Repeat problem (1) for  $l = 1.8\lambda$ .

**(REPORT)**

$$Z_0 = 50\Omega, \quad Z_L = 60 + j50\Omega, \quad l = 1.8\lambda$$

From Smith chart,  $(Z_L = 1.2 + j1.0)$

a)  $SWR = 2.46$


b)  $\Gamma = 0.422 \angle 54^\circ$

c)  $Y_L = (.492 - j.410) / 50 = 9.84 - j8.2 \text{ mS } \checkmark$

d)  $Z_{in} = 20.8 - j6.7\Omega$

e)  $l_{MIN} = 0.325\lambda$

f)  $l_{MAX} = 0.075\lambda$

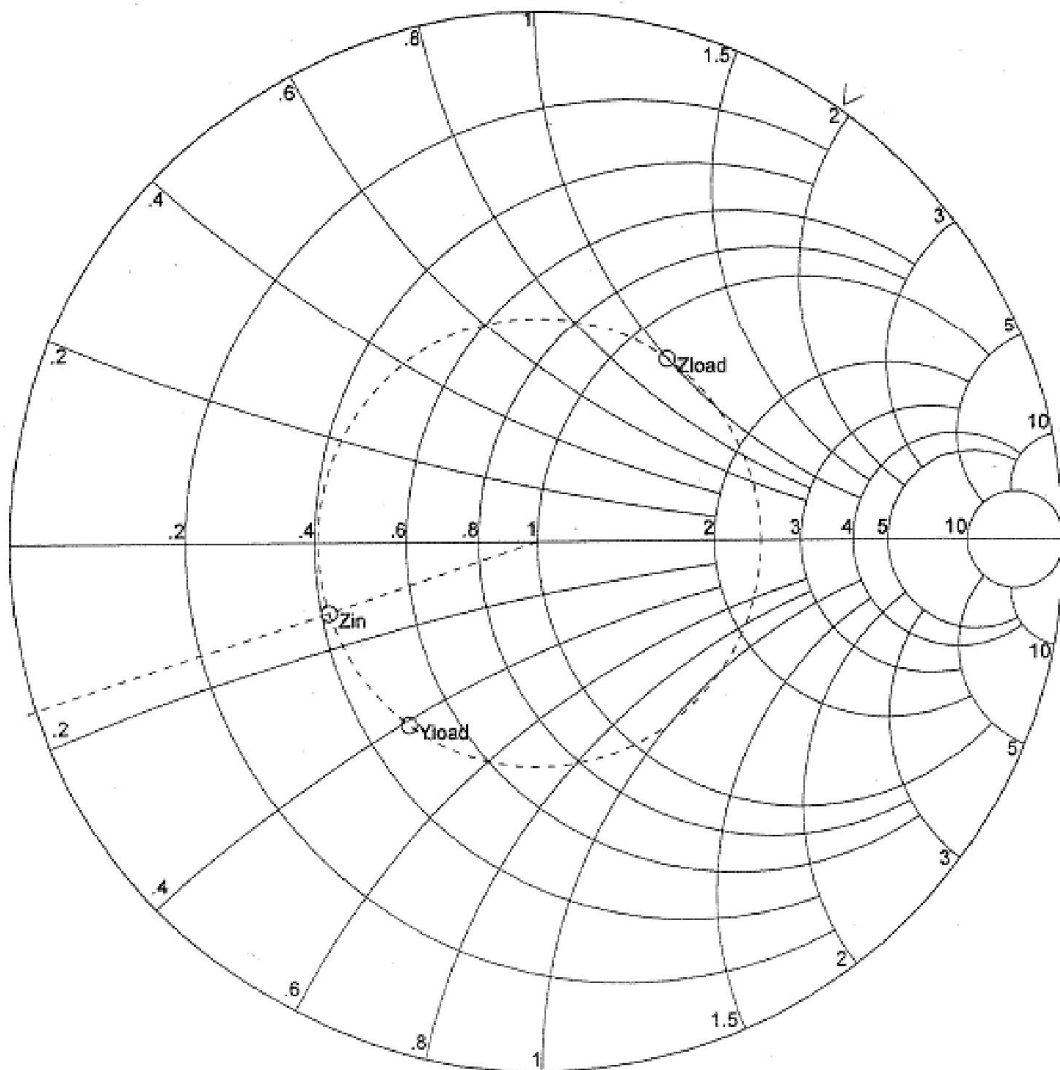

4] Use the Smith chart to find the shortest lengths of a short-circuited  $75 \Omega$  line to give the following input impedance:

- (a)  $Z_{in} = 0$ .
- (b)  $Z_{in} = \infty$ .
- (c)  $Z_{in} = j75 \Omega$ .
- (d)  $Z_{in} = -j50 \Omega$ .
- (e)  $Z_{in} = j10 \Omega$ .

a)  $l = 0$  or  $l = 0.5\lambda$  ✓

b)  $l = 0.25\lambda$  ✓

c)  $l = 0.125\lambda$  ✓

d)  $l = 0.406\lambda$  ✓

e)  $l = 0.021\lambda$  ✓

These results check with  $Z_{in} = jZ_0 \tan \beta l$ .

5] Repeat Problem (4) for an open-circuited length of  $75 \Omega$  line.

**(REPORT)**

a)  $l = 0.25\lambda$  ✓

(add  $\lambda/4$  to results of problem 4)

b)  $l = 0\lambda$  or  $0.5\lambda$  ✓

(also check with

c)  $l = 0.375\lambda$  ✓

$Z_{in} = -jZ_0 \cot \beta l$ )

d)  $l = 0.656\lambda - 0.5\lambda = 0.156\lambda$  ✓

e)  $l = 0.271\lambda$  ✓

6] A slotted-line experiment is performed with the following results: distance between successive minima = 2.1 cm; distance of first voltage minimum from load = 0.9 cm; SWR of load, = 2.5. If  $Z_0 = 50 \Omega$ , find the load impedance.

$\lambda = 4.2$  cm. From the Smith chart,  $l_{MIN} = .9/4.2 = 0.214\lambda$   
from the load, so  $Z_L = 2 - j.9 \Rightarrow Z_L = \underline{100 - j45 \Omega}$  ✓

Analytically, using (2.58)-(2.60),

$$\Gamma = |\Gamma| e^{j\theta}, \quad |\Gamma| = \frac{2.5-1}{2.5+1} = 0.428$$

$$\theta = \pi + 2\beta l_{MIN} = 180 + 2(360)(.214) = -26^\circ \checkmark$$

Then,

$$Z_L = \frac{1 + .428 \angle -26^\circ}{1 - .428 \angle -26^\circ} (50) = 50 \frac{1.4 \angle -7.7^\circ}{.643 \angle 17^\circ} = 109 \angle -25^\circ$$

$$= \underline{99 - j46 \Omega}$$

**Good Luck**

Dr. Gehan Sami