

Electrical Circuits (B) - Quiz 1

Max Time Allowed: 10 min

Q.1) for Low pass filter, At low frequency $V_{out} = 0$

- A. True
B. False

Q.2) mutual coupling exists when The inductors or coils are in far proximity

- A. False
B. True

Q.3) The magnitude of current in the reactive elements at parallel resonance is Q times Lower than the applied source current.

- A. True
B. False

Q.4) Active Filters consists of only passive elements R, L, and C.

- A. False
B. True

Q.5) in electrical circuits, the particular integral solution Represent the steady-state solution

- A. False
B. True

Q.6) M_{21} relates the induced voltage in coil 1 to the current in coil 2

- A. False
B. True

Q.7) At parallel resonance, The Power factor is unity.

- A. False
B. True

Q.8) The resonant circuit consists only of inductor with a voltage or current source.

- A. False
B. True

Q.9) Laplace Transform is more complex method for solving transient equations

- A. False
B. True

Q.10) Since the current is maximum at resonance, it follows that the power must similarly be maximum at resonance.

- A. False
B. True

Q.11) typical characteristics of filter response curve is more sharp than ideal characteristics

- A. True
B. False

Q.12) in ideal transformer the voltage ratio is directional proportional to current ratio

- A. False
B. True

Q.13) partial fraction is an urgent step to solve transient current using differential equation method

- A. True
B. False

Q.14) When two loops with or without contacts between them affect each other through the magnetic field generated by one of them, they are said to be magnetically coupled.

- A. False
B. True

Q.15) Band pass filters are also called band reject filters

- A. False
B. True

Q.16) A steady state period obtained when a circuit is switched from one condition to another.

- A. True
B. False

Q.17) in practical parallel resonance , if the internal resistance of the coil is negligible , so the resonance frequency of the circuit will be greater the resonant frequency of ideal parallel resonance

- A. True
B. False

Q.18) in series resonance, The higher the value of Q , the more selective the circuit is but more bandwidth.

- A. False
B. True

Q.19) The resonant circuit consists only of a capacitor with a voltage or current source.

- A. False
B. True

Q.20) The mutual voltage may be negative or positive

- A. False
B. True

Q.21) In RLC series resonance the Magnitude of inductive reactance must Eliminates the Magnitude of capacitive reactance to result a pure inductor


$$R + j \left(\omega L - \frac{1}{\omega C} \right)$$

- A. True
B. False

Q.22) band stop filters used to pass a certain band of frequencies

- A. True
B. False

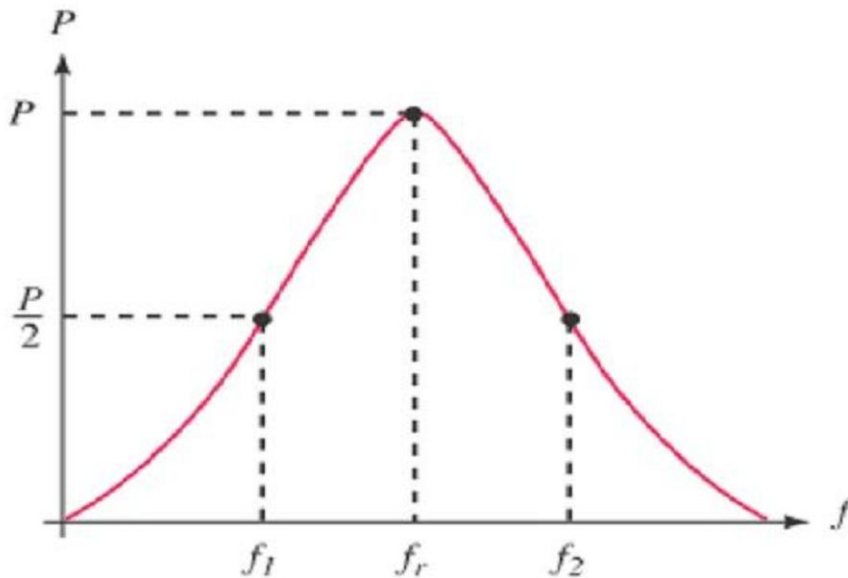Q.23) This curve indicates that power will be a maximum at f_r and varying the frequency in either direction results in a rise of the power.



- A. False
 B. True

Q.24) Differential equation give the same solution for transient current that obtained by laplace

- A. True
 B. False

Q.25) For Sinusoidal source $d/dt = 1/j\omega$

- A. False
 B. True

Q.26) Active filters can be used to perform mathematical operations as integrations

- A. True
 B. False

Q.27) The power response of a series resonant circuit has a bell-shaped curve called the selectivity curve.

- A. True
 B. False

Q.28) The RLC parallel resonant circuit provides a band-stop filter when the output is taken off the LC

- A. True
 B. False

Q.29) Active filters Can generate gains greater than one

- A. True
 B. False

Q.30) After the steady state interval , the circuit is said to be in the transient.

- A. False
 B. True

Q.31) For RC series circuit with DC supply the transient current decays with time

- A. False
 B. True

Q.32) The Bandwidth of the resonant circuit (BW) is The difference between the frequencies at which the circuit delivers half of the maximum power.

- A. True
 B. False

Q.33) current may vary in an electrical circuit when a change in the applied voltage or a change in one of the circuit elements done.

- A. False
B. True

Q.34) Passive Filters consists of only passive elements R, and C.

- A. False
B. True

Q.35) Passive Filters is more preferable than Active filters

- A. False
B. True

Q.36) The RLC parallel resonant circuit provides a bandpass filter when the output is taken off the resistor

- A. False
B. True

Q.37) passive filters can be designed to generate output voltage greater than input voltage

- A. True
B. False

Q.38) in electrical circuits, the Complementary solution Represent the transient solution

- A. True
B. False

Q.39) in step down transformer , the current at secondary coil is greater than primary.

- A. True
B. False


Q.40) A filter that prevents a band of frequencies between two designated values is called high stop filter

- A. False
B. True

Q.41) At parallel resonance, The currents through the inductor and the capacitor have the same magnitudes but are 90 out of phase.

- A. True
B. False

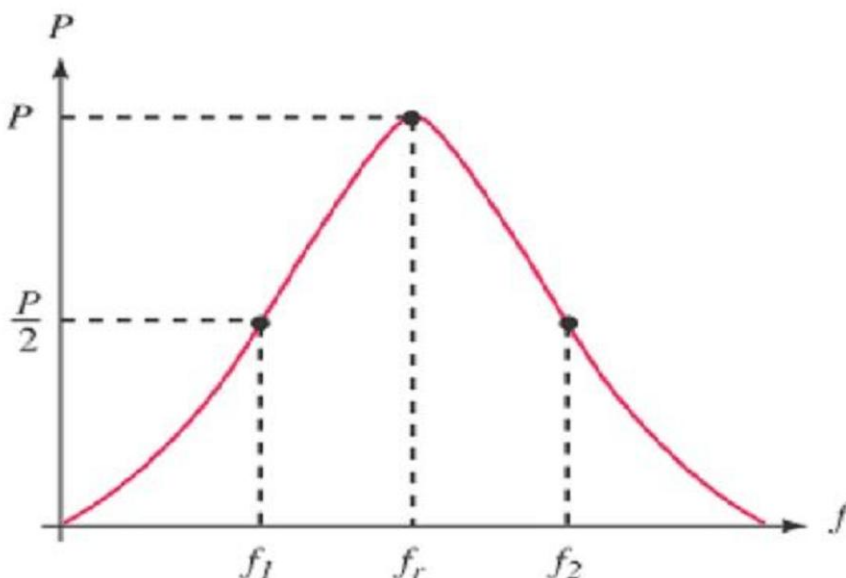Q.42) The bandwidth is the average between the half power points on the response curve of the filter.



- A. False
B. True

Q.43) in series RLC with DC supply, The particular integral function can be one of three different types according to the roots of the auxiliary equation.

- A. False
B. True

Q.44) for Ideal transformer there is no power Loss

- A. False
B. True

Q.45) When two coils are close to each other, the magnetic flux caused by current in one coil links with the other coil.

- A. True
B. False

Q.46) Second Order Filters contain two reactive elements (L and C)

- A. True
B. False

Q.47) in series resonance, If the band of frequencies to be selected or rejected is narrow, the quality factor of the resonant circuit must be high.

- A. True
B. False

Q.48) The resonant frequency is the geometric mean of the half-power frequencies. The resonant frequency is the geometric sum of the half-power frequencies.

- A. True
B. False

Q.49) Transformer is the direct application for mutual inductance phenomena

- A. True
B. False

Q.50) The value of ω that satisfies this condition is called the resonant frequency

$$\omega_s = \frac{1}{\sqrt{LC}} \text{ (Hz)}$$

- A. False
B. True

Q.51) For RC series circuit with DC supply the transient current take the form of triangle wave form

- A. True
B. False

Q.52) in ideal transformer the turns ratio inversly poroprtnal to the root of self inductance ratio

- A. True
B. False

Q.53) for high pass filter, At high frequency $V_{out} = 0$

- A. True
B. False

Q.54) At parallel resonance, the admittance consists only conductance $G = 1/2R$.

- A. False
B. True

Q.55) The phase of The current across coil in series resonant circuit is +90 when the supply is $5\sin\omega t$

- A. True
B. False

Q.56) the quality factor of resonance circuit doesn't depend on resistance

- A. False
B. True

Q.57) Mutual inductance M may be Negative or positive

- A. True
B. False

Q.58) in series RL circuit, the steady state current is zero

- A. True
B. False

Q.59) in series RLC with DC supply, the transient current obtained will be a part of solution for the same circuit but with AC supply

- A. True
B. False

Q.60) At parallel resonance, The value of current will be minimum since the total admittance is maximum

- A. False
B. True

Q.61) in dot convention, if currents enter dotted terminals of two coils , M will be positive

- A. False
B. True

Q.62) For RC series circuit with DC supply and two position switch, the boundary condition of the current of position two become 0 ampere.

- A. False
B. True

Q.63) The total impedance of RLC parallel circuit is given in the shown relation

$$R + j \left(\omega L - \frac{1}{\omega C} \right)$$

- A. True
B. False


Q.64) If the bandwidth of a circuit is kept very narrow , the circuit is said to have a Low selectivity

- A. True
B. False

Q.65) A series RLC with DC supply is considered first order circuit

- A. False
B. True

Q.66) This curve is for bandstop filter

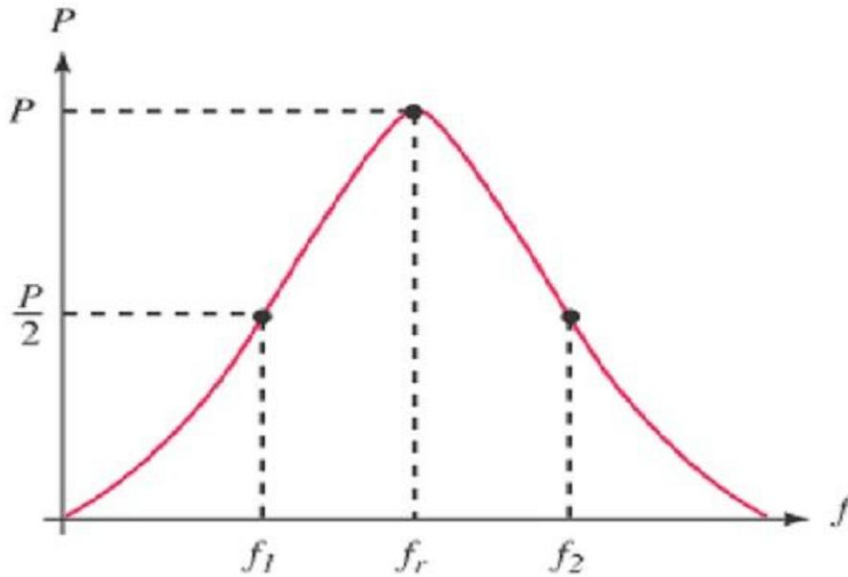

- A. True
 B. False

Q.67) mutual coupling exists when the circuits are driven by time-constant sources

- A. False
 B. True

Q.68) First-order circuits contain a single capacitor and inductor

- A. True
 B. False

Q.69) No protection needed when the inductance from one coil can interfere with the operation of another adjacent component by means of electromagnetic induction

- A. False
 B. True

Q.70) The "sharpness" of the resonance in a resonant circuit is measured quantitatively by the quality factor Q.

- A. True
 B. False