

Dr Basem El Halawany

Revision
Sheet (1)


15 Feb 2015 → 17 Feb 2015

Section (1)


Electrical Circuit (B)

Revision

Section (1)

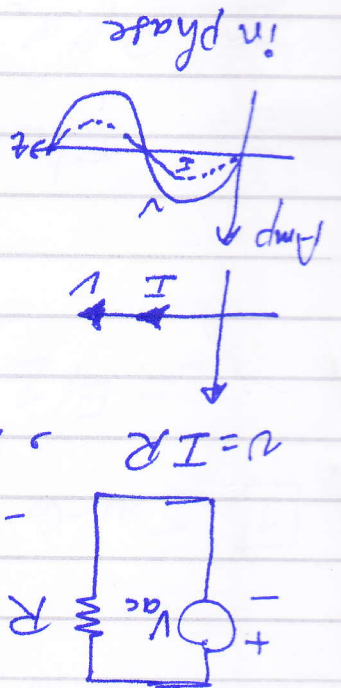


$$V = IR, \quad f = \frac{V}{R}$$


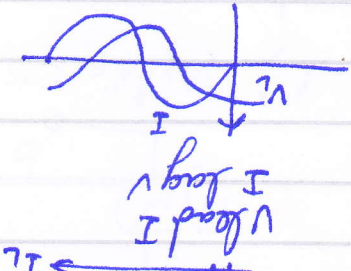


$$Z_L = j\omega L = \omega L \angle 90^\circ$$
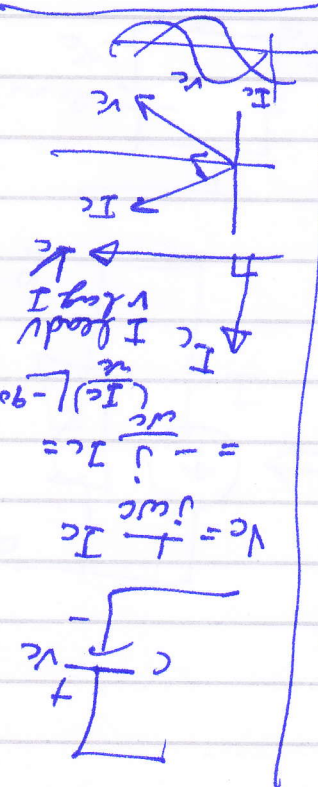
$$V_L = L \frac{dI}{dt} = I(j\omega L) \angle 90^\circ$$


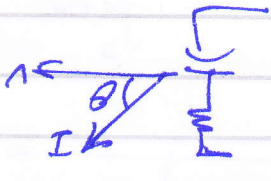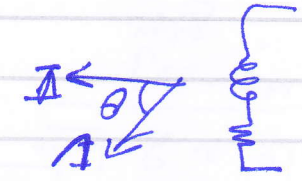
$$V_C = \frac{1}{j\omega C} I = -j \frac{1}{\omega C} I$$



$$Z = A + jB = \sqrt{A^2 + B^2} \angle \tan^{-1}\left(\frac{B}{A}\right)$$

$$Z_1 Z_2 = A_1 A_2 \angle \theta_1 + \theta_2$$

$$Z_1 = \frac{1}{A_1} \angle -\theta_1$$

$$Z_1 = \sqrt{A_1} \angle \theta_1/2$$

$$e^{j\phi} = \cos \phi + j \sin \phi$$

$$\frac{1}{j} = -j$$

②


ac Analysis Theories

- 1. Mesh (loop)
- 2. Node
- 3. Super Position
- 4. Delta-wye
- 5. Thevenin-Norton

Source Conversion

1 Source Conversion

$$I = E/Z$$

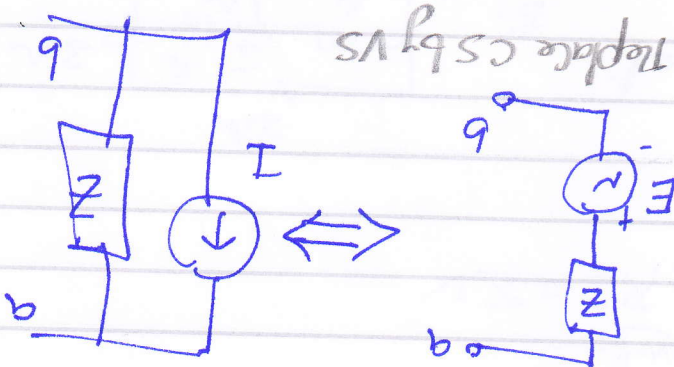

Ex Sheet 1 (Prob. 1) Replace CS by VS

$$Z = R // X_c$$

$$X_c = -j \frac{1}{\omega C} \quad (\omega = 2\pi f)$$

$$= 40 \times (-20j) = 400 \angle -90^\circ$$

$$= 800 \angle -90^\circ$$

$$\sqrt{(40)^2 + (20)^2} \angle \tan^{-1} \left(\frac{-20}{40} \right)$$

capacitive tan⁻¹ (20/40) = 26.57°

$$44.72 \angle -26.57^\circ$$

$$= 17.89 \angle -90 - (-26.57) = 17.89 \angle -63.43^\circ$$


$$= 17.89 \cos(-63.43^\circ) + j 17.89 \sin(-63.43^\circ)$$

$$Z = 8 - j16$$

★

$$E = IZ = 240 \text{ mA} \angle 30^\circ \times 17.89 \angle -63.43^\circ$$

$$= 4.29 \angle -33.43^\circ$$

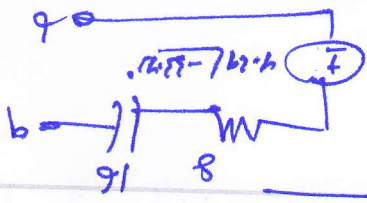

(3)

[2] Mesh (loop)

Given: 100 V & 5 A DC source

- Convert Current Source $\rightarrow$ Voltage Source.
- Redraw & simplify circuit, like Resistor
- choose loops & directions.
- Apply KVL $\Sigma RI = \Sigma V$
- So five equations

ex (2) ... Sheet (1)

Solve by loop $\rightarrow$ loop current

Sol //

loop $\rightarrow \Sigma IR = \Sigma V$

(+ & - signs)

$$3I_1 = I_1 (1+j2) = I_2 (2j) - I_3 (1) \rightarrow (1)$$

$$0 = I_2 (2+j2-j3) - I_1 (j2) - I_3 (-j3) \rightarrow (2)$$

$$+6I_2 = I_3 (1-j3) - (1) I_1 - (-j3) I_2 \rightarrow (3)$$

$$\Delta = \begin{bmatrix} 1+j2 & -2j & -1 \\ -j2 & 2-j1 & +j3 \\ -1 & +j3 & 1-j3 \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} 6 & +j3 & 1-j3 \\ 0 & 2-j1 & j3 \\ 3 & -2j & -1 \end{bmatrix}$$

$$\Delta_2 = \begin{bmatrix} 1+j2 & 3 & -1 \\ -2j & 0 & +j3 \\ -1 & 6 & 1-j3 \end{bmatrix}$$

$$\Delta_3 = \begin{bmatrix} 1+j2 & -2j & -1 \\ -2j & 2-j1 & +j3 \\ -1 & +j3 & 6 \end{bmatrix}$$

$$I_1 = \Delta_1 / \Delta = 5.26 \angle -41.25^\circ$$

$$I_2 = \Delta_2 / \Delta = 3.18 \angle -45^\circ$$


$$I_3 = \Delta_3 / \Delta = 3.39 \angle -1.03^\circ$$

4

Current division

Notes

$$I_2 = I - I_1$$

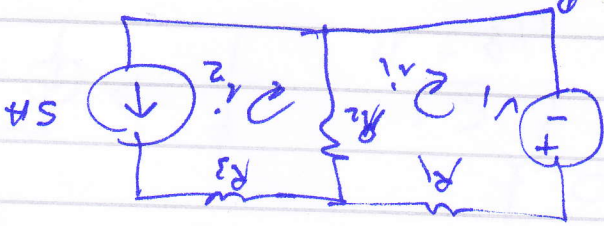


$$I_1(R_1 + R_2) - I_2 R_2 = +V_1$$

Loop 2

$$I_1 = I_2 - I_1$$

Loop 1

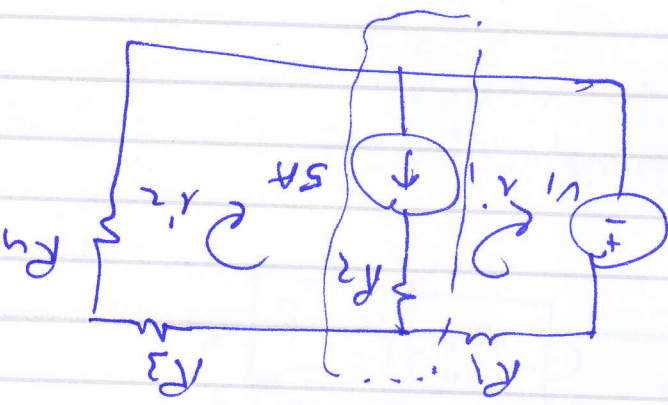


$$I_1(R_1) + I_2(R_2 + R_3) = +V_1$$


correct : C:5

Nodal Analysis

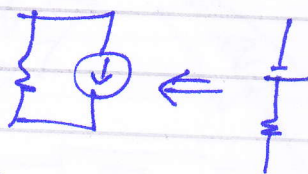- a. Select Ref Point
- b. Convert v.s to c.s



Notes

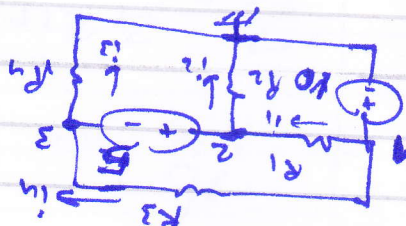


$$\begin{matrix} 1- & v_2 - v_3 = v_2 \\ 2- & v_1 - v_3 = v_2 \end{matrix}$$

at (2,3) $v_1 + v_2 = v_3$

$$\frac{v_1 - v_2}{R_1} + \frac{v_1 - v_3}{R_3} = \frac{v_2 - v_3}{R_2} + \frac{v_3 - v_4}{R_4}$$

ex (3) ... sheet 11

Nodal

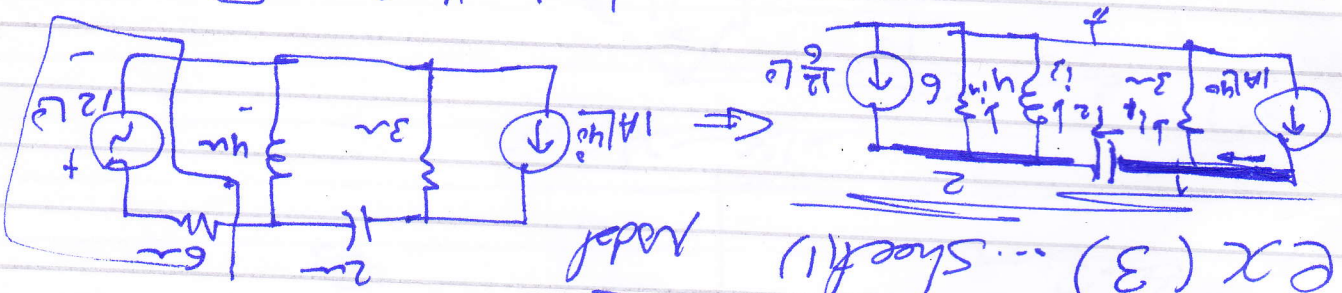


$$\begin{aligned} \text{at 1} \quad 14 = i_1 + i_2 \\ \text{at 2} \quad 2i_3 + i_2 = i_3 + i_4 \\ i_2 = \frac{v_1 - v_2}{1} = (v_1 - v_2) \\ i_3 = \frac{v_2 - v_3}{2} = \frac{v_2 - v_3}{2} \\ i_4 = \frac{v_3 - v_4}{12} = \frac{v_3 - v_4}{12} \end{aligned}$$

$$\begin{aligned} v_1 &= 5.29 \angle 48.75^\circ \\ v_2 &= 5.81 \angle 33.27^\circ \end{aligned}$$

6


$$4 - (\Delta - Y) \& (Y - \Delta)$$

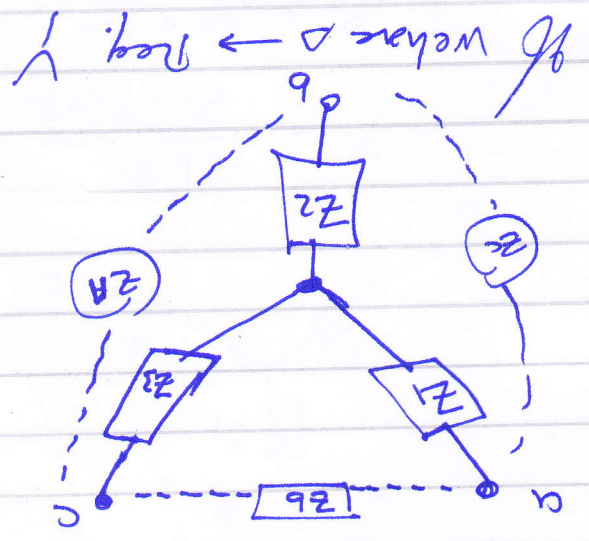

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_a Z_c}{Z_a + Z_b + Z_c}$$
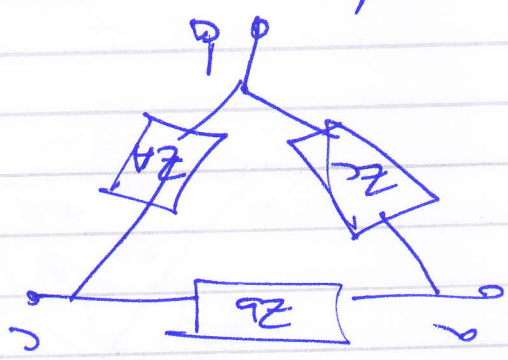
$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$




if we have $Y \rightarrow \text{Req } \Delta$

$$Z_a = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_3}$$


$$Z_b = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_2}$$
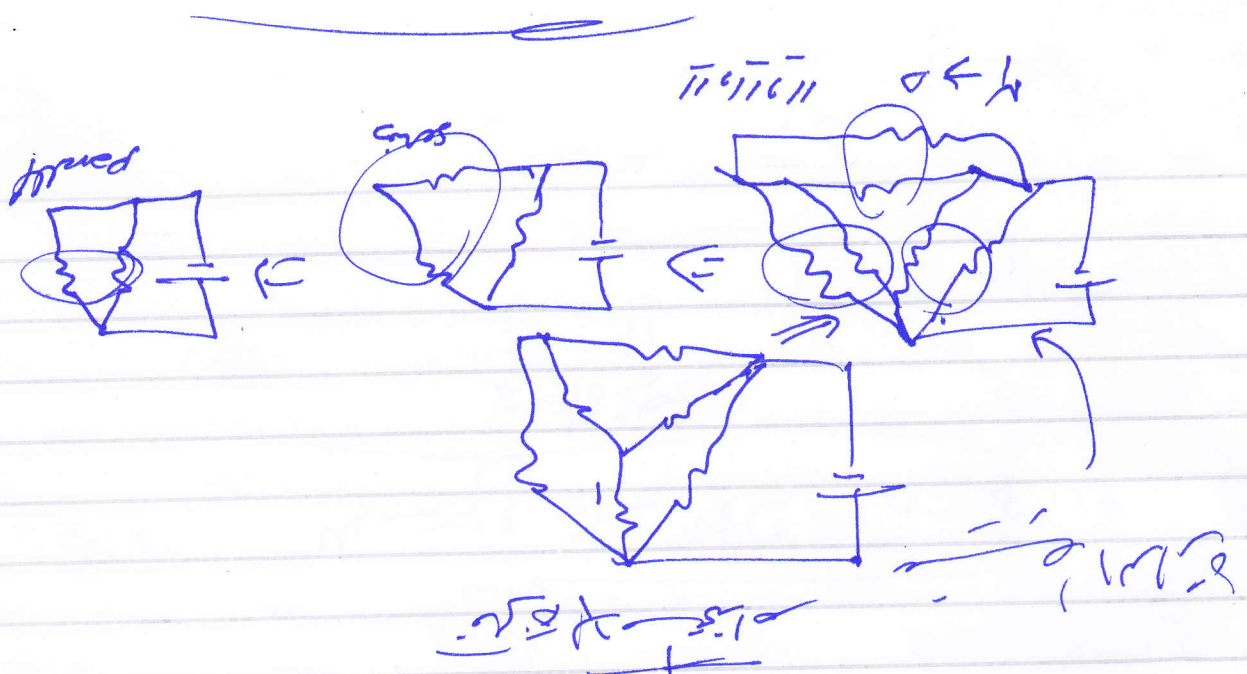
$$Z_c = \frac{Z_1 Z_2 + Z_1 Z_3 + Z_2 Z_3}{Z_1}$$



7

ex (4) star (1)

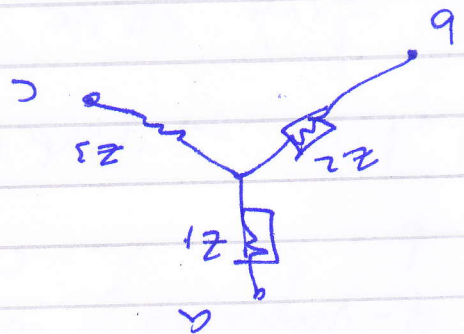

$$z_1 = \frac{z_2 z_3}{z_1 + z_2 + z_3} = \frac{-j6 \times 3}{-j6 + j9 + 3} = \frac{-j18}{3 + j3} = \frac{-j18}{4.24 \angle 45^\circ} = -j4.24 \angle -90^\circ$$


$$z_2 = \frac{z_1 + z_3}{z_1 + z_2 + z_3} = \frac{j27}{3 + j3} = \frac{j27}{4.24 \angle 45^\circ} = j6.36 \angle -45^\circ$$

$$z_3 = \frac{z_1 + z_2}{z_1 + z_2 + z_3} = \frac{j54}{3 + j3} = \frac{j54}{4.24 \angle 45^\circ} = j12.73 \angle -45^\circ$$

$$z_1 = -3 + j3$$

$$z_2 = 4.5 + j4.5$$

$$z_3 = 9 - j9$$

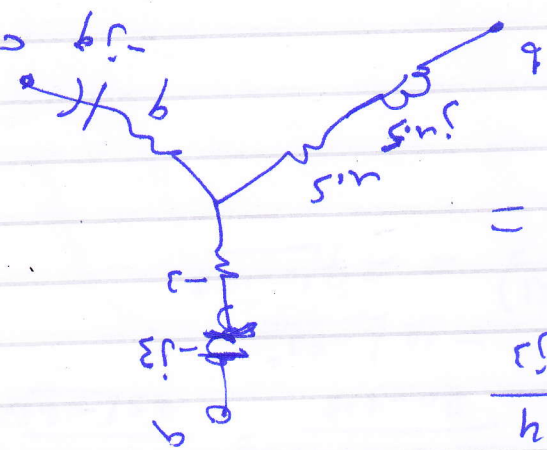

Self study


5 - Superposition

a- Replace of v.s by 5.5
b - / / / / / c.i. by o.c

Sheet (11) → Prob (5)

find $V_{R1} V_C$

[a]

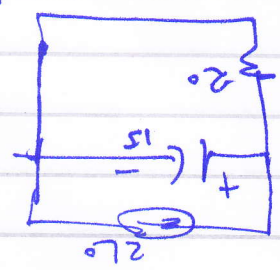


$$Z = R // X_C = 20 // -j15 =$$

$$= \frac{20 \times 15 \angle -90^\circ}{20 - j15} = \frac{300 \angle -90^\circ}{25 \angle -36.87^\circ} = 12 \angle -53^\circ$$

here $V_{R1} = V_C = I \times Z = (2 \angle 0^\circ) (12 \angle -53^\circ) = 24 \angle -53^\circ$

[b]

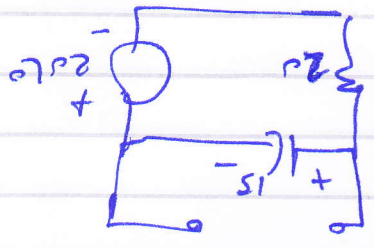

$$V_{R2} = 20 \angle 0^\circ \times \frac{20}{20 + j15} = 16 \angle -36.87^\circ$$

$$V_{Total} = 20 \angle 0^\circ \therefore V_{C2} = \frac{20 \angle 0^\circ \times 15 \angle -90^\circ}{20 - j15} = -15 \angle 90^\circ \times 20 = 20 \angle 15^\circ$$

$$V_{Rtotal} = V_{R1} + V_{R2} = 24 \angle -53^\circ + 16 \angle -36.87^\circ = 28.8 \angle -42.44^\circ$$

$$V_{Ctotal} = V_{C1} + V_{C2} = 12 \angle -53^\circ$$