

Section (10)

"2114/2015"

2114/2015

1] DC RLC

Case I $\text{if } (\frac{R}{2L})^2 > \frac{1}{LC}$ overdamped

∴ $i = c_1 e^{(\alpha+\beta)t} + c_2 e^{(\alpha-\beta)t}$

or $i_1 = e^{\alpha t} (c_1 e^{\beta t} + c_2 e^{-\beta t})$

$$\alpha = -R/2L$$

$$\beta = \sqrt{(\frac{R}{2L})^2 - (\frac{1}{LC})}$$

$D_1 = \alpha + \beta$

$D_2 = \alpha - \beta$

Case II $\text{if } (\frac{R}{2L})^2 = \frac{1}{LC}$ critically damped

$$i_2 = e^{\alpha t} (c_1 + c_2 t)$$

Case III $\text{if } (\frac{R}{2L})^2 < \frac{1}{LC}$ underdamped

$$i_3 = e^{\alpha t} (c_1 \cos \beta t + c_2 \sin \beta t)$$

at $t=0 \rightarrow i=0$
 KVL $V = iR + L \frac{di}{dt} + \frac{q}{C}$
 at $t=0, i=0, q=0$
 $V = L \frac{di}{dt}$
 $\frac{di}{dt} = \frac{V}{L}$
 initial slope

2] AC RLC

Case I overdamped $(\frac{R}{2L})^2 > \frac{1}{LC}$

$$i_1 = e^{\alpha t} (c_1 e^{\beta t} + c_2 e^{-\beta t}) + \frac{V_{max}}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \sin(\omega t + \phi + \tan^{-1}(\frac{1/\omega C - \omega L}{R}))$$

Case II

critically damped $(\frac{R}{2L})^2 = \frac{1}{LC}$

$$i_2 = e^{\alpha t} (c_1 + c_2 t) + I_p$$

Case III underdamped $(\frac{R}{2L})^2 < \frac{1}{LC}$

$$i_3 = e^{\alpha t} (c_1 \cos \beta t + c_2 \sin \beta t) + I_p$$

3] AC-RL-

$i = i_p + i_c$

$i_c = C e^{mt}$

$i_p = \frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1}(\frac{\omega L}{R}))$

at $t=0 \rightarrow i=0$

~~at $t=0, i=0$~~
~~at $t=0, i=0$~~
~~at $t=0, i=0$~~

4] AC-RC

$i = i_p + i_c$

$i_c = C e^{mt}$

$i_p = \frac{V_{max}}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \sin(\omega t + \phi + \tan^{-1}(\frac{1}{\omega RC}))$

at $t=0 \rightarrow i=?!$ KVL

at $t=0, i=?!$ KVL
 at $t=0, i=?!$ KVL

[1] A series RLC with $R=3000\ \Omega$, $L=10\text{h}$, $C=200\text{MF}$ has a constant $V=50\text{V}$ applied at $t=0$. Find the current transient and the maximum value of the current i if the capacitor has no initial charge.

Solution

$$50 = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

$$50 = 3000i + 10 \frac{di}{dt} + \frac{1}{200 \times 10^{-6}} \int i dt \quad \text{بتفاضل الطرفين} \quad (1)$$

or $(D^2 + 300D + 500) i = 0$

or $D_1 = -298.3$, $D_2 = -1.67$

كل الجذور حقيقية سالبة

$$D = \frac{-B \pm \sqrt{B^2 - 4AC}}{2A} = \alpha \pm \beta$$

$$i = C_1 e^{-0.167t} + C_2 e^{-298.3t} \quad (2)$$

Note $(\frac{R}{L})^2 > \frac{1}{LC}$

to find C_1, C_2

at $t=0, 0^+ \rightarrow i=0$ SW in 1, 2

$$0 = C_1 + C_2 \rightarrow (3)$$

and at $t=0 \rightarrow 50 = 10 di/dt$ or $(di/dt = 5) \rightarrow (4)$

at $t=0$ is $di/dt = 5$ بتفاضل الطرفين

$$5 = (-0.167)C_1 e^{-0.167t} - (298.3)C_2 e^{-298.3t}$$

$$5 = -0.167 C_1 - 298.3 C_2 \rightarrow (6)$$

كل المعادلتين 6 و 3 نضرب
 $-0.0168 C_2 + 0.168 = C_1$

$$i = 0.0168 e^{-1.67t} - 0.0168 e^{-298t}$$

to find max current \therefore at $\frac{di}{dt} = 0$ (القيمة العظمى)

or $(0.0168)(-1.67) e^{-1.67t} - (0.0168)(-298.3) e^{-298t} = 0$

$\rightarrow t = 0.0175 \text{ sec}$

- 2 -

[2] A series RL circuit with $R = 50 \Omega$ and $L = 0.2 \text{ H}$ has a sinusoidal voltage source $v = 150 \sin(500t + \phi)$ applied at a time when $\phi = 0$. Find complete current.

- Sol -

$$Ri + L \frac{di}{dt} = v$$

$$50i + 0.2 \frac{di}{dt} = 150 \sin 500t$$

$$\therefore (D + 250)i = 750 \sin 500t$$

→ complementary sol. $i_c = e^{-250t}$

Use Final equation = $C e^{-250t} + i_p$

$$i = \frac{V_{\max}}{P \sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \tan^{-1}(\frac{\omega L}{R}))$$

$$= \frac{150}{\sqrt{(50)^2 + (500)^2 (0.2)^2}} \sin(500t + 0 - \tan^{-1}(\frac{500 \times 0.2}{50}))$$

$$i(t) = C e^{-250t} + 1.34 \sin(500t - 63.4^\circ)$$

$$\text{at } t=0, i=0$$

$$\therefore 0 = C + 1.34 \sin(-63.4^\circ)$$

$$\therefore C = 1.2$$

$$\therefore i_t = 1.2 e^{-250t} + 1.34 \sin(500t - 63.4^\circ)$$

3] Series RC with $R=100$, $C=25\mu\text{f}$, sinusoidal voltage $250 \sin(500t + \phi)$, applied at a time when $\phi=0$. Find i (no initial voltage on cap)

OR ☞ $100i + \frac{1}{C} \int i dt = 250 \sin 500t$
 $(\phi + 400) i = 1250 \cos(500t)$ جواب

Sol $i = C e^{-400t} + \frac{V_{\text{max}}}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \sin(\omega t + \phi + \tan^{-1}(\frac{1}{\omega RC}))$

$i = C e^{-400t} + 1.955 \sin(500t + 38.7^\circ)$
at $t=0 \rightarrow i = \frac{250}{100} \sin 0 = 2.5$
o.c. cap t=0 is ideal

$\Rightarrow 2.5 = C e^{400 \times 0} + 1.955 \sin(0 + 38.7)$

$\therefore C = -1.22$


$\Rightarrow i = -1.22 e^{-400t} + 1.955 \sin(500t + 38.7^\circ)$

4 in RC circuit shown $v = 250 \sin(500t + \phi)$

at $\phi = 45^\circ \rightarrow$ switch closed, initial charge

$q_0 = 5000 \times 10^{-6} \text{ Col.}$ on capacitor with shown Polarity, Find i

Sol
 حل
 الحل

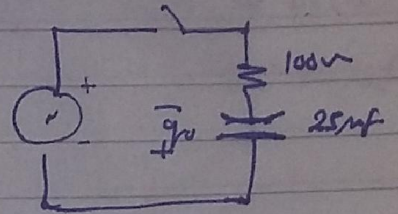

$$i = C e^{-400t} + 1.955 \sin(500t + \phi + 38.7)$$

$$= C e^{-400t} + 1.955 \sin(500t + 83.7^\circ)$$

$$\text{at } t=0 \quad i = \frac{v_{in} + V_c}{100} = \frac{(250 \sin 45) + \frac{q_0}{C}}{100} \rightarrow 200V$$

$$i = (250 \sin 45 + 200) / 100 = 3.77$$

$$\therefore \text{at } t=0 \rightarrow i = 3.77 A$$

$$3.77 = C e^0 + 1.955 \sin(\alpha + 83.7^\circ)$$

$$C = 1.83$$


$$\therefore i = 1.83 e^{-400t} + 1.955 \sin(500t + 83.7^\circ)$$

5] Series RLC has source $100 \sin(1000t + \phi)$, if switch closed $\therefore \phi = 90$, find i if no initial voltage on cap

sol.

$$50i + 0.1 \frac{di}{dt} + \frac{1}{50 \times 10^{-6}} \int i dt$$
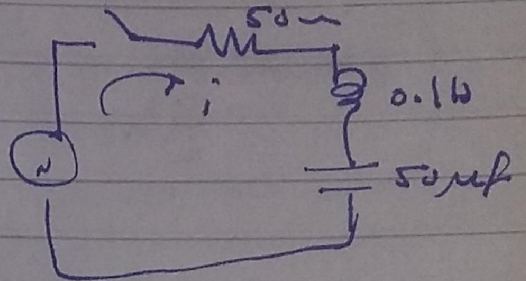
$$= 100 \sin(1000t + \phi) \rightarrow \text{I}$$



تفاضل، لطیف رضی اللہ عنہ

$$(D^2 + 500D + 2 \times 10^6) i = 10^6 \sin(1000t + 90^\circ) \rightarrow \text{II}$$

$$D_1 = -250 + j371$$

$$D_2 = -250 - j371$$

$$i_c = e^{\alpha t} [C_1 \cos \beta t + C_2 \sin \beta t] \quad \left(\frac{R}{2L} \right)^2 < \frac{1}{LC}$$

$$i_c = e^{-250t} [C_1 \cos 371t + C_2 \sin 371t] \rightarrow \text{III}$$

$$i_p = \frac{V_{max}}{\sqrt{R^2 + (\frac{1}{\omega C} - \omega L)^2}} \sin \left[\omega t + \phi + \tan^{-1} \left(\frac{\frac{1}{\omega C} - \omega L}{R} \right) \right] \rightarrow \text{IV}$$

$$i_p = 1.06 \sin(1000t + 32) \rightarrow \text{V}$$

$$\therefore i = e^{-250t} [C_1 \cos 371t + C_2 \sin 371t] + 1.06 \sin(1000t + 32)$$

at $t=0 \rightarrow i_0 = 0$ eq I $\therefore 0.1 \frac{di}{dt} = 100 \sin 90$
 $\therefore \frac{di}{dt} = 1000$

$$0 = e^0 [C_1 \cos 0 + C_2 \sin 0] + 1.06 \sin 32$$

$$\frac{di}{dt} = (1.06)(1000) \cos(1000t + 32) +$$

$$-250 e^{-250t} [C_1 \cos 371t + C_2 \sin 371t] + e^{-250t} [-371 C_1 \sin 371t + 371 C_2 \cos 371t]$$

$C_2 = 1000 = \frac{di}{dt}$ at $t=0$

-6-

$$C_1 = -0.562$$

→

$$C_2 = -0.104$$

$$i = e^{-250t} \left[-0.562 \cos 371t - 0.104 \sin 371t + 1.06 \sin(1000t + 32^\circ) \right]$$

(حالة التخميد)

1 - Underdamped
 $D_1 = \alpha + \beta$

$D_2 = \alpha - \beta$

$$\left(\frac{R}{2L} \right)^2 < \frac{1}{LC}$$

$$i_t = e^{\alpha t} [C_1 e^{\beta t} + C_2 \sin \beta t] +$$

$$\frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L \right)^2}} \sin \left[\omega t + \phi + \tan^{-1} \left(\frac{\frac{1}{\omega C} - \omega L}{R} \right) \right]$$

2 - $\left(\frac{R}{2L} \right)^2 = \frac{1}{LC}$ Critically damped


$$i_{total} = e^{\alpha t} [C_1 + C_2 t] + \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L \right)^2}} \sin \left(\omega t + \phi + \tan^{-1} \left(\frac{\frac{1}{\omega C} - \omega L}{R} \right) \right)$$

3 - $\left(\frac{R}{2L} \right)^2 > \frac{1}{LC}$ overdamped

$$i_{total} = e^{\alpha t} [C_1 e^{\beta t} + C_2 e^{-\beta t}] + I_p$$

$$\left(\frac{R}{2L} \right)^2 > \frac{1}{LC} \Rightarrow \alpha > \beta \Rightarrow I_c < I_p$$

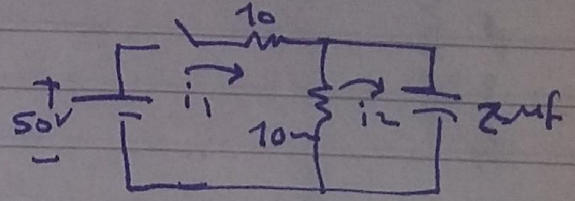(6) in two mesh shown in fig, switch closed at $t=0$
 Find transient mesh current i_1 and i_2 shown
 and V_c



at S closed sol

loop 1 $50 = 20i_1 - 10i_2$

$\therefore 0 = 20Di_1 - 10Di_2$ تفاضل الطرفين
 or $2Di_1 = Di_2$ (1)

loop 2 $0 = 10i_2 - 10i_1 + \frac{1}{C} \int i_2 dt$ تفاضل الطرفين

$0 = 10Di_2 - 10Di_1 + \frac{1}{C} i_2$
 or $-Di_1 + i_2(D + \frac{1}{10C}) = 0$ (2)

$-Di_1 + i_2(D + 5 \times 10^4) = 0$ (2)

بالتعويض من (1) في (2)

$\therefore -\frac{Di_2}{2} + (D + 5 \times 10^4)i_2 = 0$

or $(D + 10^5)i_2 = 0$

\therefore sol $i_2 = A e^{2t} = A e^{-10^5 t}$

at $t=0 \rightarrow$ From eq 2 $\therefore 0 = 10i_2 - 10i_1$

$\therefore i_1 = i_2$

From (1) $50 = 20i_1 - 10i_2 = 10i_2 = 10i_1$ والتعويض في (1)

$\therefore i_1 = i_2 = 5$
 \therefore at $t=0, i_2 = 5 = A e^0 \therefore A = 5$

so $i_2 = 5 e^{-10^5 t}$

$50 = 20i_1 - 10 \times 5 e^{-10^5 t}$ بالتعويض في (1) معادله

so $i_1 = \frac{5}{2} + \frac{5}{2} e^{-10^5 t}$

$V_c = \frac{1}{C} \int i_2 dt$
 $V_c = 25(1 - e^{-10^5 t})$

① RLC (DC) $\rightarrow \alpha = \frac{R}{2L}, \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}$

↓ $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$ overdamped

$i = e^{\alpha t} (c_1 e^{\beta t} + c_2 e^{-\beta t})$
 or $e^{(\alpha+\beta)t} + c_2 e^{(\alpha-\beta)t}$
 $= i_c$

$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$ critically damped

$i = e^{\alpha t} (c_1 + c_2 t)$
 $= i_c$

$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$ underdamped

$i = e^{\alpha t} [c_1 \cos \beta t + c_2 \sin \beta t]$
 $= i_c$

② RLC (AC) $i_c =$ dc response
 $i = i_c + i_p$

$i = i_c + i_p, i_c =$ dc response

$i = i_c + i_p, i_c =$ dc response

$I_p = \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}}$

$\sin(\omega t + \phi + \tan^{-1}\left(\frac{1/\omega C - \omega L}{R}\right))$

at $t=0 \rightarrow i \rightarrow$ calc. from KVL original equation to find $i(0)$
 to find $i(0)$ \rightarrow then sub in $i(t)$ to calc $i(0)$

من الجيب
 في الت
 في الت
 في الت

③ RL (AC)

$i = i_p + i_c \rightarrow i(0) = ? = 0$
 $i_c = C e^{mt}$

$i_p = \frac{V_{max}}{\sqrt{R^2 + (\omega L)^2}} \sin(\omega t + \phi - \tan^{-1}\left(\frac{\omega L}{R}\right))$

at $t=0 \rightarrow i=0$

من الجيب في الت

④ RC (AC)

$i = i_p + i_c \rightarrow i(0) = ? = 0$
 $i_c = C e^{mt}$

$i_p = \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \sin(\omega t + \phi + \tan^{-1}\left(\frac{1}{\omega RC}\right))$

at $t=0 \rightarrow i =$

من الجيب في الت