

Sec (11)

Laplace + Transient

3/5 - 5/5

Sheet (9)

[1] In RC Series Circuit, capacitor is initially charged with $q = 2500 \times 10^{-6} \text{ Col.}$, at $t=0$ switch closed, a constant supply 100V applied to The circuit find The Current Using Laplace.

Sol

$$V = Ri + \frac{1}{C} \int i dt$$

$$100 = 10i + \frac{1}{50 \times 10^{-6}} \int i dt \rightarrow (1)$$

Taking Laplace Transform of Previous equation

in S-domain

$$\frac{100}{s} = 10I(s) + \frac{I(s)}{50 \times 10^{-6} s} + \frac{q_0}{50 \times 10^{-6} s}$$

→ initial condition


$$I(s) = \left[\frac{100}{s} + \frac{2500 \times 10^{-6}}{50 \times 10^{-6} s} \right] / \left[10 + \frac{1}{50 \times 10^{-6} s} \right]$$

$$I(s) = \left[\frac{150}{s} \right] / \left[10 + \frac{2 \times 10^4}{s} \right]$$


$$I(s) = \frac{150}{10s + 2 \times 10^4} = \frac{15}{s + 2 \times 10^3}$$

Take inverse Laplace $L^{-1}(I(s))$


$$I(t) = 15 e^{-2 \times 10^3 t}$$

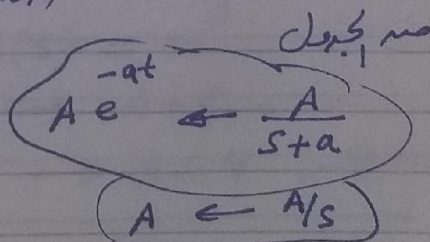

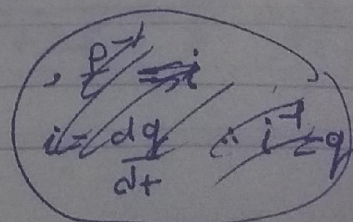Note $\int i dt = \frac{I(s)}{s} + \frac{V_C(0^+)}{s}$



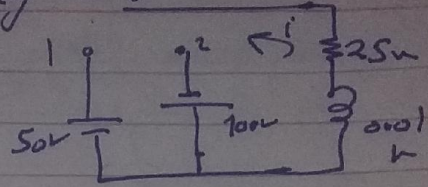2] at RL circuit, S is in position 1 long enough to establish steady state condition and at $t=0$ switched to Pos 2 Find I.



sol

$$100 = 25i + (0.01) di/dt \rightarrow \text{① at Pos 2}$$

Note at pos 1 \rightarrow steady state So $i = \frac{50}{25} = 2A$

Taking Laplace of ① $\rightarrow \int \frac{di}{dt} = sI(s) - I(0^+)$

$$\therefore \frac{100}{s} = 25I(s) + [0.01 I(s)]s - 0.01 I(0^+)$$

$$\therefore \frac{100}{s} = 25I(s) + 0.01sI(s) - 0.01 \times (2)$$

$$I(s) = \frac{100}{s(0.01s+25)} = \frac{2 \times 0.01}{(0.01s+25)} = \frac{10^4}{s(s+2500)} - \frac{2}{s+2500}$$

$$I(s) = \frac{10^4}{s(s+2500)} - \frac{2}{s+2500} = \left[\frac{A}{s} + \frac{B}{s+2500} - \frac{2}{s+2500} \right]$$

$$\text{Now } \frac{10^4}{s(s+2500)} = \frac{A}{s} + \frac{B}{s+2500}$$

$$\text{or } A(s+2500) + B(s) = 10^4$$

$$As + Bs = 0 \rightarrow A+B=0$$


$$A(2500) = 10^4 \rightarrow A=4, B=-4$$

$$\therefore I = \frac{4}{s} - \frac{4}{s+2500} - \frac{2}{s+2500} = \frac{4}{s} - \frac{6}{s+2500}$$

$$\therefore I(t) = 4 - 6e^{-2500t}$$

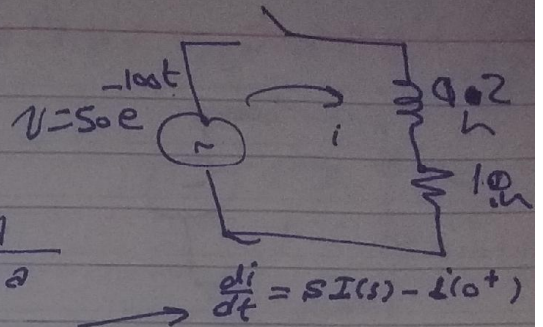3) Find i

$$50 e^{-100t} = 10i + 0.2 \frac{di}{dt}$$



Take Laplace

$$Ae^{-at} \rightarrow \frac{A}{s+a}$$

$$\frac{50}{s+100} = 10I(s) + 0.2sI(s) - 0.2i(0^+)$$

$$\therefore \frac{50}{s+100} = I(s) [10 + 0.2s]$$

$$I(s) = \frac{50}{(s+100)(0.2s+10)} = \frac{50}{(s+100)(s+50) \cdot 0.2}$$

$$I(s) = \frac{250}{(s+100)(s+50)} = \frac{A}{s+100} + \frac{B}{s+50}$$

$$\therefore A(s+50) + B(s+100) = 250$$

$$\therefore sA + Bs = 0 \quad \text{or} \quad \underline{A = -B}$$

$$50A + 100B = 250$$


$$\text{or} \quad 50B = 250, \quad B = 5, \quad A = -5$$

$$\therefore I(s) = \frac{-5}{s+100} + \frac{5}{s+50}$$

$$\therefore I(t) = -5e^{-100t} + 5e^{-50t}$$

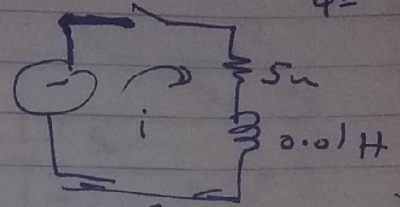4) series RL $\Rightarrow V = 100 \sin(500t + \phi)$, find I of s closed at $t = 0$
 $R = 5 \Omega$

$100 \sin(500t + \phi) = 5i + 0.01 \frac{di}{dt}$
 - take Laplace -



$$5I(s) + 0.01sI(s) - 0.01 i(0^+) = \frac{100 \sin(500t + 500 \times 0)}{s^2 + (500)^2}$$

$$5I(s) + 0.01s = 0.01 \times \text{zero} + \frac{(100)(500)}{s^2 + (500)^2}$$

$$I(s) [0.01s + 5] = \frac{5 \times 10^4}{s^2 + (500)^2}$$

$$I(s) = \frac{5 \times 10^4}{(0.01s + 5)(s^2 + 500^2)} = \frac{5 \times 10^6}{(s + 500)(s^2 + 500^2)}$$

$$I(s) = \frac{5 \times 10^6}{(s + 500)(s + j500)(s - j500)} = \frac{A}{(s + 500)} + \frac{B}{s + j500} + \frac{C}{s - j500}$$

$a_1 = -500, a_2 = -j500, a_3 = j500$

$$i(t) = \frac{P(a_1)}{Q'(a_1)} e^{-500t} + \frac{P(a_2)}{Q'(a_2)} e^{-j500t} + \frac{P(a_3)}{Q'(a_3)} e^{j500t}$$

where $P(a_1) = P(a_2) = P(a_3) = 5 \times 10^6$

$$Q(s) = s^3 + 5s^2 + (500)^2s + (500)^2 \times 5$$

$$Q'(s) = 3s^2 + 10s + (500)^2$$

$$Q'(a_1) = 3(-500)^2 - 10 \times 500 + (500)^2 = 10 \times 10^4$$

$$Q'(a_2) = 3(-500)^2 + 10 \times -j500 + (500)^2 = \checkmark$$


$$Q'(a_3) = 3(500)^2 + 10 \times j500 + (500)^2 = \checkmark$$

$$i(t) = 10 \sin 500t - 10 e^{-500t} + 10 e^{500t}$$

OR By Partial Fraction $\rightarrow i = 5 \left(\frac{-1+j}{s+j500} \right) + 5 \left(\frac{-1-j}{s+500} \right) + \frac{10}{s+500}$

(5) in series RLC, no initial charge on cap, at $t=0$ close $\frac{S}{\text{}} \text{, find } i$

Sol

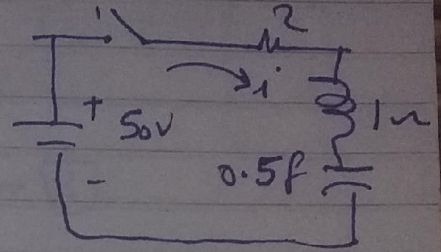

$$50 = 2i + 1 \frac{di}{dt} + \frac{1}{0.5} \int i dt$$

Take Laplace \rightarrow

$$\frac{50}{s} = 2I(s) + [sI(s) - i(0^+)] + \frac{1}{0.5} \left[\frac{I(s)}{s} + \frac{1}{s} \right]$$

$$\frac{50}{s} = 2I(s) + sI(s) + \frac{2}{s} I(s)$$

$$\frac{50}{s} = I(s) \left[2 + s + \frac{2}{s} \right]$$

$$50 = I(s) [2s + s^2 + 2]$$

$$I(s) = \frac{50}{s^2 + 2s + 2} = \frac{50}{(s+1+j)(s+1-j)}$$

$$I(s) = \frac{A}{s+1+j} + \frac{B}{s+1-j}$$

By partial Fraction

$$A = j25, B = -j25$$

$$\therefore I(s) = \frac{j25}{s+1+j} - \frac{j25}{s+1-j}$$


$$i = j25 e^{-(1+j)t} - j25 e^{-(1-j)t}$$

$$= 50 e^{-t} \sin t$$

$$e^{jx} = \cos x + j \sin x$$

where

6) In two mesh find currents i_1, i_2

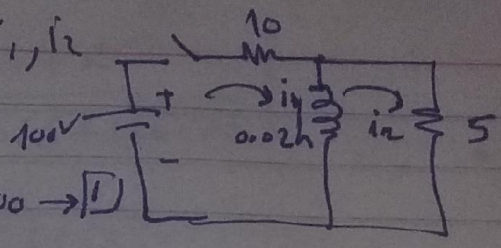

$$10 i_1 + 0.02 \frac{di_1}{dt} - 0.02 \frac{di_2}{dt} = 100 \rightarrow [1]$$

$$0.02 \frac{di_2}{dt} - 0.02 \frac{di_1}{dt} + 5 i_2 = 0 \rightarrow [2]$$

Take Laplace for 2 equations

$$10 I_1(s) + 0.02 [s I_1(s) - i_1(0^+)] - 0.02 [s I_2(s) - i_2(0^+)] = \frac{100}{s}$$

$$\therefore I_1(s) [10 + 0.02s] - I_2(s) [0.02s] = \frac{100}{s} \rightarrow [1]$$

$$\text{or } 5 I_2(s) + 0.02 [s I_2(s) - i_2(0^+)] - 0.02 [s I_1(s) - i_1(0^+)] = 0$$

$$\therefore I_1(s) [-0.02s] + I_2(s) [5 + 0.02s] = 0 \rightarrow [2]$$

$$\therefore \text{From eq (2)} \quad I_2(s) = \frac{+0.02s I_1(s)}{5 + 0.02s} = \frac{s I_1(s)}{\frac{5}{0.02} + s}$$

$$I_2(s) = I_1(s) \frac{s}{s + 250} \rightarrow [3]$$

$$\text{From (1)} \quad I_1(s) [10 + 0.02s] - \left(\frac{s}{s + 250} \right) \times (0.02s) I_1(s) = \frac{100}{s}$$

$$I_1(s) \left[10 + 0.02s - \frac{0.02s^2}{s + 250} \right] = \frac{100}{s}$$

$$I_1(s) \left[\frac{2500 + 10s + 0.02s^2 + 5s - 0.02s^2}{s + 250} \right] = \frac{100}{s}$$

$$I_1(s) = \frac{25000 + 100s}{s(15s + 2500)} = \frac{\frac{1}{15} \times 100 (s + 250)}{s(s + 166.7)}$$

- 7 -

$$I_1(s) = 6.67 \left\{ \frac{s + 250}{s(s + 166.7)} \right\}$$

$$= \frac{6.67s}{s(s + 166.7)} + \frac{6.67 \times 250}{s(s + 166.7)}$$

$$I_1(s) = \frac{6.67}{s + 166.7} + \frac{A}{s} + \frac{B}{s + 166.7}$$

$$A(s + 166.7) + Bs = 6.67 \times 250$$

$$A(166.7) = 6.67 \times 250 \quad (A = 10)$$

$$As + Bs = 0 \quad \text{or } A = -B \Rightarrow B = -10$$

$$\therefore I_1(s) = \frac{6.67}{s + 166.7} + \frac{10}{s} - \frac{10}{s + 166.7}$$

$$\text{or } I_1(s) = \frac{10}{s} - \frac{3.33}{s + 166.7}$$

$$i_1 = 10 - 3.33 e^{-166.7t}$$

$$I_2(s) = I_1(s) \frac{s}{s + 250} = 6.67 \frac{s + 250}{s(s + 166.7)} \frac{s}{s + 250}$$

$$I_2(s) = \frac{6.67}{s + 166.7}$$

$$\therefore I_2(t) = 6.67 e^{-166.7t}$$

خلاصہ لقوائے (لکھو)

$f(t)$	Laplace $f(s)$
1] A $t \geq 0$	A/s
2] At	A/s^2
3] e^{-at}	$\frac{1}{s+a}$
4] te^{-at}	$\frac{1}{(s+a)^2}$
5] $\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
6] $\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
7] $\sin(\omega t + \phi)$	$\frac{s \sin \phi + \omega \cos \phi}{s^2 + \omega^2}$
8] $\cos(\omega t + \phi)$	$\frac{s \cos \phi - \omega \sin \phi}{s^2 + \omega^2}$
9] $\frac{di}{dt}$	$sI(s) - i(0^+)$
10] $\int i dt$	$\frac{I(s)}{s} + \frac{V_c \text{ initial}}{s} \rightarrow q/c$
11]	