

Electrical Circuits (2)

Section (3)

1/3/2015 → 3/3/2015


1) What is Resonance

- Frequency Selectivity in Radio and Communication Cir.Cut.
- Resonance circuit pass range of Freq. & Reject other.

→ Filter Response

→ f_r Resonance Freq. (center)

→ BW Bandwidth (passband) = $f_2 - f_1$

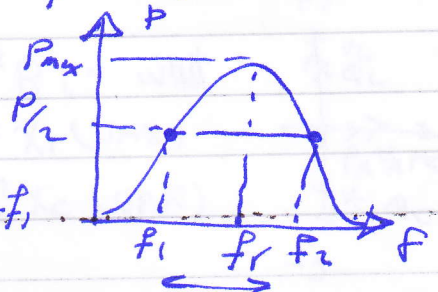


→ Resonance circuit consists of L, C, supply voltage & current.

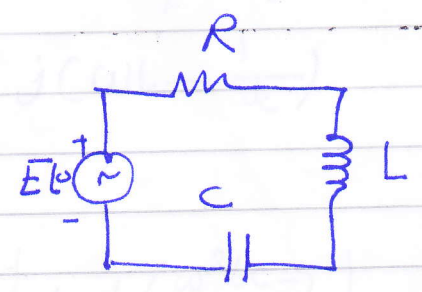2) Series Resonance

Total impedance (Z_t)

$$\begin{aligned}
 Z_t &= R + jX_L - jX_C \\
 &= R + j(X_L - X_C) \\
 &= R + j(\omega L - \frac{1}{\omega C})
 \end{aligned}$$



→ Condition of series Resonance $X_L = X_C$ or $Z_t = R$

∴ $\omega L = \frac{1}{\omega C}$ or $\omega^2 = \frac{1}{LC}$

∴ $\omega_0 = \frac{1}{\sqrt{LC}}$ rad/s or $f_0 = \frac{1}{2\pi\sqrt{LC}}$ Hz

[2]

[3] Analysis of RLC series circuit

$$Z_t = R \quad (\text{at resonance only})$$

$$I = \frac{E L_0}{Z} = \frac{E L_0}{R}$$

$$U_R = I R L_0$$


$$U_L = I X_L \angle 90^\circ$$

$$U_C = I X_C \angle -90^\circ$$

$$\leftrightarrow P_r = I^2 R L_0 \text{ watt}$$

$$\leftrightarrow Q_L = I^2 X_L \text{ (VAR)}$$
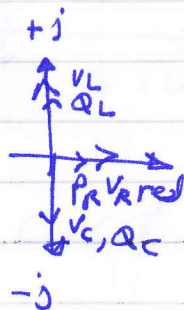
$$\leftrightarrow Q_C = I^2 X_C \text{ (VAR)}$$




[4] impedance of Series RLC versus frequency.



$$Z = R + j\omega L - j\frac{1}{\omega C} = R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$= R + j\left(\frac{\omega^2 LC - 1}{\omega C}\right)$$

$$= \underbrace{\sqrt{R^2 + \left(\frac{\omega^2 LC - 1}{\omega C}\right)^2}}_{\text{Magnitude}} \quad \left| \underbrace{\tan^{-1}\left(\frac{\omega^2 LC - 1}{\omega RC}\right)}_{\text{Phase}} \right.$$

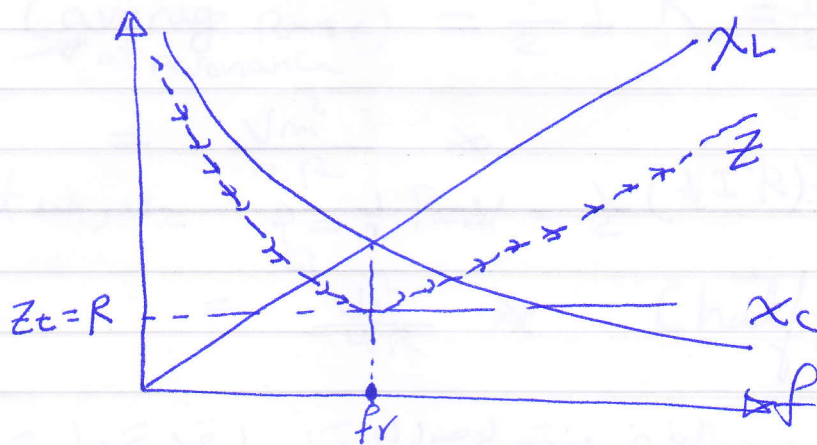Note at $\omega = \omega_s \rightarrow Z_t = R, \theta = 0^\circ$



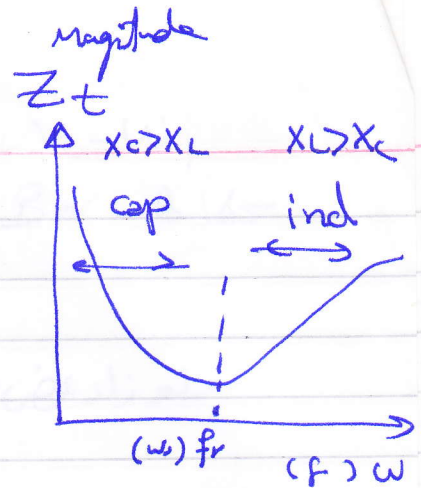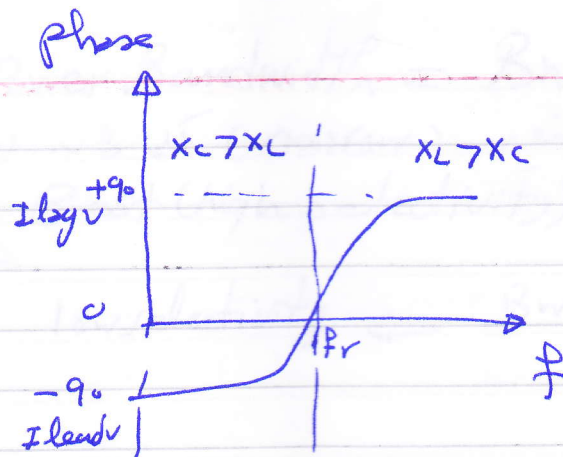

[5] Current and Power in series Resonance Circuit


→ (Resonance)

$$I = \frac{V}{Z} = \frac{V_m \angle 0}{R}$$

$I_{max} = V_m/R$

$Z = R$ (resonance)


$V_s = V_m \angle 0$

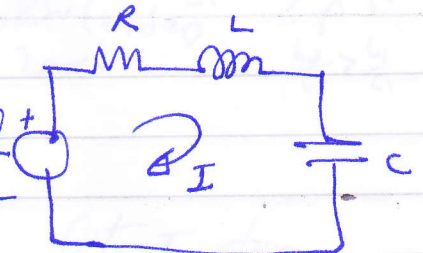

→ (Not resonance)

$I = |I| = \frac{V_m}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}}$

↓
magnitude

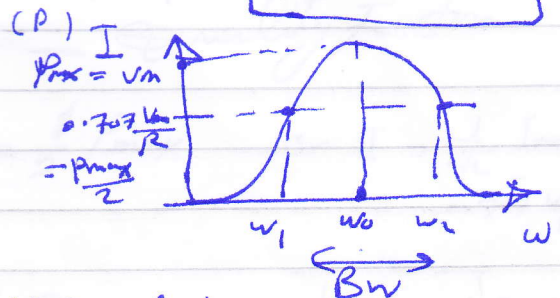

$\frac{V_m}{R}$ ← عند الرنين (resonance)
وعند تردد (Frey) (فرى) ← $\frac{V_m}{2}$

→ Power (average power) at resonance = $\frac{1}{2} I^2 R = \frac{1}{2} \left(\frac{V_m}{R}\right)^2 R$


→ at w_1, w_2 $P = \frac{1}{2} P_{max} = \frac{1}{2} \left(\frac{1}{2} I^2 R\right) = \frac{1}{4} I^2 R$

= $\frac{V_m^2}{4R}$ (Half Power Freq.)

والرسم ده لغرض منة لوصول لاصتيا، اقل ترددات للطاقة المطلوبة


[4]

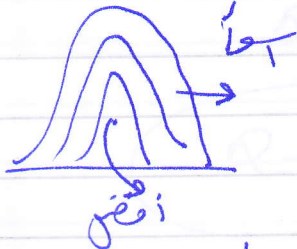[6] half power Bandwidth = $BW = \omega_2 - \omega_1$
 چەيى $\sim B \omega$ (narrow) ئەپ $BW \sim B \omega$
 = Best (high selectivity)



low selectivity \leftarrow BW چەيى زادەسى

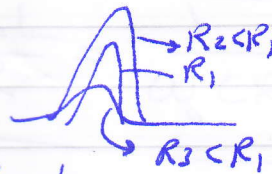Notes [1] % $L \uparrow \uparrow \rightarrow BW$ (narrower) چەيى
 [2] % L, C const ω $R \uparrow \uparrow \rightarrow BW$ (wider) چەيى



[7] Bandwidth selectivity — Quality Factor

at half Power Point $P = \frac{1}{2} P_{max}$ or $I = \frac{1}{\sqrt{2}} I_{max}$
 $\approx 0.707 \frac{V_m}{R}$

$Z = \sqrt{2} R$

$\omega \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2} = \sqrt{2} R$

ω چەيى زادەسى

$\omega_1 = \frac{R}{2L} + \sqrt{(\frac{R}{2L})^2 + (\frac{1}{Lc})}$

$\omega_2 = \frac{R}{2L} + \sqrt{(\frac{R}{2L})^2 + \frac{1}{Lc}}$

$I = \frac{1}{\sqrt{2}} \frac{V_m}{R}$
 $\frac{V}{Z} = \frac{1}{\sqrt{2}} \frac{V_m}{R}$
 $\therefore Z = \sqrt{2} R$

$BW = \omega_2 - \omega_1 = \frac{R}{L}$ rad/s

$\omega_0 = \sqrt{\omega_1 \omega_2}$ Resonance freq.

(5)

→ sharpness of response in Resonance measured by Q

$$Q \text{ (quality factor)} = 2\pi \frac{\text{Peak energy stored in circuit}}{\text{Energy dissipated by } \sigma}$$

$$Q = \frac{\text{Reactive Power}}{\text{Average Power}} \quad \text{عند الاستجابة}$$

$$Q = \frac{I^2 X_L}{I^2 R} = \frac{X_L}{R} = \frac{\omega L}{R}$$

$$\frac{OR}{\text{طرق أخرى}} \quad Q = 2\pi \frac{\frac{1}{2} L I^2}{\frac{1}{2} I^2 R (Y.F)} = \frac{2\pi F L}{R}$$

في التردد

$$Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 C R} \quad \text{at Resonance}$$

$$\therefore Q = \frac{\omega L}{R} = \frac{1}{\omega R C} \quad \text{①}$$

$$\therefore B = \frac{R}{L} = \frac{\omega_0}{Q} = \omega^2 C R \quad \text{②}$$

$$\therefore Q = \frac{\omega_0}{B} \quad \text{③} \quad Q \uparrow \rightarrow \text{more selectivity} \rightarrow \text{smaller } B$$

10 \leftarrow Q \rightarrow 10

$$\text{④} \quad \omega_1 \approx \omega_0 - B/2$$
$$\omega_2 \approx \omega_0 + B/2$$

end of lecture

6

ماضى لقوانين

$$\boxed{1} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad \text{و} \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\boxed{2} \quad Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \rightarrow \text{total series Res.}$$

$Z = R$ (at resonance).

$$\boxed{3} \quad BW = \omega_2 - \omega_1 = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\boxed{4} \quad \omega_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \approx \left. \begin{array}{l} \omega_0 - B/2 \\ \omega_0 + B/2 \end{array} \right\} \text{at } Z = \sqrt{2}R$$

$\omega_{1,2} = \frac{\pm R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \approx \left. \begin{array}{l} \omega_0 - B/2 \\ \omega_0 + B/2 \end{array} \right\} \text{at } Z = \sqrt{2}R$
→ from half power

$$\boxed{5} \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\boxed{6} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Sheet (2)

1 A series RLC has $R=2k$, $L=40mH$, $C=1\mu F$
Calc. The Impedance at Resonance and at
one fourth, one half, twice, Four times Resonant freq.

Sol

$\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}} = 5000 \text{ rad/s} = 5 \text{ krad/s}$

* $Z = R + j\omega L - j(\frac{1}{\omega C}) = (R + j(\omega L - \frac{1}{\omega C}))$

a- For Resonance $Z = R_p = 2k = \frac{100}{9} = 9 \leftarrow$

b- " one fourth ($\omega_b = \frac{5}{4} \text{ krad/s}$) = 9 \leftarrow

$Z = R + j(\omega L - \frac{1}{\omega C}) = 2000 + j(\frac{5}{4} \times 40 \times 10^{-3} - \frac{1}{\frac{5}{4} \times 1 \times 10^{-6}})$
 $= (2 - j0.75) k\Omega$

c- one half $\omega_c = \frac{1}{2} \omega \rightarrow Z = 2 - j0.3 k\Omega$

d- Twice $\omega_d = 2\omega \rightarrow Z = 2 + j0.3 k\Omega$

e- four times $\omega_e = 4\omega \rightarrow Z = 2 + j0.75 k\Omega$


$\frac{1}{(2)k\Omega} = \frac{1}{j\omega} = 0 \quad \frac{1}{2} = 0.5 \quad \frac{1}{2} = 0.5 \quad \frac{1}{2} = 0.5$
 $\frac{1}{20mH} = \frac{1}{20 \times 10^{-3}} = 50 \quad \frac{1}{100} = 0.01 \quad \frac{1}{100} = 0.01$
 $\frac{1}{20} = 0.05 \quad \frac{1}{100} = 0.01 \quad \frac{1}{100} = 0.01$

8

[2] Coil with resistance 3Ω , inductance 100mH , connected in series with capacitor 50pF , a resistor of 6Ω and signal generator 10Vrms , Calc. ω_0 , Q , B at Resonance.

Sol/

$$R = 6 + 3 = 9$$

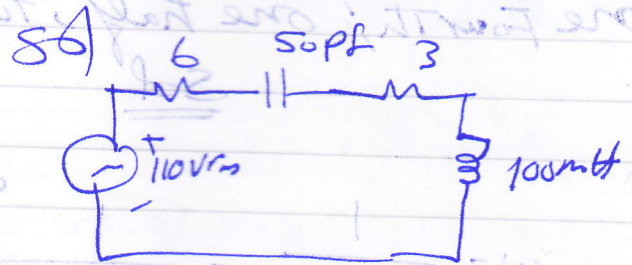

$$\omega = \frac{1}{\sqrt{LC}}$$

$$= \frac{1}{\sqrt{(100 \times 10^{-3})(50 \times 10^{-12})}} = 447.21 \text{ krad/s}$$

$$\rightarrow Q = \frac{\omega L}{R} = \frac{(447.21) \times 10^3 \times 100 \times 10^{-3}}{9} = 4969$$

$$\Rightarrow B = \frac{\omega}{Q} = \frac{447.21 \times 10^3}{4969} = 90 \text{ rad/s}$$

$$\underline{B} = R/L = \frac{9}{100 \text{mH}} = 90 \text{ rad/s}$$

[3] Design RLC circ with $B = 20 \text{ rad/s}$, $\omega_0 = 1000 \text{ rad/s}$
find Q

Sol/ Let $R = 100\Omega$

$$\because B = R/L \Rightarrow L = R/B = \frac{100}{20} = 5 \text{ H}$$

$$\omega = \frac{1}{\sqrt{LC}} \quad \omega^2 = \frac{1}{LC} \quad C = \frac{1}{\omega^2 L} = \frac{1}{(1000)^2 (5)} = 20 \text{ nF}$$

$$Q = \frac{\omega L}{R} = \frac{(1000)(5)}{100} = 50$$

9

4


a - Determine R, C (at resonance)

freq ($f_r = 25 \text{ kHz}$, rms and 25 mA)

b - power dissipated by circuit at resonance

~~sc~~ c - phasor voltage V_C, V_L, V_R at resonance

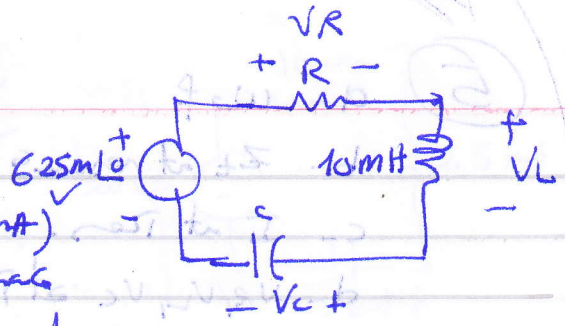d - write sinusoidal eq. for V_C, V_L, V_R



a - $f_r = 25 \text{ kHz}$, $I_{\text{rms}} = 25 \text{ mA}$, $V_{\text{rms}} = 625 \text{ mV}$

∴ $Z = R$ at resonance

∴ $Z = \frac{V}{I} = \frac{625}{25} = \boxed{25 = R}$

for C $f_r = \frac{1}{2\pi\sqrt{LC}} = 25 \times 10^3 \text{ Hz}$

∴ $\frac{1}{LC} = (25 \times 10^3 \times 2\pi)^2$

∴ $C = \frac{1}{(10 \times 10^{-3}) (25 \times 10^3 \times 2\pi)^2} = \boxed{4.05 \times 10^{-9} \text{ F}}$

b - $P = VI = (625 \text{ mV})(25 \text{ mA}) = \boxed{15.6 \text{ mW}}$

c - $V_R = IR = (25 \text{ mA})(25) = \boxed{0.625 \text{ V} \angle 0}$

$V_L = IX_L = (25 \text{ mA})(2\pi fL) = (25 \text{ mA})(2\pi \times 25 \times 10^3 \times 10 \times 10^{-3}) \angle +90$
 $= \boxed{39.25 \angle 90}$


$V_C = IX_C = (25 \text{ mA}) \left(\frac{1}{2\pi fC} \right) \angle -90 = (25 \text{ mA}) \left(\frac{1}{2\pi \times 25 \times 10^3 \times 4.05 \times 10^{-9}} \right) \angle -90$
 $= \boxed{39.31 \angle -90}$

~~$i = I_m \sin(\omega t + \phi) = 29.31 \sin(\dots)$~~

$V = \frac{W}{Q} = \frac{15.6 \text{ mW}}{25 \text{ mA}} = 0.625 \text{ V}$

20/10 Vb

101 P

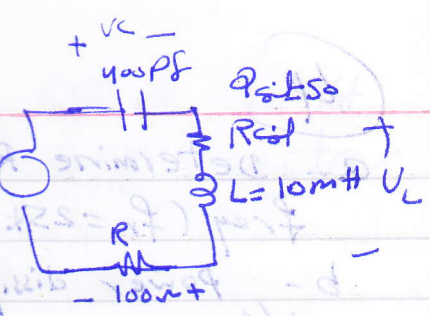

- 5
- ω of f
 - Z_t at resonance
 - I at R_{eq}
 - V_R, V_L, V_C at R_{eq}
 - P dissipated (Q_C, Q_L Power)
 - Q = Quality factor at R_{eq}

Sol

a- $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(400 \times 10^{-12})(10 \times 10^{-3})}} = 500 \text{ krad/s}$

$f = \frac{\omega}{2\pi} = 79.617 \text{ kHz}$

b- $Z_t|_{res} = R + R_{coil} = 100 + R_{coil}$

$\therefore Q = \frac{\omega L}{R_{coil}} \Rightarrow R_{coil} = \frac{\omega L}{Q} = \frac{500 \times 10^3 \times (10 \times 10^{-3})}{100} = 50$

$\therefore Z_t = R = 100 + 100 = 200 \Omega$

c- $I_{ms} = \frac{V}{Z_{tms}} = \frac{2}{200} = 0.01 \text{ A} = 10 \text{ mA}$

d- $V_R = I R = 0.01(100) = 1 \text{ V}$

$V_C = I X_C = (0.01) \left(\frac{1}{\omega C} \right) \angle -90^\circ = 0.01 \frac{1}{(500 \times 10^3)(400 \times 10^{-12})} \angle -90^\circ = 50 \angle -90^\circ$

$V_L = I(X_L + R) = (0.01)(R + jX_L)$

$= (0.01)(100 + j(500 \times 10^3)(10 \times 10^{-3})) = (0.01)(100 + j5000)$

$= 1 + j50 = \sqrt{1^2 + 50^2} \angle \tan^{-1}\left(\frac{50}{1}\right) = 50.01 \angle 88.85^\circ$

e- $P = VI = (2)(0.01) = 0.02 = 20 \text{ mW}$


$Q_C = I^2 X_C = (0.01)(50) \angle -90^\circ = 0.5 \text{ VAR}$

$Q_L = I^2 X_L = (0.01)(5000) = 0.501 \text{ VAR}$

$Q = \frac{\omega L}{R} = \frac{(500 \times 10^3)(10 \times 10^{-3})}{200} = 25$


Assign

- a- ω b- Z_{in} c- draw $I \leftrightarrow \omega$
 d- $|I| = ?!$ e- plot $|I| \leftrightarrow \omega$

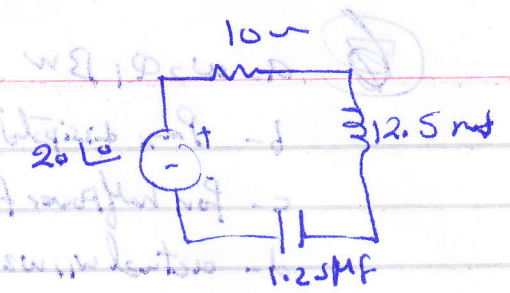


a- $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(12.5 \times 10^{-3})(1.25 \times 10^{-6})}} = 8000 \text{ rad/s}$

b- $Z_{res}(\omega) = R = 10 \Omega$
 $Z|_{0.1\omega} = R + j(\omega L - \frac{1}{\omega C}) = 10 + j(100 - \frac{100}{0.1}) = 10 + j(10 - 1000)$
 $Z|_{0.2\omega} = 10 + j(\frac{100 \times 0.2}{1} - 100/0.2) = 10 - j480 = 480 \angle -88.8^\circ$
 $Z|_{0.5\omega} = 10 + j(100 \times 0.5 - 100/0.5) = 10 - j150 = 150.3 \angle -86.18^\circ$
 $Z|_{2\omega} = 10 + j(100 \times 2 - 100/2) = 10 + j150 = 150.3 \angle 86.18^\circ$
 $Z|_{10\omega} = 10 + j(100 \times 10 - 100/10) = 10 + j990 = 990 \angle 89.42^\circ$
 $Z|_{5\omega} = 10 + j(100 \times 5 - 100/5) = 10 + j480 = 480.1 \angle 88.8^\circ$

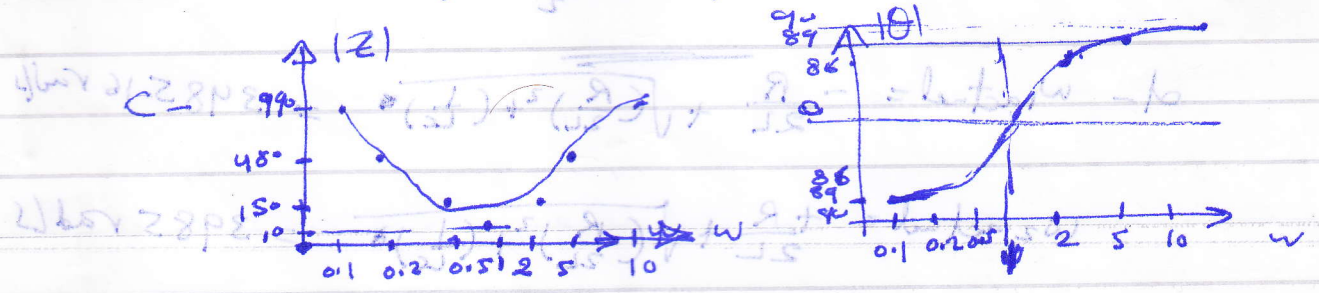

d- $I|_{\omega} = V/R = \frac{20}{10} = 2 \text{ A}$
 $I|_{0.1\omega} = V/Z = \frac{20}{990 \angle 89.42^\circ} = 0.02 \angle -89.42^\circ$
 $I|_{0.2\omega} = \frac{20}{480 \angle 88.8^\circ} = \frac{20}{480} \angle -88.8^\circ$
 $I|_{0.5\omega} = \frac{20}{150} = 0.133 \angle -86.18^\circ$
 $I|_{2\omega} = \frac{20}{150.3} = 0.133 \angle -86.18^\circ$
 $I|_{5\omega} = \frac{20}{480.1} = 0.042 \angle -88.8^\circ$
 $I|_{10\omega} = \frac{20}{990} = 0.02 \angle -89.42^\circ$

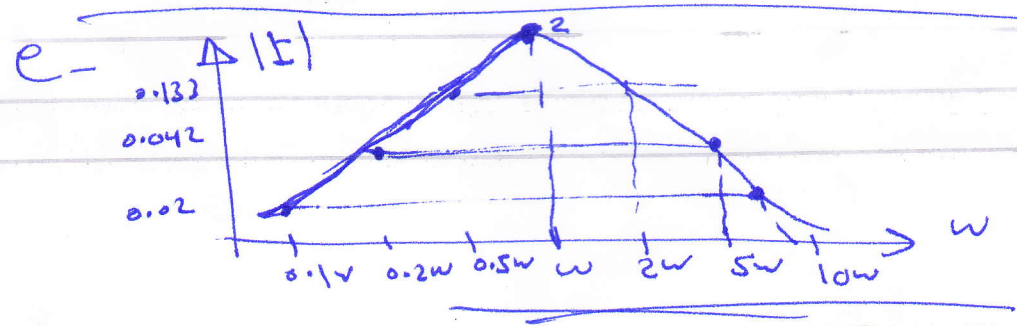


a- ω_0, Q, BW

b- P_{max} dissipated

c- for half power freq. find ω_1, ω_2

d- actual ω_1, ω_2

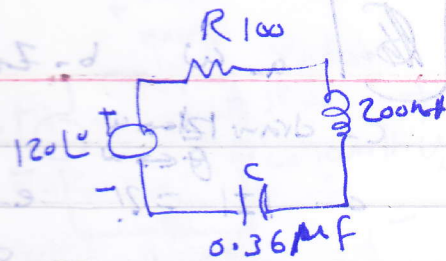

ω

$$a - \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(200 \times 10^{-3})(0.36 \times 10^{-6})}} = 3726 \text{ rad/s}$$

$$Q = \frac{\omega L}{R} = \frac{3726 \times 200 \times 10^{-3}}{100} = 7.452$$

$$BW = \omega/Q = 3726 / 7.452 = 500 \text{ rad/sec}$$

b- $P_{max} = V_m I_m = V_m \left(\frac{V_m}{R} \right) = \frac{V_m^2}{R} = \frac{(120)^2}{100} = 144 \text{ W}$

c- $\omega_1 = \omega_0 - BW/2 = 3726 - \frac{500}{2} = 3476 \text{ rad/s}$

$\omega_2 = \omega_0 + BW/2 = 3726 + \frac{500}{2} = 3976 \text{ rad/s}$

d- $\omega_{1 \text{ actual}} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$ = 3485.16 rad/s

$\omega_{2 \text{ actual}} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$ = 3985 rad/s

End of sheet?

