


Electrical Circuits (2)

Section (4)

Series Resonance & Using Proteus

8-11/3



# Sheet (3)

1. A series RLC is designed to Resonant at  $\omega_s = 10^5 \text{ rad/s}$ .  
 Have a Bandwidth of  $0.15 \omega_s$ , and draw 16 W  
 From 120V source at Resonance.

- Determine the value of R
- Find The Bandwidth in Hz.
- Find the nameplate values of L, and C.
- Determine the Qs of The circuit.

## Solution

Given //  $\omega = 10^5 \text{ rad/s}$ ,  $B = 0.15 \omega_s$ ,  $P = 16 \text{ W}$ ,  $V = 120 \text{ V}$   
 Req //  $R, BW(\text{Hz}), L, C, Q$

$$[1] R = \frac{V}{I} = Z \text{ at resonance} = \frac{120}{I} = (120) / \frac{16}{120} = 900 \Omega$$

$$[2] B(\text{rad/s}) = \frac{R}{L} = \frac{900}{L} = 0.15 \omega_s = 0.15 \times 10^5$$

$$\therefore BW = 0.15 \times 10^5 \text{ rad/s} (\Delta \omega)$$

$$BW(\text{Hz}) = (\Delta f) = \frac{\Delta \omega}{2\pi} = \frac{0.15 \times 10^5}{2\pi} = 2387.32 \text{ Hz}$$


$$[3] B(\text{rad/s}) = \frac{R}{L} = \frac{900}{L} = 0.15 \times 10^5$$

$$\therefore L = \frac{900}{0.15 \times 10^5} = 0.06 \text{ H}$$

$$\omega = \frac{1}{\sqrt{LC}} = 0.15 \times 10^5 \Rightarrow C = 1.67 \text{ nF}$$

$$[4] Q = \frac{\omega}{B(\text{rad/s})} = \frac{10^5}{0.15 \omega_s} = \frac{10^5}{0.15 \times 10^5} = \frac{1}{0.15} = 6.67$$

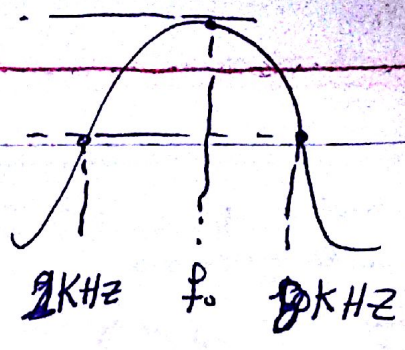For a given Response of current 0.707A in a series RLC circuit



Design find  $R, L, C, Q, B, \omega, V_L, V_R, V_C, P_t, Q_L, Q_C$

Sol  $\rightarrow B = 8 - 2 = 6 \text{ kHz}$   
 $B \text{ rad/s} = 2\pi(6000)$

$\rightarrow f_0 = \sqrt{f_1 f_2} = \sqrt{2 \times 8} = \sqrt{16} = 4 \text{ kHz}$

$\rightarrow \omega_0 = 2\pi f = 2\pi \times 4000 = 25132 \text{ rad/s}$

$\rightarrow Q = \omega_0 / B = \frac{25132}{6000} = 4.188$

$\omega_1 = 2\pi \times 2 = 12566 \text{ rad/s}$

$B = 2(\omega_0 - \omega_1) = 2(25132 - 12566) = 2 \times 12566 = 25132 \text{ rad/s}$

$\omega = 19866 \text{ rad/s} \Rightarrow Q = \frac{25132}{12566} = 2$

$B = R/L$  find  $R$   
 at  $\omega_0 = \frac{1}{\sqrt{LC}}$  find  $C$

$I_{rms} = 0.707 = \frac{1}{\sqrt{2}} I_{max} \Rightarrow I_{max} = 1 \text{ A}$

$\therefore V_t = IR = 1R$   
 $V_L = IX_L$   
 $V_C = IX_C$


$P_t = IV$   
 $P_L = IV_L$   
 $P_C = IV_C$

2

part -  
on unit

[2] For RLC

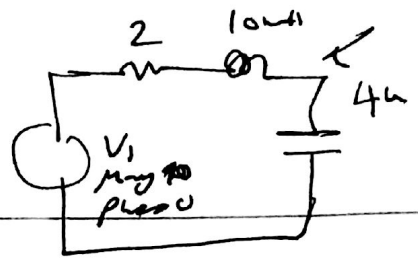- 1- calc. resonance  $F_{res}$ ,  $Q$ ,  $BW$
- 2-  $V_L, V_C$
- 3- plot  $V_L, V_C$  plots
- 4- plot freq response for  $V_C$



~~Sol~~

$$\textcircled{1} f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{\sqrt{(10 \times 10^{-3})(4 \times 10^{-6})}} (2\pi)$$

$$= 795.8 \text{ Hz}$$

$$\textcircled{2} B = R/L = \frac{2}{10 \times 10^{-3}} = 200 *$$

$$\textcircled{3} Q = \omega/B = \frac{2\pi F}{B} = \frac{2\pi \times 795.8}{200} = 25 \text{ rad/s}$$


$$\textcircled{4} I = \frac{V}{Z} = \frac{V}{R} = \frac{10}{2} = 5$$

$$\therefore V_L = I \times \omega L \angle 90^\circ = (5 \times 2\pi \times 795.8)(10 \times 10^{-3})$$

$$= 250 \angle 90^\circ$$

$$V_C = I X_C = 5 \times \frac{1}{2\pi \times 795.8 \times 4 \times 10^{-6}} \angle -90^\circ$$

$$= 250 \angle -90^\circ$$

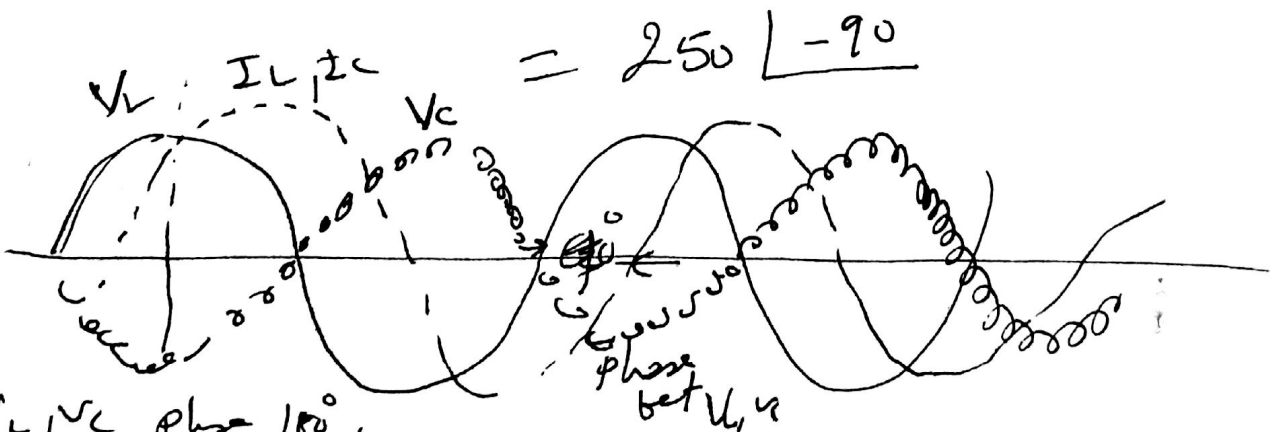

$V_L, V_C$  phase  $180^\circ$

(3)

ف : علاقة (تحت) و (أعلى) و (أدنى)

