

Electrical Circuits (2)

Section (5)

Parallel Resonance


Sheet (4)

15-17/3/2015


①

## Parallel Resonance

Ideal circuit

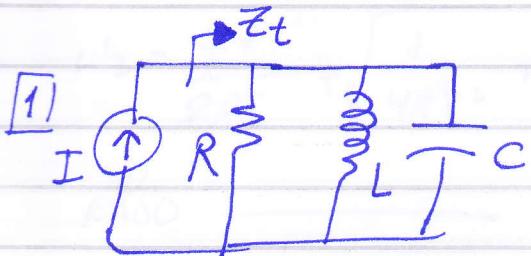

Practical circuit

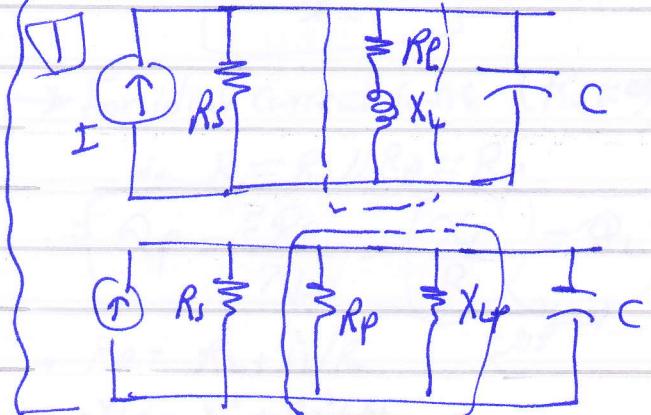


②  $X_L = X_C$  at Resonance

$$\Rightarrow \omega_p = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

③  $\gamma = \frac{1}{Z} = Y_1 + Y_2 + Y_3$   
 $= \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$

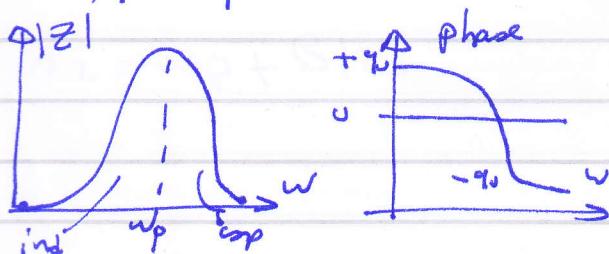④ at Resonance  $G_p = \frac{1}{R}$   
 &  $V, I$  inphase.  $\leftarrow$  admittance



⑤  $Q_p = \frac{R}{X_C} = \frac{R}{\omega L} = \frac{\omega_p}{B_W}$   
 $= R/\omega L = \omega R C$

⑥  $B_W = \omega_2 - \omega_1 = \frac{1}{RC} \text{ rad/s}$   
 $= \omega_p/Q_p$

$$Z = R_p + jX_L \Rightarrow Y = \frac{1}{Z} = \frac{1}{R_p + jX_L}$$

$$R_p = \frac{R^2 + X_L^2}{2\omega_p R C} \quad \& \quad X_{Lp} = \frac{R^2 + X_L^2}{\omega_p X_L}$$

③  $R = R_s // R_p$   
 $Y_t = \frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{\omega_p X_L}\right)$

④ at Resonance  $\frac{1}{X_C} = \frac{1}{\omega_p X_L}$   
 $\Rightarrow f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R^2 C^2}{L^2}}$

⑤ max impedance freq  $f_m \rightarrow \frac{dZ_t}{df} = 0$

$$f_m = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{4R^2 C^2}{L^2}}$$

\* Max impedance at  $f = \omega_p$

$$X_L = \omega X_C \text{ or}$$

$$\Rightarrow Z_t = R_s // R_p \approx R_s$$

$$[7] \omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \quad \text{rad/s}$$

$$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \quad \text{rad/s}$$

Also

$$[8] \omega_1 = \omega_p \sqrt{1 + \left(\frac{1}{\omega_a}\right)^2} - \omega_0/\omega_a$$

$$\omega_2 = \omega_p \sqrt{1 + \left(\frac{1}{\omega_a}\right)^2} + \omega_0/\omega_a$$

$$[6] Q_p = \frac{R}{X_{LP}} = \frac{R_s // R_p}{X_{LP}} \\ = \frac{R_s // R_p}{2\omega_c}$$

→ For ideal current source ( $R_s \approx \infty$ )

$$\therefore R = R_s // R_p = R_p$$

$$\therefore Q_p = \frac{R_p}{X_{LP}} = \left( \frac{X_L}{R_L} \right) = Q_L$$

$$\rightarrow R_p = R_L^2 + X_L^2 / R_L$$

$$\rightarrow X_{LP} = X_L^2 + R_p^2 / X_L$$

$$[7] B_w = f_r/Q_p = f_r - f_i \\ = \omega_p / Q_p = \frac{1}{RC} \text{ rad/s}$$


$$\omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$

$$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$

$$[8] Z = \frac{1}{j\omega} R = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

$$\omega_1 = \omega_p - \beta/2$$

$$\omega_2 = \omega_p + \beta/2$$

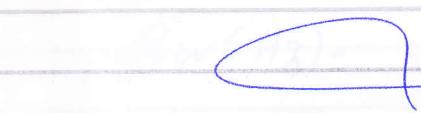

(3)


Sheet (4)[1] a. find  $\omega_p$ ,  $f_p$ b.  $Q$ 

c. Voltage across circuit at Resonance

d.  $I_L$ ,  $I_R$  at  $R_o$ 

e. BW rad/s, Hz

f. Sketch Voltage res, show voltage at half power points.

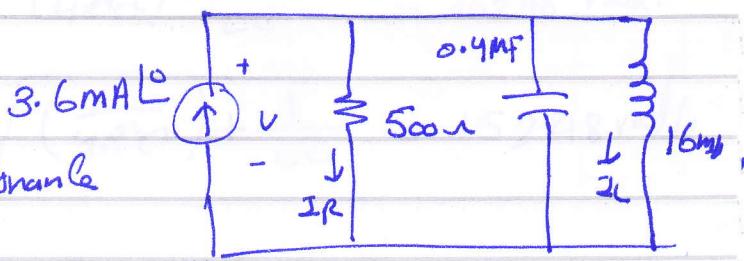g. // Selectivity curve, show  $P_{(watt)}$ ,  $P_{(dB)}$  (rad/s)Sol

$$a - \omega_p = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(16 \times 10^{-3})(0.4 \times 10^{-6})}} = 12.5 \text{ rad/s} \quad *$$

$$f_p = \omega_p / 2\pi = 1989 \text{ Hz} \quad *$$

$$b - Q_p = \frac{R_p}{X_p} = \frac{500}{\underline{\omega L = (12.5 \times 10^3)(16 \times 10^{-3})}} = 2.5 \quad *$$

$$c - \text{at Resonance } V_C = V_L = V_R \text{ and so } V = I R \\ = (3.6 \times 10^{-3})(500) = 1.8 \text{ V} \quad *$$

$$d - I_L = \frac{V}{X_L} = \frac{1.8 \text{ V}}{\underline{\omega L = (12.5 \times 10^3)(16 \times 10^{-3})}} = \frac{1.8 \text{ A}}{(12.5 \times 10^3)(16 \times 10^{-3})} = 9 \text{ mA} \quad *$$

$$I_R = \frac{V}{R} = \frac{1.8 \text{ V}}{500} = 3.6 \text{ mA} \quad *$$


$$e - \text{BW (rad/s)} = \frac{\omega_p}{Q_p} = \frac{12.5 \text{ rad/s}}{2.5} = 5 \text{ rad/s}$$

$$\text{BW (Hz)} = \frac{\text{BW (rad/s)}}{2\pi} = 795.8 \text{ Hz}$$

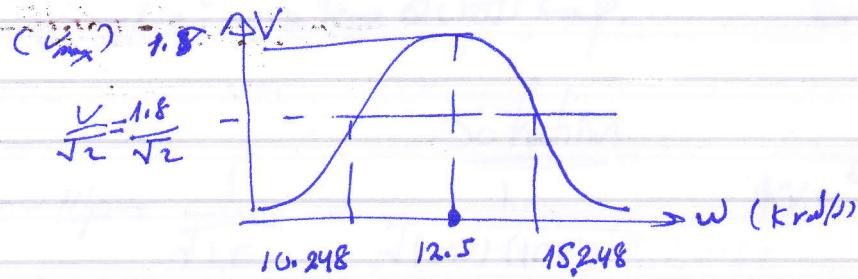
(4)

$$f - \omega_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{4R^2C^2}\right) + \frac{1}{LC}} = 16248 \text{ rad/s}$$

$$\omega_2 = +\frac{1}{2RC} + \sqrt{\left(\frac{1}{4R^2C^2}\right) + \frac{1}{LC}} = 15248 \text{ rad/s}$$


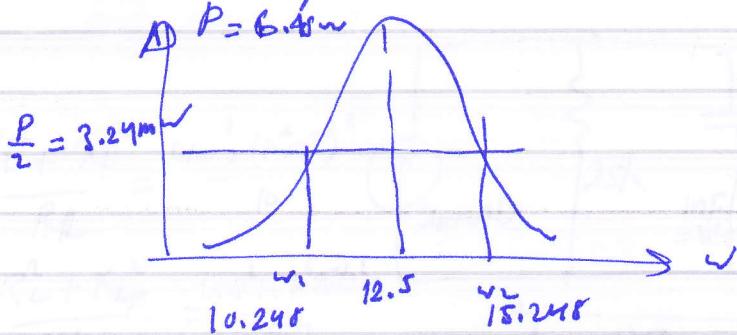
$$2- \text{Power} = P = \frac{V^2}{R} = \frac{(1.8)^2}{500} = 6.48 \text{ mW}$$



end of Prob. (1)

3

Prob  
2

(5)


a -  $\omega_p$

b - Q of coil at res.

c - sketch equivalent parallel of

d - Q of L at Res.

e - solve  $V_L$  by across cap.

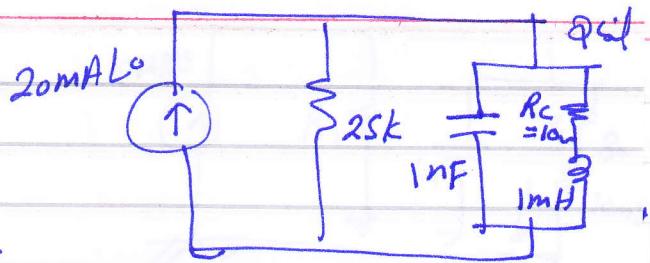

Solution

$$a - \omega_p = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(1mH)(1nF)}} = 1 \times 10^6 \text{ rad/s}$$

$$b - Q_{coil} = \frac{\omega L}{R_{coil}} = \frac{(1 \times 10^6)(1 \times 10^{-3})}{10} = 100$$

c -


$$R_p = \frac{R_L^2 + X_L^2}{R_L} = \frac{(10)^2 + (10^6 \times 10^{-3})^2}{10}$$

$$X_{Lp} = \frac{R_L^2 + X_{Lp}^2}{X_L} = \frac{(10)^2 + (10^6 \times 10^{-3})^2}{(10^6 \times 10^{-3})}$$


$$R_p = 100k\Omega \quad , \quad X_L = 1k\Omega$$

$$\Rightarrow R_{eq} = R_1 / R_p = 20k\Omega$$
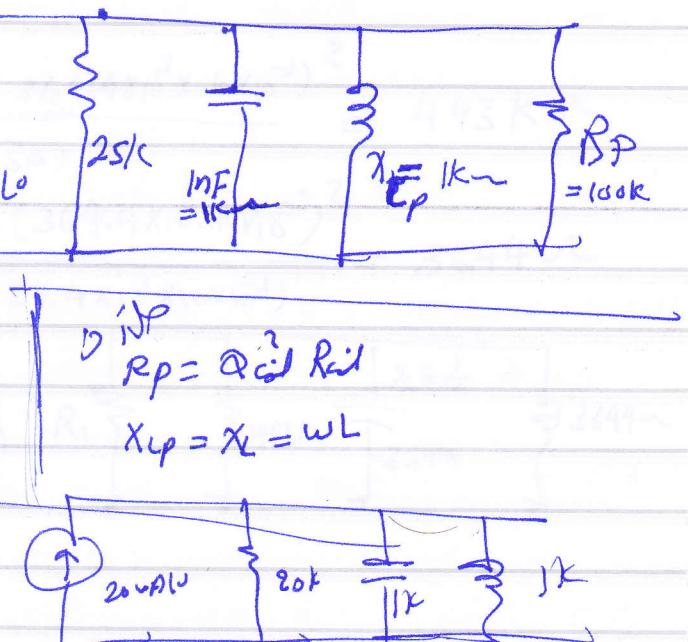
$$d - Q_p = \frac{R_{eq}}{X_L} = \frac{20k}{1k} = 20$$


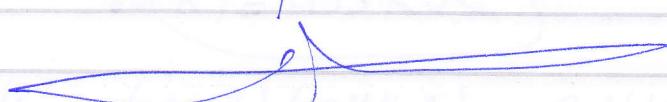
$$e - \text{at Res} \quad V_C = I_{Req} = (20mA Lo)(20k) = 400V L^o$$



Prob

$\omega_p$

6

3


(a) Neg  $R_{C1}, C$   
to solve for const  $\frac{1}{jL}$

8)

$$\Omega_p = \frac{f_p}{B_W} = \frac{58K}{1K} = 58$$

$$\omega_p = 2\pi f = 2\pi \times 58K = 364.4 \text{ rad/s}$$
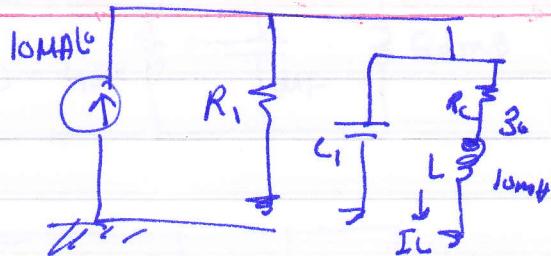
$$C = \frac{1}{\omega_p^2 L} = \frac{1}{(364.4 \times 10^3)^2 (10 \times 10^{-2})} = 753 \mu\text{F}$$



$$L = 10 \text{ mH}$$

$$R_{C1} = 0$$

$$B_W = 1 \text{ kHz}$$

$$f_p = 58 \text{ kHz}$$

$$\rightarrow Q_{Gd} = \frac{\omega_p L}{R_{Gd}} = \frac{(364.4 \times 10^3 \times 10 \times 10^{-3})}{30} = 121.5$$

$$R_p = \frac{R_{Gd}^2 + X_L^2}{R_{Gd}} = \frac{(30)^2 + (364.4 \times 10^3 \times 10 \times 10^{-3})^2}{30} = 443 \text{ kN}$$

$$X_{lp} = \frac{R_{Gd}^2 + X_L^2}{X_L} = \frac{(30)^2 + (364.4 \times 10^3 \times 10 \times 10^{-3})^2}{(364.4 \times 10^3 \times 10 \times 10^{-3})} = 3644 \text{ N}$$

prob

$$\rightarrow Q_{S12} = \frac{R}{X_C} = \frac{R}{X_L}$$

$$58 = \frac{R}{3644}$$

$$\therefore R = 211 \text{ kN}$$

$$R = R_1 // 443 \text{ k} \quad \therefore \frac{443 R_1 \times 10^3}{10^3 \times 443 + R_1} = R = 211 \times 10^3$$

$$\therefore R_1 = 405 \text{ kN}$$

$$(b) V = IR = (10 \text{ mA}) (211 \text{ kN}) = 2.11 \text{ V } \angle 0^\circ$$


$$\cancel{\text{find } I_L = \frac{V}{R_{Gd} + jX_L}} = \frac{2.11}{30 + j3644} = 549 \mu\text{A} \angle -89.9^\circ$$

Prob

4)

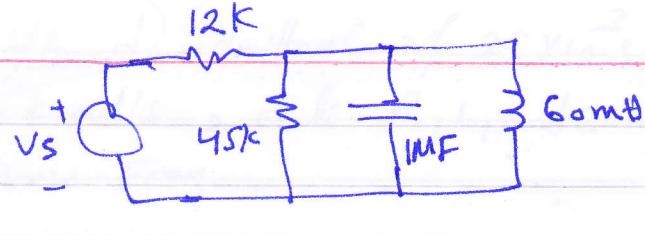7)


Let  $V_s = 20 \cos(\omega t)$ , find  
 $\omega_0$ ,  $Q$ , and  $B$  assuming  
 capacitor.



Sol

$$I_s = \frac{V_s}{12k} = \frac{20 \cos \omega t}{12k}$$
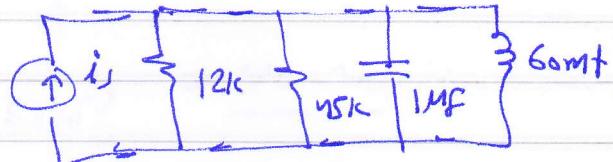
$$\therefore R = 12k // 45k = 9.47 \text{ k}\Omega$$



$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{60 \times 10^{-6} \times 1 \times 10^{-6}}} = 4.08 \text{ rad/s}$$

$$B = \frac{1}{RC} = \frac{1}{(9.47k)(1 \text{ mH})} = 105.55 \text{ rad/s}$$

$$Q = \frac{\omega_0}{B} = \frac{4082 \text{ rad/s}}{105.55 \text{ rad/s}} = 38.67$$

Prob

5)

Design a parallel Resonance RLC with  $\omega_0 = 10 \text{ rad/s}$   
 $(Q = 20, \text{ calc } \text{BW of circuit})$ , let  $R = 10 \Omega$

$$\text{Sol} / \rightarrow Q_p = \frac{\omega_0 L}{R} \Rightarrow L = \frac{R}{\omega_0 Q} = \frac{10}{10 \times 20} = 0.05 \text{ H}$$

$$\rightarrow \omega^2 = \frac{1}{LC} \quad \text{or} \quad \omega^2 = \frac{1}{(Q \cdot R)^2} \quad \text{or} \quad C = \frac{1}{\omega^2 L} = 0.2 \text{ F}$$

$$\rightarrow B = \frac{1}{RC} = \frac{1}{10 \times 0.2} = 0.5 \text{ rad/s}$$

2

6

(8)

parallel RLC, has a midband admittance of  $25 \times 10^{-3}$

1)  $\Phi = 80^\circ \Rightarrow \omega_0 = 200 \text{ krad/s} \Rightarrow \text{cst. } R, L, \text{ and } C$   
Find BW and half power Freq.

Ans

$$\rightarrow Y = \frac{1}{R} \quad \therefore R = \frac{1}{Y} = \frac{1}{25 \times 10^{-3}} = 40 \Omega$$

$$\rightarrow Q_p = \omega_0 R C = (200 \times 10^3)(40)(C) = 80 \Rightarrow C = 10 \mu\text{F}$$

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \rightarrow \omega_0^2 = \frac{1}{LC} \Rightarrow L = \frac{1}{\omega_0^2 C} \Rightarrow L = 2.5 \mu\text{H}$$

$$\rightarrow B = \frac{\omega_0}{Q_p} = \frac{200 \times 10^3}{80} = 2.5 \text{ krad/s}$$

$$\rightarrow \omega_1 = \omega_0 - B/2 = 200 - 1.25 = 198.75 \text{ krad/s} \quad (\text{Midband})$$

$$\omega_2 = \omega_0 + B/2 = 200 + 1.25 = 201.25 \text{ krad/s}$$


Ans  Midband  $\omega_0$  is the frequency where  $Y = 80$ . At resonance,  $Y = 80$ .

For tank circuit shown, find resonant freq.

$$80 \Rightarrow Y = \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{1}{Z_t}$$
$$= \frac{1}{Y_j w_c} + \frac{1}{R + j w L} = Y$$

$$\therefore Y = j w C + \frac{1}{R + j w L} = \frac{1 + j w R C - w^2 L C}{R + j w L}$$
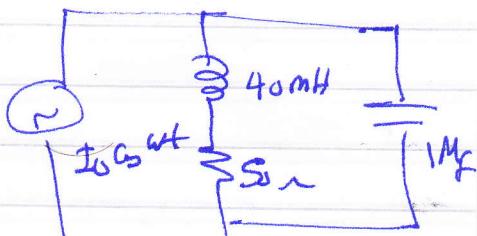
$$Y = j w C + \frac{R - j w L}{R^2 + (wL)^2} = \frac{R}{R^2 + (wL)^2} + j \left( w_C - \frac{wL}{R^2 + (wL)^2} \right)$$



At Resonance Imaginary of  $Y = 0$

$$w_C = \frac{wL}{R^2 + w^2 L^2} \quad \therefore R^2 + w^2 L^2 = 4/C$$

$$\therefore w^2 = 4/C - R^2 \quad \text{or} \quad \omega^2 = \frac{4/C - R^2}{L^2} = \frac{1}{L^2 C} - \frac{R^2}{L^2}$$

$$\therefore \omega = \sqrt{\frac{1}{L^2 C} - \frac{R^2}{L^2}} = 48.41 \text{ rad/s}$$

Ans