


Electrical Circuits (2)

Section (6)

الجزء الثاني




17/3/2015

18/3/2015

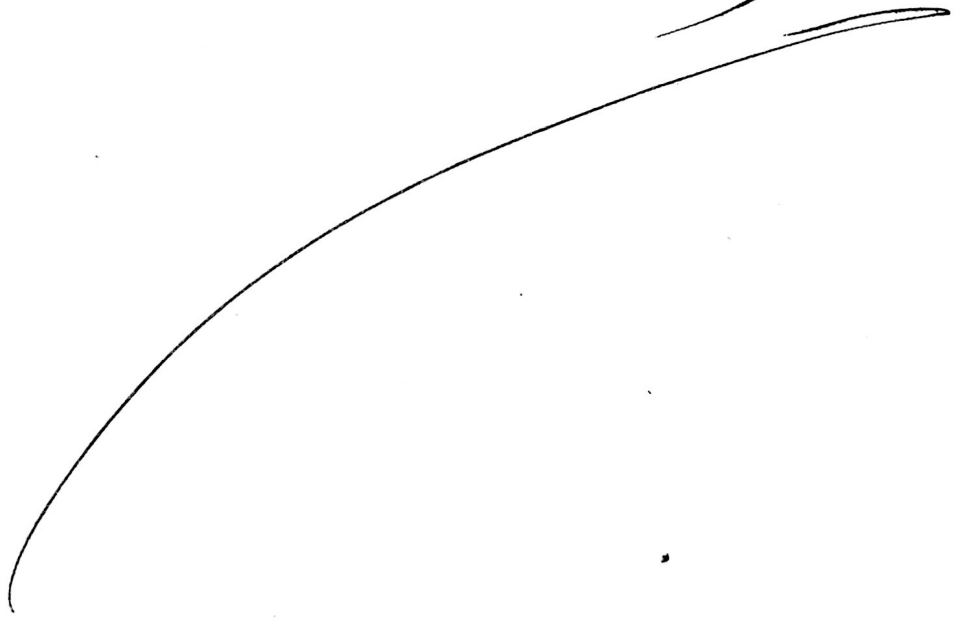

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

Filters

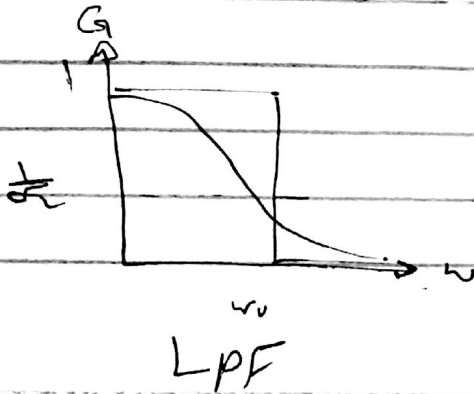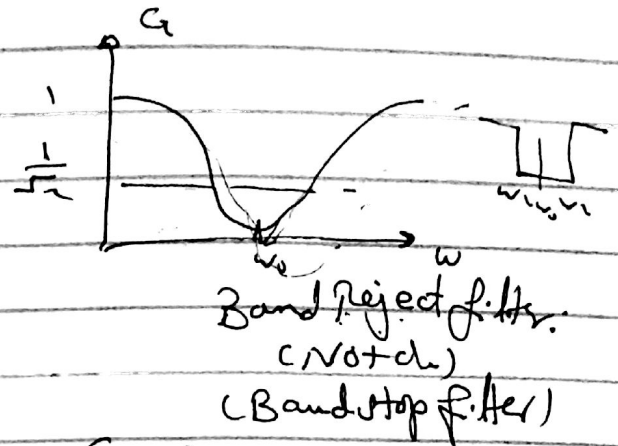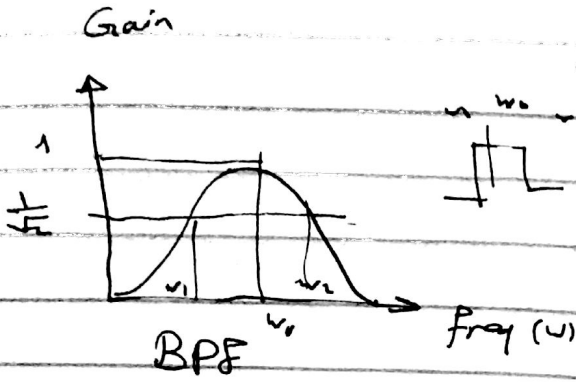

Circuits

① passive BPF

a - O/P From Resistance

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = +\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


$$BW = R/L = \omega_2 - \omega_1$$

$$H(\omega) = v_o/v_i \rightarrow H(\omega) = \frac{1}{\sqrt{2}} H(\omega_0)$$



series Res.

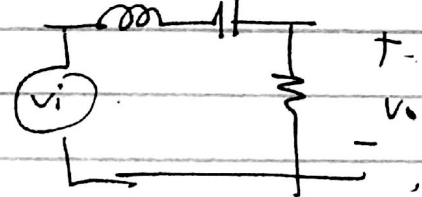

OR parallel R_s

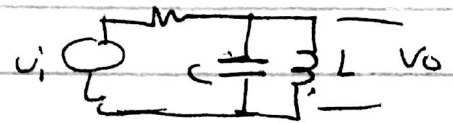


② Band Stop filter (Notch) (Reject)

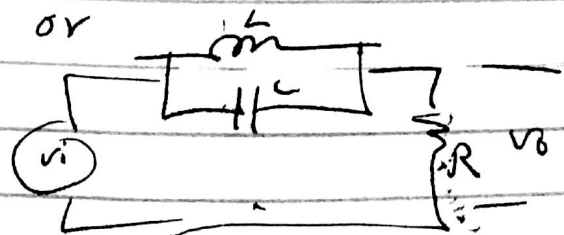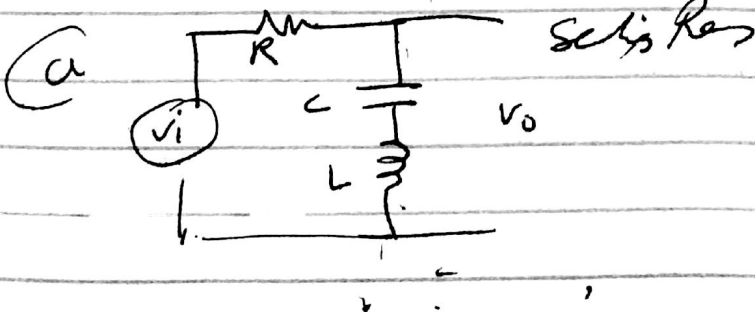


(b)

(2)


(3) HPF

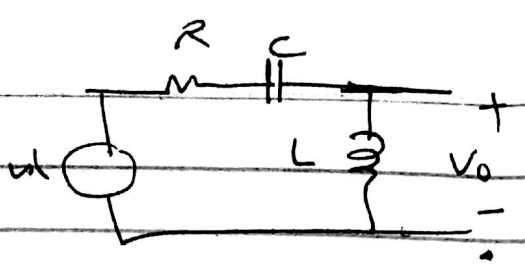


\underline{OR} $\underline{R_C}$

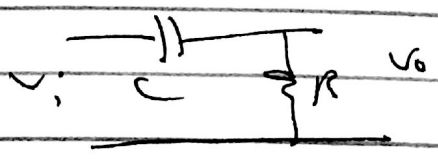

(4) LPF

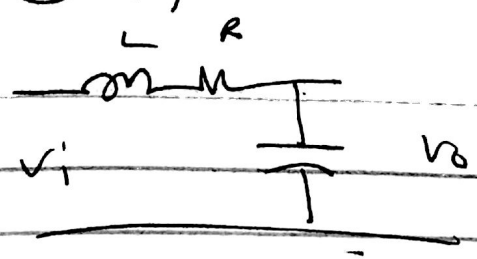

\underline{OR} $\underline{R_S}$

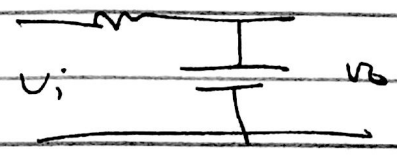

$H(f) = \frac{v_o}{v_i} = \frac{R}{R + j\omega C}$ \underline{ex} $v_i \xrightarrow{X_C} \frac{1}{R} v_o$ $v_o = v_i \frac{R}{R + X_C}$

$\frac{v_o}{v_i} = H(f) = \frac{R}{R + j\omega C}$ at $\omega = 0$ $H(f) = 1$ at $\omega = \infty$ $H(f) = 0$

$|H(f)| = \frac{RL}{\sqrt{R^2 + \omega^2 L^2}}$ or $|H(f)| = \frac{R}{\sqrt{R^2 + \omega^2 C^2}}$ or $\frac{1}{\sqrt{1 + (\frac{\omega C}{R})^2}}$ *

Self Study = p. 122 - 13

Serial R_1, R_2 Serial R_1, R_2 Parallel R_1, R_2
 Parallel Parallel



(3)

Sheet (5)

① Show that a series LR circuit is a LPF if o/p taken across a resistor & calc. Corner Freq. for $L = 2\text{mH}$ & $R = 10\text{k}$



— (Solution) —

$$V_o = V_i \frac{R}{R + j\omega L}$$

$$\frac{V_o}{V_i} = H(f) = \frac{R}{R + j\omega L}$$

$$\text{at } \omega = 0 \rightarrow H(f) = 1$$

$$\omega = \infty \rightarrow H(f) = 0$$

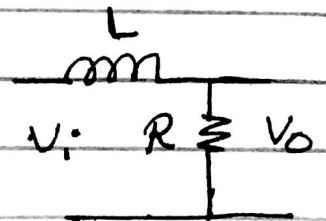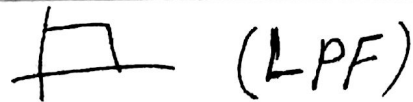

Corner Freq. at $|H(f)| = \frac{1}{\sqrt{2}} H(0)$

$$H(f) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}} \quad f = \frac{\omega}{2\pi}$$

$$|H(f)| = \frac{1}{\sqrt{1 + (\omega \frac{L}{R})^2}} = \frac{1}{\sqrt{1 + (\frac{\omega L}{R})^2}} = \frac{1}{\sqrt{2}}$$

$$\therefore 1 + (\frac{\omega L}{R})^2 = 2$$


$$\text{or } \frac{\omega L}{R} = 1$$

$$\therefore \omega = \frac{R}{L}$$

$$\therefore 2\pi f = \frac{R}{L} \quad \text{or } f = \frac{1}{2\pi} \frac{R}{L} = 796 \text{ kHz}$$

(4)

(2)

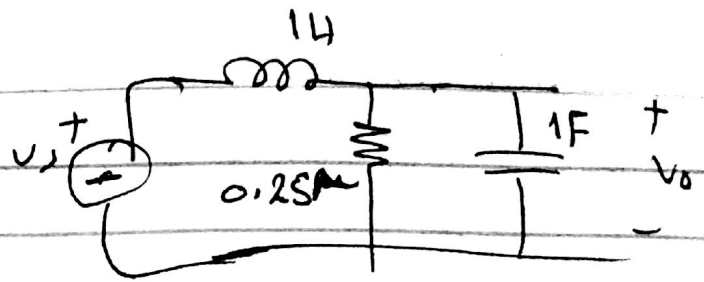

$$H(f) = \frac{R // X_c}{X_L + R // X_c}$$

$$= \frac{R \left(\frac{1}{j\omega C} \right) / \left(R + \frac{1}{j\omega C} \right)}{j\omega L + R \left(\frac{1}{j\omega C} \right)}$$

$$= \frac{R \left(\frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}}$$

$$= \frac{R \left(\frac{1}{j\omega C} \right)}{\left(R + \frac{1}{j\omega C} \right) (j\omega L) + R \left(\frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L)(R + \frac{1}{j\omega C})}$$

$$= \frac{R}{R - \omega^2 LC \left(R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R - \omega^2 LRC - \frac{1}{j} \omega L} = \frac{R}{R - \omega^2 LRC + j\omega L}$$

at $\omega = 0 \rightarrow H(f) = 1$

$\omega = \infty \rightarrow H(f) = 0$

\Rightarrow LPF



(5)

(3) Determine cutoff freq of LPF. $H(\omega) = \frac{4}{2+j\omega 10}$
& Find gain in dB & Phase of $H(\omega)$ at $\omega = 2 \text{ rad/s}$

sol/ cutoff freq calculated when
 $|H(\omega)| = \frac{1}{\sqrt{2}} |H(\omega)|_{\text{max}}$

$$H(0) = \frac{4}{2} = 2 \rightarrow \text{or max}$$

$$H(\infty) = 0$$

~~∴~~ ∴ ~~∴~~ cutoff freq calculated when $|H(\omega)| = \frac{1}{\sqrt{2}} (2)$

$$\text{But } |H(\omega)| = \frac{4 L_0}{\sqrt{2^2 + (10\omega)^2} L_0} = \frac{4^2}{\sqrt{4 + 100\omega^2}} = \frac{2}{\sqrt{2}}$$

$$\text{or } \frac{4}{4 + 100\omega^2} = \frac{1}{2} \quad \text{or } \omega^2 = \frac{4}{100}$$

$$\text{or } 100\omega^2 + 4 = 8$$
$$\boxed{\omega = 0.2} \text{ rad/s}$$

$$H(2) = \frac{4}{2 + j20} = \frac{2}{1 + j10}$$

$$|H(2)| = \frac{2 L_0}{\sqrt{101} \tan^{-1} 10} = \frac{2 L_0}{\sqrt{101} \underline{84.3^\circ}}$$

$$\text{Phase } (0 - \tan^{-1} 10) = \underline{\underline{-84.3^\circ}}$$


$$\text{Mag} = \frac{2}{\sqrt{101}} = 0.199$$

$$\text{Mag dB} = 20 \log 0.199 = -14.02$$

(8)

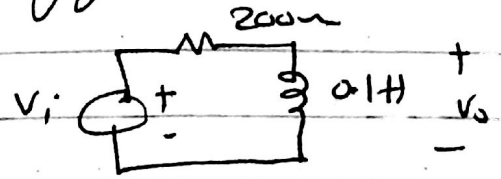4) Determine what type of filter in figure, calc f_c

sol/ $N_o = N_i \left(\frac{X_L}{R + jX_L} \right)$



$$H(f) = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} \quad \text{at } \omega = 0 \rightarrow H(f) = 0$$
$$\omega = \infty \rightarrow H(f) = 1$$

\therefore HPF

$$\rightarrow |H(\omega)| = \frac{1}{\sqrt{2}} \text{ max} = \frac{1}{\sqrt{2}} H(\infty) = \frac{1}{\sqrt{2}}$$

$$= \left| \frac{1}{1 + \frac{R}{j\omega L}} \right| = \left| \frac{1}{1 - j\frac{R}{\omega L}} \right| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}} = \frac{1}{\sqrt{2}}$$

or $1 + \left(\frac{R}{\omega L}\right)^2 = 2 \quad \therefore \left(\frac{R}{\omega L}\right)^2 = 1$

$$\therefore \omega = \frac{R}{L}, \quad 2\pi f = \frac{R}{L} \rightarrow f = 318.3 \text{ Hz}$$

5) in HPF with cutoff freq 100kHz, $L = 40\text{mH}$, find R

sol/ So it is RL

$$\omega = \frac{R}{L} = 2\pi f \rightarrow 100\text{K}$$

$\hookrightarrow 40\text{mH}$

$$R = 25.13 \text{ k}\Omega$$

(7)

6 Design a Series RLC type BPF with cutoff freq. 10 kHz, 11 kHz, assuming $C = 80 \text{ pF}$, find R , L , and Q

Sol

$$\omega_1 = 2\pi f_1 = 20\pi \times 10^3$$

$$\omega_2 = 2\pi f_2 = 22\pi \times 10^3$$

$$B = \omega_2 - \omega_1 = 2\pi \times 10^3$$

$$\omega_0 = \frac{\omega_1 + \omega_2}{2} = 21\pi \times 10^3$$

$$Q = \frac{\omega_0^2}{B} = 10.5$$

$$\rightarrow \omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow L = 2.87 \text{ H}$$

$$B = R/L \Rightarrow R = BL = 18 \text{ k}\Omega$$

Series RLC
as series Resonance

7 Determine the range of frequencies that will be passed by a series RLC BPF, $R = 10 \Omega$, $L = 25 \text{ mH}$, $C = 0.4 \mu\text{F}$
find Q

Sol series RLC $\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}} = 10 \text{ krad/s}$

$$B = R/L = 0.4 \text{ krad/s}$$

$$Q = \omega_0/B = 25$$

\rightarrow range of freq ω_1, ω_2

$$\omega_1 = \omega_0 - B/2 = 9.8 \text{ krad/s}, \quad f_1 = 1.56 \text{ kHz}$$

$$\omega_2 = \omega_0 + B/2 = 10.2 \text{ krad/s}, \quad f_2 = 1.62 \text{ kHz}$$

$$f_1 < f < f_2$$

8) a series parameter for series RLC band stop filter are $R = 2k$, $L = 0.1H$, $C = 40pF$ calc
 a) center freq b) half power freq c) quality factor

8) a - $\omega_0 = \frac{1}{\sqrt{LC}} = 0.5 \times 10^6 \text{ rad/s}$

b - $\omega_1 = \omega_0 - B/2$
 $\omega_2 = \omega_0 + B/2$ } $B = R/L = 2 \times 10^4$
 $\omega_1 = 490 \text{ krad/s}$
 $\omega_2 = 510 \text{ krad/s}$

c - $Q = \omega_0/B = 25$

(Assignment)

9) find BW & center freq. of Bandstop filter

a - find for BW's $\text{Im}(Z) = 0$

b - " " $H(f) = \frac{1}{\sqrt{2}}$ $H(\omega_{max})$



a $Z = 6 + 4 \parallel (X_L + X_C)$
 $= 6 + 4 \parallel (j\omega L + \frac{1}{j\omega C})$
 $= 6 + 4 \parallel (\frac{1 - \omega^2 LC}{j\omega C})$
 $= 6 + \frac{4(1 - \omega^2 LC)}{4 + \frac{1 - \omega^2 LC}{j\omega C}}$
 $= 6 + \frac{4(1 - \omega^2 LC)}{4j\omega C + (1 - \omega^2 LC)}$
 $= 6 + \frac{4(1 - \omega^2 LC)(1 - \omega^2 LC - j\omega C)}{(1 - \omega^2 LC)^2 + (4\omega C)^2}$

b - $H(f) = \frac{4 \parallel (X_L + X_C)}{6 + 4 \parallel (X_L + X_C)}$
 $= \frac{4(1 - \omega^2 LC)(1 - \omega^2 LC - 4j\omega C)}{(1 - \omega^2 LC)^2 + (4\omega C)^2}$
 $6 + \dots$

at $A(0) = \text{max}$
 $H(0) = \frac{4}{6+4}$
 at ω_1, ω_2 $H(f) = \frac{1}{\sqrt{2}} \times \frac{4}{6+4}$

$\text{Im}(Z) = 0$
 $\frac{(4j\omega C)(4)(1 - \omega^2 LC)}{(1 - \omega^2 LC)^2 + (4\omega C)^2} = 0$

$\therefore \omega = 0$ refused
 $1 - \omega^2 LC = 0$ or $\omega = \frac{1}{\sqrt{LC}}$

$\therefore \omega = 15.8 \text{ krad/s}$
 center freq $f_c = \omega/2\pi$

$B = \dots$

$14.65 \text{ krad/s} = \omega_1$
 $17.06 \text{ krad/s} = \omega_2$

$\therefore BW = \omega_2 - \omega_1 = 2.408 \text{ krad/s}$

