

### 1 Self inductance

$$L = \frac{\mu A N^2}{l} = N \frac{d\phi}{di} = \frac{N\phi}{I}$$

$$V_{L1} = L \frac{di}{dt} = N \frac{d\phi}{dt}$$


### 2 Mutual inductance

$$M = N_1 \frac{\phi_{21}}{I_2} = N_2 \frac{\phi_{12}}{I_1} = k \sqrt{L_1 L_2}$$


$$\phi_1 = \phi_{11} + \phi_2 \quad \text{Total flux}$$

Coupling  
coeff.

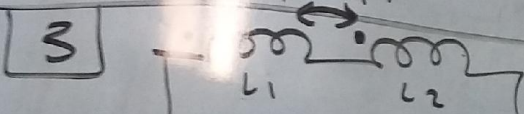
$$k = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2}$$




$$L_{eq} = L_1 + L_2 + 2M$$

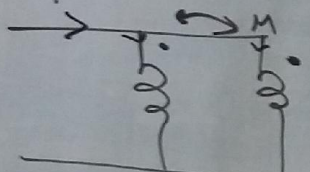
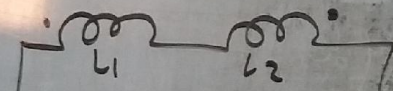
$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$




$$L_{eq} = L_1 + L_2 - 2M$$

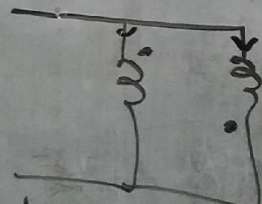

$$L_{eq} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$
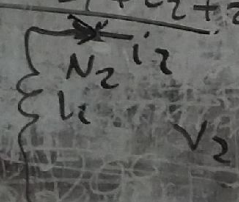
### 4 Transformer


$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1} = \sqrt{\frac{L_1}{L_2}}$$



(1)  
 ملخص لقوانين

[1] Self inductance

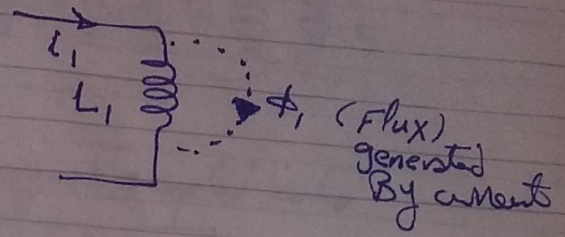a)  $V_{L_1}$  (induced emf) =  $N_1 \frac{d\phi_1}{dt}$   
 $= L_1 \frac{di_1}{dt}$




b)  $L_1 = N_1 \frac{d\phi_1}{di_1}$

For linear sy  $L_1 = N_1 \phi_1 / i_1$   
 For sinusoidal  $V_{L_1} = L_1 \frac{di_1}{dt} = j\omega L_1 i_1$

[2] Mutual inductance

a-  $M = K \sqrt{L_1 L_2}$  Henry

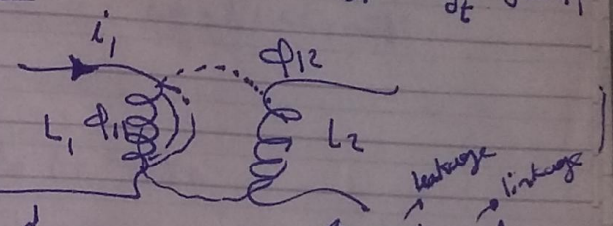where b-  $M = \frac{N_1 d\phi_{21}}{di_2} = \frac{N_2 d\phi_{12}}{di_1}$



$\phi_1 = \phi_{11} + \phi_{12}$   
 $\phi_2 = \phi_{22} + \phi_{21}$

c-  $K = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2} = \text{coupling coeff} \leq 1$

d-  ~~$M = K \sqrt{L_1 L_2}$~~

depends on  
 - space bet coils  
 -  $\mu$  of medium bet  
 - orientation of axis

[3] self inductance Parameters

$L = \frac{N^2 \mu A}{l}$  (henery)  
 N: no. of turns  
 A: area  
 l: length of coil


$M = \mu_0 \mu_r$   
 permeability of free space  $4\pi \times 10^{-7}$   
 $\mu_r$ : relativity of iron

(2)

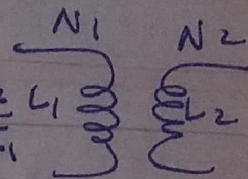3) Transformer

→ Turns Ratio =


$$\frac{N_1}{N_2} = \frac{N_p}{N_s} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$



$$\rightarrow \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$


Magnetically coupled coils

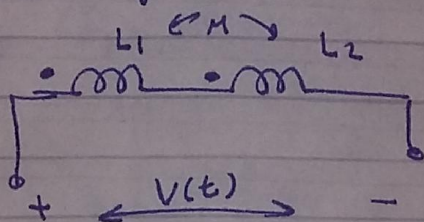[4] Sign of M (series/parallel) .. dot convention



$$L_{t1} = L_1 + L_2 + 2M$$


في اتجاه واحد

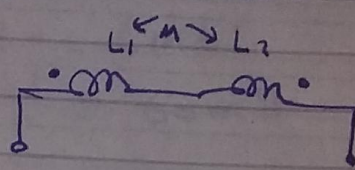


$$L_{t2} = L_1 + L_2 - 2M$$

Note  $L_{t1} > L_{t2}$

Parallel

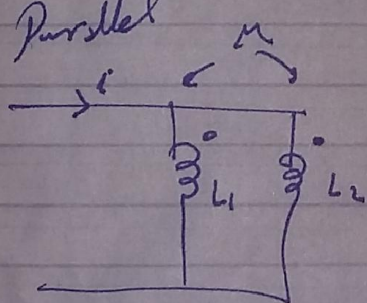

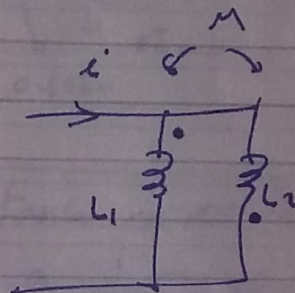
$$L_{t1} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$




$$L_{t2} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

$L_{t1} > L_{t2}$

شكل (2) series

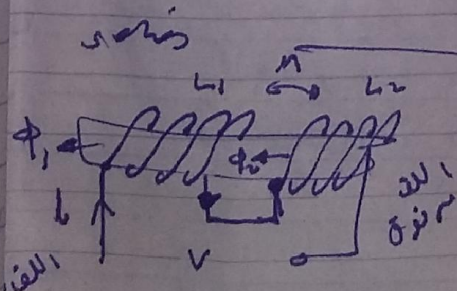

$$L_{eq} = L_1 + L_2 + 2M$$

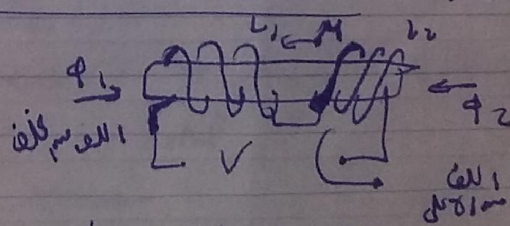

$$L_{eq} = L_1 + L_2 - 2M$$

(3)

### Sheet (6)

1) one coil of magnetically coupled pair has current 5A  
 $\Phi_{11}, \Phi_{12}$  are 0.2 mwb, 0.4 mwb respectively  
 If  $N_1 = 500, N_2 = 1500$ , Find  $L_1, L_2, M, K$ ?

Sol

$$\rightarrow \Phi_1 = \Phi_{11} + \Phi_{12} = 0.2 + 0.4 = 0.6 \text{ mwb}$$

$$\rightarrow L_1 = \frac{N_1 \Phi_1}{I_1} = \frac{500(0.6)}{5} = 60 \text{ mH}$$

$$\rightarrow K = \frac{\Phi_{12}}{\Phi_1} = \frac{0.4}{0.6} = 0.6667$$

$$\rightarrow M = \frac{N_2 \Phi_{12}}{I_1} = \frac{1500(0.4)}{5} = 120 \text{ mH}$$

$$\rightarrow K = \frac{M}{\sqrt{L_1 L_2}} \quad \text{or} \quad M = K \sqrt{L_1 L_2}$$


$\swarrow$   $120 \text{ mH}$        $\searrow$   $60 \text{ mH}$   
 $0.6667$

$$\text{so } L_2 = 540 \text{ mH}$$

2) find the equivalent inductance across terminals a, b!

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13}$$

$$= 6 - 2 - 2 + 2 = 4 \text{ H}$$

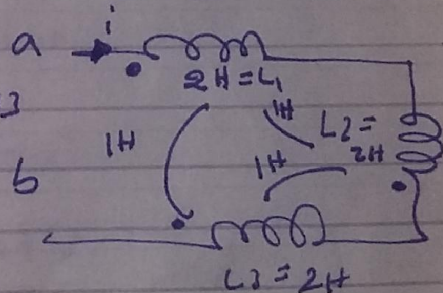

Wp

$$V = (j\omega L_1 i - j\omega M_{12} i - j\omega M_{13} i) +$$

$$(j\omega L_2 i - j\omega M_{12} i + j\omega M_{23} i) +$$

$$(j\omega L_3 i + j\omega M_{23} i - j\omega M_{13} i) = j\omega [L_1 + L_2 - 2M_{12} -$$

$$2M_{13} + 2M_{23}] = j\omega L_{total}$$


4

Loop 1  
 ط. ب. ل. ك. ا  
 2 3 4 5

$$= j\omega L_1 i_1 + (i_1 - i_2) j\omega L_2 + j\omega M i_2$$

$$= i_1 (j\omega L_1 + j\omega L_2) + i_2 (j\omega M - j\omega L_2)$$

→ ①

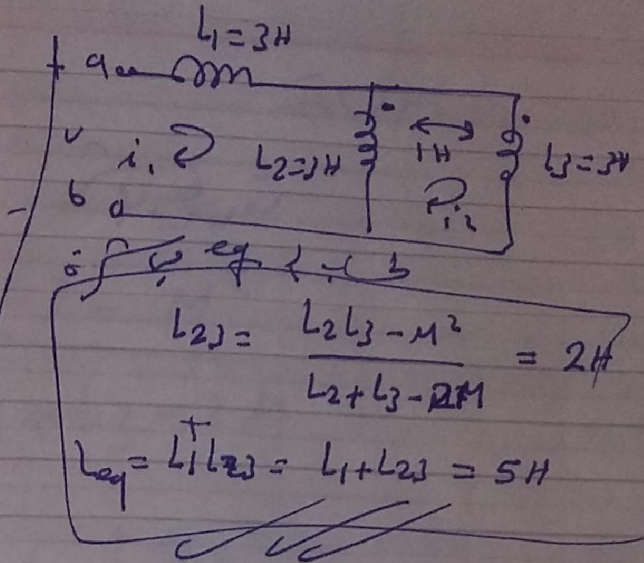

$$L_{23} = \frac{L_2 L_3 - M^2}{L_2 + L_3 - 2M} = 2H$$

$$L_{eq} = L_1 + L_{23} = L_1 + L_2 = 5H$$

np 2

$$0 = [j\omega L_3 i_2 - j\omega M i_2] + (i_2 - i_1) j\omega L_2 - j\omega M (i_2 - i_1)$$

$$0 = i_1 [j\omega M - j\omega L_2] + i_2 [j\omega L_3 - j\omega M + j\omega L_2 - j\omega M]$$

→ ②

$$\Delta = \begin{bmatrix} j\omega(L_1 + L_2) & j\omega(M - L_2) \\ j\omega(M - L_2) & j\omega(L_2 + L_3 - 2M) \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} v & j\omega(M - L_2) \\ 0 & j\omega(L_2 + L_3 - 2M) \end{bmatrix}, I_1 = \frac{\Delta_1}{\Delta}$$

$$\Delta_2 = \begin{bmatrix} j\omega(L_1 + L_2) & v \\ j\omega(M - L_2) & 0 \end{bmatrix}, I_2 = \frac{\Delta_2}{\Delta}$$

Z<sub>2</sub> = Δ<sub>2</sub>/Δ

Note  $Z_{in} = Z_{ab} = \frac{\Delta}{\Delta_{11}} \rightarrow$  الفزائل لى الف الف

$$Z_{in} = \frac{(j\omega)^2 \cdot 20}{j\omega(4)} = j\omega(5)$$

L<sub>total</sub> = 5H

5


صدا ذلالت م لبق

تقریر

$$L_{23} = \frac{L_2 L_3 - M^2}{L_2 + L_3 - 2M} = 2H$$

$$L_{eq} = L_1 + L_{23} = 5H$$

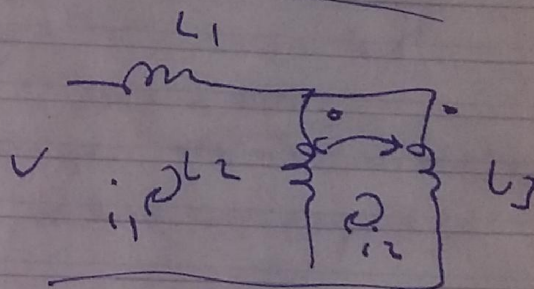①  $\psi = i_1 (X_{L1} + X_{L2}) - i_2 X_{L2} + i_2 X_M$




②  ~~$0 = i_2 (X_{L2} + X_{L3}) + X_{L2} + i_1 X_M - X_{L1} X_{L2}$~~

$0 = i_2 (X_{L2} + X_{L3}) - (i_2 - i_1) j\omega M + (i_2 - i_1) X_{L2} + X_{L3} i_2 - j\omega M i_2$  (2)

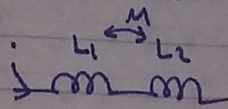(6)

3] Calc. mutual inductance of 2 coils of self inductance 100mH and 200mH are connected in series to yield a total inductance of 146mH.



sol.

$$L_{eq} = L_1 + L_2 \pm 2M$$

$$146m = 100m + 200m \pm 2M$$

$$\therefore \pm 2M = (146 - 300)m \Rightarrow \pm M = \pm 77mH$$

$$\text{or } \pm 2M = 0 \Rightarrow M = -77mH \text{ or } M = 77mH$$


M - ve

checked

$$L_1 + L_2 > 146mH \Rightarrow \text{in series or in series } M - ve$$

4] 3 similar coil wound on along common core, The voltage of mutual inductance between each set of coil is +ve, The self inductance of each coil is 0.2H. The effective inductance of first 2 coils is 0.6H, and of all 3 in series is 1H. (When terminals of first coil is interchanged, the effective inductance of 3 coils in series become 0.5H) determine self inductance of each set of coil.

sol

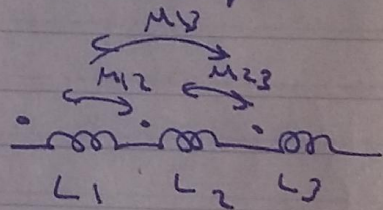

$$\rightarrow L_1 = L_2 = L_3 = L = 0.2H$$

$$\rightarrow L_{12} = 0.6H, L_{total} = 1H$$

$$\rightarrow L_{12} = L_1 + L_2 + 2M_{12} = 0.6$$


$$\therefore M_{12} = 0.1H$$

$$\rightarrow M_{12} = K_{12} \sqrt{L_1 L_2} = K_{12} \sqrt{0.2 \times 0.2} = K_{12} \times 0.2 \therefore K_{12} = 0.5$$

$$\rightarrow L_{total} = L_1 + L_2 + L_3 \pm 2M_{12} + 2M_{23} + 2M_{13}$$

$$1 = 3 \times 0.2 + 2 \times 0.1 + 2M_{23} + 2M_{13} \therefore M_{13} + M_{23} = 0.1$$

When coil 1 is ~~is~~ ~~is~~

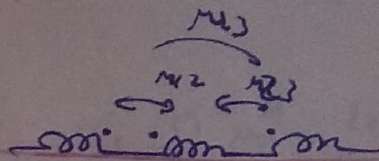

∴  $M_{12}, M_{21} \rightarrow -ve$

$L_{T_{new}} = 0.5$

$$0.5 = L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13}$$

$$0.6 = 0.6 - 0.2 + 2M_{23} - 2M_{13}$$

∴  $M_{23} - M_{13} = 0.05 \rightarrow 2$

Solve 1, 2


$$\therefore M_{13} = 0.025 = k_{13} \sqrt{L_1 L_3} \rightarrow k_{13} = 0.125$$

$$M_{23} = 0.075 = k_{23} \sqrt{L_2 L_3} \rightarrow k_{23} = 0.275$$


Find  $V_1, V_2, V_3$

$$\begin{aligned} \rightarrow V_1 &= L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt} \\ &= 10 \times 2 + 2 \times 5 = 36V \end{aligned}$$
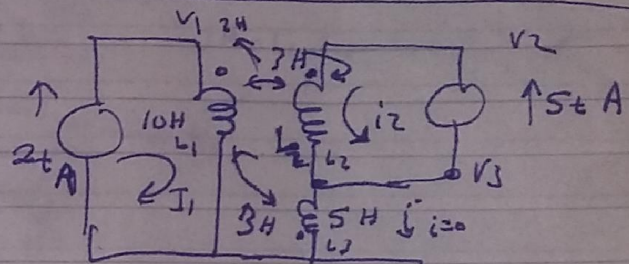
$$\rightarrow V_3 = M_{13} \frac{dI_1}{dt} + L_3 \frac{dI_3}{dt} = 3 \times 2 = 6V$$



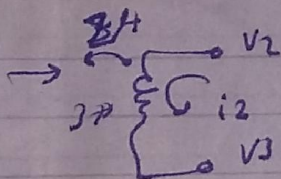( $I_3 = 0$ )  
 در این صورت ولتاژ  $V_3$  فقط از  $M_{13}$  و  $L_3$  به دست می آید.  
 ولتاژ  $V_2$  و  $V_3$  را با هم مقایسه می کنیم.  
 $V_2 - V_3 = L_2 \frac{dI_2}{dt} + M_{21} \frac{dI_1}{dt}$




$$V_2 - V_3 = L_2 \frac{dI_2}{dt} + M_{21} \frac{dI_1}{dt}$$

$$V_2 - V_3 = 3 \times 5 + 2 \times 2 = 19V$$

$$V_2 = V_3 + 19 = 25V$$



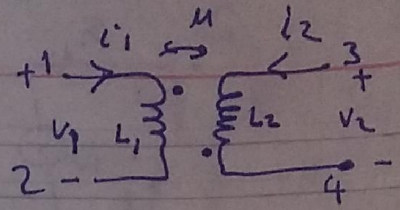5) →  $L_2 = 2H$ , The inductance at 1,2 is  $3H$   
when terminals 3, 4 opened  
→ And  $1H$  when shorted,  
Determine self of coupled  $\odot^+$ .



$$1- \quad v_{12} = L_1 \frac{di_1}{dt} - M_{12} \frac{di_2}{dt}$$

$$2- \quad v_{34} = L_2 \frac{di_2}{dt} - M_{21} \frac{di_1}{dt}$$

for 3, 4 (o.c) →  $i_2 = 0 \quad \therefore \frac{di_2}{dt} = 0$

$$\therefore v_1 = L_1 \frac{di_1}{dt} = j\omega L_1 i_1 = jX_L \cdot i_1$$

$L_1 = 3H$

$v_1$  دالة  $i_1$  بس  $\therefore L_1 = 3H$

for 3, 4 s.c  $v_2 = 0$  only

$$0 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$L_2 \frac{di_2}{dt} = M \frac{di_1}{dt}$$

$$\therefore \frac{di_2}{dt} = \frac{M}{L_2} \frac{di_1}{dt}$$

$$\therefore v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = L_1 \frac{di_1}{dt} - \frac{M^2}{L_2} \frac{di_1}{dt} = \left( L_1 - \frac{M^2}{L_2} \right) \frac{di_1}{dt}$$

$$L_{eq} = L_1 - \frac{M^2}{L_2} = 1H$$


$$\therefore 3 - \frac{M^2}{2} = 1$$

$$\therefore M = 2H$$

$$M = K \sqrt{L_1 L_2}$$

$$\therefore K = 0.816$$

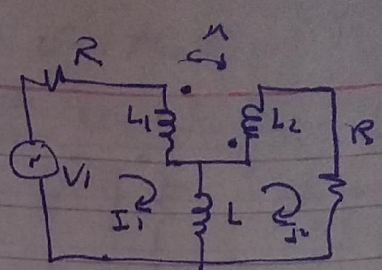7) ratio  $I_1/I_2 = ?$  Using  $\left\{ \begin{array}{l} \text{direct coupled} \\ \text{conductively coupled} \end{array} \right.$  at sl.



$$V_1 = I_1 (R + j\omega(L_1 + L)) + I_2 j\omega M$$

$$V_1 = I_1 (R + j\omega(L_1 + L)) + j\omega(M - L) I_2$$

$$0 = I_2 (R + j\omega(L_2 + L)) + j\omega(M - L) I_1$$

$$\Delta = \begin{vmatrix} R + j\omega(L_1 + L) & j\omega(M - L) \\ j\omega(M - L) & R + j\omega(L_2 + L) \end{vmatrix}$$

$$= V_1 [R + j\omega(L_1 + L)]$$

$$\Delta_1 = \begin{vmatrix} V_1 & j\omega(M - L) \\ 0 & R + j\omega(L_2 + L) \end{vmatrix}$$

$$= V_1 [R + j\omega(L_2 + L)]$$


$$\Delta_2 = \begin{vmatrix} R + j\omega(L_1 + L) & V_1 \\ j\omega(M - L) & 0 \end{vmatrix}$$

$$= -V_1 (j\omega(M - L)) = V_1 (j\omega(L - M))$$

$$I_1 = \Delta_1 / \Delta \quad I_2 = \Delta_2 / \Delta$$

$$I_1 / I_2 = \Delta_1 / \Delta_2 = \frac{R + j\omega(L_2 + L)}{j\omega(L - M)}$$

Conductively coupled equivalent

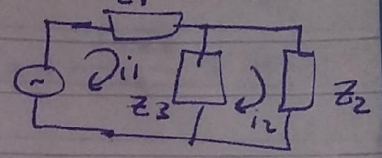

$$V = (Z_1 + Z_3) I_1 - Z_3 I_2 \rightarrow (3)$$

$$0 = -Z_3 I_1 + (Z_2 + Z_3) I_2 \rightarrow (4)$$

compare 3, 4 by 1, 2

$$\Rightarrow Z_1 + Z_3 = R + j\omega(L_1 + L) \rightarrow (5)$$


$$-Z_3 = j\omega(M - L)$$

$$\text{or } Z_3 = j\omega(L - M) \rightarrow (6)$$

$$\therefore Z_1 = R + j\omega(L_1 + M) \rightarrow (7)$$

$$Z_2 = R + j\omega(L_2 + L) - j\omega(L - M)$$
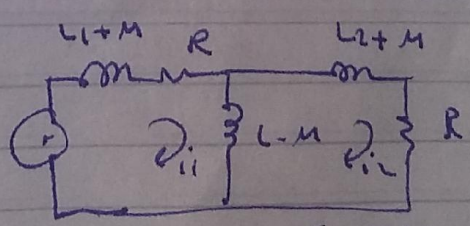
$$\therefore Z_2 = R + j\omega(L_2 + M) \rightarrow (8)$$




الناظرية المكافئة

Find impedance faced by Voltage source  $V$  in the circuit

Sol

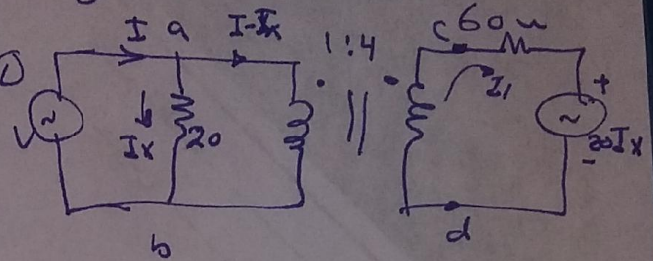From figure  $V = V_{ab} = 20I_x \rightarrow (1)$



→ Current through Primary  
 $= I - I_x = I_p$

$$\therefore \frac{N_p}{N_s} = \frac{I_s}{I_p} = \frac{1}{4} = \frac{I_s}{I - I_x} \rightarrow I_s = \frac{I - I_x}{4} = I_1 \rightarrow (2)$$

$$\rightarrow \frac{N_p}{N_s} = \frac{1}{4} = \frac{V_p}{V_s} = \frac{V}{V_{cd}}$$

$$\therefore V_{cd} = 4V = \frac{I_s \times 60}{I_p} + V_{source} = 60 \times \frac{I - I_x}{4} + 20I_x$$

$$\therefore 4V = 15(I - I_x) + 20I_x$$

from (1)

$$4V = 15I - 15I_x + 20I_x$$


$$4V = 15I + 5I_x$$

$$4V = 15I + 5\left(\frac{V}{20}\right)$$

$$\therefore V = 4I \quad \therefore \frac{V}{I} = 4 = \text{impedance}$$

Q.11)

Determine the current  $I_x$  ?

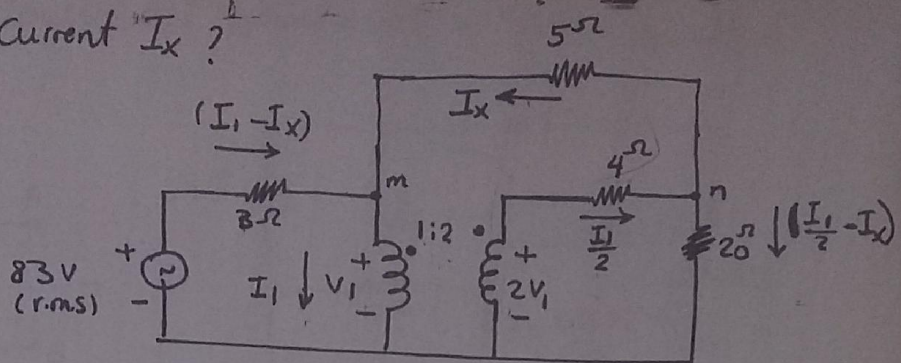

answer.

•  $V_1 =$  primary voltage,  $I_1 =$  primary current

$$\frac{N_1}{N_2} = \frac{N_p}{N_s} = \frac{1}{2} = \frac{V_p}{V_s} = \frac{I_s}{I_p}$$

$$V_s = 2V_p = 2V_1$$

$$I_s = \frac{I_p}{2} = \frac{I_1}{2}$$

$$\text{• KCL at } m \Rightarrow I(\text{on } 3\Omega \text{ resis}) = I_1 - I_x$$

$$\text{• KCL at } n \Rightarrow I(\text{on } 20\Omega \text{ resis}) = \frac{I_1}{2} - I_x$$

• KVL at primary loop:

$$83 = 3(I_1 - I_x) + V_1 \rightarrow \textcircled{1}$$

• KVL at secondary loop:

$$2V_1 = 4\left(\frac{I_1}{2}\right) + 20\left(\frac{I_1}{2} - I_x\right) \rightarrow \textcircled{2}$$

• apply the KVL for the loop shown

$$2V_1 = 4 \cdot \frac{I_1}{2} + 5I_x + V_1$$

$$\downarrow$$

$$\therefore V_1 = 2I_1 + 5I_x \rightarrow \textcircled{3}$$

عوض من ③ في ① و ②

$$\therefore 83 = 3(I_1 - I_x) + (2I_1 + 5I_x) = 5I_1 + 2I_x \rightarrow \textcircled{4}$$



$$\& 2(2I_1 + 5I_x) = 4\left(\frac{I_1}{2}\right) + \frac{20}{2}I_1 - \frac{20}{2}I_x$$

$$\therefore 8I_1 = 30I_x \rightarrow \textcircled{5}$$

, solve ④ & ⑤

$$\therefore \boxed{I_x = 4A} \text{ r.m.s}$$

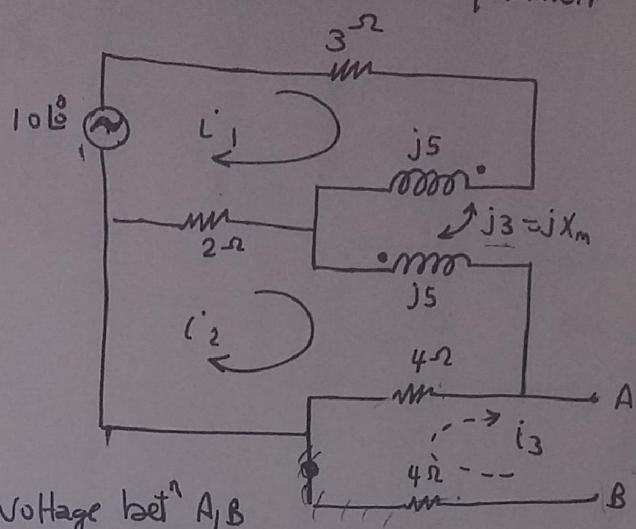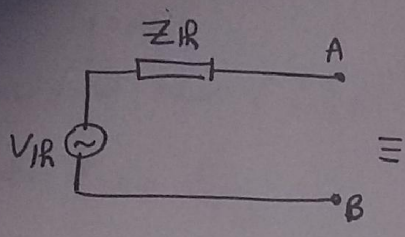22  
 Replace the coupled net<sup>K</sup> shown with a Thevenin equivalent to A, B:



answer

$V_{IR} = V_{AB} = \text{open-circuit voltage bet}^n A, B$

$= I_2 (4^{\Omega})$   
 ??

⇒ the other (4<sup>Ω</sup>) resistor has no voltage drop on it (open).

We need to write the mesh equations of the (2-loop) Ⓢ:

Loop ① ⇒  $10 \angle 0^\circ = i_1 (3^\Omega) + 2^\Omega (i_1 - i_2) + [j5 (i_1) + j3 i_2]$  → ①

Loop ② ⇒  $0 = 2 (i_2 - i_1) + 4 (i_2) + [j5 (i_2) + j3 i_1]$  → ②

∴  $\Delta = \begin{bmatrix} 5 + j5 & -2 + j3 \\ -2 + j3 & 6 + j5 \end{bmatrix}$

$\Delta_2 = \begin{bmatrix} 5 + j5 & 10 \angle 0^\circ \\ -2 + j3 & 0 \end{bmatrix} \Rightarrow I_2 = \frac{\Delta_2}{\Delta} = 0.533 \angle -137.8^\circ \text{ A}$

∴  $V_{IR} = [0.533 \angle -137.8^\circ] * 4^\Omega = 2.13 \angle -137.8^\circ$

- ⇒ To find  $Z_{IR}$  ?
- 1) S.C all voltage sources.
  - 2) o.c all cur sources.
  - 3) find  $Z_{in}$  bet<sup>n</sup> A, B


we have now (3-loops)<sub>x</sub> looking from A, B as followi  
 when

we need 3-equations of the loops:

⇒ find new  $(\Delta') \equiv \begin{bmatrix} a & b & c \\ d & e & f \\ g & h & i \end{bmatrix}$

⇒  $Z_{in} = \frac{\Delta'}{\Delta_{33}}$

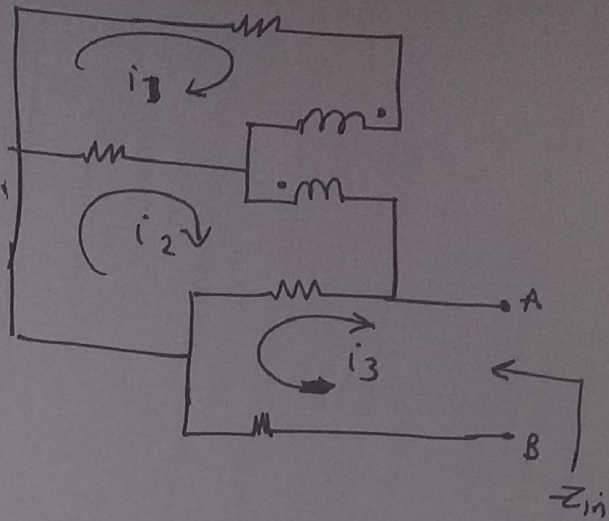$\Delta_{33} = \begin{bmatrix} a & b \\ d & e \end{bmatrix}$



Loop ① ⇒  $0 = i_1(3) + 2(i_1 - i_2) + [j5 i_1 + j3 i_2] \rightarrow$   
self mut

$0 = i_1(5 + j5) + i_2(-2 + j3) + i_3(0) \rightarrow \text{①}$

Loop ② ⇒  $0 = 2(i_2 - i_1) + 4(i_2 - i_3) + [j5 i_2 + j3 i_1]$   
self mut

$0 = i_1(-2 + j3) + i_2(6 + j5) + i_3(-4) \rightarrow \text{②}$

Loop ③  $0 = 4(i_3 - i_2) + 4(i_3)$


$0 = i_1(0) + i_2(-4) + i_3(8) \rightarrow \text{③}$

$\Delta' = \begin{bmatrix} 5 + j5 & -2 + j3 & 0 \\ -2 + j3 & 6 + j5 & -4 \\ 0 & -4 & 8 \end{bmatrix} = \checkmark$


$\Delta_{33} = \begin{bmatrix} 5 + j5 & -2 + j3 \\ -2 + j3 & 6 + j5 \end{bmatrix} = \checkmark$

$Z_R = Z_{in} = Z_{AB} = \frac{\Delta'}{\Delta_{33}} = 6.74 \angle 8.5^\circ \Omega$

$= 6.65 + j 0.996$

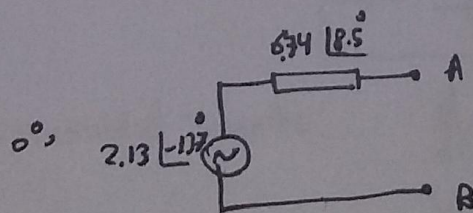

⇒ For parallel Connections:

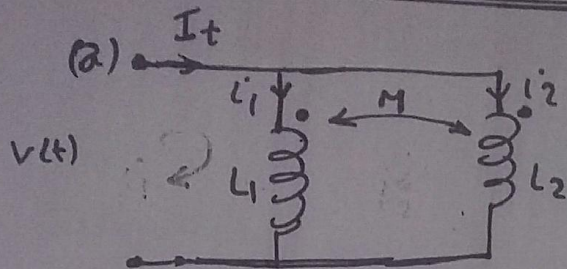

$$v(t) = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$

&

$$v(t) = L_2 \frac{di_2}{dt} + M \frac{di_1}{dt}$$

or sinus.

$$j\omega L_1 i_1 + j\omega M i_2 = v$$

$$j\omega M i_1 + j\omega L_2 i_2 = v$$

$$\Delta = \begin{bmatrix} j\omega L_1 & j\omega M \\ j\omega M & j\omega L_2 \end{bmatrix}$$

$$= \omega^2 (M^2 - L_1 L_2)$$

$$\Delta_1 = \begin{bmatrix} v & j\omega M \\ v & j\omega L_2 \end{bmatrix} = v(j\omega)(L_2 - M)$$

$$\Delta_2 = \begin{bmatrix} j\omega L_1 & v \\ j\omega M & v \end{bmatrix} = v(j\omega)(L_1 - M)$$


$$I_t = I_1 + I_2 = \frac{\Delta_1}{\Delta} + \frac{\Delta_2}{\Delta}$$

$$I_t = \frac{j\omega (L_1 + L_2 - 2M)v}{\omega^2 (M^2 - L_1 L_2)}$$

$$\frac{v}{I_t} = Z_{in} = \frac{\omega (M^2 - L_1 L_2)}{j (L_1 + L_2 - 2M)}$$

$$\begin{aligned} \therefore Z_{in} &= \frac{\omega (M^2 - L_1 L_2)}{j (L_1 + L_2 - 2M)} \cdot \frac{j}{j} \\ &= j\omega \left[ \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \right] \\ &= j\omega L_{eq} = j\omega L_a \end{aligned}$$
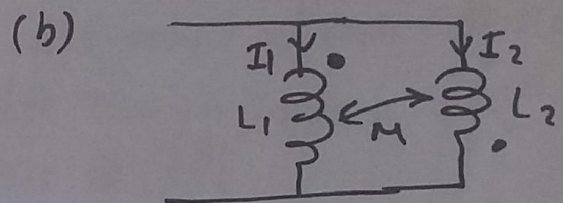
$$\therefore L_a = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$



$$L_{eq} = L_b = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$

#