

Section (7)

MidTerm - Solution


Question (1)

a- Determine the Quality Factor and Bandwidth for a series Resonance Circuit whose response curve is shown in figure 1.

b- For $C = 10\text{pF}$, determine L , and R and Applied Voltage.

Solution

$$\frac{I_{max}}{\sqrt{2}} = 141$$

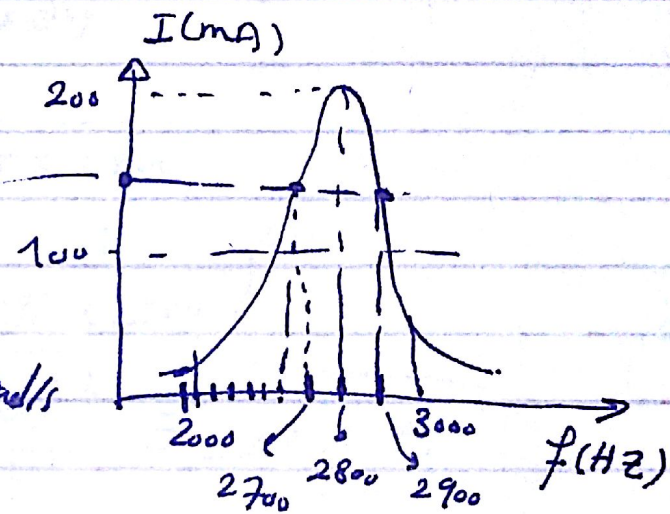

→ f_r from curve at 2800 Hz

$$\omega_0 = 2\pi \times 2800 = 17952.9 \text{ rad/s}$$

→ BW at $I = \frac{200}{\sqrt{2}} = 141 \text{ mA}$

$$\omega \rightarrow F_1 = 2700 \text{ Hz}$$

$$F_2 = 2900 \text{ Hz}$$

∴ Bandwidth = $2900 - 2700 = 200 \text{ Hz}$ → (1)

or $BW (\text{rad/s}) = 200 \times 2\pi = 1256.6 \text{ rad/s}$

∴ $Q = \frac{\omega_0}{B} = \frac{17952.9}{1256.6}$ or $\frac{2800}{200}$ or $\frac{17952.9}{1256.6} = 14$

→ (2)

b - $C = 10 \text{ pF}$

$$\omega_c = \frac{1}{\sqrt{LC}} \quad \text{or} \quad f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$2800 = \frac{1}{2\pi\sqrt{L \times (10 \times 10^{-12})}}$$

$$2\pi \times 2800 = \frac{1}{\sqrt{L(10 \times 10^{-12})}}$$

$$\sqrt{L(10 \times 10^{-12})} = \frac{1}{2\pi \times 2800}$$

$$L \times (10 \times 10^{-12}) = \left(\frac{1}{2\pi \times 2800}\right)^2$$

$$L = \frac{\left(\frac{1}{2\pi \times 2800}\right)^2}{10 \times 10^{-12}} \approx 323.1 \text{ H}$$

فرسنتج به ما علینا (:

Now $B_{rad/s} = R/L$ or $B_{Hz} = \frac{R}{2\pi L}$

$$1256.6 = \frac{R}{323.1} \quad \therefore R \approx 406 \text{ k}\Omega$$

$$V = I_{max} R = (200 \text{ mA})(406 \text{ k}\Omega)$$

$$V = 81.19 \text{ MV}$$

رقم فراغی (:

- 4 -

To calculate $H(\omega_0)$

جواب

$$H(\omega_0) = \frac{1}{\sqrt{2}} H_{max} = \frac{1}{\sqrt{2}} (1)$$

$$\text{or } \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(1-\omega^2)^2 + (4\omega)^2}}$$

$$\text{or } 2 = (1-\omega^2)^2 + (4\omega)^2$$

$$2 = 1 + \omega^4 - \underline{2\omega^2} + \underline{16\omega^2}$$

$$\text{or } \omega^4 + 14\omega^2 - 1 = 0$$

$$x^2 + 14x - 1 = 0$$

$$\text{or } x = \omega^2$$

$$x = \frac{-14 \pm \sqrt{(14)^2 - 4(-1)}}{2}$$

$$= \frac{-14 \pm \sqrt{200}}{2}$$

$$= 0.071 \quad \text{or } -14.07 \quad \times \text{ refused}$$

$$\text{or } \omega^2 = 0.071$$

$$\boxed{\omega = 0.2665}$$

$$H(\omega) = \frac{1}{\sqrt{2}}$$
