

1

Sheet (7)

1] A series RL with $R=50\ \Omega$, and $L=10\text{H}$, has a constant voltage $V=100\text{V}$ applied at $t=0$ by closing of a switch. Find

(a) equations for i , V_R , and V_L .

(b) The current at $t=0.5\text{s}$

(c) The time at which $V_R=V_L$

(d) Find the equations for P_R and P_L and show that the power in inductance accounts for the steady state energy in the magnetic field.

← Solution →

By closing switch $\sum V=0$

$$+100 - (i)(50) - L \frac{di}{dt} = 0$$

$$100 = 50i + 10 \frac{di}{dt}$$

$$100 = i(50 + 10D) = 10i(5 + D)$$

$$\therefore \boxed{10 = i(5 + D)}$$

→ 2 solutions → P.I
→ Complementary

for P.I complementary sol.

$$\text{put } D=0 \therefore i = 10/5 = 2$$

for complementary sol.

$$(D + 5)i = 10$$

$$0 = m + 5$$

$$m = -5$$


\therefore sol \underline{c}

$$= Ae^{mt}$$

$$= Ae^{-5t}$$

تفاضل الطرفين

$$\boxed{i/t = Ae^{-5t} + 2}$$

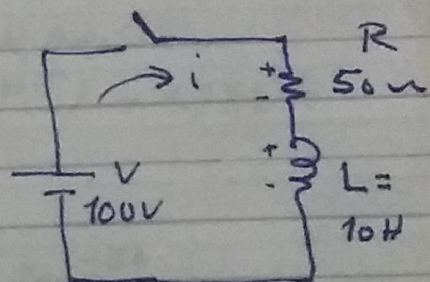

at $t=0 \rightarrow i_0=0$



-2-

$$0 = 2 + Ae^{-0} \quad \therefore A = -2$$

$$i(t) = -2e^{-5t} + 2 = 2(1 - e^{-5t})$$

$$\rightarrow V_R = iR = 100(1 - e^{-5t})$$
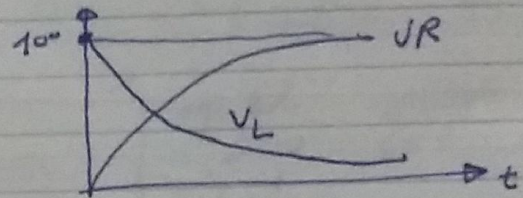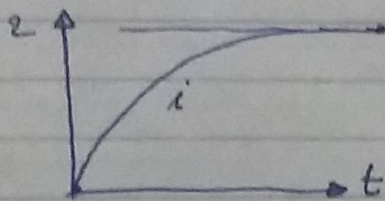
$$\rightarrow V_L = L \frac{di}{dt} = 10 \times [-2e^{-5t} \times -5] = 100e^{-5t}$$



(b) Current at $t=0.5$

المؤقتة لاجل التوضيح

$$i = 2(1 - e^{-5t}) = 2(1 - e^{-5 \times 0.5}) = 1.836 \text{ A}$$

(c) when $V_R = V_L$ find t

$$100(1 - e^{-5t}) = 100e^{-5t} \quad \therefore 100 = 200e^{-5t}$$

$$\therefore e^{-5t} = \frac{1}{2} \quad \ln e^{-5t} = \ln \frac{1}{2}$$

$$\therefore -5t = \ln \frac{1}{2} / \ln e \quad \text{or} \quad t = \frac{-1}{5} \ln \frac{1}{2} / \ln e$$

$$t = 0.1386 \text{ sec}$$

(d) P_R, P_L $\ast P_R = V_R i = 100(1 - e^{-5t})(2(1 - e^{-5t}))$

$$= 200(1 - 2e^{-5t} + e^{-10t})$$


$$P_L = V_L i = (100e^{-5t})(2(1 - e^{-5t})) = 200(e^{-5t} - e^{-10t})$$

~~* steady~~

$$\omega = \frac{1}{L} \quad \therefore \omega = \frac{1}{0.1} = 10 \text{ rad/s} = 2\pi f \quad \therefore f = \frac{10}{2\pi} = 1.59 \text{ Hz}$$

2 In the series circuit shown in fig. 1, the switch is closed on position 1 at $t=0$, thereby applying the 100 Volt source to the RL branch, and at $t=500 \mu\text{sec}$ the switch is moved to position 2 obtain the equations for current in both intervals and sketch transient.

Sol.

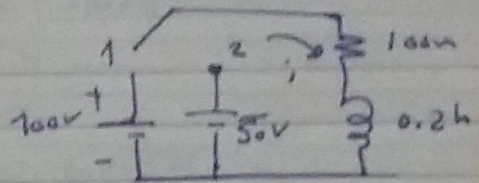

→ at Pos. 1

$$+100 = 100i + 0.2 \frac{di}{dt}$$

$$500 = 500i + di/dt$$

$$(D + 500)i = 500$$

$$i_{t_1} = 1 + A e^{-500t}$$

at $t=0$ $i_0 = 0$ $A = -1$

$$i_{t_1} = 1 - e^{-500t} \rightarrow I \quad \text{for } 0 < t < t_1$$

→ at $t = 500 \mu\text{sec}$ $i = 1 - e^{-500 \times 500 \mu\text{s}} = 0.221 \text{ A}$

Switch now at position 2, $V_{\text{source}} = 50\text{V}$

$$50 = 100i + 0.2 \frac{di}{dt}$$

$$i_{t_2} = 0.5 + B e^{-500t_2}$$


or $(D + 500) = 250$

where $t_2 = t - t_1$
↳ $500 \mu\text{s}$

at $t = t_1 = t_2 = 0$, $i_2 = 0.221 \text{ A}$

$$\therefore 0.22 \text{ A} = 0.5 + B \quad \therefore B = -0.279$$

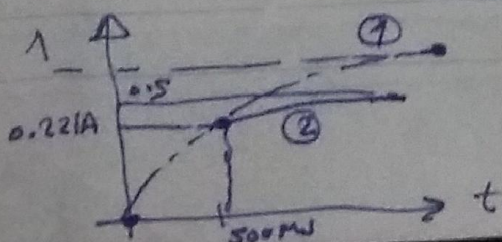for $t > t_1$ $\therefore i_{t_2} = 0.5 - 0.279 e^{-500(t-t_1)}$
↳ $500 \mu\text{s}$



- 4 -

3 Repeat 2 with 50 volt polarity Reversed.

$$i(t_1) = 1 - e^{-500t} \rightarrow I$$

i is in $\frac{V}{\Omega}$


$$i \text{ at } 500 \mu\text{sec} = 0.221 \text{ A}$$

Now $100i + 0.2 \frac{di}{dt} = -50$ $(D + 500)i = -250$

$$i = B_2 e^{-500t_2} - 0.5$$

For $t = t_1 \Rightarrow i_2 = 0.221$ $B_2 = +0.721$
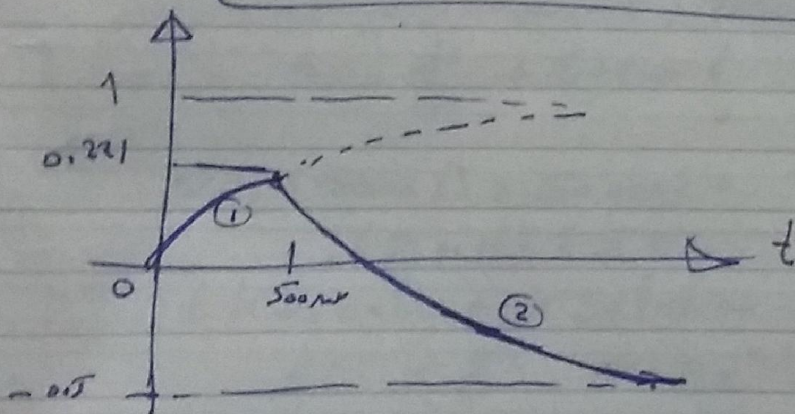
$$i_{2t} = +0.721 e^{-500(t-t_1)} - 0.5$$




[4] A series RC circuit with $R=5000 \Omega$ and $C=20 \mu F$ has a constant voltage $V=100V$ applied at $t=0$ and the capacitor has no initial charge. Find the equations of i , V_R , and V_C .

Sol.
S closed

$$100 = i(5000) + \frac{1}{C} \int i dt \rightarrow \boxed{1} \quad 100V$$
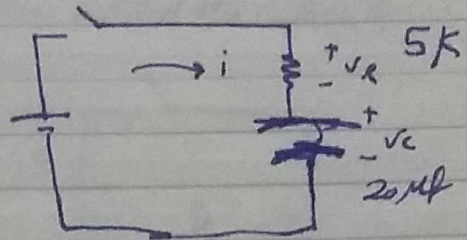
$$100 = 5000i + \frac{1}{20 \times 10^{-6}} \int i dt$$



$$100 = 5000i + 50000 \int i dt$$

نفاضل الطرفين للتخلص من التكامل

$$0 = 5000 \frac{di}{dt} + 50000 i$$

$$0 = (5000D + 50000) i$$

$$(D+10) i = 0$$

it has only one solution (P.I)

$$i = A e^{mt} = A e^{-10t}$$

$$m+10=0$$

$$m=-10$$

at $t=0 \rightarrow$ sub in 1 $\therefore 100 = 5000i$ or $i = 100/5000$

$$i = 0.02A$$

$$\therefore \boxed{i = 0.02 e^{-10t}}$$

$$X_C = \frac{1}{2\pi f C} = 0$$

$$\frac{m}{2\pi C} = 0$$

$$E_C = \int V_C dt = V_R$$

$$V_R = Ri = 5000 \times 0.02 e^{-10t} = 100 e^{-10t}$$

$$V_C = \frac{1}{C} \int i dt = \frac{1}{20 \times 10^{-6}} \int 0.02 e^{-10t} dt = 100 (1 - e^{-10t})$$

$$V_C = -100 e^{-10t} + C$$



at $t=0 \quad V_R = 100, V = 100 - V_C = 0$

$$\therefore 0 = -100 e^0 + C \quad \therefore C = 100$$

$$\therefore V_C = 100 - 100 e^{-10t} = 100 (1 - e^{-10t})$$

$$\int e^{-10t} dt = -\frac{1}{10} e^{-10t} + C = V_C$$

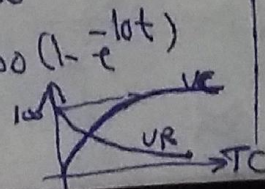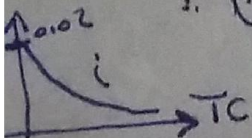
at $t=0 \quad V_C = 0$
 $\Rightarrow 100 - 100 e^{-10 \cdot 0} = 0$



5] The 20mF in RC circuit shown in Fig. 2 has an initial charge $q_0 = 500$ microcoulombs, with polarity shown, at $t = 0$ the switch is closed thereby applying the constant voltage $V = 50$ volts, Find the current transient.

Sol.

S → closed

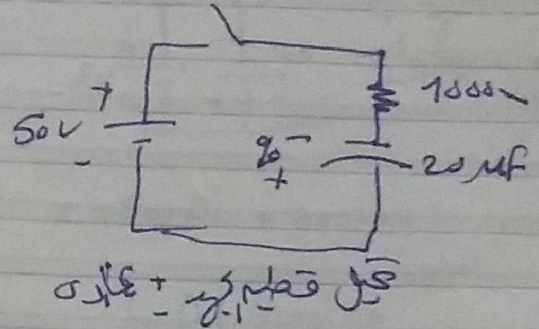

$$50 = 1000i + \frac{1}{c} \int i dt \rightarrow$$

$$50 = 1000i + \frac{1}{20 \times 10^{-6}} \int i dt$$

$$50 = 1000i + 50000 \int i dt$$

$$0 = 1000 \frac{di}{dt} + 50000 i \quad \text{بتفاضل الطرفين}$$

$$0 = \frac{di}{dt} + 50i \quad \therefore (50 + D)i = 0$$

one solution only \rightarrow P.I $i = A e^{mt}$

$$m = -50$$

\rightarrow at $t = 0$ $i = 50/1000 + \text{initial voltage due to initial charge}/R$

\rightarrow ~~initial current~~ ^{voltage} due to charge = q_0/c \Rightarrow $q_0 = CV$

$$= 500 \times 10^{-6} / 20 \times 10^{-6} = 25V$$

و چونکہ $t = 0$ پر $i = 50/1000 + 25$ ہے اور $q_0 = CV$ ہے لہذا $25V = q_0/c$ ہے۔
 وقتی تعین لگنا ہے $i = A e^{-50t}$ میں A کی قیمت کا تعین کرنا ہے۔


$$i_0 = (V + q_0/c)/R = (50 + 25)/1000 = 0.075 A$$

\rightarrow at $t = 0$ $i = 0.075 = A e^0 \quad \therefore A = 0.075$

$$\therefore i = 0.075 e^{-50t}$$

6 In the RC circuit shown in figure 3 the switch is closed in Position 1 at $t=0$, after $1 \tau_c$ moved to 2 Find complete current transient

Sol.

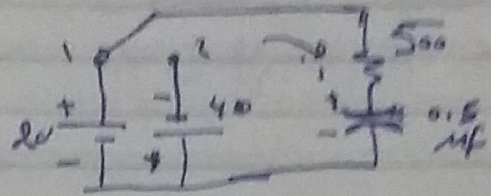

at Position 1

$$20 = 500i + \frac{1}{C} \int i dt$$

بقانون: $0 = 500 \frac{di}{dt} + \frac{1}{0.5 \times 10^{-6}} i$

$$0 = 500 Di + 2000000 i$$

$$0 = Di + 4000 i$$

$$i(D + 4000) = 0$$

$$i_1 = A e^{-4000t}$$

at $t=0 \rightarrow i = 20/500 = 0.04 = A$

$$i_1 = 0.04 e^{-4000t}$$

$250 \mu\text{sec} = (1RC) = 1TC$ *تحتوي على*

after $1TC = 1RC = 250 \mu\text{sec}$


$$i = 0.04 \times e^{-400 \times 250 \mu} = 0.147 A$$

Now switch moved to 2

$$-40 = 500i + \frac{1}{C} \int i dt$$

$$0 = 500 di/dt + \frac{1}{0.5 \times 10^{-6}} i$$

$$i_2 = B e^{-4000(t-t_1)}$$

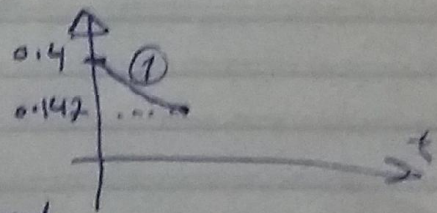

at $t=t_1 = 250 \mu\text{sec}$ *تحتوي على*

$$\frac{1}{C} \int i dt = V_c$$

$$V_c = -20 e^{-4000t} + K$$

at $t=0$ $K = +20$ ($V_c = 0$)
 $V_c = 20(1 - e^{-4000t}) \rightarrow t = RC = 1TC$

250×10^{-6}

∴ $V_C = 20(1 - e^{-4000t}) = 20(1 - e^{-4000 \times RC})$
 طنة زمة RC

$$= 20(1 - e^{-1}) = 12.65 \text{ Volt}$$

∴ $i_2 = B e^{-4000(t-t_1)}$


لا مقدار ايمان قطة C
 مع ايمان قطة B = 40V

at $t = t_1 \Rightarrow i = \frac{V_{total}}{R}$

$i = \frac{40 + 12.65}{500} = 0.1053 \text{ A}$

لا مقدار ايمان قطة B مع ايمان قطة A
 ايمان قطة A = 40V

∴ $i_2 = -0.1053 e^{-4000(t-t_1)}$

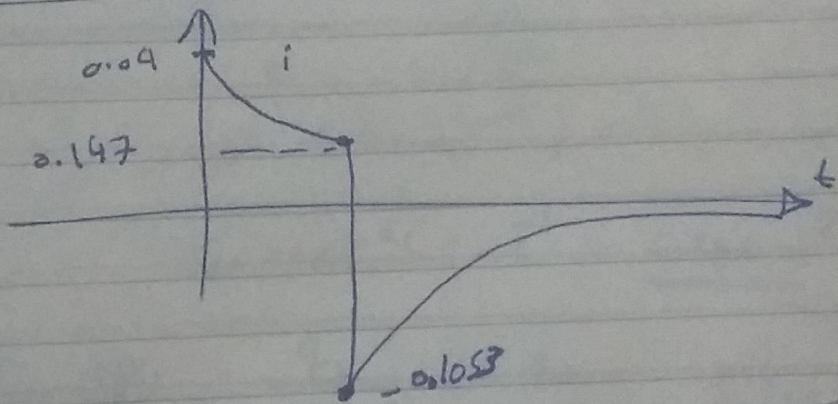

$-40 = V_C = 500i + \frac{1}{C} \int i dt$
 الجهد المتبقية من نظام بعد $t = T$ توضيح

$V_C = \frac{1}{C} \int i dt = \square + K = 20(1 - e^{-4000t}) = 12.65$

∴ $-40 - 12.65 = 500i + \frac{1}{C} \int i dt$

$i_2 = B e^{-4000(t)}$

at $t = 0 : i_2 = B$

$-40 - 12.65 = 500i$

$i = -0.1053 = B$

∴ $i = -0.1053 e^{-4000t}$

- 9 -

[7] Determine the charge transient for prob. 6 and differentiate to obtain current

at position 1

$$500 \frac{dq_1}{dt} + \frac{q_1}{0.5 \times 10^{-6}} = 20$$

$\therefore (D + 4000) q_1 = 0.04$

Sol

$$q_1 = A e^{mt} + B$$

$m = -4000$

$$B = \frac{0.04}{4000} = 10 \times 10^{-6}$$

$\therefore q_1 = A e^{-4000t} + 10 \times 10^{-6}$

at $t=0$, $q_1=0 \quad \therefore A = -10 \times 10^{-6}$

or $q_1 = 10 \times 10^{-6} (1 - e^{-4000t})$

after $t = 1TC$ $q_1 = 10 \times 10^{-6} (1 - e^{-1}) = 6.32 \times 10^{-6}$ sln

at S2

$$500 \frac{dq_2}{dt} + \frac{q_2}{0.5 \times 10^{-6}} = -40$$

$$(D + 4000) q_2 = -0.08$$

Solution

$$q_2 = C e^{m_2 t} + K$$

$$m_2 = -4000$$

$$K = \frac{-0.08}{4000} = -20 \times 10^{-6}$$

$$q_2 = C e^{-4000t_2} - 20 \times 10^{-6}$$

at $t = 0$ ($t = t_1$) $\rightarrow q_2 = 6.32 \times 10^{-6}$

$$\therefore C = 26 \times 10^{-6}$$

$\therefore q_2 = 26 \times 10^{-6} e^{-4000t} - 20 \times 10^{-6}$

$t < t_1$

— 10 —

$$i_1 = \frac{d}{dt} \left\{ 10 \times 10^{-6} (1 - e^{-4000t}) \right\} = 0.04 e^{-4000t}$$

$t > t_1$

$$i_2 = \frac{d}{dt} \left\{ 26.32 \times 10^{-6} e^{-4000(t-t_1)} - 20 \times 10^{-6} \right\}$$

$$= -0.153 e^{-4000(t-t_1)}$$

