



---

## Sheet (10) ... Three Phase Systems

1. A three-phase, three-wire 100 volt, ABC system supplies a balanced delta-connected load with impedances of  $20\angle 45^\circ$  ohms. Determine the line currents and draw the phasor diagram.
2. Three identical impedances of  $5\angle 30^\circ$  ohms are connected in wye to a three-phase, three-wire, 150 volt, CBA system. Find the line currents and draw the phasor diagram.
3. Three identical impedances of  $10\angle 30^\circ$  ohms in a wye connection and three identical impedances of  $15\angle 0^\circ$  ohms also in a wye connection are both on the same three-phase, three-wire 250 volt system. Find the total power.
4. Three identical impedances of  $12\angle 30^\circ$  ohms in a delta connection and three identical impedances of  $5\angle 45^\circ$  ohms in a wye connection are on the same three-phase, three wire, 208 volt, ABC system. Find the line currents and the total power.
5. A three-phase, three-wire, 240 volt, CBA system supplies a delta-connected load in which  $Z_{ab} = 25\angle 90^\circ$ ,  $Z_{bc} = 15\angle 30^\circ$  and  $Z_{ca} = 20\angle 0^\circ$  ohms. Find the line currents and the total power.
6. A three-phase, four-wire, 208 volt, ABC system supplies a wye-connected load in which  $Z_A = 10\angle 0^\circ$ ,  $Z_B = 15\angle 30^\circ$  and  $Z_C = 10\angle -30^\circ$  ohms. Find the line currents, the neutral current and the total power.
7. The load impedances of Problem 6 are connected to a three-phase, three-wire, 208 volt, ABC system. Find the line currents and the voltages across the load impedances.

*Best Wishes;*

*Dr. Basem ElHalawany*