



Sheet (2)... Series Resonance

1. A series RLC network has $R=2\text{k}\Omega$, $L=40\text{ mH}$, and $C=1\mu\text{F}$. Calculate the impedance at resonance and at one-fourth, one-half, twice, and four times the resonant frequency.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}} = 5 \text{ krad/s}$$

$$\mathbf{Z(\omega_0) = R = 2 \text{ k}\Omega}$$

$$\mathbf{Z(\omega_0/4) = R + j\left(\frac{\omega_0}{4}L - \frac{4}{\omega_0 C}\right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j\left(\frac{5 \times 10^3}{4} \cdot 40 \times 10^{-3} - \frac{4}{(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j(50 - 4000/5)}$$

$$\mathbf{Z(\omega_0/4) = 2 - j0.75 \text{ k}\Omega}$$

$$\mathbf{Z(\omega_0/2) = R + j\left(\frac{\omega_0}{2}L - \frac{2}{\omega_0 C}\right)}$$

$$\mathbf{Z(\omega_0/2) = 2000 + j\left(\frac{(5 \times 10^3)}{2}(40 \times 10^{-3}) - \frac{2}{(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(\omega_0/2) = 200 + j(100 - 2000/5)}$$

$$\mathbf{Z(\omega_0/2) = 2 - j0.3 \text{ k}\Omega}$$

$$\mathbf{Z(2\omega_0) = R + j\left(2\omega_0 L - \frac{1}{2\omega_0 C}\right)}$$

$$\mathbf{Z(2\omega_0) = 2000 + j\left((2)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(2)(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(2\omega_0) = 2 + j0.3 \text{ k}\Omega}$$


$$\mathbf{Z(4\omega_0) = R + j\left(4\omega_0 L - \frac{1}{4\omega_0 C}\right)}$$

$$\mathbf{Z(4\omega_0) = 2000 + j\left((4)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(4)(5 \times 10^3)(1 \times 10^{-6})}\right)}$$

$$\mathbf{Z(4\omega_0) = 2 + j0.75 \text{ k}\Omega}$$



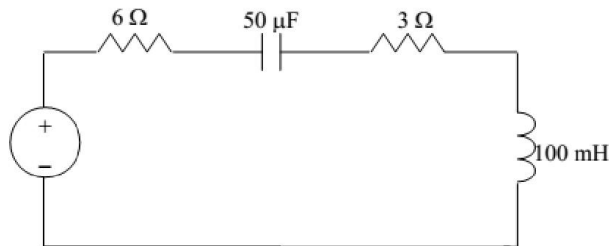2. A coil with resistance 3Ω and inductance 100 mH is connected in series with a capacitor of $50\text{ }\mu\text{F}$, a resistor of 6Ω and a signal generator that gives 110 V rms at all frequencies. Calculate ω_0 , Q , and B at resonance of the resultant series RLC circuit.



$$R = 6 + 3 = 9\ \Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{100 \times 10^{-3} \times 50 \times 10^{-12}}} = 447.21\ \text{krad/s}$$

$$Q = \frac{\omega_0 L}{R} = \frac{447.21 \times 10^3 \times 100 \times 10^{-3}}{9} = 4969$$

$$B = \frac{\omega_0}{Q} = \frac{447.21 \times 10^3}{4969} = 90\ \text{rad/s}$$

3. Design a series RLC circuit with $B=20\text{ rad/s}$ and $\omega_0=1000\text{ rad/s}$. Find the circuit's Q .

Let $R = 10\ \Omega$.

$$L = \frac{R}{B} = \frac{10}{20} = 0.5\ \text{H}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(1000)^2 (0.5)} = 2\ \mu\text{F}$$



$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$

Therefore, if $R = 10\ \Omega$ then

$$L = \underline{0.5\ \text{H}}, \quad C = \underline{2\ \mu\text{F}}, \quad Q = \underline{50}$$



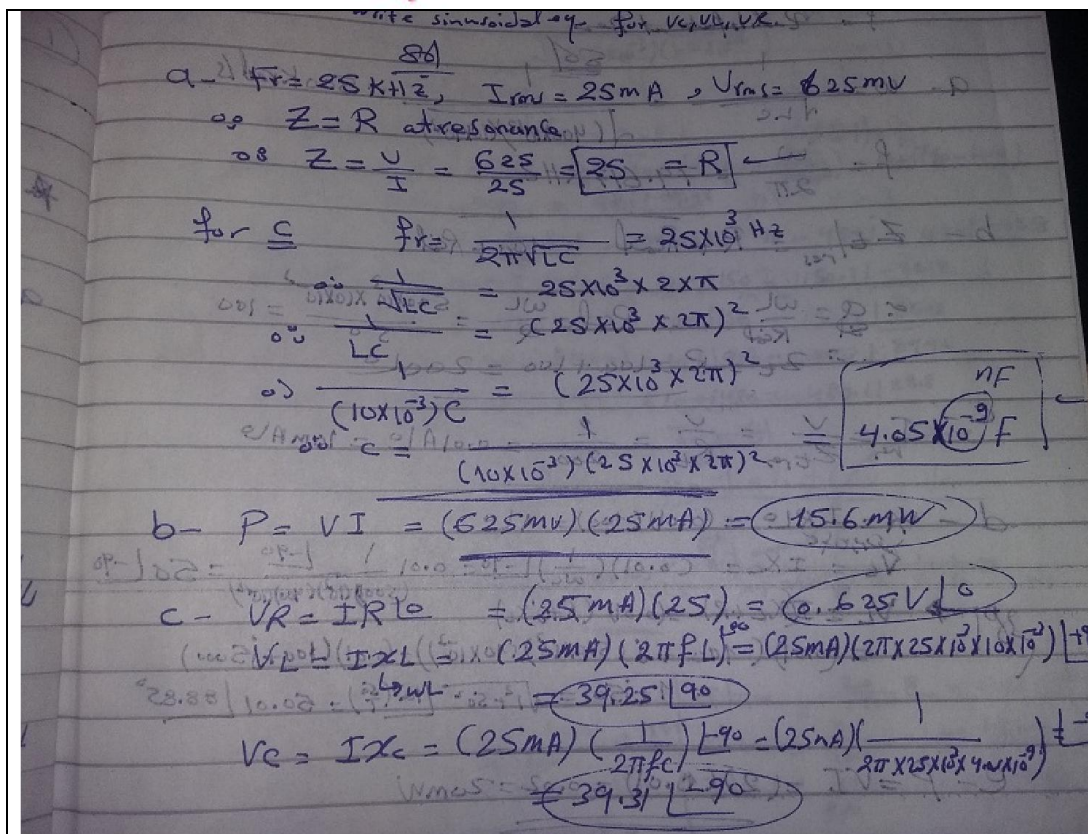
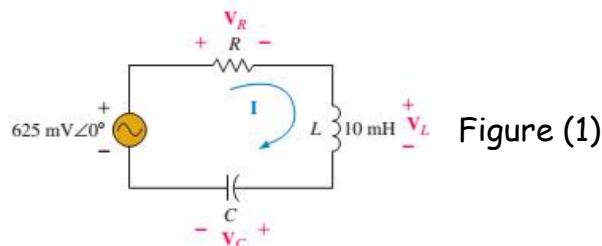
4. Consider the circuit of Figure 1
- Determine the values of R and C such that the circuit has a resonant frequency of 25 kHz and an rms current of 25 mA at resonance.
 - Calculate the power dissipated by the circuit at resonance.
 - Determine the phasor voltages, V_C , V_L , and V_R at resonance.



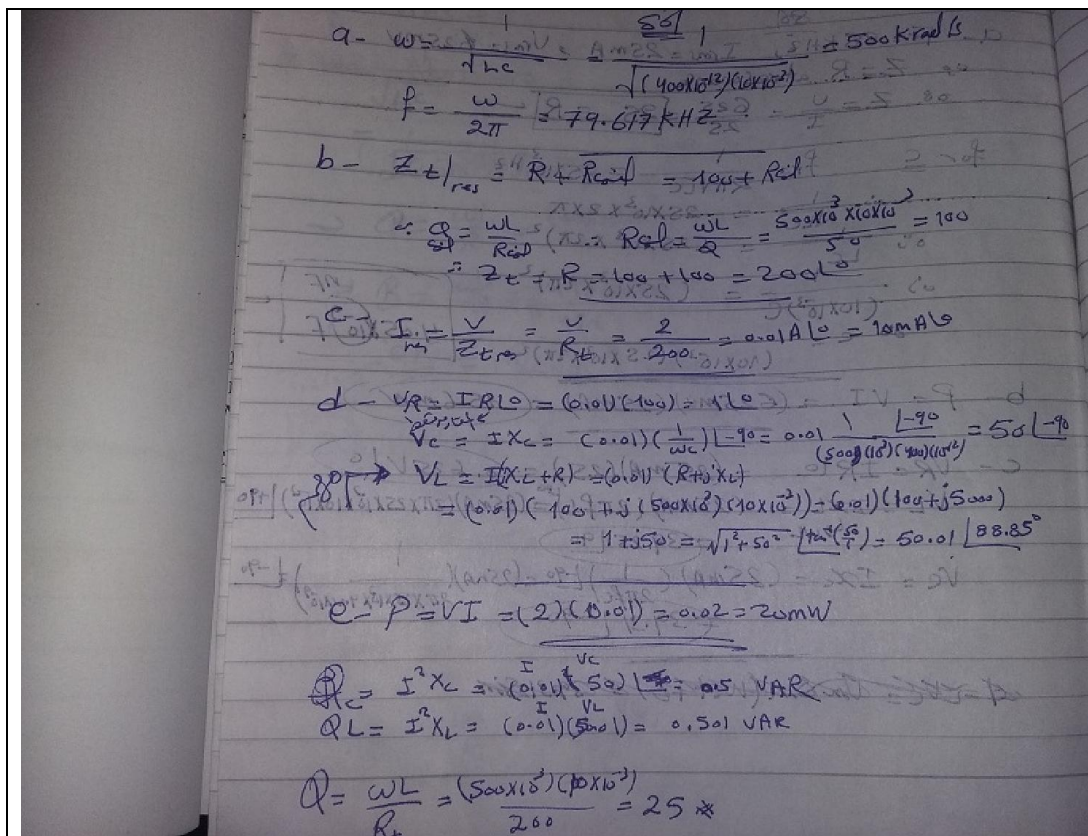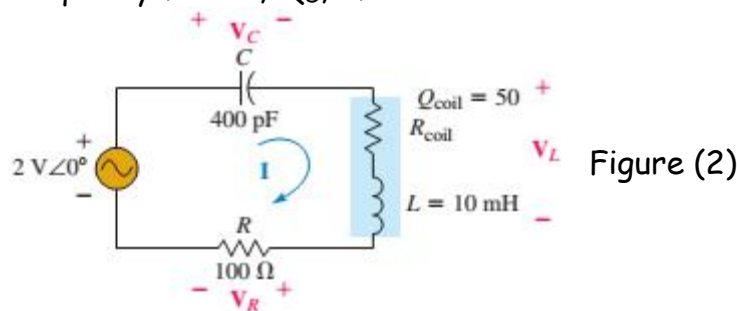5. Refer to the circuit of Figure 2.
- Determine the resonant frequency expressed as ω (rad/s) and f (Hz).
 - Calculate the total impedance, Z_T , at resonance.





- Solve for current I at resonance.
- Solve for V_R , V_L , and V_C at resonance.
- Calculate the power dissipated by the circuit and evaluate the reactive powers, Q_C and Q_L .
- Find the quality factor, Q_S , of the circuit.



- Refer to the circuit of Figure 3.
 - Find ω_S , Q , and BW (in radians per second).
 - Calculate the maximum power dissipated by the circuit.



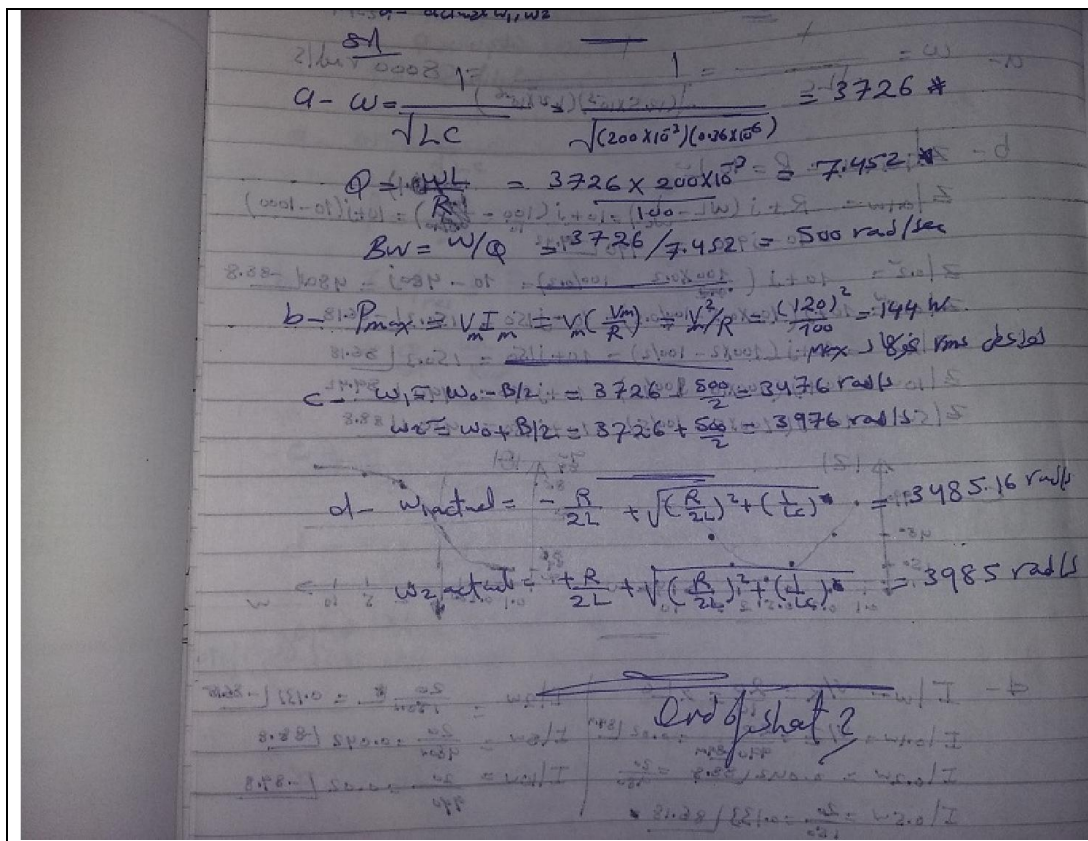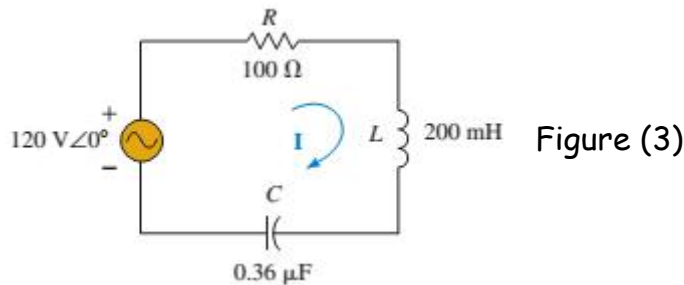- c. From the results obtained in (a) solve for the approximate half-power frequencies, ω_1 and ω_2 .
- d. Calculate the actual half-power frequencies, ω_1 and ω_2 , using the component values and the appropriate equations.



Home Assignment (1):

- For the circuit in Fig. 4, find the frequency ω for which $v(t)$ and $i(t)$ are in phase.

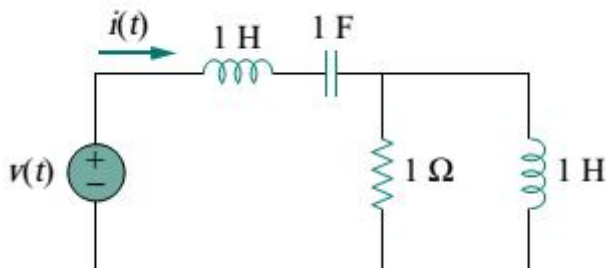


Figure (4)

2. Refer to the series resonant circuit of Figure 5.
- Determine the resonant frequency, ω_S .
 - Solve for the input impedance, $Z_T = Z \angle \theta$, of the circuit at frequencies of $0.1 \omega_S$, $0.2 \omega_S$, $0.5 \omega_S$, ω_S , $2 \omega_S$, $5 \omega_S$, and $10 \omega_S$.
 - Using the results from (b), sketch a graph of Z (magnitude in ohms) versus ω (in radians per second) and a graph of θ (in degrees) versus ω (in radians per second).
 - Using your results from (b), determine the magnitude of current at each of the given frequencies.
 - Use the results from (d) to plot a graph of I (magnitude in amps) versus ω (in radians per second).

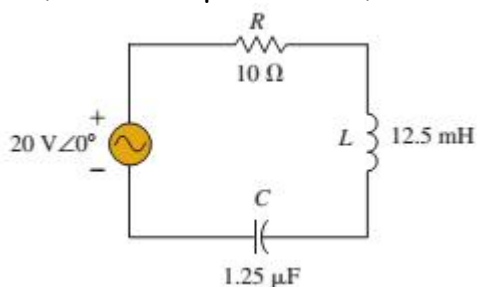


Figure (5)



Assigned

a- $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(12.5 \times 10^{-3})(1.2 \times 10^{-6})}} = 8000 \text{ rad/s}$

b- $Z_{res}(\omega) = R = 40 \Omega$
 $Z|_{0.1\omega} = R + j(\omega L - \frac{1}{\omega C}) = 10 + j(100 - \frac{100}{0.1}) = 10 + j(10 - 1000)$
 $Z|_{0.2\omega} = 10 + j(\frac{100 \times 0.2}{2} - 100/0.2) = 10 - 480j = 480 \angle -88.8^\circ$
 $Z|_{0.5\omega} = 10 + j(100 \times 0.5 - 100/0.5) = 10 - j150 = 150.3 \angle -86.18^\circ$
 $Z|_{2\omega} = 10 + j(100 \times 2 - 100/2) = 10 + j150 = 150.3 \angle 86.18^\circ$
 $Z|_{10\omega} = 10 + j(100 \times 10 - 100/10) = 10 + j990 = 990 \angle 89.42^\circ$
 $Z|_{5\omega} = 10 + j(100 \times 5 - 100/5) = 10 + j480 = 480.1 \angle 88.8^\circ$

c- draw $|Z| \rightarrow \omega$

d- $|I| = ?$

e- plot $|I| \rightarrow \omega$

Diagram: A series RLC circuit with a voltage source of 20V, a resistor of 10Ω, an inductor of 1mH, and a capacitor of 12.5μF.

d- $I|_{\omega} = V/R = \frac{20}{10} = 2 \text{ A}$
 $I|_{0.1\omega} = \frac{20}{Z} = \frac{20}{990.3} = 0.02 \angle 89.4^\circ$
 $I|_{0.2\omega} = \frac{20}{480.1} = 0.042 \angle 88.8^\circ$
 $I|_{0.5\omega} = \frac{20}{150.3} = 0.133 \angle 86.18^\circ$
 $I|_{2\omega} = \frac{20}{150.3} = 0.133 \angle -86.18^\circ$
 $I|_{5\omega} = \frac{20}{480.1} = 0.042 \angle -88.8^\circ$
 $I|_{10\omega} = \frac{20}{990.3} = 0.02 \angle -89.4^\circ$

e- $|I|$ vs ω plot showing a resonance peak at $\omega = 8000 \text{ rad/s}$ with a current of 2A.

Good Luck