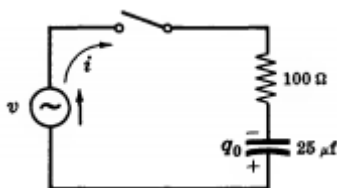




---

## Sheet (8)... AC and DC transient (Advanced)


1. A series RLC circuit with  $R = 3000$  ohms,  $L = 10$  h and  $C = 200 \mu\text{f}$  has a constant voltage  $V = 50$  volts applied at  $t = 0$ . Find the current transient and the maximum value of the current if the capacitor has no initial charge.
2. A series RL circuit with  $R = 50$  ohms and  $L = 0.2$  H has a sinusoidal voltage source  $v = 150 \sin(500t + \emptyset)$  applied at a time when  $\emptyset = 0$ . Find the complete current.
3. A series RC circuit with  $R = 100$  ohms and  $C = 25 \mu\text{f}$  has a sinusoidal voltage source  $v = 250 \sin(500t + \emptyset)$  applied at a time when  $\emptyset = 0^\circ$ . Find the current, assuming there is no initial charge on the capacitor.
4. In the RC circuit shown in Fig. 1, the sinusoidal voltage source  $v = 250 \sin(500t + \emptyset)$  is applied by closing the switch at a time when  $\emptyset = 45^\circ$ . There is an initial charge  $q_0 = 5000 \times 10^{-6}$  coulomb on the capacitor with polarity shown on the diagram. Find the complete current.



*Fig.1*




5. The series RLC circuit shown in Fig. 2 has a sinusoidal voltage source  $v = 100 \sin(1000t + \phi)$ . If the switch is closed when  $\phi = 90^\circ$ , find the current assuming zero initial charge on the capacitor.

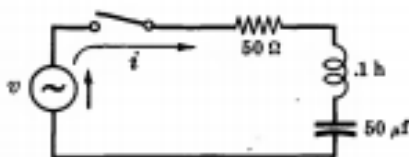

*Fig.2*

6. In the two-mesh network shown in Fig.3 the switch is closed at  $t = 0$ . Find the transient mesh currents  $i_1$  and  $i_2$  shown in the diagram, and the transient capacitor voltage  $v_c$ .

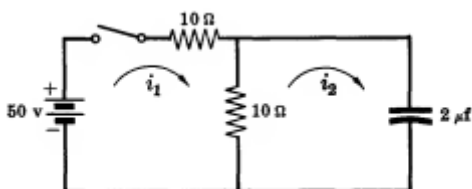

*Fig.3*

*Good Luck*