



Sheet (9)... AC and DC transient (Laplace)

1. In the series RC circuit of Fig. 1, the capacitor has an initial charge $q = 2500 \times 10^{-6}$ coulomb. At $t = 0$, the switch is closed and a constant voltage source $V = 100$ volts is applied to the circuit. Use Laplace transform method to find the current.

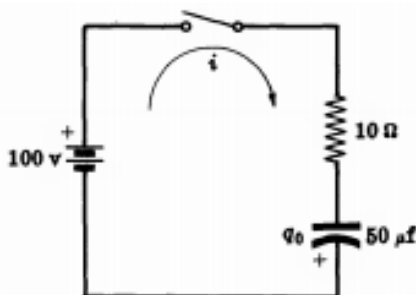


Figure 1

2. In the RL circuit shown in Fig. 2 below, the switch is in position 1 long enough to establish steady state conditions and at $t = 0$ is switched to position 2. Find the resulting current.

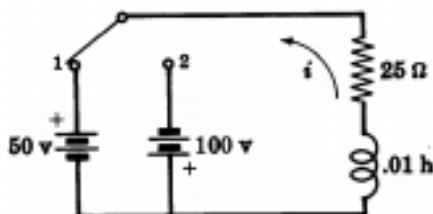


Figure 2

3. In the series RL circuit of Fig. 3 an exponential voltage $v = 50e^{-100t}$ is applied by closing the switch at $t = 0$. Find the resulting current.

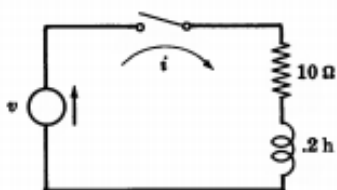


Figure 3



4. The series RC circuit of Fig. 4 has a sinusoidal voltage source $v = 180 \sin(2000t + \phi)$ and an initial charge on the capacitor $q = 1250 \times 10^{-6}$ coulomb with polarity as shown. Determine the current if the switch is closed at a time corresponding to $\phi = 90^\circ$.

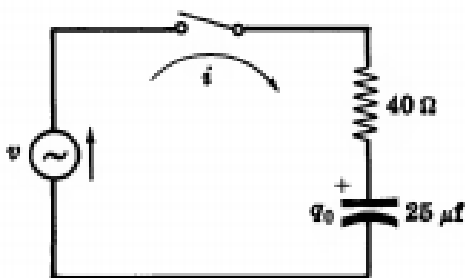


Figure 4

5. In the series RL circuit of Fig. 5 the sinusoidal source is given by $v = 100 \sin(500t + \phi)$. Determine the resulting current if the switch is closed when $\phi = 0$.

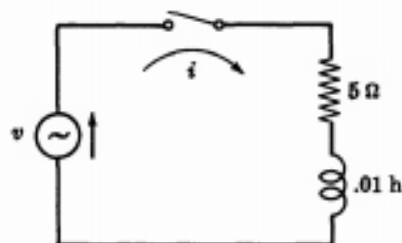


Figure 5

6. In the series RLC circuit shown in Fig. 6, there is no initial charge on the capacitor. If the switch is closed at $t = 0$, determine the resulting current.

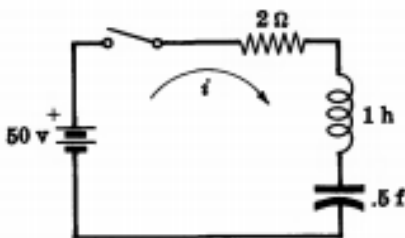


Figure 6



-
7. In the two mesh network of Fig. 7, find the currents which result when the switch is closed.

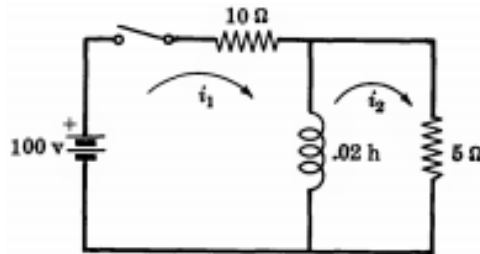


Figure 7

8. In the two-mesh network shown in Fig. 8 there is no initial charge on the capacitor. Find the mesh currents i_1 and i_2 which result when the switch is closed at $t = 0$.

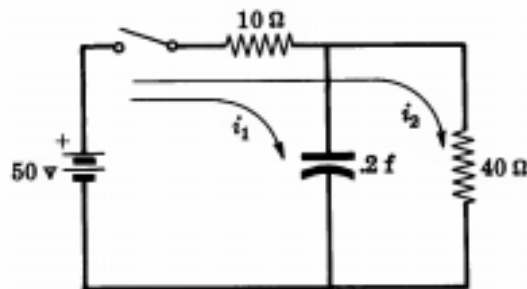


Figure 8

Good Luck



LAPLACE TRANSFORMS

	$f(t)$	$F(s)$
1.	$A \quad t \geq 0$	$\frac{A}{s}$
2.	$At \quad t \geq 0$	$\frac{A}{s^2}$
3.	e^{-at}	$\frac{1}{s + a}$
4.	te^{-at}	$\frac{1}{(s + a)^2}$
5.	$\sin \omega t$	$\frac{\omega}{s^2 + \omega^2}$
6.	$\cos \omega t$	$\frac{s}{s^2 + \omega^2}$
7.	$\sin (\omega t + \theta)$	$\frac{s \sin \theta + \omega \cos \theta}{s^2 + \omega^2}$
8.	$\cos (\omega t + \theta)$	$\frac{s \cos \theta - \omega \sin \theta}{s^2 + \omega^2}$
9.	$e^{-at} \sin \omega t$	$\frac{\omega}{(s + a)^2 + \omega^2}$
10.	$e^{-at} \cos \omega t$	$\frac{(s + a)}{(s + a)^2 + \omega^2}$
11.	$\sinh \omega t$	$\frac{\omega}{s^2 - \omega^2}$
12.	$\cosh \omega t$	$\frac{s}{s^2 - \omega^2}$
13.	df/dt	$s F(s) - f(0+)$
14.	$\int f(t) dt$	$\frac{F(s)}{s} + \frac{f^{-1}(0+)}{s}$
15.	$f(t - t_1)$	$e^{-t_1 s} F(s)$
16.	$f_1(t) + f_2(t)$	$F_1(s) + F_2(s)$