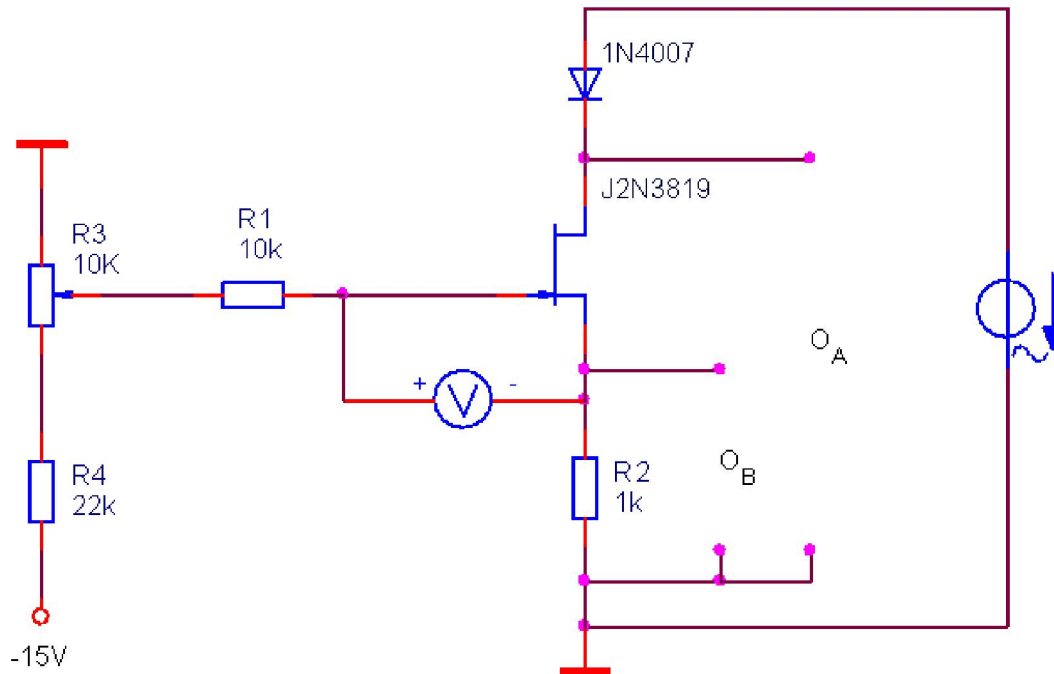


Experiment 1

Circuit diagram


The following circuit diagram is used for this experiment:



Components



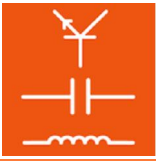

The following components are needed for this experiment:

Parts	Id no.	Designation
3	SO5126-5M	Cables
15	SO5124-6F	Bridges, small
1	PS4121-3C	R 1k
1	PS4121-3Q	R 10k
1	PS4121-3U	R 22k
1	PS4121-8G	Potentiometer 10k
1	PS4122-7C	Diode 1N4007
1	PS4123-2H	FET 2N3819



Cable connections

The following cable connections are used in this experiment:





Designation	Symbol	Equipment	Sockets
FG		FUNCTION GENERATOR	0...20V _{ss} / 0,3A 
GND		MULTI POWER SUPPLY 60VA / 500KHz	

Connect the specified sockets to the plug-in connection locations indicated on the layout diagram.



Equipment

The following equipment is needed for this experiment including the corresponding settings:

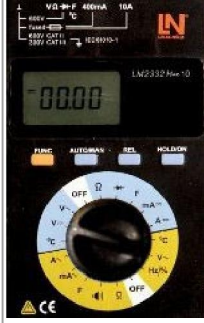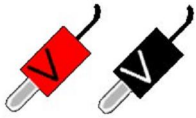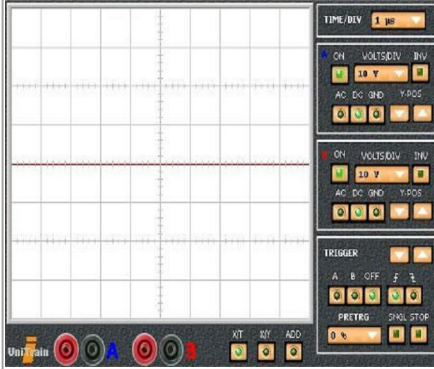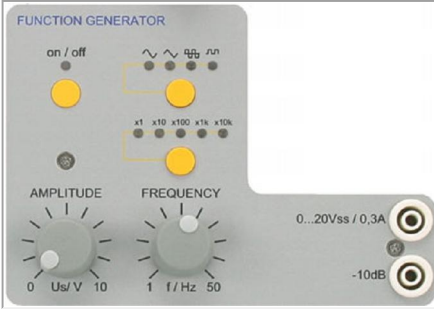
Equipment	Settings																												
	Black cable	Ground																											
	Red cable	V Ohm input																											
	Control knob	V DC																											
		Please insert the red and black probes into the connection locations indicated																											
	<table border="1"> <thead> <tr> <th></th> <th>Channel A</th> <th>Channel B</th> </tr> </thead> <tbody> <tr> <td>Sensitivity</td> <td>1 V/DIV</td> <td>2 V/DIV</td> </tr> <tr> <td>Coupling</td> <td>DC</td> <td>DC</td> </tr> <tr> <td>Polarity</td> <td>norm</td> <td>norm</td> </tr> <tr> <td>y-pos</td> <td>0</td> <td>0</td> </tr> <tr> <td>Time base</td> <td colspan="2">2 msec/DIV</td> </tr> <tr> <td>Mode</td> <td colspan="2">X/Y</td> </tr> <tr> <td>Trigger channel</td> <td colspan="2">-</td> </tr> <tr> <td>Trigger edge</td> <td colspan="2">-</td> </tr> </tbody> </table>		Channel A	Channel B	Sensitivity	1 V/DIV	2 V/DIV	Coupling	DC	DC	Polarity	norm	norm	y-pos	0	0	Time base	2 msec/DIV		Mode	X/Y		Trigger channel	-		Trigger edge	-		
	Channel A	Channel B																											
Sensitivity	1 V/DIV	2 V/DIV																											
Coupling	DC	DC																											
Polarity	norm	norm																											
y-pos	0	0																											
Time base	2 msec/DIV																												
Mode	X/Y																												
Trigger channel	-																												
Trigger edge	-																												
	<table border="1"> <tbody> <tr> <td>Curve shape</td> <td>sinusoidal</td> </tr> <tr> <td>Amplitude</td> <td>4V</td> </tr> <tr> <td>Frequency factor</td> <td>x1</td> </tr> <tr> <td>Frequency</td> <td>50Hz</td> </tr> </tbody> </table>	Curve shape	sinusoidal	Amplitude	4V	Frequency factor	x1	Frequency	50Hz																				
Curve shape	sinusoidal																												
Amplitude	4V																												
Frequency factor	x1																												
Frequency	50Hz																												



Experiment procedure and exercises

- Use the values specified above for the oscilloscope and function generator settings. Set the potentiometer so that the voltage at the gate of the FET is approximately 230 mV.

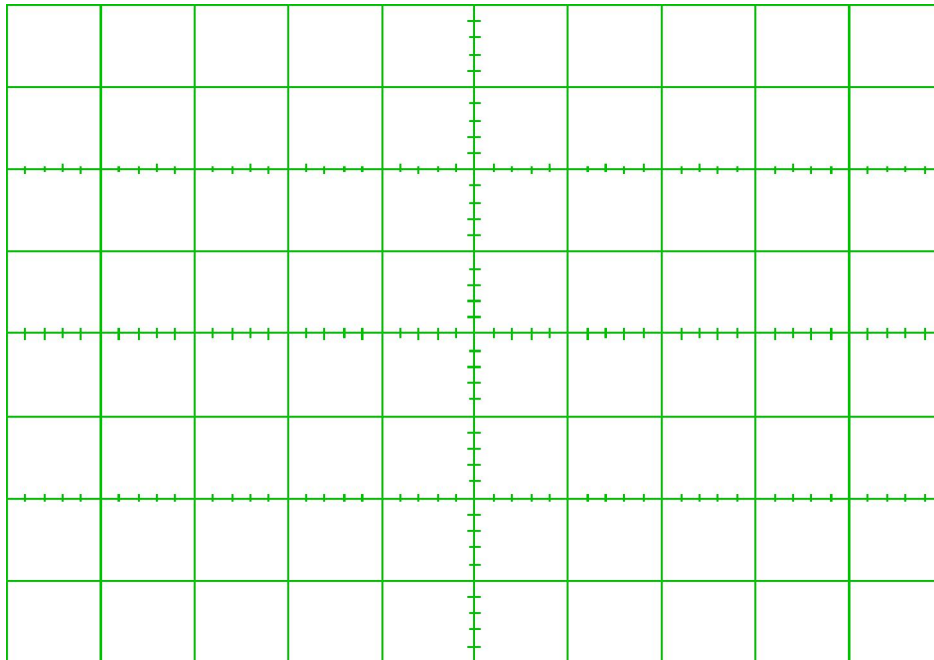Display the output characteristics on the oscilloscope and enter the oscillograph trace below:



Then repeat the procedure but for voltage levels of 0.6 V, 0.9 V and 1.3 V.

Next draw the working line for the FET in the diagram.


-
- How high is the no-load voltage?

$U_{nn} =$ _____ V

Experiment 2

Circuit diagram

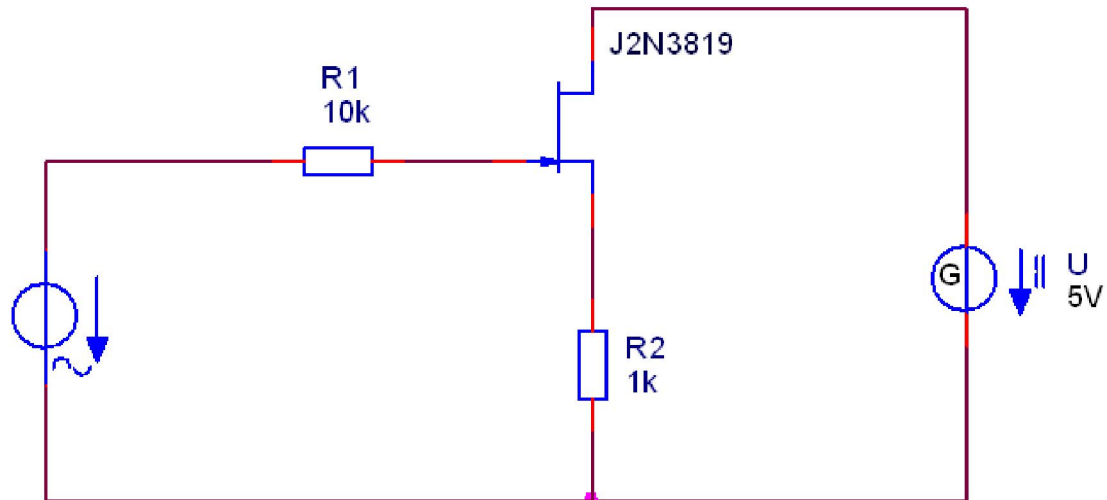The following circuit diagram is used for this experiment:



Components



The following components are needed for this experiment:

Parts	Id no.	Designation
2	SO5126-5M	Cables
1	SO5126-5E	Bridges, large
10	SO5124-6F	Bridges, small
1	PS4121-3C	R 1k
1	PS4121-3Q	R 10k
1	PS4123-2H	FET 2N3819



Equipment


The following equipment including the corresponding settings are needed for this experiment:

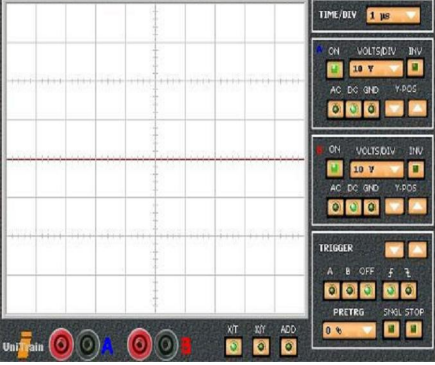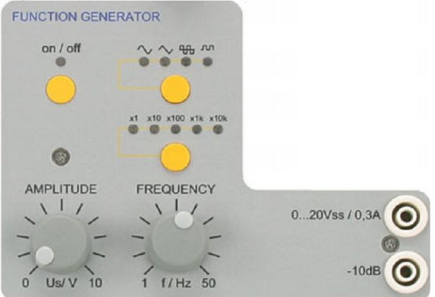Equipment	Settings																												
	<table border="1"> <thead> <tr> <th></th> <th>Channel A</th> <th>Channel B</th> </tr> </thead> <tbody> <tr> <td>Sensitivity</td> <td>1 V/DIV</td> <td>2 V/DIV</td> </tr> <tr> <td>Coupling</td> <td>DC</td> <td>DC</td> </tr> <tr> <td>Polarity</td> <td>norm</td> <td>norm</td> </tr> <tr> <td>y-pos</td> <td>0</td> <td>0</td> </tr> <tr> <td>Time base</td> <td colspan="2">2 msec/DIV</td> </tr> <tr> <td>Mode</td> <td colspan="2">X/Y</td> </tr> <tr> <td>Trigger channel</td> <td colspan="2">-</td> </tr> <tr> <td>Trigger edge</td> <td colspan="2">-</td> </tr> </tbody> </table>			Channel A	Channel B	Sensitivity	1 V/DIV	2 V/DIV	Coupling	DC	DC	Polarity	norm	norm	y-pos	0	0	Time base	2 msec/DIV		Mode	X/Y		Trigger channel	-		Trigger edge	-	
	Channel A	Channel B																											
Sensitivity	1 V/DIV	2 V/DIV																											
Coupling	DC	DC																											
Polarity	norm	norm																											
y-pos	0	0																											
Time base	2 msec/DIV																												
Mode	X/Y																												
Trigger channel	-																												
Trigger edge	-																												
	<table border="1"> <tbody> <tr> <td>Curve shape</td> <td colspan="2">sinusoidal</td> </tr> <tr> <td>Amplitude</td> <td colspan="2">5V</td> </tr> <tr> <td>Frequency Factor</td> <td colspan="2">x1</td> </tr> <tr> <td>Frequency</td> <td colspan="2">50Hz</td> </tr> </tbody> </table>		Curve shape	sinusoidal		Amplitude	5V		Frequency Factor	x1		Frequency	50Hz																
Curve shape	sinusoidal																												
Amplitude	5V																												
Frequency Factor	x1																												
Frequency	50Hz																												

Experiment set-up

Now please set up the experiment as a testing station in the upper right hand corner of the patch panel. Commence with the following:

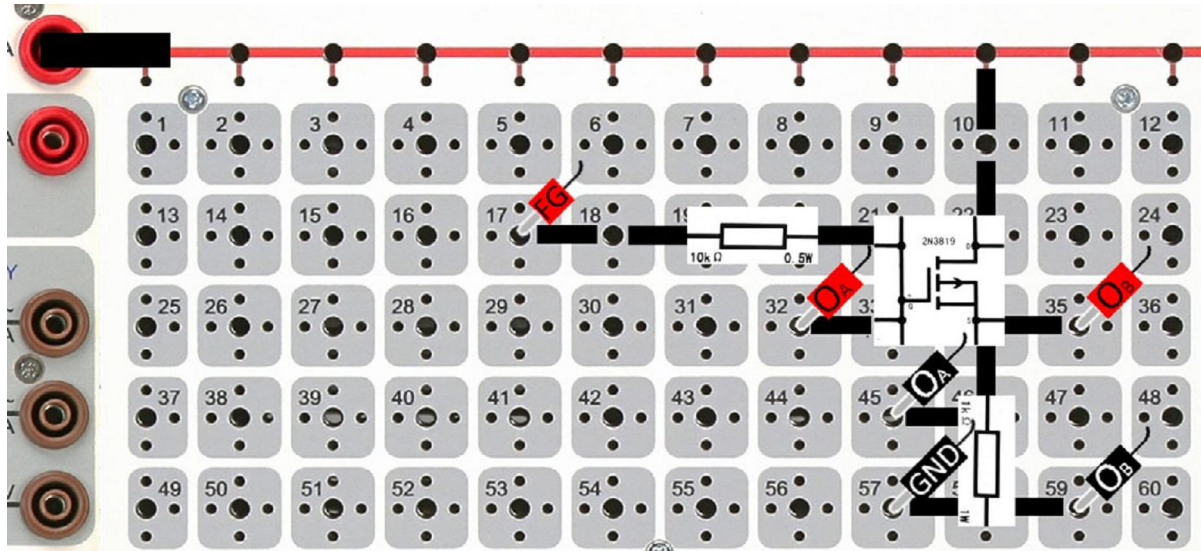- Bridging plugs
- Electronic components
- Measuring instruments and cables





Experiment procedure and exercises

- Record the characteristics of the circuit on the oscilloscope and enter the oscillograph trace below:

