

OP AMP Design Problems

1. A non-inverting amplifier has R_i of $1\text{K}\Omega$ and R_f of $100\text{K}\Omega$. Determine V_f and B if $V_{out} = 5\text{V}$.

$$B = \frac{R_i}{R_i + R_f} = \frac{1.0\text{ k}\Omega}{101\text{ k}\Omega} = 9.90 \times 10^{-3}$$

$$V_f = BV_{out} = (9.90 \times 10^{-3})5\text{ V} = 0.0495\text{ V} = 49.5\text{ mV}$$

2. For the non-inverting amplifier shown in figure (1). Determine $A_{cl(NI)}$, V_{out} , and V_f .

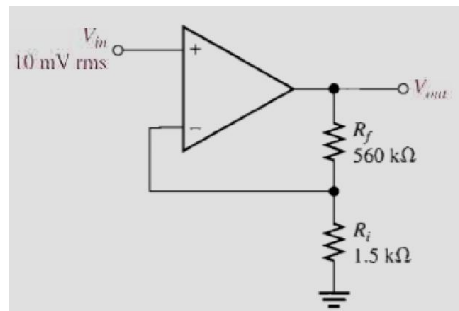


Figure (1)

$$(a) A_{cl(NI)} = \frac{1}{B} = \frac{1}{1.5\text{ k}\Omega / 561.5\text{ k}\Omega} = 374$$

$$(b) V_{out} = A_{cl(NI)}V_{in} = (374)(10\text{ mV}) = 3.74\text{ V rms}$$

$$(c) V_f = \left(\frac{1.5\text{ k}\Omega}{561.5\text{ k}\Omega} \right) 3.74\text{ V} = 9.99\text{ mV rms}$$

3. Calculate the closed loop gain for non-inverting amplifier has $R_1=4.7\text{K}\Omega$, $R_F=47\text{K}\Omega$, and $A_{OL}=150,000$.

$$ACL = 1 + R_f/R_1 = 11$$

4. For an inverting amplifier with closed loop gain of -300 , and R_1 of $10\text{K}\Omega$, calculate the value required to R_f to satisfy this gain.

$$\frac{R_f}{R_i} = A_{cl(I)}$$

$$R_f = -R_i(A_{cl(I)}) = -10\text{ k}\Omega(-300) = 3\text{ M}\Omega$$

5. Determine the approximate values for I_{in} , I_f , V_{out} , A_{cl} in figure (2).

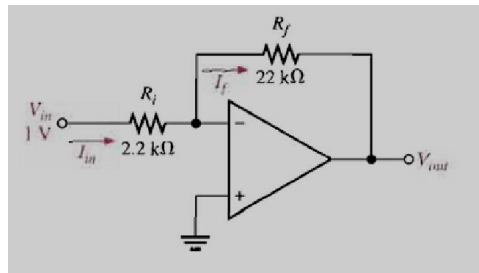


Figure (2)

$$(a) I_{in} = \frac{V_{in}}{R_{in}} = \frac{1 \text{ V}}{2.2 \text{ k}\Omega} = 455 \mu\text{A}$$

$$(b) I_f \cong I_{in} = 455 \mu\text{A}$$

$$(c) V_{out} = -I_f R_f = -(455 \mu\text{A})(22 \text{ k}\Omega) = -10 \text{ V}$$

$$(d) A_{cl(I)} = -\left(\frac{R_f}{R_i}\right) = -\left(\frac{22 \text{ k}\Omega}{2.2 \text{ k}\Omega}\right) = -10$$