

Exercise 5

Base bias:

① For the circuit shown

$R_C = 2.2\text{ k}\Omega$ $R_B = 240\text{ k}\Omega$ $\beta = 50$

and $V_{CC} = 12\text{ V}$ Find:

- a) I_{BQ} and I_{CQ} b) V_{CEQ} c) V_B and V_C
 d) V_{BC} e) $I_{E\text{sat}}$



② $R_C = 2.7\text{ k}\Omega$ $R_B = 470\text{ k}\Omega$ $\beta = 90$ and $V_{CC} = 16\text{ V}$ Find:

- a) I_{BQ} and I_{CQ} b) V_{CEQ} c) V_C , V_B and V_E

③ $I_B = 40\text{ }\mu\text{A}$ $V_C = 6\text{ V}$ $\beta = 80$ and $V_{CC} = 12\text{ V}$

Find: a) I_C b) R_C c) R_B and d) V_{CE}

④ $I_B = 20\text{ }\mu\text{A}$ $R_C = 2.2\text{ k}\Omega$ $I_E = 4\text{ mA}$ and $V_{CE} = 7.2\text{ V}$


Find: a) I_C b) V_{CC} c) β d) R_B

⑤ For the circuit shown:

$R_B = 430\text{ k}\Omega$ $R_C = 2\text{ k}\Omega$ $R_E = 1\text{ k}\Omega$

$\beta = 50$ and $V_{CC} = 20\text{ V}$ Find:

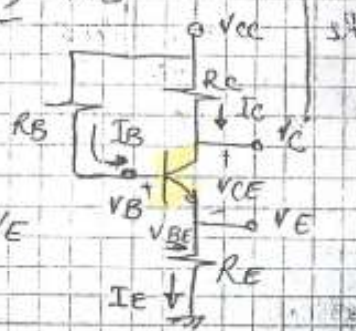- a) I_B and I_C b) V_{CE} c) V_C , V_B , V_E
 d) V_{BC} e) $I_{CE(\text{sat})}$



⑥ $R_B = 510\text{ k}\Omega$ $R_C = 2.4\text{ k}\Omega$ $R_E = 1.5\text{ k}\Omega$ $\beta = 100$

$V_{CC} = 20\text{ V}$ Find: a) I_B and I_C b) V_{CE}

c) V_C , V_B , V_E d) V_{BC} e) $I_{CE\text{sat}}$ $I_{E\text{sat}}$


⑦ $V_{CC} = 12\text{ V}$ $I_C = 2\text{ mA}$ $V_C = 7.6\text{ V}$ $V_E = 2.4\text{ V}$

$\beta = 80$ Find: a) R_C b) R_E c) R_B d) V_{CE}


Emitter Bias:

① Find V_C , V_E and V_{CE} for the circuit shown, for $\beta = 100$ and $V_{BE} = 0.7V$

Pnp

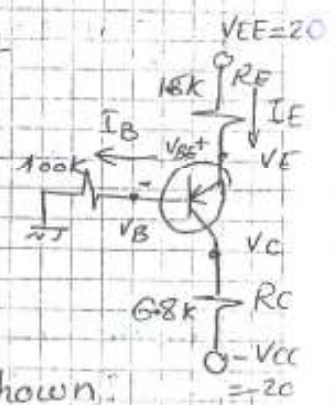


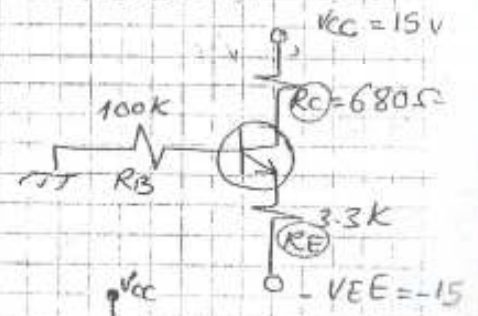② Find I_B , I_C and V_{CE} for the circuit shown. $\beta = 150$



Voltage Divider bias:

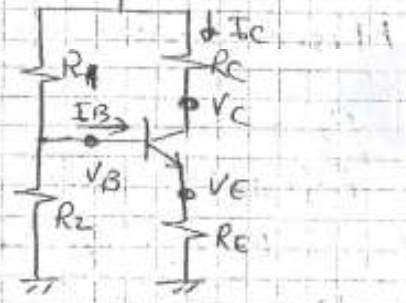① $V_{CC} = 16V$, $R_C = 5.9K$, $R_E = 0.68K$
 $R_1 = 6.2K$ & $R_2 = 9.1K$ and $\beta = 80$
 Find a) I_{BQ} , I_{CQ} and V_{CEQ}
 b) V_C , V_E and V_B
 c) $I_{C(sat)}$




② $V_{CC} = 18V$, $V_C = 12V$, $R_C = 4.7K$ and $R_E = 1.2K$ & $R_2 = 5.6K$
 Find a) I_C b) V_E and V_B c) R_1

③ Given $R_C = 2.7K$ and $R_E = 1.2K$ & $\beta = 100$ & $I_B = 20\mu A$
 and $R_2 = 8.2K\Omega$ (and $V_C = 10.6V$) Find a) I_C b) V_{CC} and V_{CE} and V_B
 c) R_1

Collector feed back bias


(80)

Find a) I_B b) I_C d) V_C

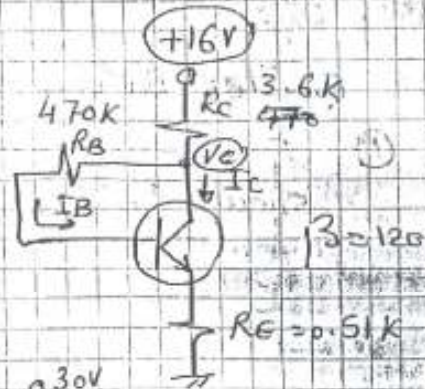

(2) For the circuit shown:

Find a) I_C b) V_C c) V_E
d) V_{CE}

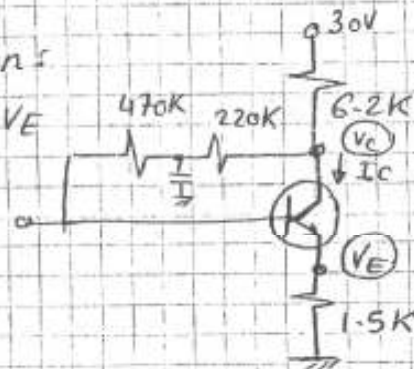


Miscellaneous Bias

(1) $\beta = 120$

Find a) I_{CQ} and V_{CEQ}

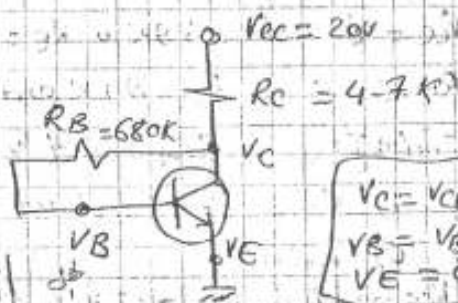b) V_B , V_C , V_E and V_{BC}

$$I_{CQ} = 1.86 \text{ mA} \quad V_{CEQ} = 11.26 \text{ V}$$



$$\begin{aligned} V_C &= V_{CE} = 11.26 \text{ V} \\ V_B &= V_{BE} = 0.7 \text{ V} \\ V_E &= 0 \end{aligned}$$

(2) Find V_C and V_B

Solution:

$$I_B R_B + V_{BE} - V_{EE} = 0$$


$$I_B = \frac{V_{EE} - V_{BE}}{R_B} = \frac{8.3}{100 \text{ K}\Omega}$$

$$= 83 \text{ }\mu\text{A}$$

$$I_C = \beta I_B = 3.735 \text{ mA}$$

$$V_C = -I_C R_C = -4.25 \text{ V}$$

$$V_B = -I_B R_B = -8.3 \text{ V}$$

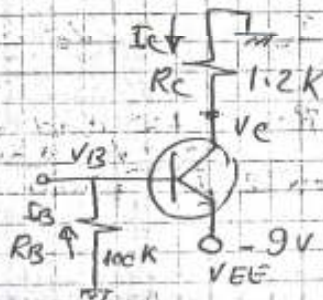

③ Find V_{CEQ} and I_E

solution

$$I_B R_B + V_{BE} + I_E R_E - V_{EE} = 0$$


but $I_E \approx (\beta + 1) I_B = 4.16 \text{ mA}$

$$I_B = \frac{V_{EE} - V_{BE}}{R_B + (\beta + 1) R_E} = 45.73 \mu\text{A}$$

$$I_C = \beta I_B = 4.12 \text{ mA}$$

$$V_{CE} + I_E R_E - V_{EE} = 0 \Rightarrow V_{CE} = V_{EE} - I_E R_E$$
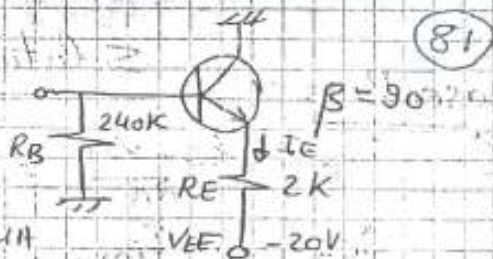
$$V_{CE} = V_{EE} - (\beta + 1) I_B R_E = 11.68 \text{ V}$$



④ For the circuit shown:

$$I_{CQ} = 2 \text{ mA} \quad V_{CEQ} = 10 \text{ V}$$

Find R_1 and R_C

solution

$$V_E = I_E R_E \approx I_C R_E = 2 \times 10^{-3} \times 1.2 \text{ k} = 2.4 \text{ V}$$


$$V_B = V_{BE} + V_E = 3.1 \text{ V}$$

$$V_B = V_{CC} \frac{R_2}{R_1 + R_2} = 3.1 \Rightarrow R_1 = 86.52 \text{ k}\Omega$$

$$R_C = \frac{V_{CC} - V_C}{I_C}$$

$$V_C = V_{CE} + V_E = 10 + 2.4 = 12.4 \text{ V}$$
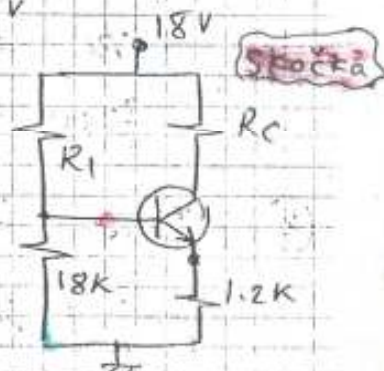
$$R_C = \frac{18 - 12.4}{2 \times 10^{-3}} = \frac{5.6}{2 \times 10^{-3}} = 2.8 \text{ k}\Omega$$



⑤ For the circuit shown $\beta = 110$

$$I_{CQ} = \frac{1}{2} I_{C \text{ sat}} \quad I_{C \text{ sat}} = 8 \text{ mA}$$

solution


$$I_{CQ} = \frac{1}{2} I_{C \text{ sat}} = 4 \text{ mA}$$

$$R_C = \frac{V_{CC} - V_C}{I_{CQ}} = \frac{28 - 18}{4} = 2.5 \text{ k}\Omega$$

$$I_{C \text{ sat}} = \frac{V_{CC}}{R_C + R_E} \Rightarrow R_E = 1 \text{ k}\Omega$$

$$I_{BQ} = \frac{I_{CQ}}{\beta} = \frac{4 \text{ mA}}{110} = 36.36 \mu\text{A} = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1) R_E}$$

$$R_B = 639.8 \text{ k}\Omega$$

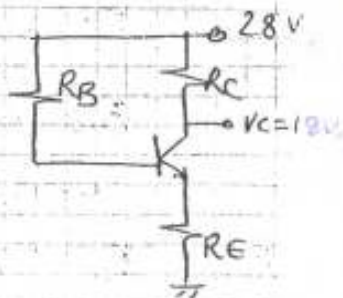

U Kork

⑤

M

Base Bias

Solution for the Exercise

SKÖEKA

I_{BQ} = (V_{CC} - V_{BE}) / R_B = (12 - 0.7) / (220 × 10³) = 47 μA

I_{CQ} = β I_{BQ} = 50 × 47 = 2350 μA = 2.35 mA


V_{CEQ} = V_{CC} - I_{CQ} R_C = 12 - 2.35 × 2.2 = 6.83 V

V_B = V_{BE} = 0.7 V

V_C = V_{CE} = 6.83 V

V_{BC} = V_B - V_C = -6.13 V

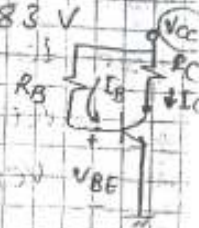I_{Csat} = V_{CC} / R_C = 12 / (2.2 × 10³) = 5.455 mA



I_{BQ} = (V_{CC} - V_{BE}) / R_B = (16 - 0.7) / (470 × 10³) = 32.55 μA

I_{CQ} = β I_{BQ} = 90 × 32.55 = 2.93 mA

V_{CEQ} = V_{CC} - I_{CQ} R_C = 16 - 2.93 × 2.7 = 8.1 V

V_C = V_{CEQ} = 8.1 V

V_B = V_{BE} = 0.7 V, V_E = 0

I_C = β I_B = 80 × 40 = 3200 μA = 3.2 mA

R_C = (V_{CC} - V_C) / I_C = (12 - 6) / (3.2 × 10⁻³) = 1.875 kΩ

R_B = (V_{CC} - V_{BE}) / I_B = (12 - 0.7) / (40 × 10⁻⁶) = 282.5 kΩ

V_{CE} = V_C = 6 V

I_C ≈ I_E = 4 mA

β = I_C / I_B = (4 × 10⁻³) / (20 × 10⁻⁶) = 200

V_{CE} = V_{CC} - I_C R_C ∴ V_{CC} = V_{CE} + I_C R_C =

V_{CC} = 7.2 + 4 × 2.2 = 7.2 + 8.8 = 16 V

R_B = (V_{CC} - V_{BE}) / I_B = (16 - 0.7) / (20 × 10⁻⁶) = 765 kΩ

(5)

$$I_B = \frac{V_{CC} - V_B}{R_B}$$

$$V_B = V_{BE} + I_C R_E$$

$$R_B I_B = V_{CC} - V_{BE} + \beta I_B R_E$$

$$I_B (R_B + \beta R_E) = V_{CC} - V_{BE}$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = \frac{20 - 0.7}{(430 + 50) \times 10^3} = 40.2 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 80 \times 40.2 = 2010.0 \mu A = 2.01 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_C (R_C + R_E) = 20 - 2.01(2+1) = 13.97$$

$$V_C = I_C R_E + V_{CEQ} = V_{CC} - I_C R_C = 20 - 2.01 \times 2 = 15$$

$$V_E = I_C R_E = 2.01 \times 1 = 2.01 \text{ V}$$

$$V_B = V_{BE} + V_E = 0.7 + 2.01 = 2.71 \text{ V}$$

$$I_{CE \text{ sat}} = \frac{V_{CC}}{R_C + R_E} = \frac{20}{3 \times 10^3} = 6.667 \text{ mA}$$



(6)

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B + \beta R_E} = \frac{20 - 0.7}{(510 + 150) \times 10^3} = 29.2 \mu A$$

$$I_{CQ} = \beta I_{BQ} = 2.92 \text{ mA}$$

$$V_{CEQ} = V_{CC} - I_C (R_C + R_E) = 20 - 2.92 \times 3.9 = 8.61$$

$$V_E = I_C R_E = 2.92 \times 10^{-3} \times 1.5 \times 10^3 = 4.38 \text{ V}$$

$$V_C = V_{CE} + V_E = 12.992 \text{ V}$$

$$V_B = V_{BE} + V_E = 0.7 + 4.38 = 5.08 \text{ V}$$

$$V_{BC} = V_B - V_C = -7.912 \text{ V}$$

$$I_{CE \text{ sat}} = \frac{V_{CC}}{R_C + R_E} = \frac{20}{3.9 \text{ k}} = 5.13 \text{ mA}$$

(7)

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{12 - 7.6}{2 \times 10^{-3}} = 2.2 \text{ k}\Omega$$

$$R_E = \frac{V_E}{I_C} = \frac{2.4}{2 \times 10^{-3}} = 1.2 \text{ k}\Omega$$

$$R_B = \frac{V_{CC} - V_B}{I_B} \quad V_B = V_{BE} + V_E = 0.7 + 2.4 = 3$$

$$I_B = \frac{I_C}{\beta} = \frac{2 \times 10^{-3}}{80} = 25 \mu A$$

Sol.
Ex 7
P. 78

$$R_B = \frac{12 - 3 - 1}{2.5 \times 10^{-6}} = 356 \text{ k}\Omega$$

$$V_{CE} = V_C - V_E = 7.6 - 2.4 = 5.2 \text{ V}$$

Her Bias

$$V_B = +V_{BE} - I_E R_E + V_{EE}$$

$$\beta I_B + \beta I_B R_E = V_{EE} + V_{BE}$$


$$I_{BQ} = \frac{V_{EE} + V_{BE}}{R_B + \beta R_E} = \frac{20 - 0.7}{(100 + 180) \times 10^3} = 68.9 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 6.89 \text{ mA}$$

$$V_E = V_{EE} - I_E R_E = 20 - 6.89 \times 1.8 = 7.6 \text{ V}$$

$$V_C = I_C R_C - V_{CC} = 6.89 \times 6.8 - 20 = 26.85 \text{ V}$$
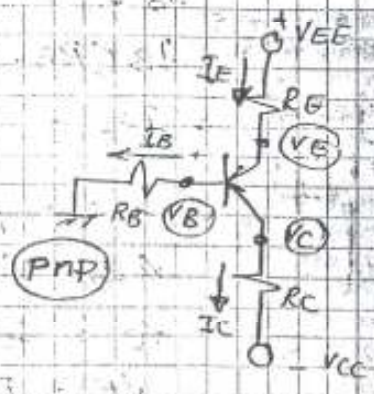
$$V_{CE} = V_C - V_E = 26.85 - 7.6 = 19.25 \text{ V}$$



$$I_B R_B + V_{BE} + I_E R_E - V_{EE} = 0$$

$$I_B (R_B + \beta R_E) = V_{EE} - V_{BE}$$

$$I_{BQ} = \frac{V_{EE} - V_{BE}}{R_B + \beta R_E} = \frac{15 - 0.7}{(100 + 180 \times 3.3) \times 10^3} = 24 \mu\text{A}$$

$$I_{CQ} = \beta I_{BQ} = 3.6 \text{ mA}$$

$$V_{CC} = I_C R_C + V_{CE} + I_E R_E - V_{EE}$$

$$V_{CE} = (V_{CC} + V_{EE}) - I_C (R_C + R_E) = 30 - 3.6 \times 10^{-3} \times (3.3 + 0.68) \times 10^3 = 15.672 \text{ V}$$

