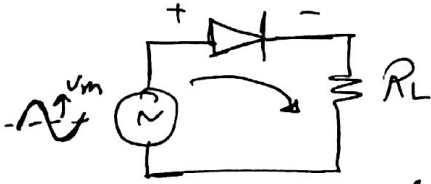



diode applications
Half and Full wave Rectifier

1 (a) half-wave Rectifier



① assume ideal diode

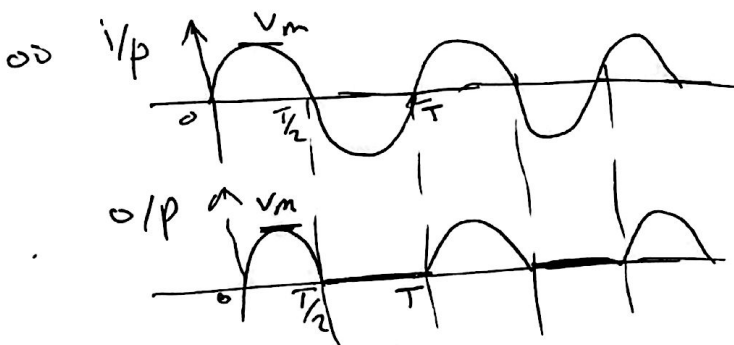- The input signal is sinusoidal wave
- for +ve half cycle of signal, the diode becomes forward Bias ∴ act as short circuit (SC), and current pass through the load resistor and produce an output voltage across the load (RL) with the same shape of input signal (+ve half cycle)
- for -ve half cycle the diode is Reverse Bias connection, so no current pass, the output at load resistor is zero.



← ideal diode

المتوسط (average) = $\frac{2V_m}{2\pi}$

$$V_{out \text{ average}} = \frac{1}{T} \int_0^T V_m \sin \omega t dt = \frac{1}{T} \left[\int_0^{T/2} V_m \sin \omega t dt + 0 \right]$$

$$= \frac{V_m}{2\pi} \int_0^{\pi} \sin \omega t d\omega t = \frac{V_m}{2\pi} [-\cos \omega t]_0^{\pi} = \frac{V_m}{2\pi} [+1 + 1] = \frac{2V_m}{2\pi}$$

$$V_{out} = \frac{V_m}{\pi}$$

∴ the average value of the output (measured by DC voltmeter) is $\frac{V_m}{\pi}$ → maximum value of input signal


→ (b) For practical diode (diode act as battery in forward)

So $V_{out \text{ average}} = \frac{V_m - 0.7}{\pi}$ → of diode (silicon)


$= \frac{V_m - 0.3}{\pi}$ → of diode (Germanium)

* PIV (Peak inverse Voltage) : It is the maximum value of Reverse voltage = peak value of input (ideal, Practical)
 $\therefore V_{PIV} = V_{in}$

حلقة (HWR) : في نصف الموجة الموجب يكون الديود كأنه سلك يمرر التيار ويكسر الخرج على المقاومة (جهد) هو نفس الجهد الداخل مباشرة .. أو يكون هو نفس الجهد الداخل مطروح منه جهد الديود $\frac{0.7}{0.3}$ لم اعتبرنا الديود Practical بينما في نصف الموجة السبي يكون الديود (ideal أو Practical) عبارة عن سلك مقطوع (open) لا يمرر تيار وبالتالي لا يوجد خرج على المقاومة = ملاحظة لو قلبت الديود ~~في الدارة~~ سينعكس اداء الديود اذ انه سيرر تيار في حالة ~~التيار~~ نصف سبب من الموجب وله يمرر تيار في حالة نصف موجب

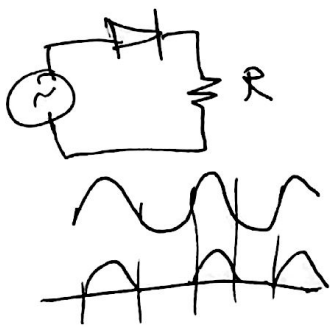

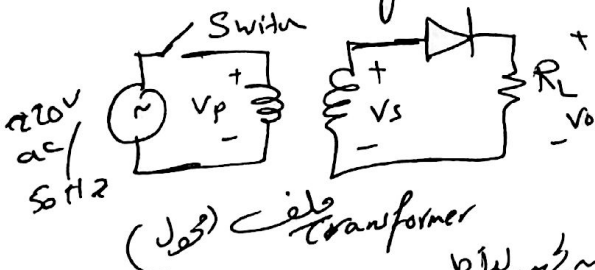Half wave Rectifier with transformer coupled input voltage



$$V_{sec} = \left(\frac{N_{sec}}{N_{pri}} \right) V_{pri}$$

$$V_o = \frac{N_{sec}}{N_{sec} - 0.7} V_{pri}$$
 (ideal) or (Practical)

transformer ملف (محول)

لوعند ملفات الملف الثانوي (sec) < عدد ملفات (pri) ...
 و وقتها لو $N_{pri} > N_{sec}$: الجهد ينزل

- ① - Transformer Step down For i/p
- ② - عزل ا ل i/p (او 220V) عن دائرة ال rectifier لتقليل shock hazard

Full wave Rectifier is better for Power supply circuit than Half wave Rectifier

2 Full wave Rectifier : The output is twice half wave rectifier


(a)

for ideal diode $N_{out} = \frac{2V_m}{\pi}$
 Practical - $N_{out} = \frac{2V_{out}}{\pi}$

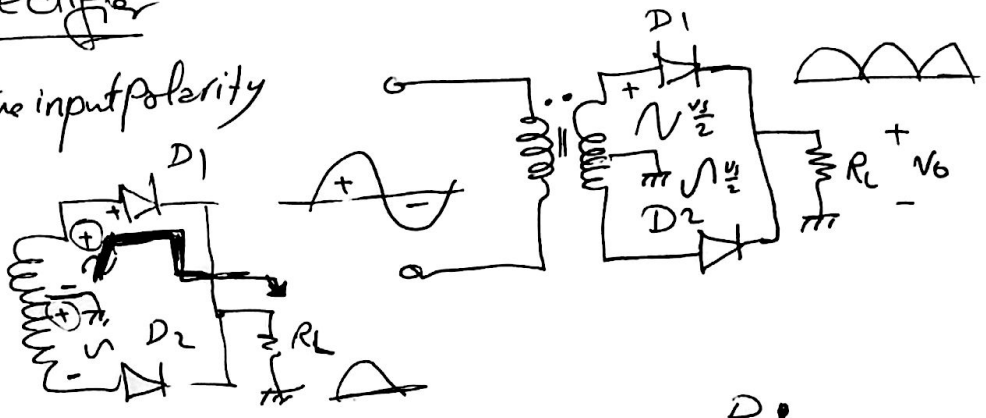(a) FWR Center tapped rectifier


For Positive half cycle the input polarity be as shown

- $\Rightarrow D_1$ (Forward)
- D_2 (Reverse)



\Rightarrow Current pass through $D_1 \rightarrow R_L$

for -ve half cycle D_1 off, D_2 on

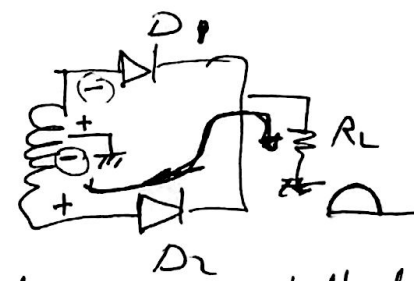


Current pass through $D_2 \rightarrow R_L$, The o/p also in phase with +ve half cycle

$N \ll N$ (i) 180° phase, $N \leftarrow 2$ center tap
 (ii) 2 diodes (D1, D2) N_1 & N_2

Effect of turns Ratio on o/p Voltage

* If turns Ratio of transformer 1:1 $\therefore N_{sec} = N_{prim}$
 $\therefore N_{out}(R_L)$ in ideal diodes = $\frac{N_{sec}}{2} = \frac{V_{prim}}{2}$
 \rightarrow " " " Practical = $\frac{N_{sec}}{2} - 0.7 = \frac{V_{prim}}{2} - 0.7$

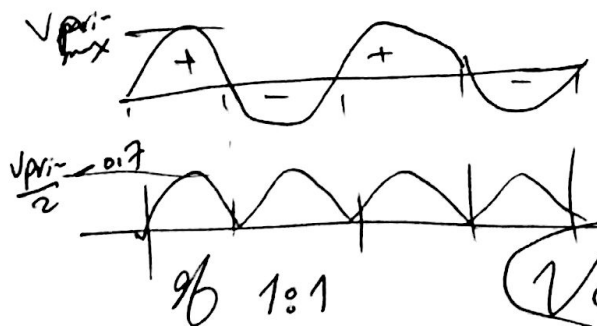
* If turns Ratio is 1:2 $\therefore N_{sec} = 2N_{prim}$
 $\therefore \rightarrow V_{out}(ideal) = \frac{N_{sec}}{2} = \frac{2V_{prim}}{2} = V_{prim}$
 $\rightarrow V_{out}(practical) = \frac{N_{sec}}{2} - 0.7 = V_{prim} - 0.7$



2 diodes, center tap, half wave rectifier

$V_{avg} = \frac{2V_{out}}{\pi}$

How to Calc PIV in Center tap FWR

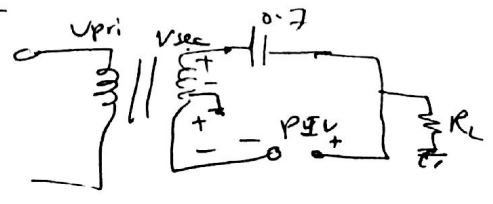

$$V_{sec} = 0.7 + PIV$$

$$PIV = V_{sec} - 0.7$$

∴ $V_{out} = \frac{V_{sec}}{2} - 0.7$ (Practical)


∴ $2V_{out} + 1.4 = V_{sec}$

$V_{sec} = 2V_{out}$
 $V_{out} = 24.3$

$$PIV = (2V_{out} + 1.4) - 0.7 = 2V_{out} + 0.7$$




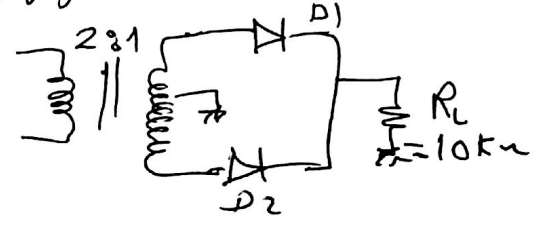draw the waveform across R_L and across half of the secondary winding of 100 v peak sine wave is applied & find PIV




sol $V_{sec} = (\frac{1}{2})V_p = 50v$

$\frac{V_{sec}}{2} = 25V$

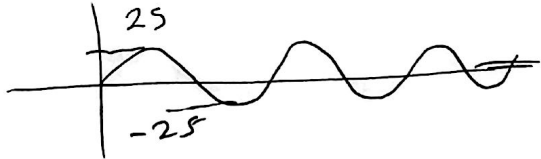

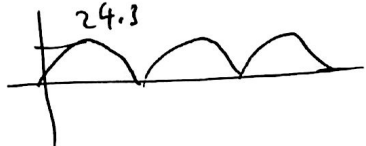→ $V_{out} (practical) = \frac{V_{sec}}{2} - 0.7$




→ PIV

$= V_{sec} - 0.7$


$= 50 - 0.7 = 49.3V$

$\delta V = 2V_{out} + 0.7$

$= 2 \times 24.3 + 0.7 = 49.3V$

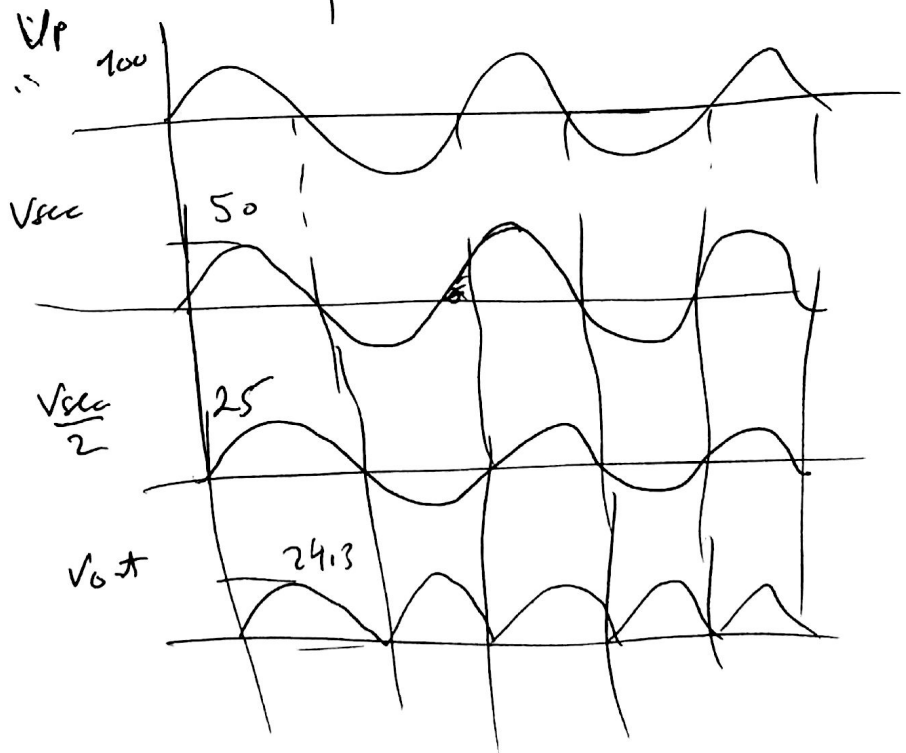

2- b Full wave Rectifier using bridge

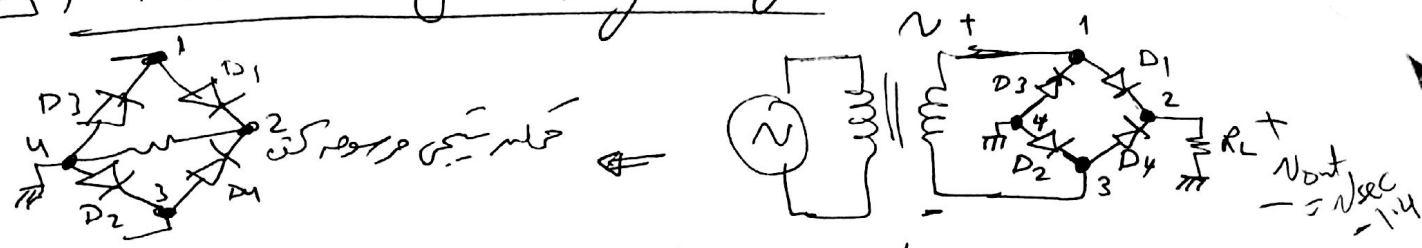

① during +ve half cycle بافتراض الایدال

تدخل نصف الموجة الموجبة إلى ارتفاع node 1 قطبها أمامها

في الارتفاع D_1 (Open) D_3 قطبها أمامها

في الارتفاع D_4 Reverse R_L في الارتفاع D_1 كأنه short

المقاومة R_L R_L في الارتفاع D_4 كأنه short

تكون قيمة $V_{sec} = V_{out}$ المقاومة R_L صغرى

ثم يدخل نصف الموجة D_3 في الارتفاع D_3 كأنه short

في الارتفاع D_2 في الارتفاع D_2 كأنه short

المقاومة R_L R_L في الارتفاع D_2 كأنه short

تكون قيمة $V_{sec} = V_{out}$ في الارتفاع D_2 كأنه short

ثم يدخل نصف الموجة D_4 في الارتفاع D_4 كأنه short

في الارتفاع D_1 في الارتفاع D_1 كأنه short

المقاومة R_L R_L في الارتفاع D_1 كأنه short





تكون قيمة $V_{sec} = V_{out}$ في الارتفاع D_1 كأنه short

ثم يدخل نصف الموجة D_3 في الارتفاع D_3 كأنه short

في الارتفاع D_2 في الارتفاع D_2 كأنه short

المقاومة R_L R_L في الارتفاع D_2 كأنه short

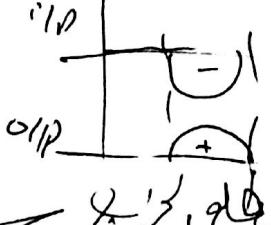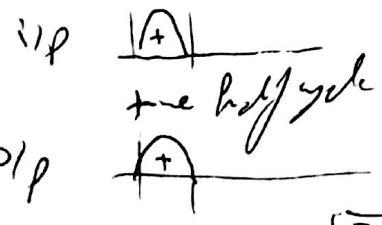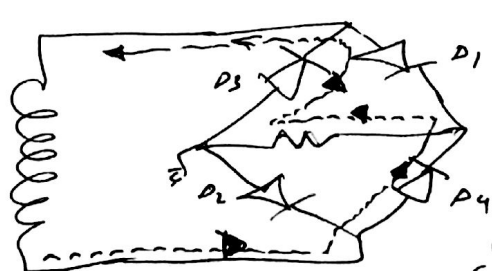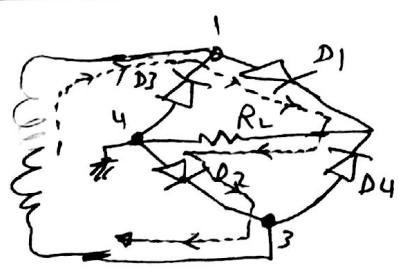تكون قيمة $V_{sec} = V_{out}$ في الارتفاع D_2 كأنه short



لا تظهر في صورة الجهد
من الجهد في الجهد
صورتها في الجهد
وهي في الجهد
التي هي في الجهد

$V_{out} = V_{sec} - 1.4$

How to calc PIV in FWR bridge

$$V_{psec} = 0.7 + V_{PIV}$$

$$\Sigma V = 0 \therefore V_{PIV} = V_{out} + 0.7$$

$$V_{out} = V_{sec} - 1.4$$

$$\therefore V_{PIV} = V_{sec} - 1.4 + 0.7 = V_{sec} - 0.7$$


$$\text{or } V_{sec} = V_{PIV} + 0.7$$



2pi/3


HWR

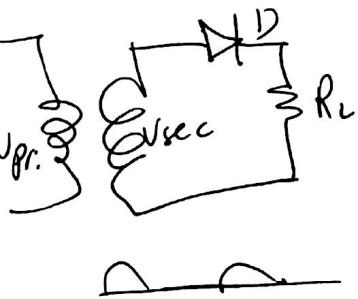- $V_{out} = V_{sec} - 0.7$
- $V_{out\ avg} = \frac{V_{out}}{\pi}$
- $V_{PIV} = V_{sec} = N_p (1:1)$



FWR (center tap)

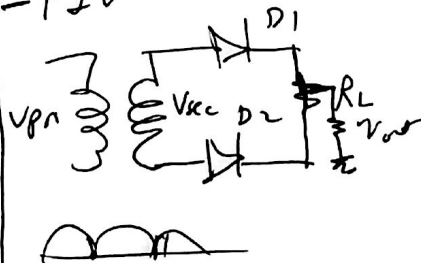
- $V_{out} = \frac{V_{sec}}{2} - 0.7$
- $V_{out\ avg} = \frac{2V_{out}}{\pi}$
- $PIV = 2V_{out} + 0.7$



$$V_{PIV} = V_{sec} - 0.7$$

FWR (bridge)

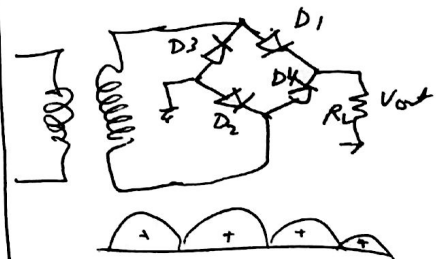- $V_{out} = V_{sec} - 0.7$
- $V_{out\ avg} = \frac{2V_{out}}{\pi}$
- $V_{oid} = V_{out} + 0.7$




$$V_{PIV} = V_{sec} - 0.7$$

7

Example (1)

find V_o , I_D (current of each diode)

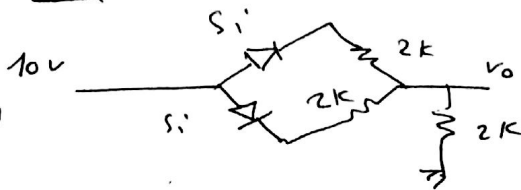


Sol assume total current is $2I_D$

loop (1)

$$-0.7 + 0.7 = 4(2k + 2k) - 2k I_2$$
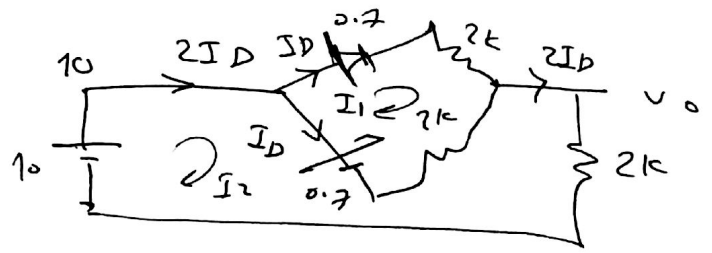
$$0 = 4I_1 - 2I_2 \quad \text{or} \quad \underline{I_2 = 2I_1}$$



loop (2)

$$10 - 0.7 = I_2 (2 + 2)k - 2k I_2$$

$$9.3 = 4k I_2 - 2k I_2 = 2k I_2$$

$$= (4k - 2k) I_2$$

$$9.3 = 4000 I_2 - 2000 \left(\frac{I_2}{2}\right) = 3000 I_2$$

$$\therefore I_2 = \frac{9.3}{3000} = 3.1 \text{ mA}$$

$$I_1 = \frac{I_2}{2} = \frac{3.1}{2} \text{ mA} = 1.55 \text{ mA}$$

But $I_1 = I_2$ $\therefore I_D = 1.55 \text{ mA}$


$$V_o = [I_2 \times 2k] = (3.1 \text{ mA}) \times 2k = 6.2 \text{ V}$$

4.4/2008



8

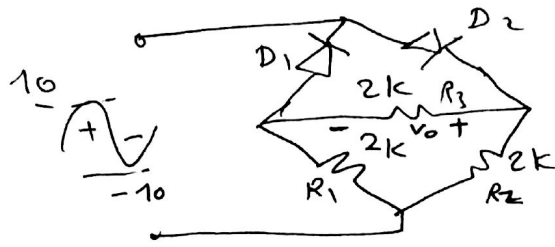(222)

EX(2) assume ideal diodes
Find op (v_o) & calc. The
dc level & PIV



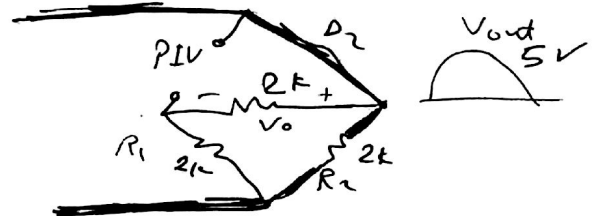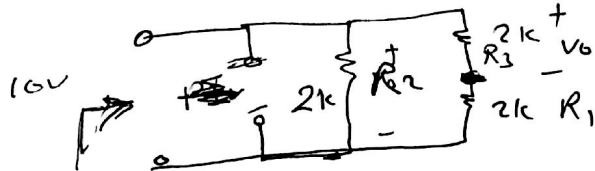Sol
at +ve half cycle \uparrow D_2 on D_1 off



$$V_o = \frac{10 \times 2k}{2k + 2k} = 5V$$





PIV = $V_{in} - V_{R1} = 10 - 5 = 5V$
or PIV = v_o (Corrected)



$$V_{DC} = V_{avg} = \frac{2V_{outmax}}{\pi} = \frac{2(5)}{\pi} = \frac{10}{\pi} = 3.18V$$

* at -ve half cycle

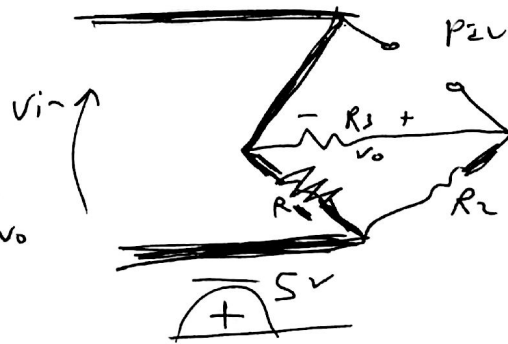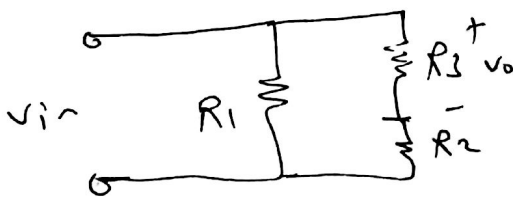

$$v_o = \frac{v_{in} \times R_2}{R_1 + R_2} = 5V$$

$$V_{DC} = \frac{2(5)}{\pi} = 3.18V$$

$$PIV = v_{out} = 5V$$

