



BJT Transistor

\* Bjt  $\rightarrow$  Bipolar junction transistor [2 PN junction connected Back to Back]  $\rightarrow$  It has 3 terminal device & has 3 set of Voltage-current characteristics.


\* Bjt used to perform amplifications for  $\begin{matrix} \rightarrow V \\ \rightarrow I \\ \rightarrow P \end{matrix}$   
 (holes  $\rightarrow$  2 carriers,  $\rightarrow$  electrons  $\rightarrow$  Bi)

Operation

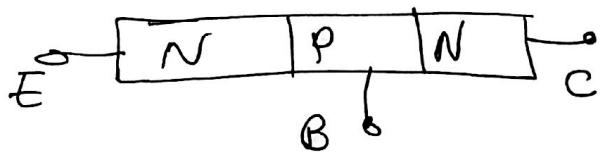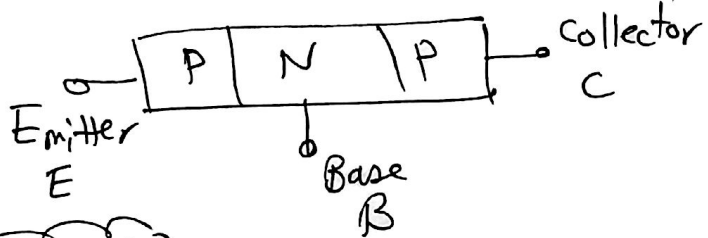
$\rightarrow$  a semiconductor layer (N, or P) between two other type layers (N between 2P or P between 2N)



Symbol


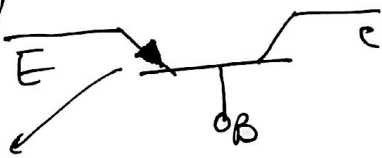


Conventional current

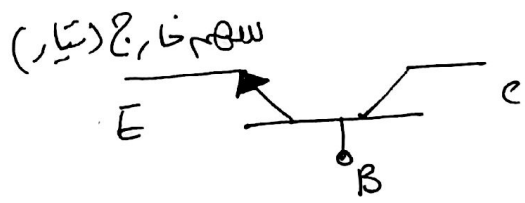


Barrier Potential

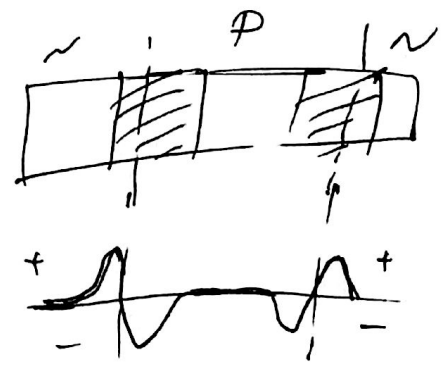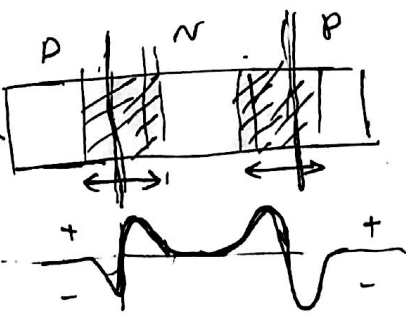$\rightarrow$  Barrier potential is +ve on N side & -ve on P side



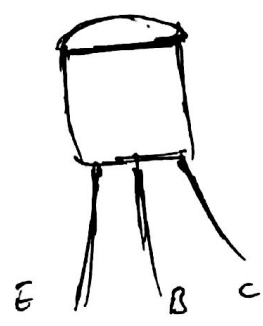Switch  $\rightarrow$  Tr.  $\rightarrow$  لا يوصل على نفسه  
 amplifier  $\rightarrow$  Basic  $\rightarrow$  operation



# operation (cont.)

→ There are 2 PN junction in BJT  
 (Collector-Base junction, Emitter Base junction (EB))  
 CB


→ to operate as amplifier, (EB must be forward & CB Reverse)

→ The middle layer (Base) → very thin (narrow) than the  
 Two layers (more lightly doped)

• Because of lightly doped layer ∴ Conductivity of Base (decreased)  
 and so, the resistance (increased), the distance bet<sup>n</sup> CB & EB  
 is minimized & free electrons

• The Barrier Potential are +ve in n-type & -ve in p-type

EX) NPN WITH EB forward & CB reverse

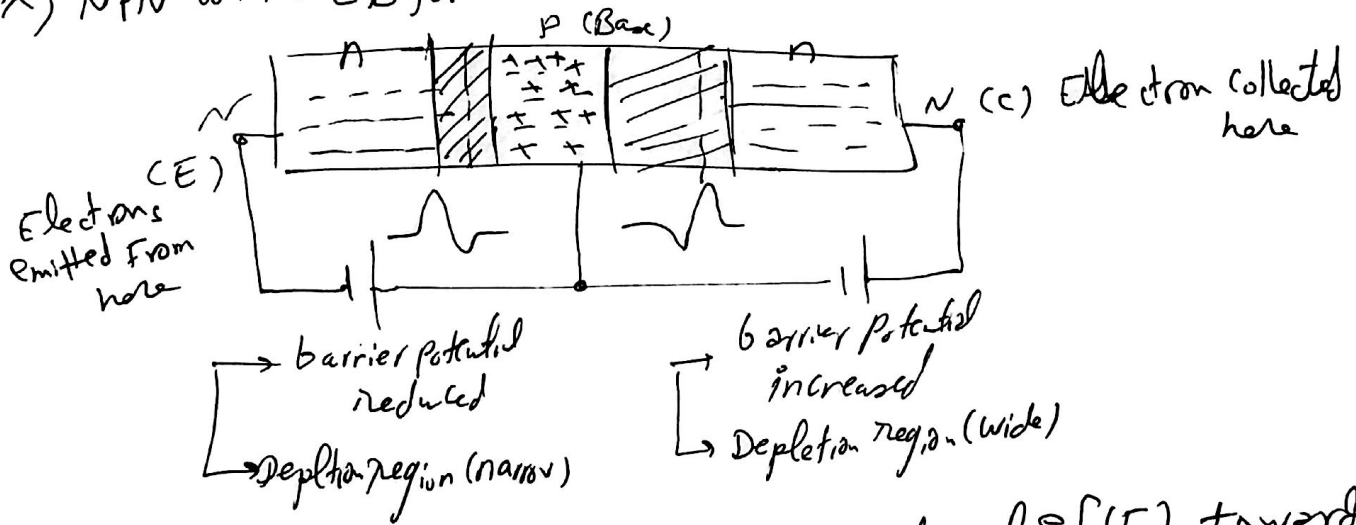

→ electrons emitted from (E) and leave n-material = f(E) towards  
 p material (Base) & move easily because depletion region is narrow  
 between EB & potential barrier is reduced.

→ when arrive pN junction (CB), the electrons move forward rapidly  
 towards collector (because of positive supply voltage =  $V_{CC}$ )  
 collector  $\rightarrow$   $V_{CC}$

# Transistor current

3


- ∴ BE junction is Forward Bias → depletion region is reduced due to reduction of Potential Barrier, BC is Reverse  
⇒ large no. of majority carriers (Electrons) diffuse across BE junction (Forward) → These electrons enter the (Base region) and will have 2 choices.

↳ Exit to the Voltage source through Base terminal (X)  
↳ Continue flowing to the Collector across (wide depletion region (Because the positive voltage across collector layer > voltage of Base])

- Since the Base region is lightly doped (high resistance) & " " " " is Thin, the electrons need to travel less distance to be attracted to the high positive potential of collector potential terminal,

- But (small amount of electrons leave Base through the source connection, while the Big (major) amount of current flow into Collector.

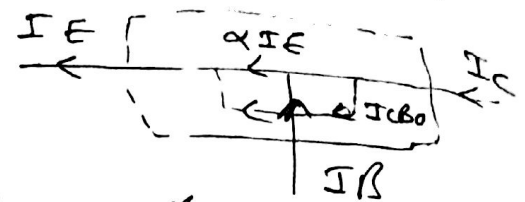- The current is result from (minority carrier in P (E)  
+ Electrons emitted from emitter & reaches P (Base)



1.  $I_C = \alpha I_E + I_{CBO}$

Reverse current  $\rightarrow$   $I_{CBO}$

Portion of emitter current  $\rightarrow$   $\alpha I_E$

$\alpha \rightarrow$  Common Base Current gain =  $\frac{\Delta I_C}{\Delta I_E} \Big|_{V_{CB} \text{ const.}}$

$I_{CBO} \rightarrow$  Leakage Current due to Reverse Bias between (B & C)

2.  $I_E = I_C + I_B$

Solve 1 & 2  $I_B = I_E - I_C = \frac{I_C - I_{CBO}}{\alpha} - I_C = (1 - \frac{\alpha}{\alpha}) I_C - \frac{I_{CBO}}{\alpha}$

3.  $\beta = \text{current gain} = (\frac{\Delta I_C}{\Delta I_B}) = \frac{\alpha}{1 - \alpha}$

4.  $I_B = \frac{I_C}{\beta} - \frac{I_{CBO}}{\alpha}$

Note  $I_{CBO}$  very small value [can be neglected]

$\therefore$  after neglecting  $I_{CBO}$

- ①  $I_C \cong \alpha I_E$
- ②  $I_E = I_C + I_B$
- ③  $I_C = \beta I_B$
- ④  $\beta = \frac{\alpha}{1 - \alpha}$

Ex)  $\alpha = 0.9 \rightarrow 0.998$

$\beta = 20 \rightarrow 800$

Handwritten notes in Urdu script.

EX(1)

Calculate the value of Collector current & Emitter current for transistor with  $\alpha_{dc} = 0.98$  &  $I_{CBO} = 5\mu A$  &  $I_B = 10\mu A$

Sol

$$I_C = \alpha I_E + I_{CBO}$$



$$I_E = \alpha [I_C + I_B] + I_{CBO}$$

$$\therefore I_C = 0.98 I_C + 0.98 \times 10 \times 10^{-6} + 5 \times 10^{-6}$$

$$0.02 I_C = 103 \times 10^{-6}$$

$$\therefore I_C = 5.15 \text{ mA}$$

\* Transistor Voltage \*

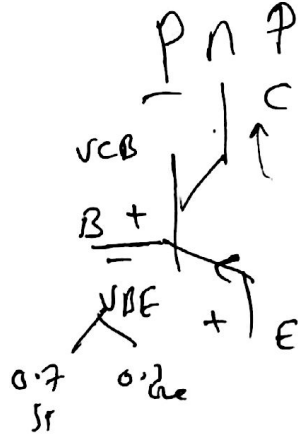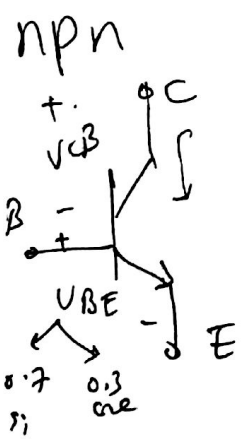

$V_{BE}$  Li (Si) 0.7 =  $V_{BE}$   
(Ge) 0.3

EX(2)

the Collector & Base currents of transistor are measured as

$I_C = 5.202 \text{ mA}$ ,  $I_B = 50 \mu A$   
 $I_{CBO} = 2 \mu A$ , calculate (a)  $\alpha_{dc}$   
 (b) The new  $I_B$  value that make  $I_C = 10 \text{ mA}$

Sol

(a)  $I_C = \alpha I_E + I_{CBO}$

$$5.202 \times 10^{-3} = \alpha [I_C + I_B] + 2 \times 10^{-6}$$

$$5.202 \times 10^{-3} = \alpha [5.202 \times 10^{-3} + 50 \times 10^{-6}] + 2 \times 10^{-6}$$

$$\therefore \alpha = 0.9999$$

$$\beta = \frac{\alpha}{1-\alpha} = \frac{0.9999}{1-0.9999} \approx 100$$

(b)  $I_C = 10 \text{ mA}$

$$10 \times 10^{-3} = 0.99 [10 \times 10^{-3} + I_B] + 2 \times 10^{-6}$$



$$\therefore I_B = 98 \mu A$$

الجهد الكافي لتفعيل الترانزستور

فيما يخصه

# Transistor characteristics and parameters

6

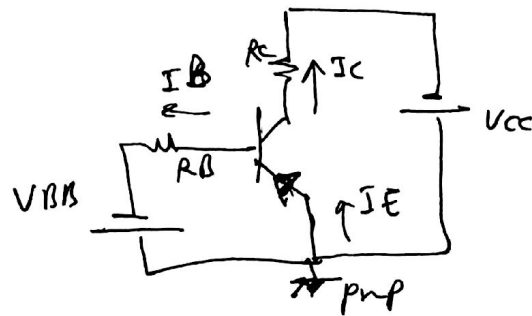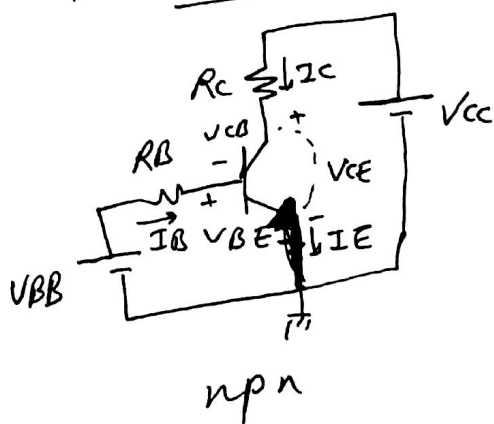

\*  $V_{BE}$  Forward biased (Base emitter) junction  
 $V_{CC}$  Reverse " (Base collector) junction

\* when (BE) forward  $\rightarrow$  like Diode forward with voltage drop (0.7V)

①  $V_{BE} = 0.7$

② \*  $I_B = \frac{V_{BB} - V_{BE}}{R_B}$

③  $V_{CE} = V_{CC} - I_C R_C$

④  $V_{CB} = V_{CE} - V_{BE}$

There are 6 parameters  
 $I_C, I_B, I_E$   
 $V_{BE}, V_{CE}, V_{CB}$   
 $I_{CBO} (\beta, V_{BB}, V_{CC} \text{ side})$

EX(3) if  $R_C = 100 \Omega, R_B = 10k\Omega, V_{CC} = 10V, V_{BB} = 5V, \beta = 150$   
 find  $I_B, I_C, I_E, V_{BE}, V_{CE}$  and  $V_{CB}$

Sol // ①  $V_{BE} = 0.7$

②  $I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5 - 0.7}{10k} = 430 \mu A$

③  $I_C = \beta I_B = 150 \times 430 \mu A = 64.5 \text{ mA}$

④  $I_E = I_C + I_B = 64.5 \text{ mA} + 430 \mu A = 64.93 \text{ mA}$

⑤  $V_{CE} = V_{CC} - I_C R_C = 10 - (64.5 \times 10^{-2} \times 100) = 3.55 \text{ V}$

⑥  $V_{CB} = V_{CE} - V_{BE} = 3.55 - 0.7 = 2.85 \text{ V}$

Solve yourself:  $R_B = 22k, R_C = 220\Omega, V_{BB} = 6V, V_{CC} = 9V, \beta = 90$   
 Find  $I_B, I_C, I_E, V_{CE}, V_{CB}$  Ans.  $[0.241 \text{ mA} / 21.68 \text{ mA} / 21.92 \text{ mA}$   
 $4.23 \text{ V} / 3.53 \text{ V}]$