

11


lec (3)
G161)

Sunday 9/10/2016

Δ (delta) \rightarrow Y (star) Conversion
& vice versa ($Y \rightarrow \Delta$)

\rightarrow it is used to simplify the circuit to be easy to model
and to calculate total Resistance easily


ex)

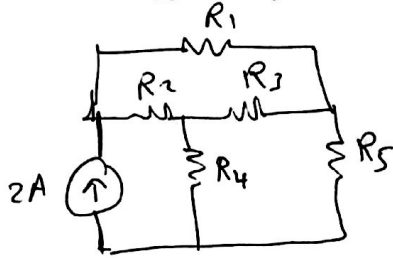

it is difficult to calculate R_{total}

So

we may convert

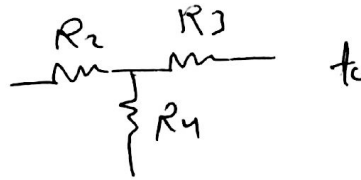


to



How?!

11

$Y \rightarrow \Delta$

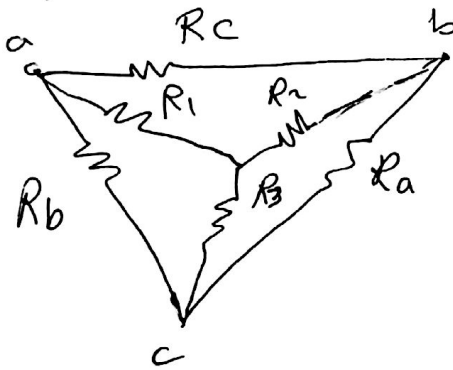

$$R_c = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_3} \quad (\text{القاعدة})$$

$$R_a = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_1}$$

$$R_b = \frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_2}$$

2 $\Delta \rightarrow Y$

$$R_1 = \frac{R_b R_c}{R_a + R_b + R_c} \quad (\text{القاعدة})$$

$$R_2 = \frac{R_a R_c}{R_a + R_b + R_c}$$

$$R_3 = \frac{R_a R_b}{R_a + R_b + R_c}$$

2

Problem (1)

Use Y-to- Δ to find (V)

Solution

$$R_a = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{5} = 70 \Omega$$

$$R_c = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{10} = 35 \Omega$$

$$R_b = \frac{5 \times 10 + 5 \times 20 + 10 \times 20}{20} = 17.5 \Omega$$

Now 28 parallel to 70

$$\therefore R_{1eq} = 28 \parallel 70 = \frac{28 \times 70}{28 + 70} = 20 \Omega$$



& 105 \parallel to 17.5

$$R_{2eq} = \frac{105 \times 17.5}{105 + 17.5} = 15 \Omega$$




$$R_{total} = 35 \parallel (R_{1eq} + R_{2eq})$$

$$= 35 \parallel (15 + 20) = 35 \parallel 35 = \frac{35 \times 35}{35 + 35} = 17.5 \Omega$$
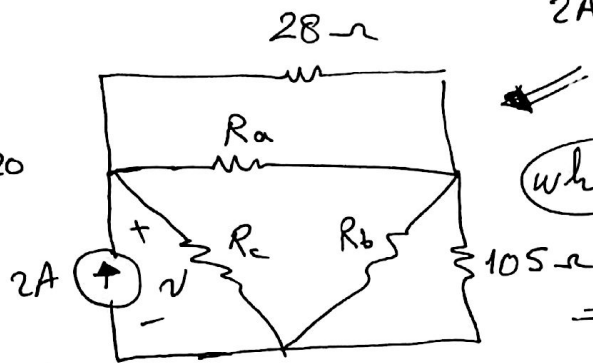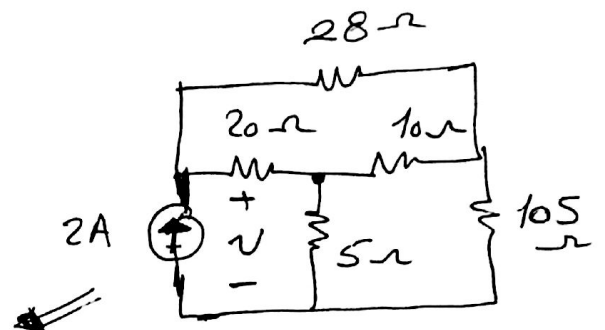
$$\therefore V_{total} = i_{total} \times R_{total} = 2 \times 17.5 = 35 \text{ Volt}$$




where

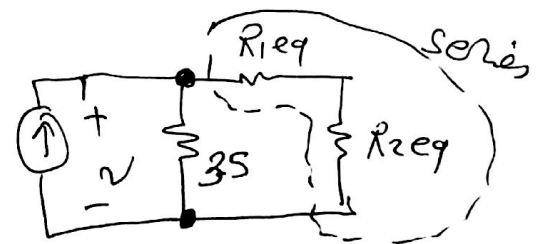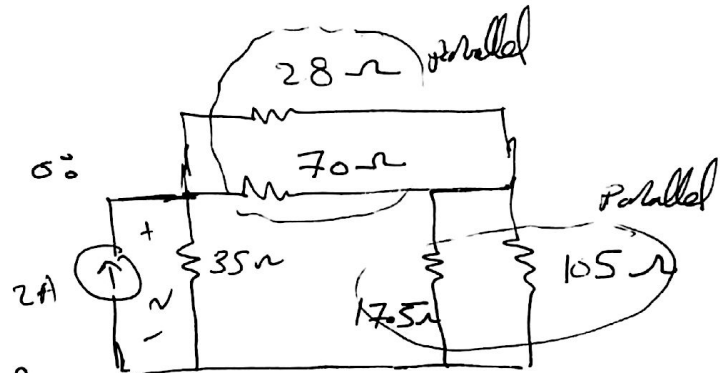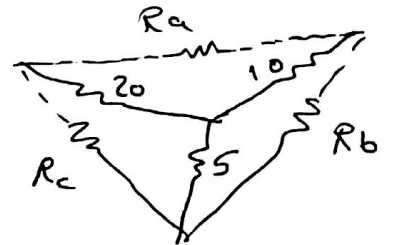


3

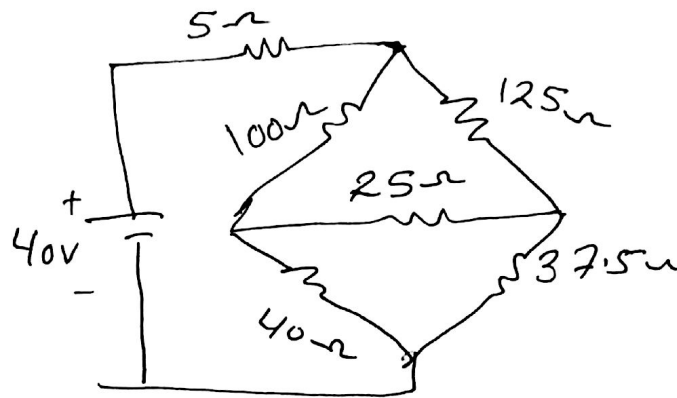Problem(2) Find I and Power Supplied by 40V source





we Replace upper delta Δ by Y

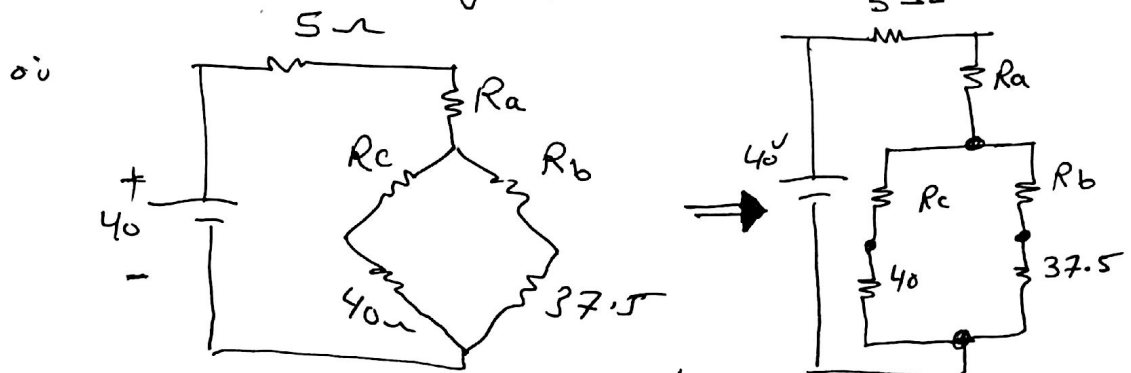

$$R_a = \frac{125 \times 100}{100 + 125 + 25} = 50 \Omega$$

$$R_b = \frac{125 \times 25}{100 + 125 + 25} = 12.5 \Omega$$

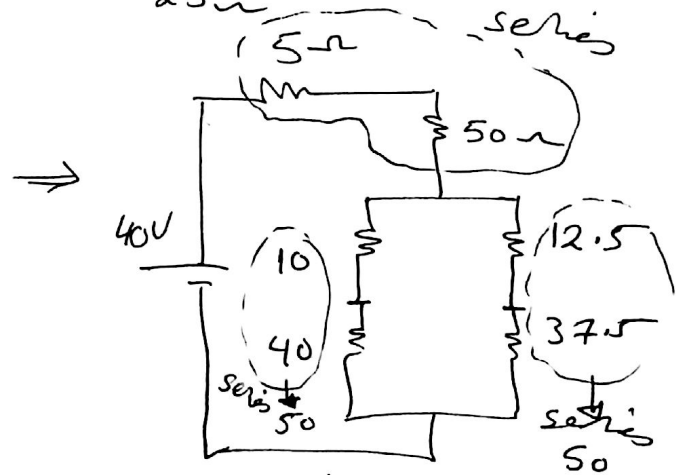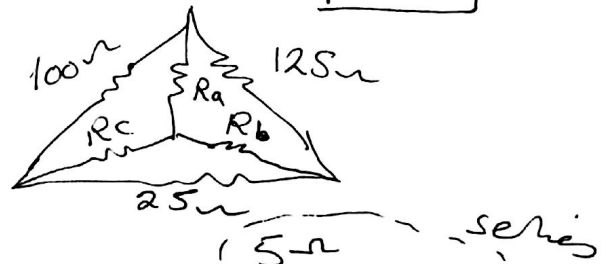
$$R_c = \frac{100 \times 25}{100 + 125 + 25} = 10 \Omega$$



$$\begin{aligned} \text{Total } R_{total} &= 5 + 50 + (50 \parallel 50) \\ &= 55 + 25 = 80 \Omega \end{aligned}$$

$$i = \frac{V}{R_t} = \frac{40}{80} = 0.5 \text{ A}$$

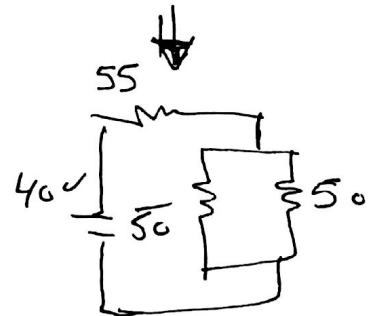
$$\text{Power} = V \times i = 40 \times 0.5 = 20 \text{ W}$$



4


Problem(3)

Find R_{ab}

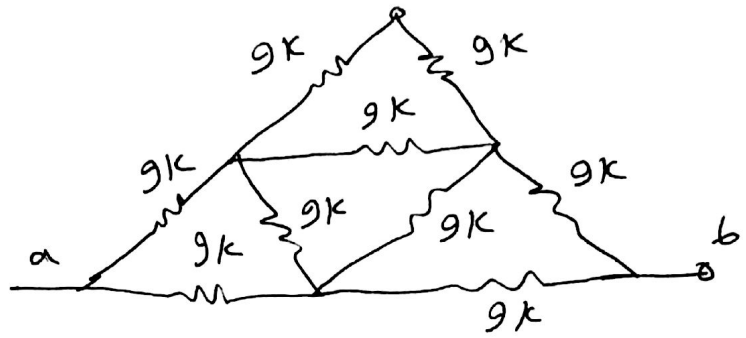


$(9+9) // 9 = 6k$

Parallel \rightarrow series \leftarrow

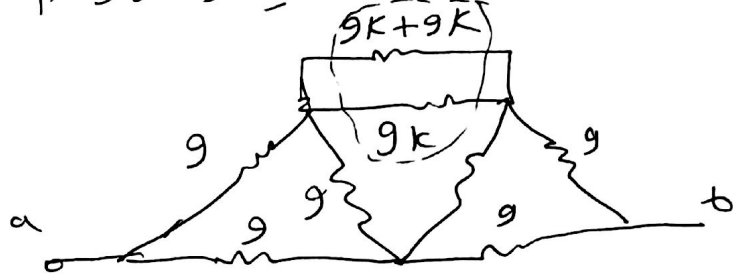


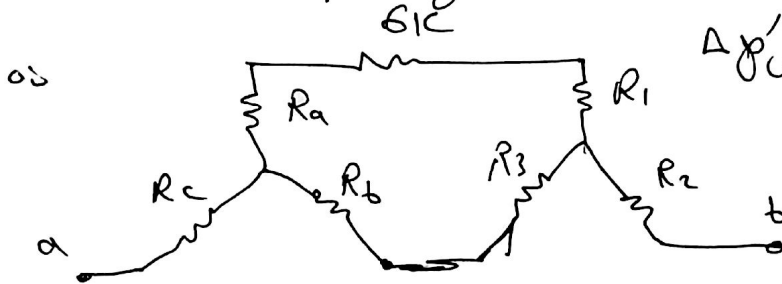نبدأ بتقليل Δ عن Δ \rightarrow Δ \rightarrow Δ \rightarrow Δ



$R_3 = R_2 = R_1$ \rightarrow $R_c = R_b = R_a =$

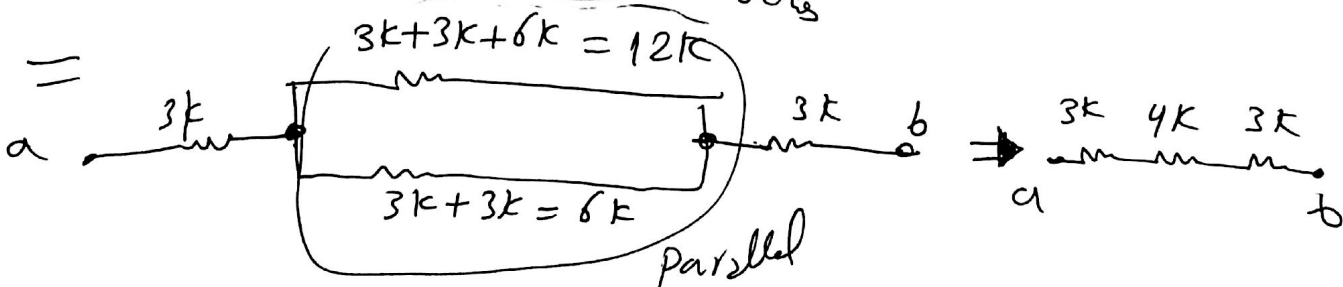$R_1 = R_2 = R_3 = R_a = R_b = R_c = \frac{(9 \times 9)k}{9+9+9} = 3k$




$R_{total} = 3k + 4k + 3k = 10k$

5

Problem (4) find i_d in a detector if the voltage drop across detector be neglected.


Solution/

we may calculate total current firstly

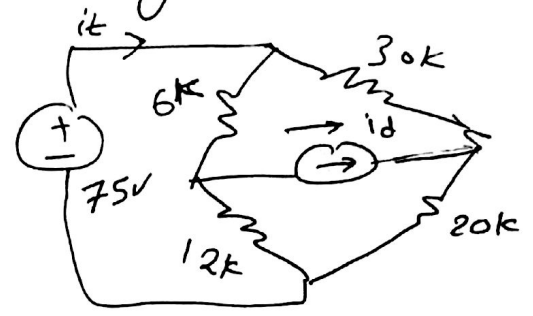


→ we replace detector with (short circuit)

$i_t = ?!$

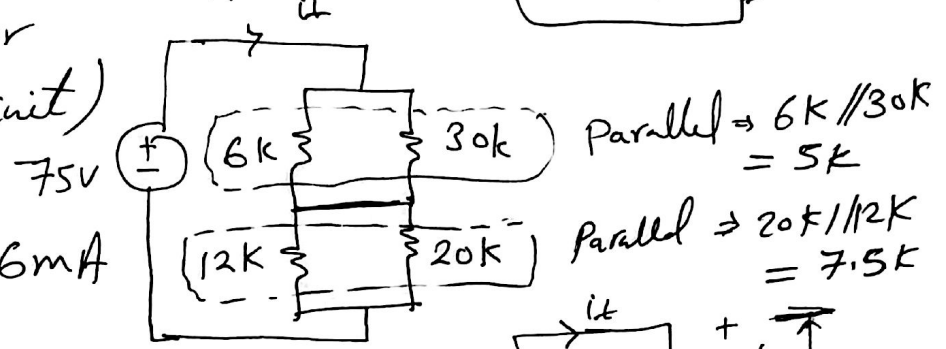

$$i_{total} = \frac{75}{5k + 7.5k} = 6mA$$

Parallel of 2 branches

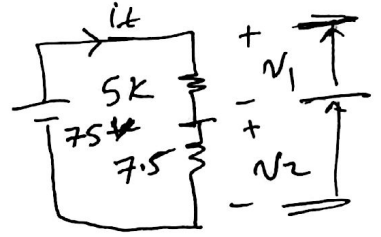

now using voltage divider

$$V_1 = V_{across\ 6k} = \frac{75 * (5k)}{(5k) + (7.5k)} = 30V$$

= V across 30k
= V across (equivalent 6/30)

$$V_2 = V_{across\ 12k} = V_{across\ 20k} = \frac{75 * (7.5k)}{(5k) + (7.5k)} = 45V$$

6k resistor

$$i_1 = \frac{V_1}{6k} = \frac{30}{6k} = 5mA$$


12k resistor

$$i_2 = \frac{V_2}{12k} = \frac{45}{12k} = 3.75mA$$

at node (a)

$$i_1 = i_d + i_2$$
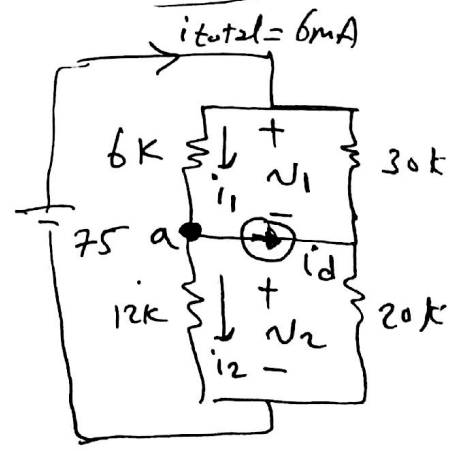
$$or\ i_d = i_1 - i_2 = 5mA - 3.75mA = 1.25mA$$



Good Luck