


Lec (4) Node Voltage

Node :- any joint tie 2 branches or more
 essential Node :- " " " " $\begin{matrix} 1 \\ 2 \end{matrix} \Omega$

ex


∴ this circuit has 3 essential nodes

∴ need (3-1) equations

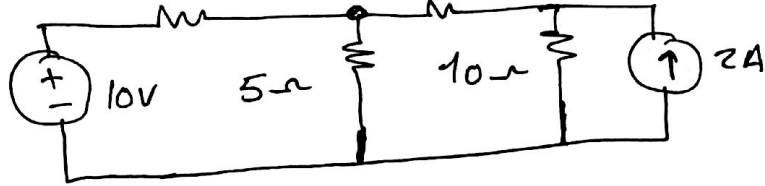

2) Select reference node (أول نقطة تحديد nodes ترتبط 3 branches من قبل)
 node

(V=0) Reference

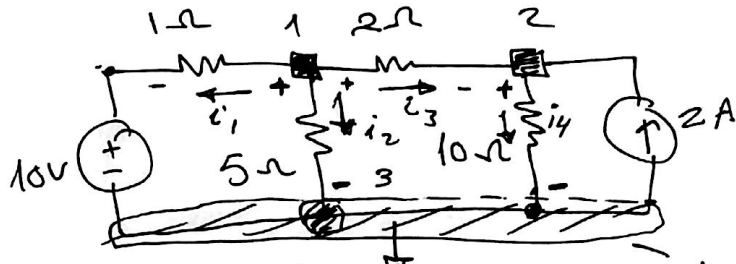

3) KCL في كل node
 direction of current
 polarity

تعتبر نقطة واحدة (نظام للتيار المتجه)
 direction of current
 polarity

(- = ref) مع اعتبار
 direction of current

$$0 = i_1 + i_2 + i_3$$

$$\sum I_{in} = \sum I_{out} \quad \frac{V_1 - 10}{1\Omega} + \frac{V_1 - 0}{5} + \frac{(V_1 - V_2)}{2} = 0 \rightarrow (1)$$

at node 2 $\sum I_{2in} = \sum I_{2out}$
 $i_3 + 2A = i_4$

$$\left(\frac{V_2 - V_1}{2}\right) + 2 = \frac{V_2 - 0}{10} = 0 \rightarrow (2)$$

Solve (1) & (2)

from (2)
 $V_2 = 20 + 5V_1$
 $V_2 = \frac{20 + 5V_1}{6}$

at (1)
 $V_1 - 10 + \frac{V_1}{5} + \frac{V_1}{2} - \frac{V_2}{2} = 0$
 $\frac{10V_1 + 2V_1 + 5V_1}{10} - 10 - \frac{20 + 5V_1}{12} = 0$

$$1.7V_1 - 10 - \frac{20}{12} - \frac{5}{12}V_1 = 0$$

$$1.283V_1 = 11.667 \rightarrow V_1 = 9.09V$$

$$V_2 = 10.91V$$

node voltage
 direction of current
 polarity
 correct
 same

سٲٲٲٲٲٲٲٲٲٲ

$$V_2 = 8.4V_1 + 20 = 0$$

$$-3.4V_1 + V_2 + 20 = 0$$

$$0.5V_1 + 0.6V_2 + 2 = 0$$

$$= \begin{bmatrix} -3.4 & 1 \\ 0.5 & -0.6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -20 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} -3.4 & 1 \\ 0.5 & -0.6 \end{vmatrix} = -3.4 \times 0.6 - 1 \times 0.5 = -1.54$$

$$\Delta_1 = \begin{vmatrix} 20 & 1 \\ 2 & -0.6 \end{vmatrix} = -20 \times 0.6 + 2 \times 1 = +14$$


$$\Delta_2 = \begin{vmatrix} -3.4 & 20 \\ 0.5 & 2 \end{vmatrix} = -3.4 \times 2 + 20 \times 0.5 = +16.8$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{+14}{-1.54} = 9.09V$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{+16.8}{-1.54} = 10.91V$$

Case 2 Dependent Source

ex Find Power dissipated in 5Ω Resistor

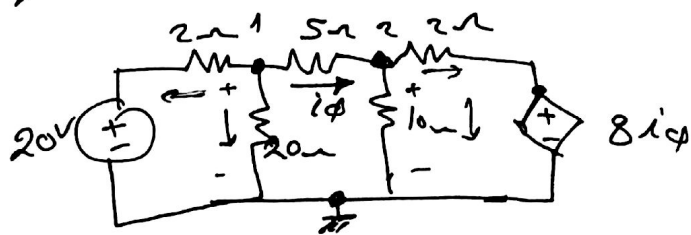

Node ①

$$\frac{V_1 - 20}{2} + \frac{V_1}{20} + \frac{V_1 - V_2}{5} = 0 \rightarrow \textcircled{1}$$

note $i_\phi = \frac{V_1 - V_2}{5}$

Node ②

$$\frac{V_2 - V_1}{5} + \frac{V_2}{10} + \frac{V_2 - 8i_\phi}{2} = 0 \rightarrow \textcircled{2}$$

|| ∞ ||

$$\frac{8V_2}{10} - \frac{V_1}{5} - 4i_\phi = 0$$

$$\Rightarrow \frac{4}{5}V_2 - \frac{V_1}{5} - 4\left(\frac{V_1 - V_2}{5}\right) = 0$$

$\frac{8}{5}V_2 - V_1 = 0 \rightarrow \textcircled{2}$

$$V_4 = \frac{8}{5}V_2 \quad V_2 = \frac{5}{8}(V_1) \rightarrow \textcircled{3}$$

in ①

$$\frac{V_1}{2} + \frac{V_1}{20} + \frac{V_1}{5} - 10 - \frac{V_2}{5} = 0$$

$$\frac{10V_1 + V_1 + 4V_1}{20} - 10 - \frac{5}{8}(V_1) = 0$$

$$\frac{315V_1}{20} - \frac{1}{8}V_1 - 10 = 0$$


$$10 = \frac{6V_1 - V_1}{8} = \frac{5V_1}{8} \quad \therefore V_1 = \frac{8 \times 10}{5} = 16V$$

$$V_2 = \frac{5}{8} \times 16 = 10V$$

$$i_\phi = \frac{V_1 - V_2}{5} = \frac{16 - 10}{5} = 1.2A$$

$$Power = i_\phi^2 \times 5 = 1.44 \times 5 = 7.2W$$

Case 3:- Special Case

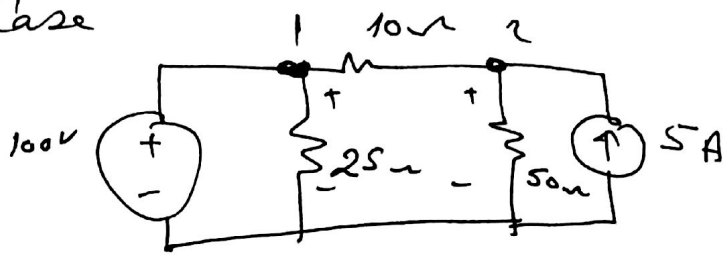

Node 1


at Node 1

at Node 1 $V_1 = 100V$

Node 2 $\frac{V_2 - V_1}{10} + \frac{V_2}{50} = 5$

Sub 1 in 2 $\frac{V_2}{10} - 10 + \frac{V_2}{50} = 5 \Rightarrow V_2 = 125V$

Case 4:- Supernode

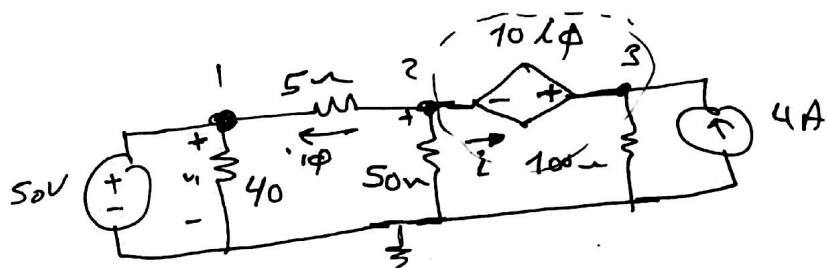

at Supernode

$V_3 - V_2 = 10i \rightarrow I$

* at node 1 $V_1 = 50V \rightarrow I$

$i = \frac{V_2 - V_1}{5}$

* at node 2 $\frac{V_2 - V_1}{5} + \frac{V_2}{50} + i = 0 \rightarrow III$

* at node 3 $i + 4 = \frac{V_3}{100} \rightarrow IIII$

∴ I rewritten as $V_3 - V_2 = 10 \left[\frac{V_2 - V_1}{5} \right]$

$V_3 - V_2 - 2V_2 = -2V_1 = -100$

$V_3 - 3V_2 = -100 \rightarrow (a)$

from node 2 $i = \frac{V_3}{100} - 4$

∴ $\frac{V_2 - 50}{5} + \frac{V_2}{50} + \left(\frac{V_3}{100} - 4 \right) = 0$

$\frac{V_2}{5} + \frac{V_2}{50} - 14 + \frac{V_3}{100} = 0$

$\frac{11V_2}{50} + \frac{V_3}{100} = 14 \rightarrow (b)$

Solve a, b

$V_2 = 60V$

$V_3 = 80V$

Find i_0


sol

(1) $\frac{V_1 - 20}{2k} + \frac{V_1 - V_2}{5k} + \frac{V_1 - 0}{30k} = 0$

(2) $\frac{V_2 - 20}{5k} + \frac{V_2 - 0}{1k} + \frac{V_2 - V_1}{5k} = 0$

$\therefore V_1 = 15, V_2 = 5$

$i_0 = \frac{V_1 - V_2}{5k} = 2mA$

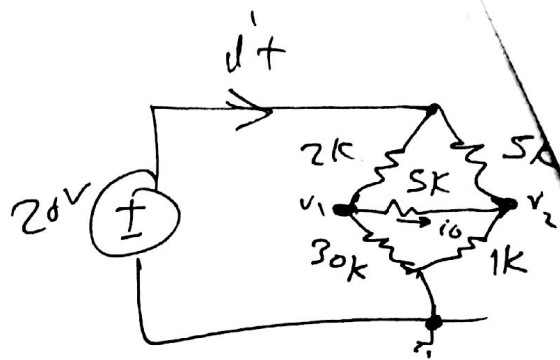

Trick: $i_t = ?!$

$i_t = i_1 + i_2$


$i_1 = \frac{20 - V_1}{2k} = 2.5mA$

$i_2 = \frac{20 - V_2}{5k} = 3mA$ $i_t = 5.5mA$

Report

(1) $\frac{V_1 - 20}{2} + \frac{V_1}{20} + \left[\frac{V_3 - V_2}{4} + \frac{V_3}{80} + 3.125V_0 \right]$

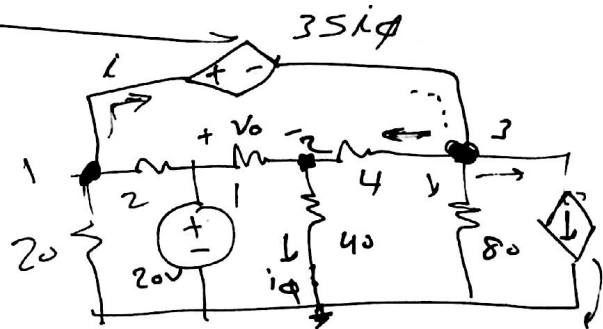(2) $\frac{V_2 - V_3}{4} + \frac{V_2}{40} + \frac{V_2 - V_1}{1}$



(3) $\frac{V_3}{80} + 3.125V_0 + \frac{V_3 - V_2}{4} = i_0 = 0$

$i_0 = 0$

Find P developed by 20V

(4) $V_1 - V_3 = 35kA$

(5) $i_0 = \frac{V_2}{40}$

(6) $V_0 = 20 - V_2$

$\therefore i_0 = 30 \cdot 10^{-5}, V_1 = -20.25V, V_2 = 10V, V_3 = -29V$

$P_g = i_0 \times 20 = 602.5W$