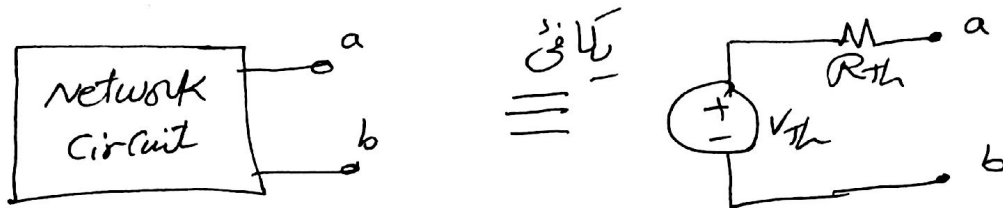


4.10, 4.11

## Thevenin and Norton Theorem



There are ③ methods to find equivalent circuit of any circuit to find  $I$ , or  $V$ , or  $P$  between (a,b) terminals

Method ①

- 1] make O.C between a,b and calculate  $V_{ab} = V_{th}$
- 2] " " " " " " " " " "  $I_{sc}$

∴  $R_{th} = \frac{V_{th}}{I_{sc}}$

(Handwritten note:  $\frac{V_{th}}{I_{sc}}$ )

Method ② Source Eliminations (independent sources only)

- remove Voltage source (S.C)
- " " " " " " " " " " (O.C)

Method ③ - assume voltage source ( $V_{test}$ ) & has a current ( $I_{test}$ )

- apply source elimination  $\rightarrow \infty$

∴ then  $V_{test} = V_{th}$  &  $R_{th} = \frac{V_{test}}{I_{test}}$

(Handwritten note:  $\frac{V_{test}}{I_{test}}$ )


---

(2)

### Example (1)


1- Find equivalent thevenin's

Solution

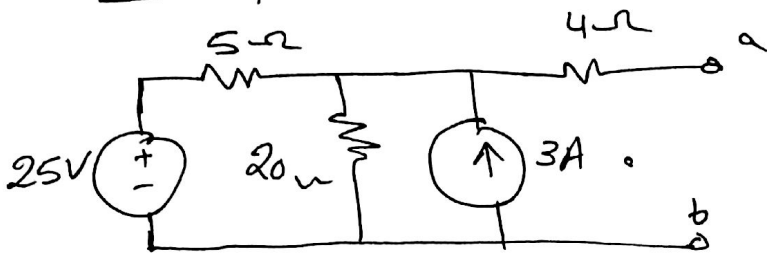

step (1)  
 → First open circuit between a, b  
 → Calculate  $V_{ab} = V_{Th}$

We can use Node

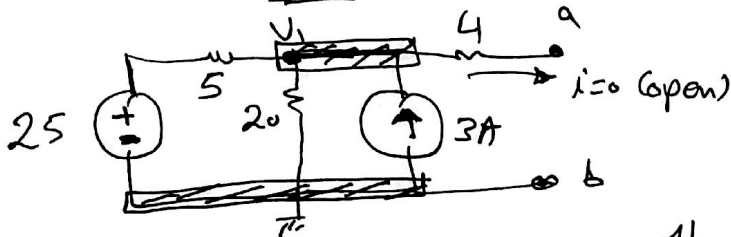


$$\frac{V_1 - 25}{5} + \frac{V_1}{20} - 3 = 0$$

$$\therefore V_1 = 32V$$

$V_1 = V_{ab}$  (المقاومة مفتوحة،  $i = 0$ )

step (2)

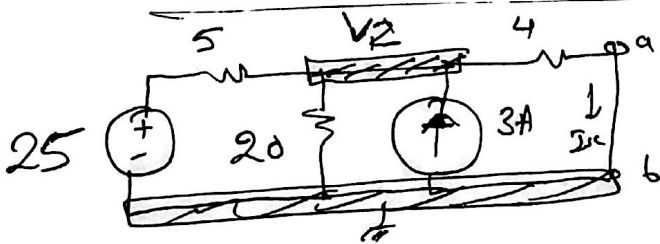make short circuit between a, b to find  $I_{sc}$




$$\frac{V_2 - 25}{5} + \frac{V_2}{20} - 3 + \frac{V_2}{4} = 0$$

$$\therefore V_2 = 16V$$

$$I_{sc} = \frac{V_2}{4} = 4A$$

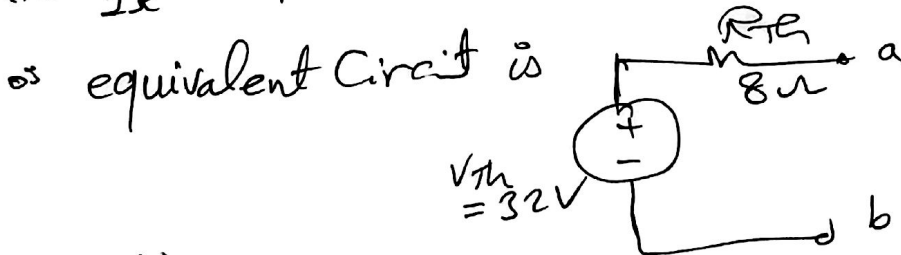
$$R_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{32}{4} = 8\Omega$$






CV → step 2 mode we calculate  $V_{Th}$  and  $I_{sc}$

We can Re-answer the Previous Problem using  
Source transformation

3

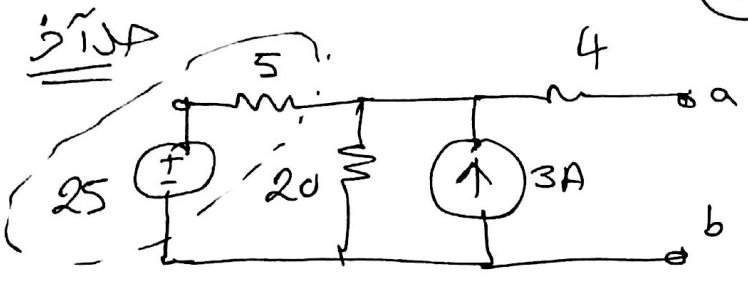

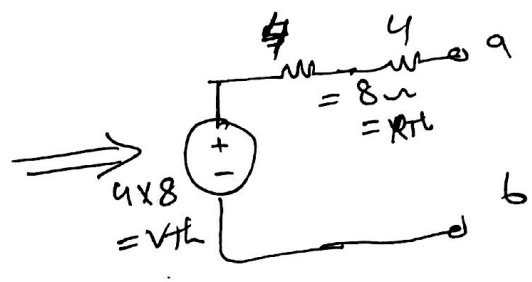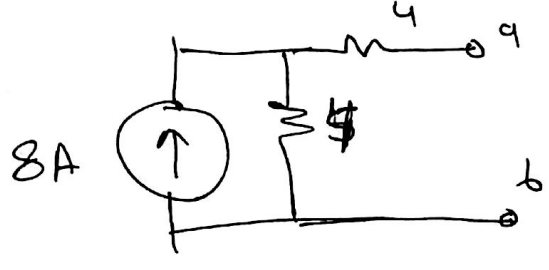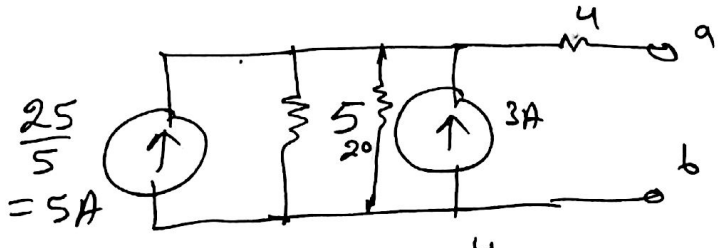
المسألة الأولى  
Thevenin's  
من الدارة  
source transformation



Method 2 Source elimination (  $R_{th}$  )  
 (  $R_{th}$  )

let Voltage source  $\underline{8V}$   
 current "  $\underline{5A}$


because  $R_{th}$  is  $4\Omega$

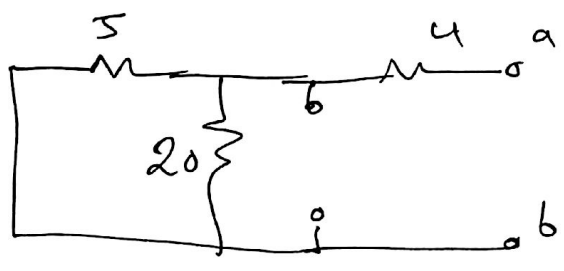

$5 \parallel 20 + 4 = R_{th}$   
 $R_{th} = 8\Omega$


then  $V_{th}$  is  $32V$   $V_{th}$

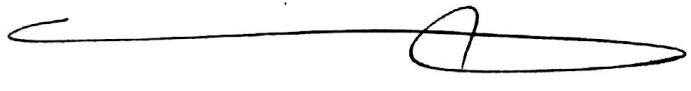التيار  $I_{test}$  و  $V_{test}$  في الدارة  
 (  $V_{test}$  )




# 2. Norton equivalent

Thevenin's

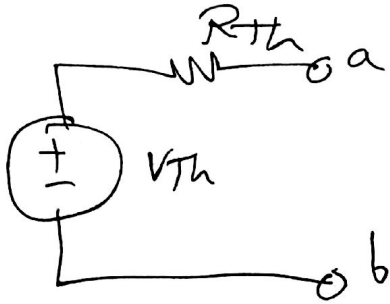


Norton

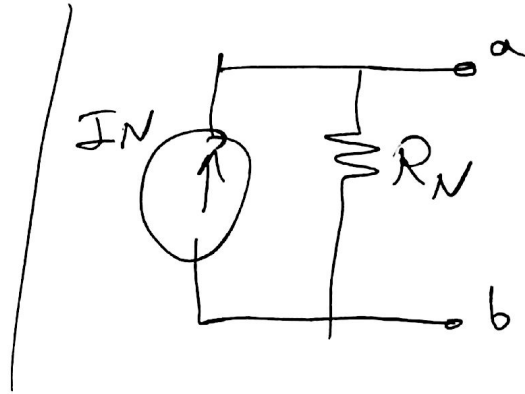

$$R_{th} = R_N$$

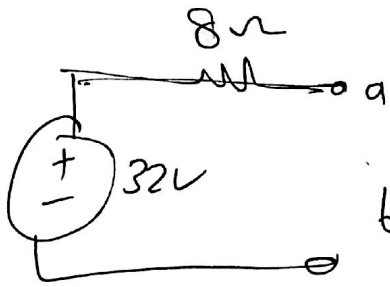
$$I_N = I_{SC} \text{ or } \frac{V_{th}}{R_{th} = R_N}$$



Thevenin's equivalent circuit


Norton

$$\frac{32}{8} = 4A$$

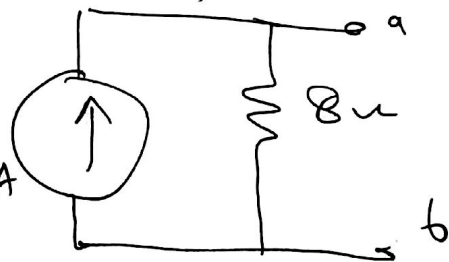


Source Transformation

Source Transformation

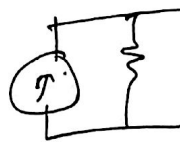

Source Transformation

Example (2)

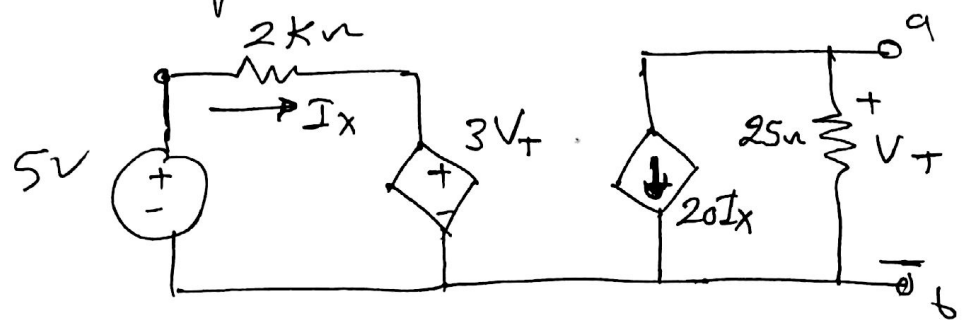

if there is dependant source  
لا حظ لو فيه ا source  
independant source  
بوصلة (البارنة)  
∴ Vth = 0  
و حسب بقية

Find Thevenin's equivalent & Norton's equivalent

Step 1

\*  $V_{th} = V_{ab} = V_T = V_{25\Omega}$

$V_T = (25)(-20I_x) = -500I_x$


But  $I_x = \frac{5 - 3V_T}{2k}$  ~~or  $2000 I_x = 5 - 3V_T$~~

∴  $V_T = -500 \left[ \frac{5 - 3V_T}{2k} \right] = -500 \left[ \frac{5 - 3V_T}{2000} \right]$

$V_T = -\frac{5}{4} + \frac{3}{4} V_T$  or  $\frac{1}{4} V_T = -\frac{5}{4}$  or  $V_T = -5V$

∴  $V_{th} = -5V$


Step 2

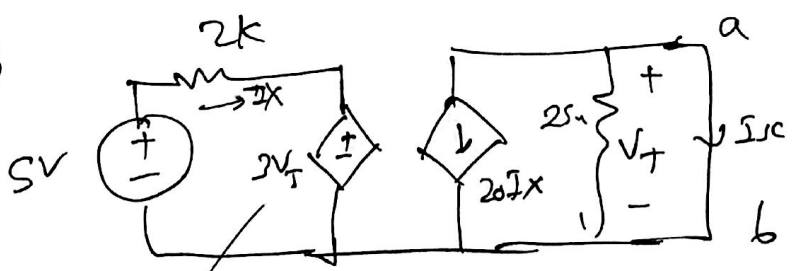

ال SC ال 25Ω  
و ال 20Ix ال 25Ω  
و ال 3Vt ال 25Ω

∴  $25\Omega // SC \therefore V_T = 0V$

∴  $3V_T = 0$  also

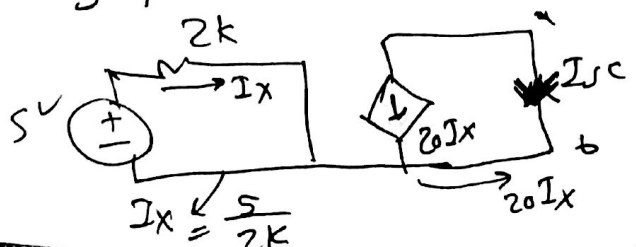

$I_{sc} = -20I_x$

$I_{sc} = -20 \left[ \frac{5}{2000} \right] = -0.05A$

∴  $R_{th} = V_{th} / I_{sc} = \frac{-5}{-0.05} = 100\Omega$

