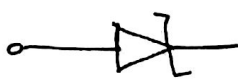


Zener diode (diode Applications)


(a) symbol 

it is a semiconductor diode designed to operate in both Forward and Reverse Connection.

→ in Forward connection it looks like normal diode (battery of 0.7V), while in Reverse connection it is still open until the voltage across its terminals exceeds the input voltage, so it acts as a constant voltage source (constant battery) and passes a current through it → Zener diode also called (breakdown diode)

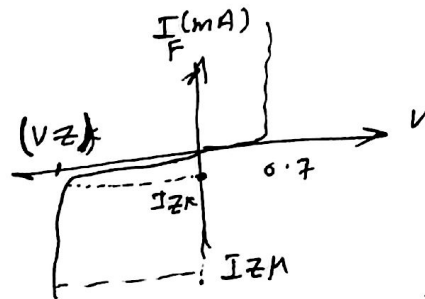(b) characteristics of Zener

- I_{ZK} .. Knee current (minimum Zener current at V_Z)



- I_{ZM} .. Maximum safe current, *بیشترین مقدار مجاز*


(c) Uses of Zener diode

→ it is used as a voltage Regulator, so it is found in Power supply (charger) circuits.

منظور از ولتاژ منظم

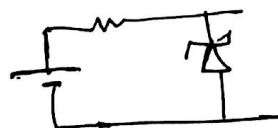
(d) Connection of Zener diode

to use Zener as a Regulator, so it is connected in Reverse Connection with Supply (the +ve of supply with Cathode of Zener)



⑤ Zener Model [Zener Connected in Shunt with source] ②

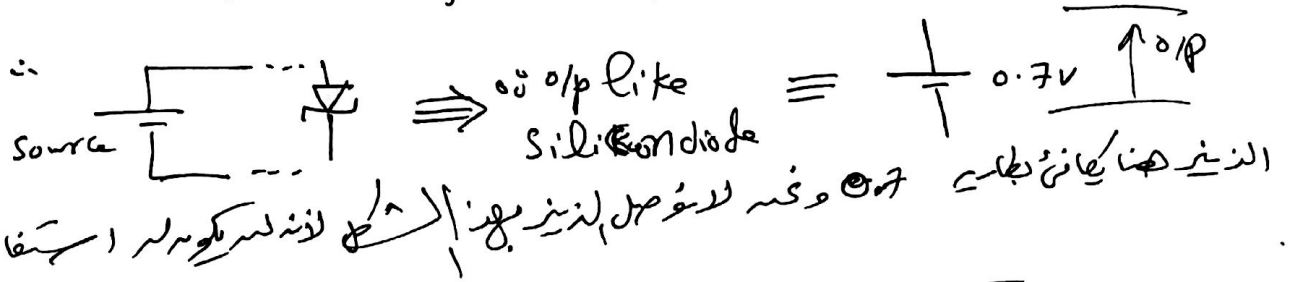→ if Anode Connected to +ve of source (forward)




So → Zener Connected as Shown




There are 2 cases in this connection-

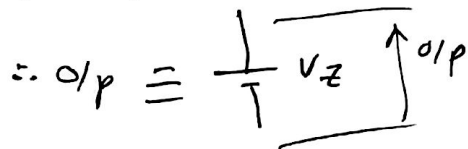(1) On state ($V_{in} > V_z$) → So o/p like Battery (voltage source) $\overset{\text{constant}}{= V_z}$



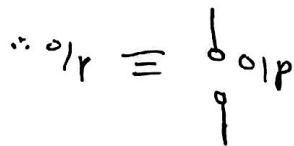(2) off state ($V_{in} < V_z$) → So it like (open circuit) $\overset{\text{acts}}$



⑥ Zener diode Analysis


① at V_i and R_L const

② at fixed V_i and Variable R_L
load Regulation

③ fixed R_L and Variable (V_i)
(line regulation)

① Const (Fixed) V_i and Fixed R_L

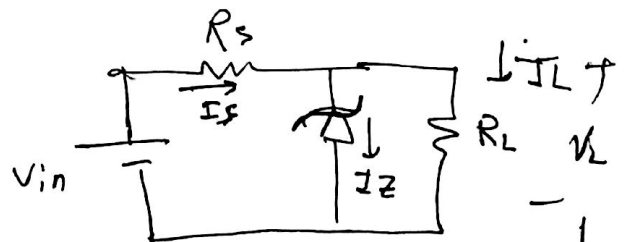* First step assume Zener (open) and calculate the voltage across it




* If $V_{in} < V_z$: Zener really on and its equivalent circuit is $\frac{1}{V_z}$

* If $V_{in} > V_z$: Zener off & acts as open circuit

using voltage divider

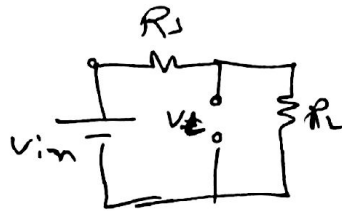
$$\therefore V_L = \frac{V_{in} R_L}{R_L + R_S}$$



(3)

Now, if $V_L < V_Z$ $\therefore$ Zener (off) $\Rightarrow$ open & $V_Z = \frac{V_{in} R_L}{R_L + R_S}, I_Z = 0$
 $\Rightarrow$ if $V_L > V_Z$ $\therefore$ Zener (on) $\Rightarrow \frac{1}{I} V_Z$

assume on $\therefore$

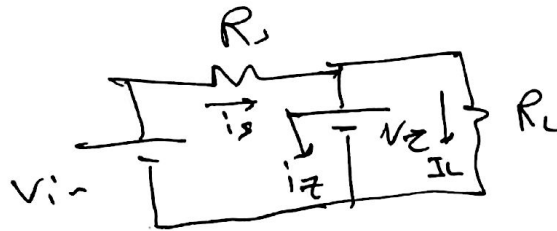


$$\rightarrow \therefore V_L = V_Z \quad \& \quad I_L = \frac{V_Z}{R_L}$$

$$\rightarrow I_S = \frac{V_{in} - V_Z}{R_S}$$

$$\rightarrow I_S = I_Z + I_L \quad \text{or} \quad I_Z = I_S - I_L$$
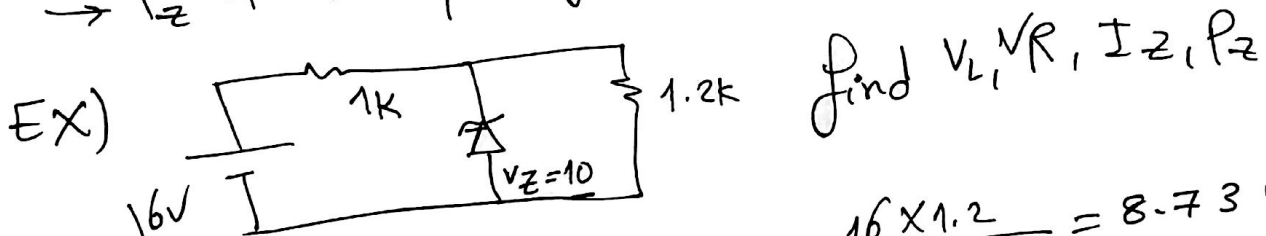
$$\rightarrow P_Z \text{ (Power dissipated by Zener)} = V_Z I_Z$$



Assume Zener open $\therefore V_L = \frac{16 \times 1.2}{1 + 1.2} = 8.73 \text{ V}$
 $\therefore 8.73 < 10 \text{ V} \quad (\text{V}_Z) \therefore$ Zener off (open)

$$\rightarrow \text{and } \underline{V_L = 8.73}$$

$$\rightarrow V_R = V_{in} - V_L = 16 - 8.73 = 7.27 \text{ V}$$

$$\rightarrow I_L = \frac{V_L}{R_L} = \frac{8.73}{1.2 \text{ K}} = 7.27 \text{ mA}$$

$$I_R = \frac{16 - 8.73}{1 \text{ K}} = 7.27 \text{ mA}$$


$$\therefore P_Z = V_Z I_Z = 0$$

4

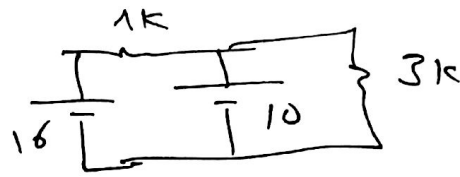b) % $R_L = 3k$ repeat problem

$$V_L = \frac{16 \times 3k}{1k + 3k} = 12V$$

$$V_L > V_Z \Rightarrow \text{Zener on}$$



$$V_Z = V_L = 10V$$

$$I_L = \frac{10}{3k} = 3.33mA$$


$$I_Z = I_R - I_L = (6 - 3.33)mA = 2.67mA$$

$$I_R = \frac{16 - 10}{1k} = 6mA$$

$$P_Z = V_Z I_Z = (2.67mA)(10) = 26.7mW$$

2 Load Regulator [Fixed V_i & Variable R_L]

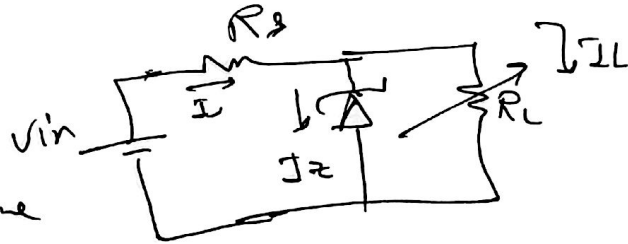R_L changed between minimum & maximum value



(R_{Lmin} & R_{Lmax})

Note of R_L (small) $\rightarrow V_L$ (small) = ~~generally~~

by the same previous equations [on state]

$$V_Z = V_L = V_{in} \frac{R_{Lmin}}{R_{Lmin} + R_s}$$

$$\% R_{Lmin} \Rightarrow R_{Lmin} \Rightarrow I_{Lmax}$$

$$R_{Lmin} = \frac{V_Z}{I_{Lmax}}$$

$$R_{Lmax} = \frac{V_Z}{I_{Lmin}}$$

$$\rightarrow V_R = V_{in} - V_Z, \quad I_R = V_R / R_s$$

$$\rightarrow I_Z = I_R - I_L \quad \text{of } I_{Lmax} \text{ as } I_{Zmax} = I_R - I_{ZK}$$

$$\rightarrow I_Z = I_R - I_L \quad \text{of } I_{Lmin} \text{ as } I_{Lmin} = I_R - I_{Zmax}$$


for $(I_{smin}) R_s$... (I_{ZK}) ...

(5)

Example For The Circuit shown

(a) find the range of R_L and I_L that will result in V_{RL} being maintained at 10V

(b) Find The maximum voltage rating of the diode

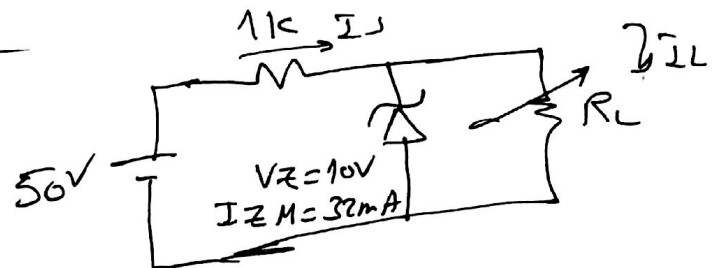Sol

$$V_L = \frac{50 R_{Lmin}}{R_{Lmin} + (1k)}$$

Let $V_L = 10V$ (as)

$$\therefore 10 = \frac{50 R_{Lmin}}{R_{Lmin} + 1000}$$

$$\therefore R_{Lmin} = 5 R_{Lmin} + 4000$$

$$\therefore R_{Lmin} + 1000 = 5 R_{Lmin}$$

$$\text{or } 4 R_{Lmin} = 1000$$

$$R_{Lmin} = \frac{1000}{4} = 250 \Omega$$

$$\therefore V_R = V_{in} - V_L = 50 - 10 = 40V$$

$$I_R = \frac{40}{1k} = 40mA$$

$$I_{Zmax} = 32mA$$

$$\therefore I_{Lmin} = I_R - I_{Zmax} = 40 - 32 = 8mA$$

$$\therefore V_L = 10 \quad \therefore R_{Lmax} = \frac{V_L}{I_{Lmin}} = \frac{10}{8mA} = 1.25k\Omega$$

$$\rightarrow R_{Lmin} = \frac{V_L}{I_{Lmax}} \quad \& \quad I_{Lmax} \text{ at } I_{Zmin} (\approx 0) \text{ or } I_{Lmax} \approx I_R = 40mA$$

$$\therefore R_{Lmin} = \frac{10}{40mA} = 250 \Omega$$

Range of Resistance is between 250Ω & $1.25k\Omega$

(b) $P_{max} = V_Z I_{Zmax} = (10)(32 \times 10^{-3}) = 320mW$

(6)

[C] Fixed R_L and Variable input (line Regulation)

note V_{in} must be large to turn on Zener, minimum voltage required to turn on Zener can be calculated from relation


where $V_L = \frac{V_{in}(R_L)}{R_L + R_S}$

or $V_{in(min)} = \frac{V_L(R_L + R_S)}{R_L}$

and $I_{Zmax} = I_{Smax} - I_L$

→ So $I_{Smax} = I_{Zmax} + I_L$

→ $V_{R_S} = I_{Smax} \times R_S$

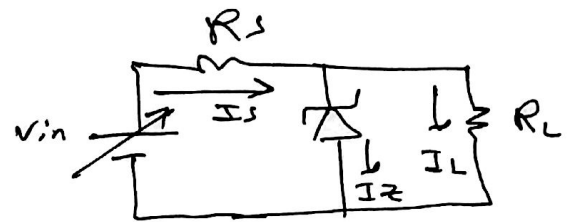

→ $V_{in(max)} = I_{Smax} R_S + V_Z = I_{Smax} R_S + V_L = (I_{Zmax} + I_L) R_S + V_Z$


Ex(3) For the shown circuit, find the range of V_i that will Zener ON

$I_L = \frac{V_Z}{R_L} = \frac{20}{1.2k} = 16.67mA$

$V_{in(min)} \Rightarrow$

$V_Z = 20 = \frac{V_{in(min)}(1.2k)}{(1.2k) + 220}$

$\therefore V_{in(min)} = 23.67V$

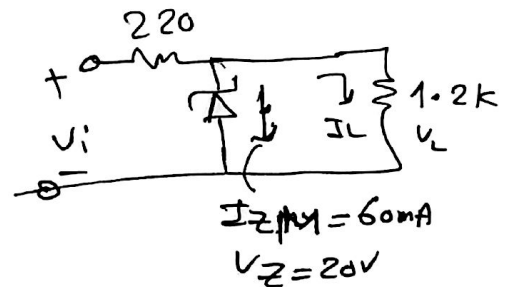

$I_{Smax} = I_{Zmax} + I_L = 60mA + 16.67mA = 76.67mA$

$\therefore V_{in(max)} = I_{Smax} \times R_S + V_Z = 220 \times 76.67 \times 10^{-3} + 20 = 36.87V$

$\therefore V_{in}$ changed from $(23.67 \rightarrow 36.87V)$


Example (4)

Suppose Zener diode in shown circuit with the following specifications

$$V_Z = 10V, I_{ZK} = 0.25mA, P_{Dmax} = 1W$$

Find the i/p limits for Regulation.

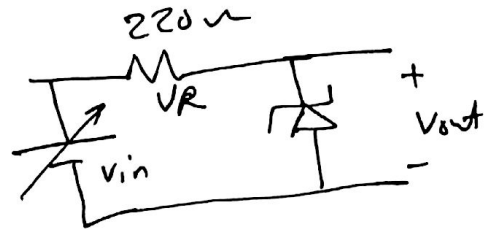Sol • $I_{ZMax} = \frac{P_{Dmax}}{V_Z} = \frac{1W}{10V} = 0.1A = 100mA$



• $I_{ZK} = 0.25mA$ (minimum)

$$V_{in} = V_R + V_{out}$$

$$= 10 + I_S \times 220$$

$$V_{inmin} = 10 + 220 I_{Smin} = 10 + 220 [I_{Zmin}]$$

$$= 10 + 220 \times 0.25 \times 10^{-3} = 10.055V$$

$$V_{inmax} = 10 + 220 I_{Smax} = 10 + 220 [I_{Zmax}]$$

$$= 10 + 220 \times 100 \times 10^{-3} = 32V$$

$\therefore$ input changes from $10.055 \rightarrow 32V$