


# Lec (11)



## Electronic Fundamentals Circuits, Devices, and Applications

### Diodes and Applications

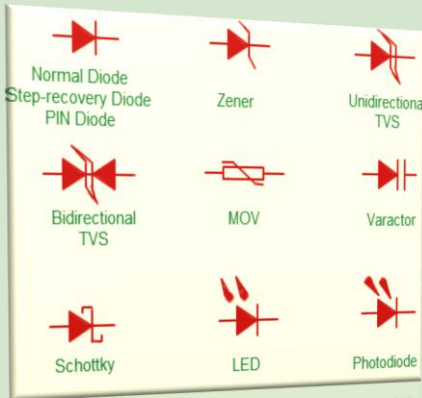
### Power Supply Filters and Special-Purpose Diodes



[ 1 ]
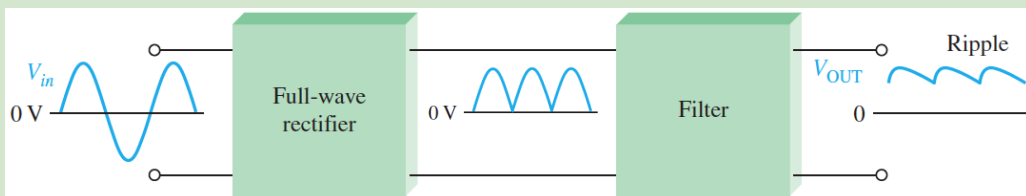
## Power supply filters

- A power supply filter ideally eliminates the fluctuations in the output voltage of a half-wave or full-wave rectifier and produces a constant-level dc voltage.
- In most power supply applications, the standard (60 Hz or 50 Hz) ac power line voltage must be converted to an approximately constant dc voltage.




[ 2 ]

# Capacitor-Input Filter

Initial charging of the capacitor (diode is forward-biased) happens only once when power is turned on.


The capacitor discharges through  $R_L$  after peak of positive alternation when the diode is reverse-biased.

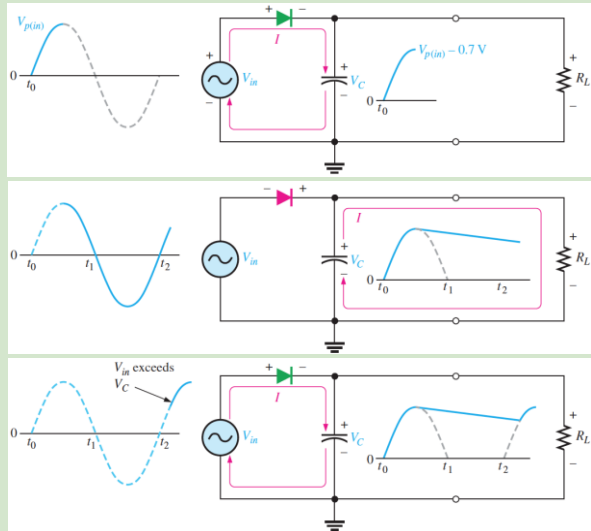The capacitor charges back to peak of input when the diode becomes forward-biased.


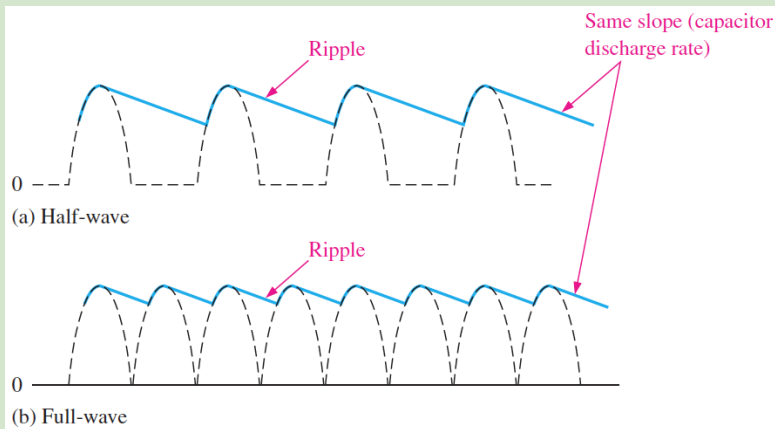
# Ripple Voltage

**Ripple voltage** is the variation in the capacitor voltage due to the charging and discharging.



# Ripple Factor

The **ripple factor (r)** is an indication of the effectiveness of the filter


$$r = \frac{V_{r(pp)}}{V_{DC}}$$

$V_{r(pp)}$  is the peak-to-peak ripple voltage  
 $V_{DC}$  is the dc (average) value of the filter's output voltage

$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)}$$

$$V_{DC} \cong \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)}$$

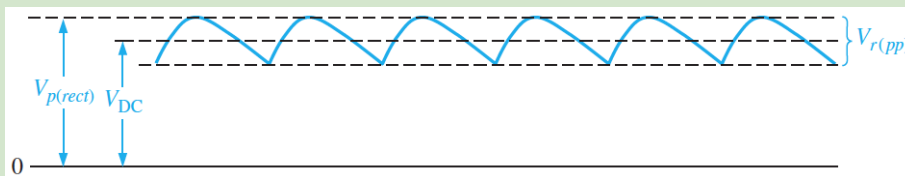
When  $R_L$  or  $C$  increases, the ripple voltage decreases and the dc voltage increases.



[ 5 ]
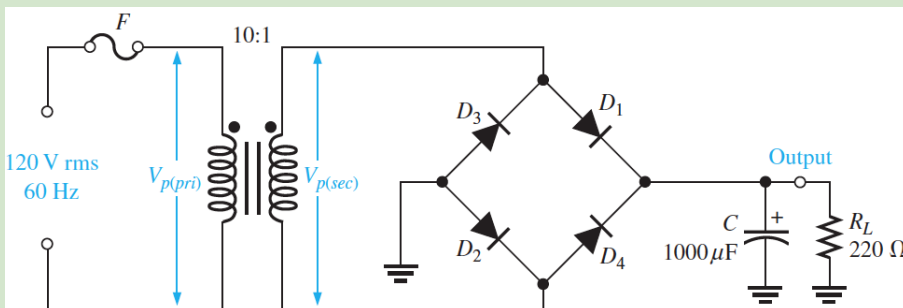
# Example

Determine the ripple factor for the filtered bridge rectifier with a load as indicated in the Figure



[ 6 ]

## Solution

- The transformer turns ratio is  $n = 1/10 = 0.1$ . The peak primary voltage is

$$V_{p(prim)} = 1.414V_{rms} = 1.414(120 \text{ V}) = 170 \text{ V}$$

- The peak secondary voltage is

$$V_{p(sec)} = nV_{p(prim)} = 0.1(170 \text{ V}) = 17.0 \text{ V}$$

- The unfiltered peak full-wave rectified voltage is

$$V_{p(rect)} = V_{p(sec)} - 1.4 \text{ V} = 17.0 \text{ V} - 1.4 \text{ V} = 15.6 \text{ V}$$

$$V_{r(pp)} \cong \left( \frac{1}{fR_L C} \right) V_{p(rect)} = \left( \frac{1}{(120 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 0.591 \text{ V}$$

$$V_{DC} = \left( 1 - \frac{1}{2fR_L C} \right) V_{p(rect)} = \left( 1 - \frac{1}{(240 \text{ Hz})(220 \Omega)(1000 \mu\text{F})} \right) 15.6 \text{ V} = 15.3 \text{ V}$$

- The resulting ripple factor is

$$r = \frac{V_{r(pp)}}{V_{DC}} = \frac{0.591 \text{ V}}{15.3 \text{ V}} = 0.039$$


*The percent ripple is 3.9%.*

{ 7 }
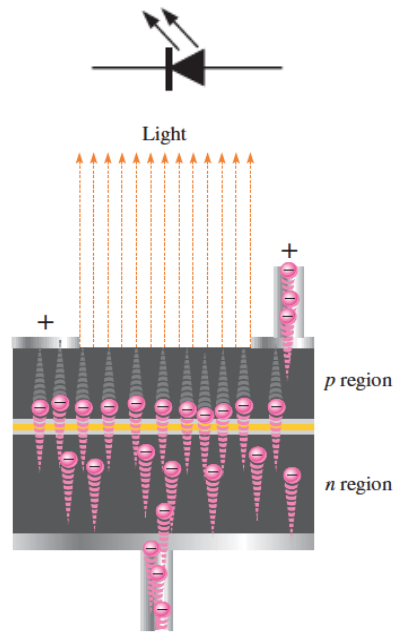
## The Light-Emitting Diode (LED)

The basic operation of an LED (light-emitting diode) is as follows:


- When the device is **forward biased**, electrons cross the pn junction from the n-type material and recombine with holes in the p-type material.
- When **recombination** takes place, the recombining electrons release energy in the form of heat and **light**.



{ 8 }
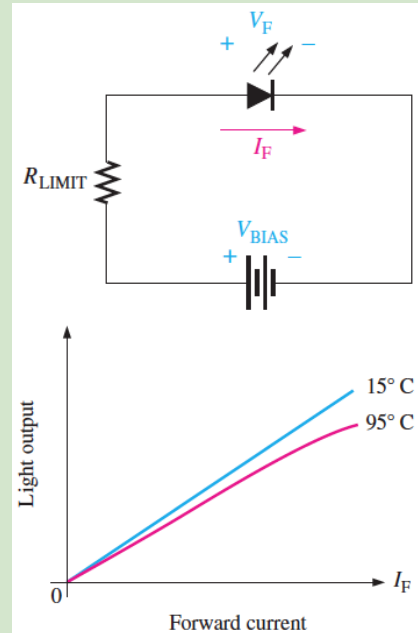
## LED Biasing

- The amount of power output translated into light is directly proportional to the forward current.
- An increase in  $I_F$  corresponds proportionally to an increase in light output.
- The light output (both intensity and color) is also dependent on temperature. Light intensity goes down with higher temperature as indicated in the figure.




[09]

## The Photodiode

The **photodiode** is a device that operates in reverse bias, where  $I_\lambda$  is the reverse light current. The photodiode has a small transparent window that allows light to strike the *pn* junction.


A photodiode differs from a rectifier diode in that when its *pn* junction is exposed to light, the reverse current increases with the light intensity. When there is **no incident light**, the reverse current,  $I_\lambda$ , is almost negligible and is called the **dark current**.

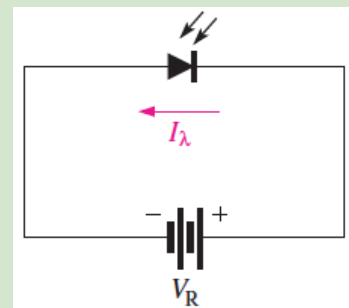An increase in the amount of light intensity, expressed as irradiance ( $\text{mW}/\text{cm}^2$ ), produces an increase in the reverse current




[10]

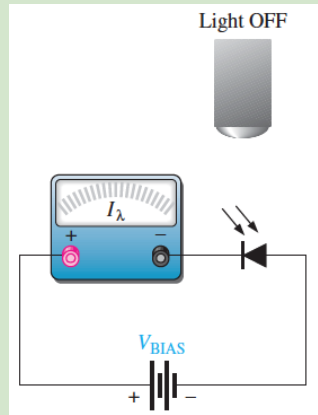The photodiode allows essentially no reverse current (except for a very small dark current) when there is no incident light.



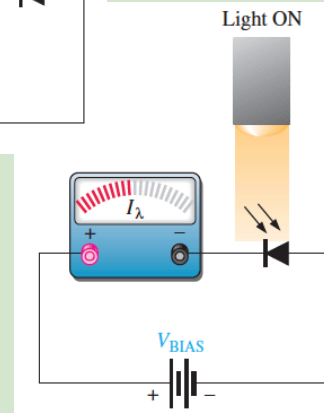When a light beam strikes the photodiode, it conducts an amount of reverse current that is proportional to the light intensity (irradiance).



# Self-test

Try to solve the Self-test in your text book

Electronic Devices

by  
Floyd

9th Edition

Pages 99-105

Pages 161-169

