

## FET

FET.. Field effect Transistor

- The Current Flow between the two terminal (Source S & Drain D) is controlled by an electric field applied to the third terminal (Gate G).
- FET is called (Unipolar) because current depends only on majority carriers (E or h) = one carrier only. while NPN or PNP depends on 2 carriers.

### Advantages & disadvantages of FET compared to BJT

- 1- FET is Voltage controlled current source Device (VCCS) while BJT is current controlled current source ~ (CCCS).
- 2- FET has large i/p impedance, so it is preferred than BJT as input stage to multistage amplifier.
- 3- FET generates lower noise level than BJT.
- 4- FET more Temperature stable than BJT.
- 5- FET is easier to be fabricated than BJT.
- 6- FET acts as VCR (voltage controlled resistor)


### disadvantages

- 1- FET has poor frequency response (low BW)
- 2- Poor linearity (non linear relation between  $I_D, V_{GS}$ )
- 3- Due to static charges → Damage occurred.

→ Uses of FET → Flash memory, USB drive, Camera, laptop, CPU, -- etc



(2)

# Transistor Family


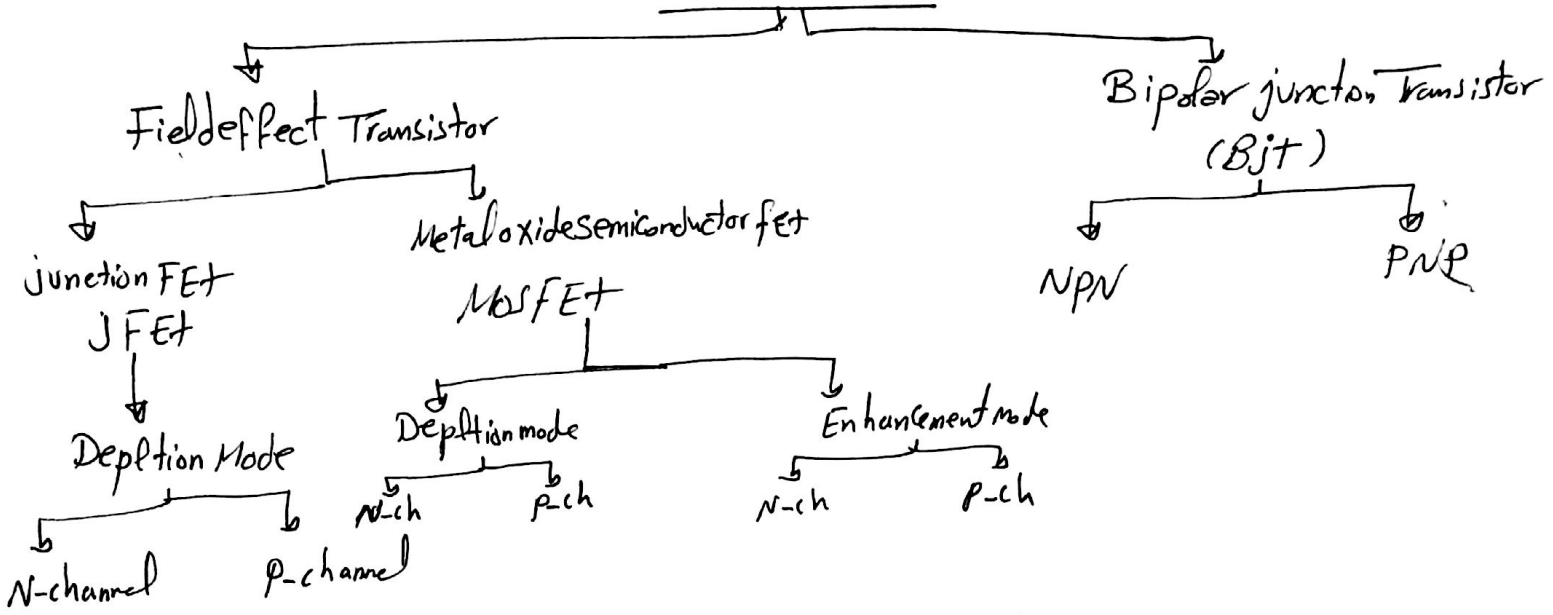


## 1 JFET (Junction Field effect Transistor)

1- N-channel

 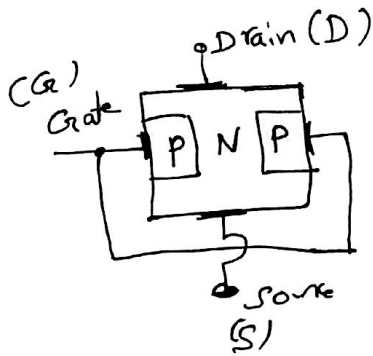

2- P-channel

  


9

- it is a 3 terminals semiconductor devices, The current conduction by one type of carriers (Electrons, holes)

- uses of FET more than BJT. (Nowadays)


Notes (operation of JFET)

 - [1] The voltage between gate and source (gate reverse biased)
- [2] The input circuit (gate-to-source) of JFET is reverse biased ∴ device has high input impedance.
- [3] The drain is so biased with respect to source, so  $I_D$  pass (flow) from source to drain.
- [4] in All JFETs,  $I_S = I_D$



Working

- [1] The two PN junction at the sides form depletion regions. The current conduction by charge carriers (free electrons) flow through the channel between the 2 depletion layers & out of the drain.
- [2] the width of this channel (Resistance) can be controlled by changing the input voltage ( $V_{GS}$ )  
 if  $V_{GS} \uparrow \rightarrow$  depletion region (wider)  $\rightarrow$  conduction channel (narrower)
- [3] JFET operates on principle that width of hence Resistance of conducting channel can be varied by changing  $V_{GS}$

 


OR [ the magnitude of Drain current  $I_D$  changed by  $V_{GS}$  ]

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

(4)
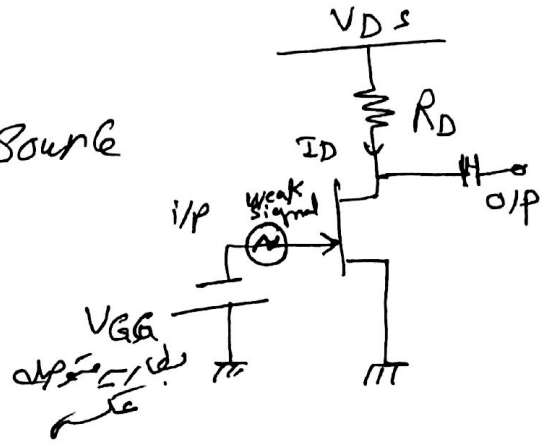
# JFET as amplifier

\* a weak signal applied between gate & source & amplified output obtained in the Drain source circuit.



\*  $V_{GS}$  reverse connected with weak signal

\* A small change in the reverse bias on gate  $\rightarrow$  produce large change in  $I_D$ .


1. \* During <sup>negative</sup> ~~positive~~ half cycle of the signal, the reverse voltage on gate increases &  $I_D$  decreases  $\rightarrow$  The result is small change in voltage at the gate large change in drain current. ( $I_D$ )

2. \* during positive half cycle  $\rightarrow$  The reverse bias on gate decrease this increase channel width & increase drain current.


3. \* Now, large variation of drain current  $\rightarrow$  produce output across load  $R_D \rightarrow$  so FET act as an amplifier
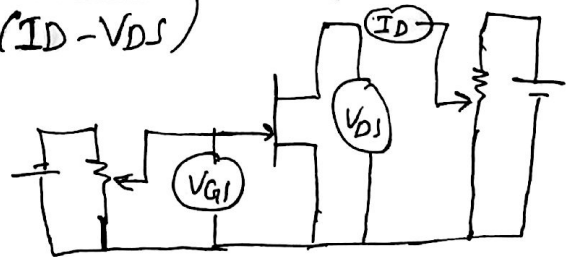
## output characteristics of JFET ( $I_D - V_{DS}$ )

\* Firstly,  $I_D$  increased rapidly with  $V_{DS} \uparrow$  but then become constant. (where  $V_{DS} = V_p$  pinchoff)



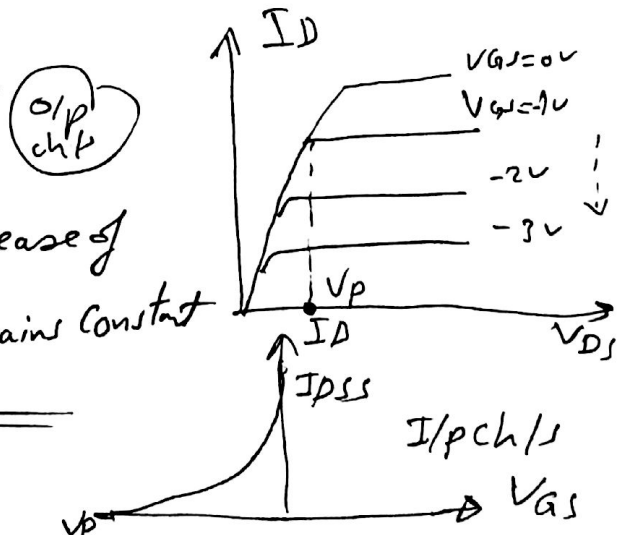\* after  $V_{DS}$  increased than  $V_p$ , the channel width become narrow, depletion region touch each other,  $I_D$  pass through small area between these layers  $\therefore$  The increase of  $I_D$  is very small with ( $V_{DS} > V_p$ )  $\therefore I_D$  remains constant



(JFET)  $\approx$   $\mu$