

Benha University
Faculty Of Engineering at Shoubra



ECE 122
Electrical Circuits (2)(2016/2017)
Lecture (10)
Transient Analysis (P1)

Prepared By :

Dr. Moataz Elsherbini

motaz.ali@feng.bu.edu.eg

Reference Chapter 16

Schaum's Outline Of Theory And Problems Of Electric Circuits
<https://archive.org/details/TheoryAndProblemsOfElectricCircuits>

1st Order R-C

DC

First-Order RC Transient Step-Response

- Assume the switch S is closed at $t = 0$
- Apply KVL to the series RC circuit shown:

$$\frac{1}{C} \int i dt + Ri = V$$

- Differentiating both sides which gives:

$$\frac{i}{C} + R \frac{di}{dt} = 0 \quad \text{or} \quad \left(D + \frac{1}{RC}\right)i = 0$$

- The solution to this homogeneous equation consists of only the complementary function since the particular solution is zero.
- To find the complementary Solution, solve the auxiliary equation:

$$m + \frac{1}{RC} = 0$$

$$m = \frac{-1}{RC} = \frac{-1}{\tau}$$


$$\tau = RC$$

Time constant

The complementary Solution is :

$$i = Ae^{mt}$$

$$i = Ae^{\frac{-t}{\tau}}$$

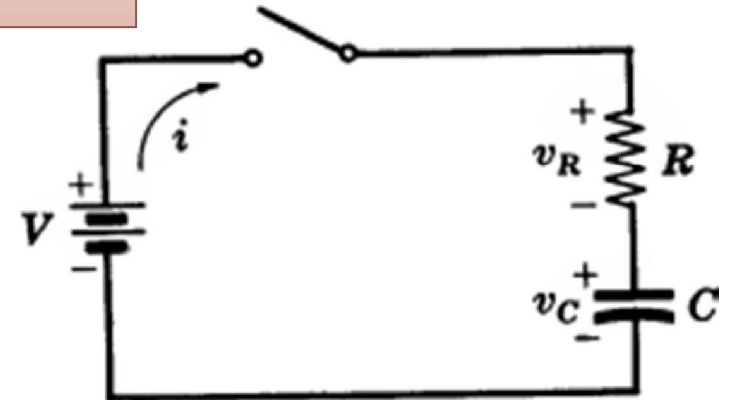

First-Order RC Transient Step-Response

- To determine the constant “A” we note that :



at $t = 0$ is $Ri_0 = V$ or $i_0 = V/R$.

Where $V_c(0) = 0$

- Now substituting the value of i_0 into current equation
- We obtain $A = V/R$ at $t = 0$.

$$i = \frac{V}{R} e^{-t/RC}$$

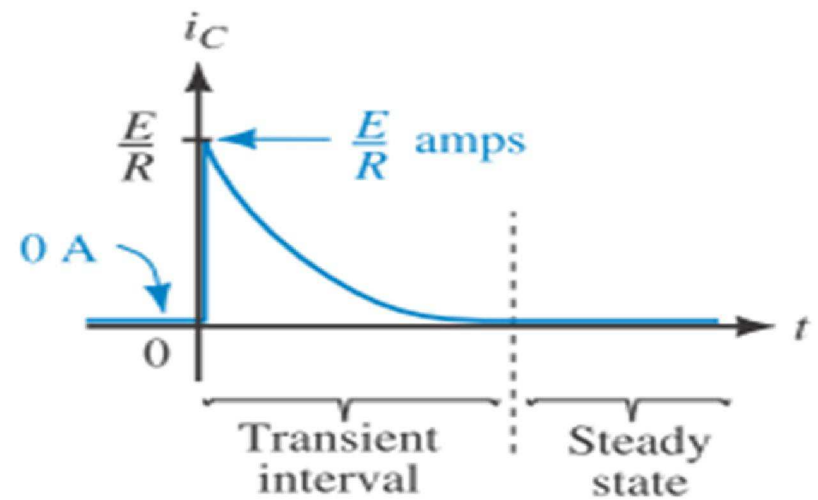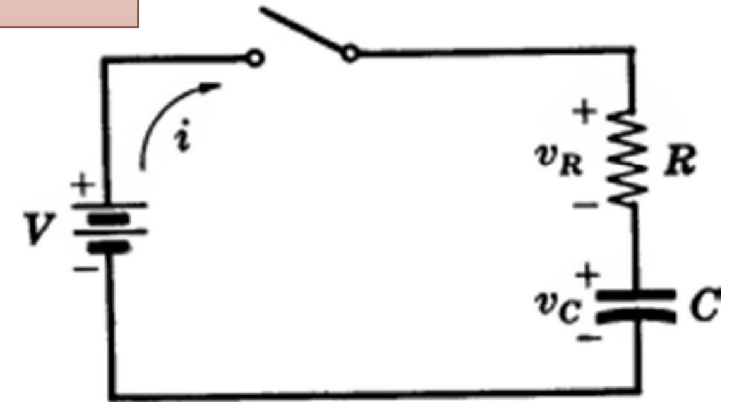has the form of an exponential decay starting from the transient value to the final steady-state value of 0 ampere in 5 time-constants




First-Order RC Transient Step-Response

- The voltage across the resistor is:

$$v_R = Ri = Ve^{-t/RC}$$

- The voltage across the capacitor is:
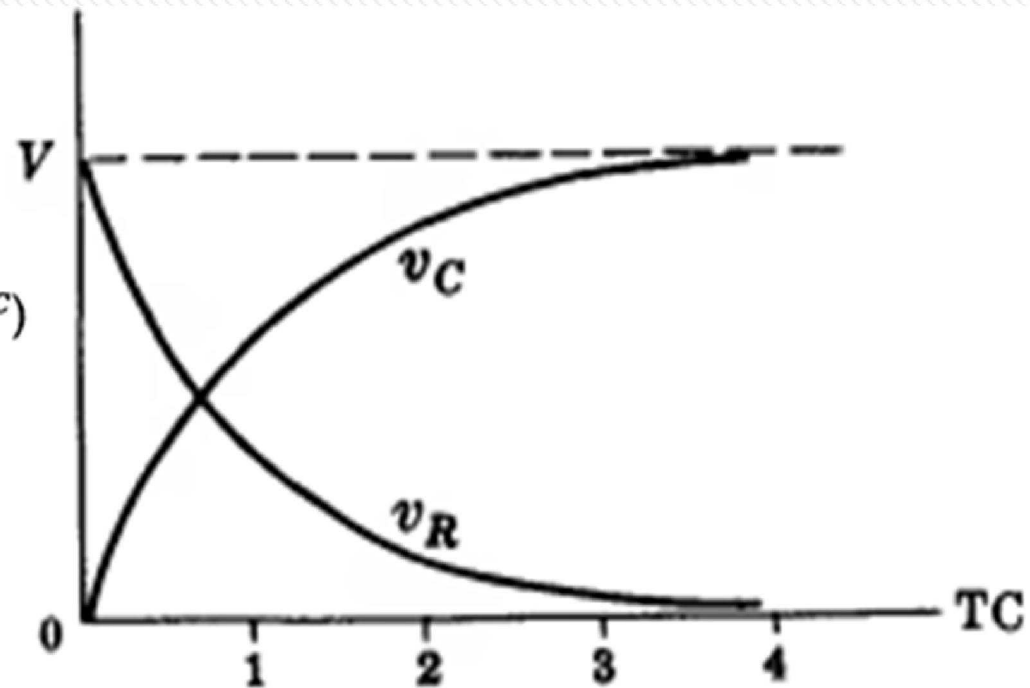
$$v_C = \frac{1}{C} \int i dt = V(1 - e^{-t/RC})$$




Transient-response is almost finished after 5τ , then steady state

1st Order R-C

AC

Alternating Current Transients

RC Sinusoidal Transient

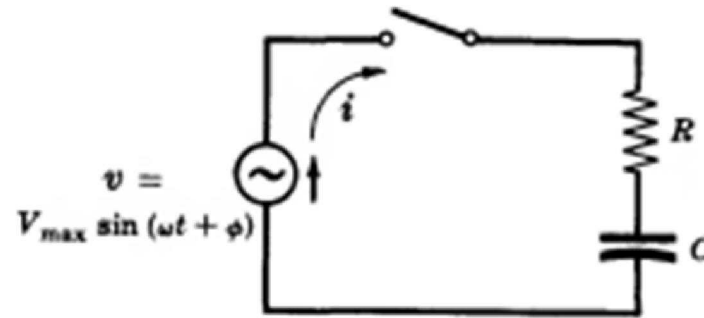

$$Ri + \frac{1}{C} \int i dt = V_{\max} \sin(\omega t + \phi)$$

$$\left(D + \frac{1}{RC}\right)i = \frac{\omega V_{\max}}{R} \cos(\omega t + \phi)$$

$$i_c = ce^{-t/RC}$$

$$i_p = \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\omega t + \phi + \tan^{-1} 1/\omega CR)$$

$$i = ce^{-t/RC} + \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin(\omega t + \phi + \tan^{-1} 1/\omega CR)$$

Alternating Current Transients

RC Sinusoidal Transient

To determine the constant c , let $t = 0$ then the initial current $i_0 = \frac{V_{\max}}{R} \sin \phi$. Substituting this into (63) and setting $t = 0$, we obtain

$$\frac{V_{\max}}{R} \sin \phi = c(1) + \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin (\phi + \tan^{-1} 1/\omega CR)$$

or

$$c = \frac{V_{\max}}{R} \sin \phi - \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin (\phi + \tan^{-1} 1/\omega CR)$$

Substitution of c from (65) into (63) results in the complete current

$$i = e^{-t/RC} \left[\frac{V_{\max}}{R} \sin \phi - \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin (\phi + \tan^{-1} 1/\omega CR) \right] + \frac{V_{\max}}{\sqrt{R^2 + (1/\omega C)^2}} \sin (\omega t + \phi + \tan^{-1} 1/\omega CR)$$

Examples

Example (4-sheet6)

A series RC circuit with $R = 5000$ ohms and $C = 20 \mu\text{f}$ has a constant voltage $V = 100$ v applied at $t = 0$ and the capacitor has no initial charge. Find the equations of i , V_R and V_C .

closed

Sol.

$$100 = i(5000) + \frac{1}{C} \int i dt \rightarrow \boxed{1} \quad 100 \text{ V}$$


$$100 = 5000i + \frac{1}{20 \times 10^{-6}} \int i dt$$

$$100 = 5000i + 50000 \int i dt$$

نفاضل الطرفين للتخلص من التكامل

$$0 = 5000 \frac{di}{dt} + 50000 i$$

$$0 = (5000 D + 50000) i$$

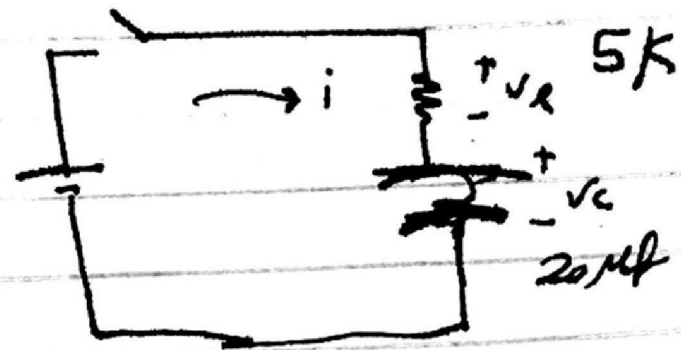

Example (4-sheet6)

$$(D+10) i = 0$$

it has only one solution (P.I)

$$\begin{aligned} m+10 &= 0 \\ m &= -10 \end{aligned}$$

$$i = A e^{mt} \Rightarrow A e^{-10t}$$

at $t=0 \rightarrow$ sub in 1 $\therefore 100 = 5000 i$ or $i = 100/5000$

$$i = 0.02 \text{ A}$$

$$i = 0.02 e^{-10t}$$

$$V_R = R i = 5000 \times 0.02 e^{-10t} = 100 e^{-10t}$$

$$\begin{aligned} V_C &= V - V_R \\ &= 100 - 100 e^{-10t} \end{aligned}$$

Example (8-sheet 7)

A series RC circuit with $R = 100$ ohms and $C = 25 \mu\text{f}$ has a sinusoidal voltage source $v = 250 \sin(500t + \phi)$ applied at a time when $\phi = 0^\circ$. Find the current, assuming there is no initial charge on the capacitor.

Sol.

$$100i + \frac{1}{C} \int i dt = 250 \sin 500t$$

مع تقاطع

$$i = 1.250 e^{-400t} + 1.955 \sin(500t + 38.7^\circ)$$

Sol

$$i = C e^{-400t} + \frac{V_{\text{max}}}{\sqrt{R^2 + (\frac{1}{\omega C})^2}} \sin(\omega t + \phi + \tan^{-1}(\frac{1}{\omega RC}))$$

$$i = C e^{-400t} + 1.955 \sin(500t + 38.7^\circ)$$

at $t=0 \rightarrow i = \frac{250}{100} \sin 0 = 2.5$

initial current


$$2.5 = C e^{-400 \times 0} + 1.955 \sin(0 + 38.7)$$

$$\therefore C = -1.22$$

$$i = -1.22 e^{-400t} + 1.955 \sin(500t + 38.7^\circ)$$

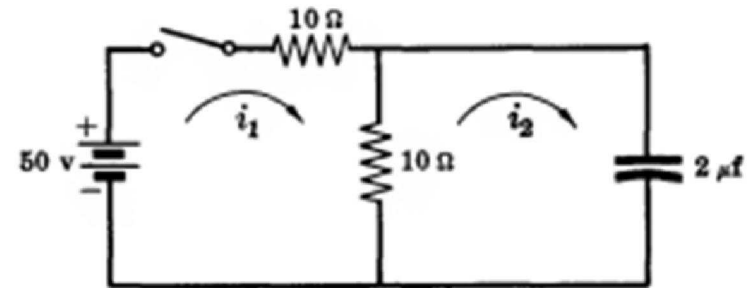Example (6-sheet 7)

In the two-mesh network shown in Fig.4 the switch is closed at $t = 0$. Find the transient mesh currents i_1 and i_2 shown in the diagram, and the transient capacitor voltage V_c .



$$\text{Loop 1} \quad 50 = 20i_1 - 10i_2$$

$$\therefore 0 = 20Di_1 - 10Di_2$$

$$\text{or } \boxed{2Di_1 = Di_2}$$

تفاضل الزمن

$$\text{Loop 2} \quad 0 = 10i_2 - 10i_1 + \frac{1}{C} \int i_2 dt$$

تفاضل الزمن

$$0 = 10Di_2 - 10Di_1 + \frac{1}{C} i_2$$

$$\text{or } -Di_1 + i_2 \left(D + \frac{1}{10C} \right) = 0$$

$\hookrightarrow 2 \times 10^{-6}$

$$\boxed{-Di_1 + i_2 (D + 5 \times 10^4)} = 0 \quad \textcircled{2}$$

Example (6-sheet 7)

المقدار المطلوب (1) (2)

$$\therefore -\frac{Di_2}{2} + (Dt + 5 \times 10^4)i_2 = 0$$

$$\text{or } (D + 10^5)i_2 = 0$$

$$\therefore \text{sol } i_2 = A e^{mt} = A e^{-10^5 t}$$

at $t=0 \rightarrow$ From eq 2 $\therefore 0 = 10i_2 - 10i_1$

$$\therefore i_1 = i_2$$

From (1) $50 = \frac{20i_1 - 10i_2}{2} = 10i_2 = 10i_1$ المقدار المطلوب

$$\therefore i_1 = i_2 = 5$$

at $t=0 \quad i_2 = 5 = A e^0 \quad \therefore A = 5$

$$i_2 = 5 e^{-10^5 t}$$

$$50 = 20i_1 - 10 \times 5 e^{-10^5 t}$$

المقدار المطلوب

$$i_1 = \frac{5}{2} + \frac{5}{2} e^{-10^5 t}$$

$$V_c = \frac{1}{C} \int i_2 dt$$

$$V_c = 25(1 - e^{-10^5 t})$$

Example (5-sheet 7)

In the RC circuit of Fig. 3 the switch is closed on position 1 at $t=0$ and after 1 TC is moved to position 2. Find the complete current transient.

at Position 1

$$20 = 500 i + \frac{1}{C} \int i dt$$

بقانون كيرشوف:


$$0 = 500 \frac{di}{dt} + \frac{1}{0.5 \times 10^{-6}} i$$

$$0 = 500 D i + 2000000 i$$

$$0 = D i + 4000 i$$

$$i_1 = A e^{-4000 t_1}$$

$$i (D + 4000) = 0$$

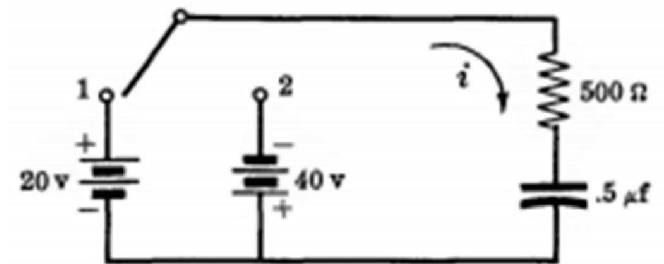

Example (5-sheet 7)

at $t=0 \rightarrow i = 20/500 = 0.04 = A$

$i_1 = 0.04 e^{-4000t}$

$250 \mu\text{sec} = (1RC) = 1TC$ ← *سنة لهذا التاربط*

after $1TC = 1RC = 250 \mu\text{sec}$


$i = 0.04 \times e^{-4000 \times 250 \mu} = 0.0147 A$

Now switch moved to \approx

$-40 = 500 \frac{di}{dt} + \frac{1}{0.1 \times 10^{-6}} i$

$0 = 500 \frac{di}{dt} + \frac{1}{0.1 \times 10^{-6}} i$

$i_2 = B e^{-4000(t-t_1)}$ ~~instant~~

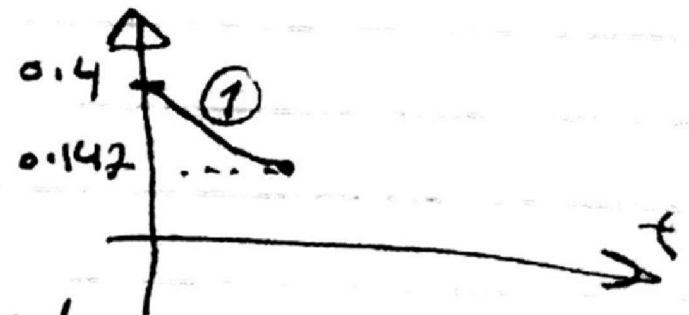

Example (5-sheet 7)

$$V_c = 20 \left(1 - e^{-\frac{4000 t}{RC}} \right) = 20 \left(1 - e^{-4000 \times (RC)} \right)$$
 250×10^{-6}
 where $RC = \text{time constant}$

$$= 20(1 - e^{-1}) = 12.65 \text{ Volt}$$

$$i_2 = B e^{-4000(t-t_1)}$$

لاضافة اتيان قطبي C
 مع اتيان قطبي B = 40V

at $t = t_1 \Rightarrow i = \frac{V_{total}}{R}$

$$i = \frac{40 + 12.65}{500} = 0.1053 \text{ A}$$

لا اتيان ب عنده ~~لا اتيان ب~~ ليبارك عكسه
 اتيان i بترسيم


$$i_2 = -0.1053 e^{-4000(t-t_1)}$$

Example (5-sheet 7)

لا صفا انزعنا سائر القساع ل \geq لا زال كالتف
 عند $t = t_1 = 250 \mu\text{s}$

$$\int i dt = v_c \quad \text{وهو } \int \frac{0.04}{0.5 \times 10^{-6}} e^{-4000t} + K = \int i dt = v_c$$

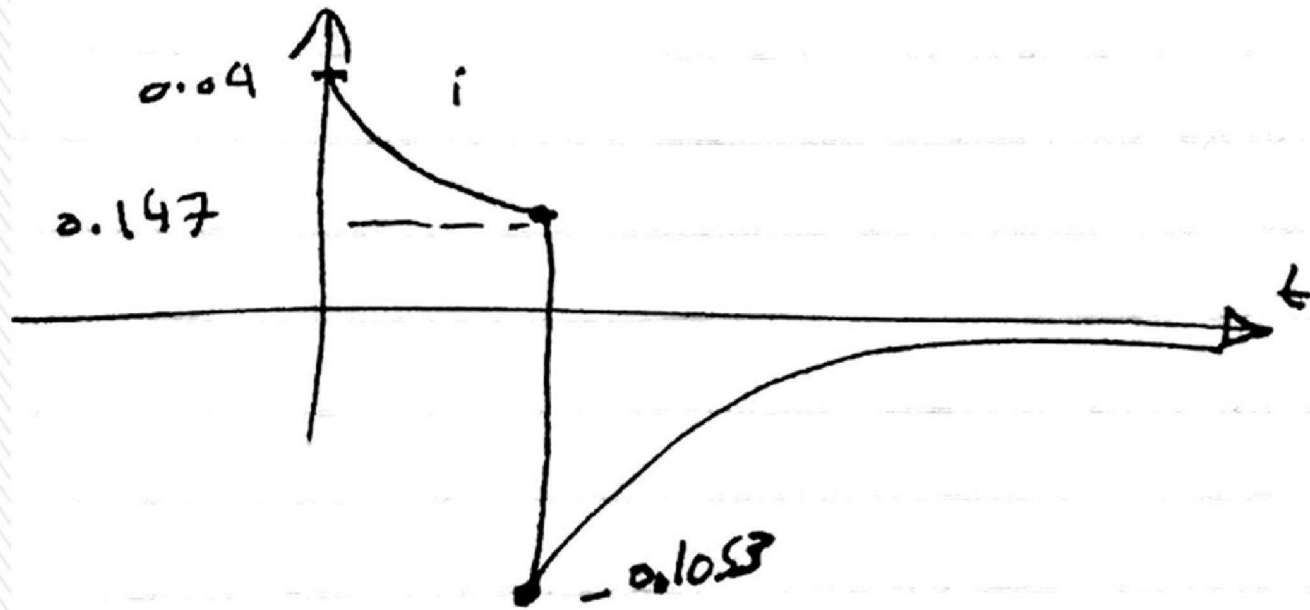عند $t=0$ $K = +20$ ($v_c = 0$)
 $\therefore v_c = 20(1 - e^{-4000t}) \rightarrow \tau = RC = 1 \tau_c$



Thank You

