

Benha University
Faculty Of Engineering at Shoubra



ECE 122
Electrical Circuits (2)(2016/2017)
Lecture (3)
Parallel Resonance

Prepared By :

Dr. Moataz Elsherbini

motaz.ali@feng.bu.edu.eg

Remember

Series Resonance

$$\boxed{1} \quad \omega_0 = \frac{1}{\sqrt{LC}} \quad , \quad f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$\boxed{2} \quad Z = R + j\left(\omega L - \frac{1}{\omega C}\right) \rightarrow \text{total series Res.}$$

$Z = R$ (at resonance).

$$\boxed{3} \quad BW = \omega_2 - \omega_1 = \frac{R}{L} = \frac{\omega_0}{Q}$$

$$\boxed{4} \quad \left. \begin{aligned} \omega_{1, \text{actual}} &= \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \cong \omega_0 - B/2 \\ \omega_{2, \text{actual}} &= \frac{+R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \cong \omega_0 + B/2 \end{aligned} \right\} \begin{array}{l} \text{at} \\ Z = \sqrt{2}R \\ \begin{array}{l} \rightarrow \text{from half power} \\ \rightarrow \text{from half power} \end{array} \end{array}$$

$$\boxed{5} \quad \omega_0 = \sqrt{\omega_1 \omega_2}$$

$$\boxed{6} \quad Q = \frac{\omega_0 L}{R} = \frac{1}{\omega_0 RC}$$

Parallel Resonance Circuit

It is usually called tank circuit

Ideal Circuits

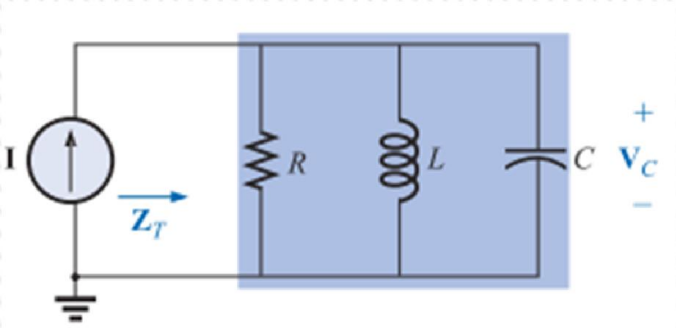


FIG. 20.21

Ideal parallel resonant network.

Practical Circuits


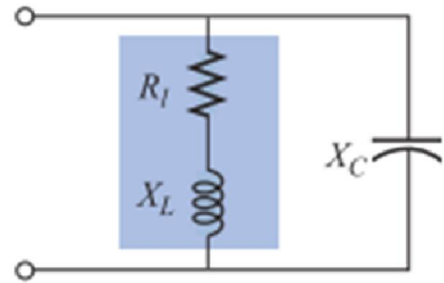


FIG. 20.22

Practical parallel L-C network.

Complex Configuration

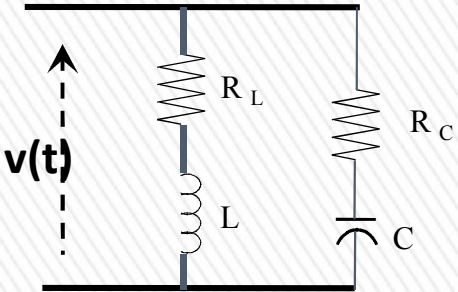

Ideal Parallel Resonance Circuit


The total admittance

$$Y = Y_1 + Y_2 + Y_3$$

$$Y = \frac{1}{R} + \frac{1}{(j\omega L)} + \frac{1}{(-j/\omega C)}$$

$$Y = \frac{1}{R} + \frac{-j}{\omega L} + j\omega C$$
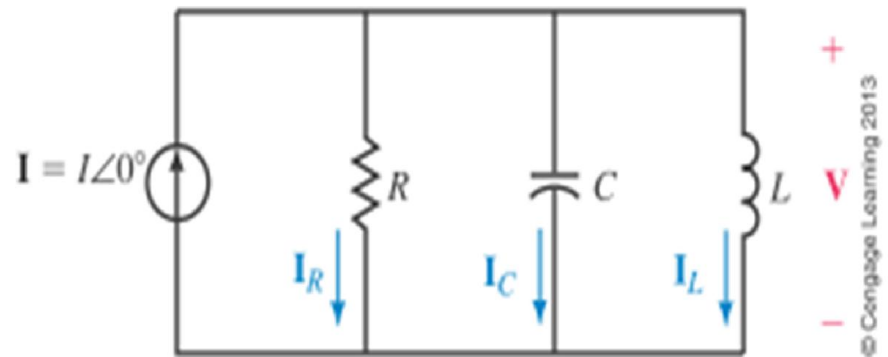
$$Y = \frac{1}{R} + j(\omega C - 1/\omega L)$$



Condition for Ideal Parallel Resonance

Resonance occurs when the imaginary part of Y is zero

$$\omega C - \frac{1}{\omega L} = 0$$

$$X_C = X_L$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$$


Ideal Parallel Resonance Circuit

At parallel resonance:


- ✓ At resonance, the admittance consists only conductance $G = 1/R$.
- ✓ The value of current will be minimum since the total admittance is minimum.
- ✓ The voltage and current are in phase (Power factor is unity).
- ✓ The inductor reactance and capacitor reactance canceled, resulting in a circuit voltage simply determined by Ohm's law as:

$$V = IR = IR \angle 0^\circ$$

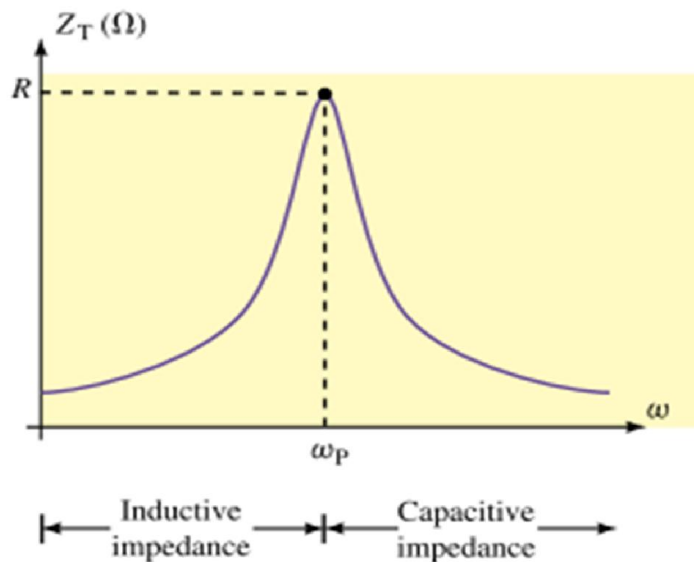- ✓ The frequency response of the impedance of the parallel circuit is shown



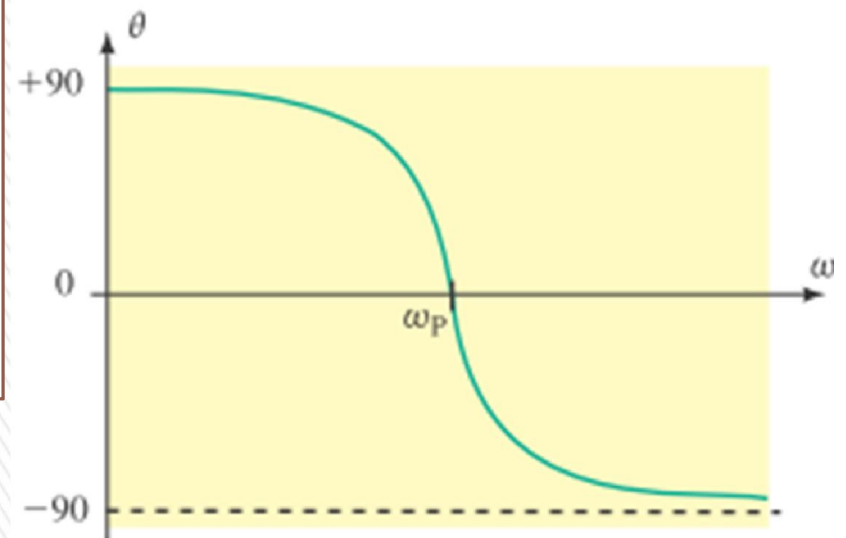exactly
opposite to
that in
series
resonant
circuits,



Ideal Parallel Resonance Circuit

The Q of the parallel circuit is determined from the definition as

$$Q_P = \frac{\text{reactive power}}{\text{average power}} \\ = \frac{V^2/X_L}{V^2/R}$$

$$Q_P = \frac{R}{X_{LP}} = \frac{R}{X_C}$$

Reciprocal of series case

The current

$$I_R = \frac{V}{R} = I$$

$$I_L = \frac{V}{X_L \angle 90^\circ} \\ = \frac{V}{R/Q_P} \angle -90^\circ \\ = Q_P I \angle -90^\circ$$

$$I_C = \frac{V}{X_C \angle -90^\circ} \\ = \frac{V}{R/Q_P} \angle 90^\circ \\ = Q_P I \angle 90^\circ$$

- ✓ The currents through the inductor and the capacitor have the same magnitudes but are 180 out of phase.
- ✓ Notice that the magnitude of current in the reactive elements at resonance is Q times greater than the applied source current.

Ideal Parallel Resonance Circuit

➤ Parallel resonant circuit has same parameters as the series resonant circuit.

Resonance frequency:

$$\omega_p = \frac{1}{\sqrt{LC}} \text{ rad/s}$$

Half-power frequencies:

$$\omega_1 = -\frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

$$\omega_2 = \frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ (rad/s)}$$

Bandwidth and Q-factor:

$$BW = \omega_2 - \omega_1 = \frac{1}{RC} \text{ (rad/s)}$$


$$BW = \frac{\omega_p}{Q_p} \text{ (rad/s)}$$

$$BW = \frac{\omega_p}{R(\omega_p C)} = \frac{X_C}{R} \omega_p$$

$$Q = \frac{\omega_0}{B} = \omega_0 RC = \frac{R}{\omega_0 L}$$

ملخص قوانين المحاضرة


↓
Ideal circuit

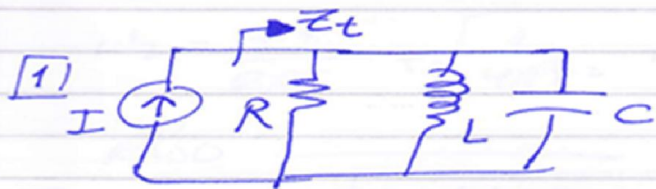

[2] $X_L = X_C$ at Resonance
 $\omega_p = \frac{1}{\sqrt{LC}}$ rad/s

[3] $Y = \frac{1}{Z} = Y_1 + Y_2 + Y_3$
 $= \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$

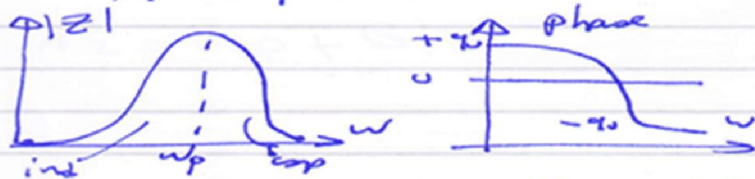[4] at Resonance $G = \frac{1}{R}$
 ω, V, I in phase. \leftarrow admittance



[5] $Q_p = \frac{R}{X_C} = \frac{R}{X_L} = \frac{\omega_p R}{1} = \frac{\omega_p R}{1}$
 $= R/\omega L = \omega R C$

[6] $BW = \omega_2 - \omega_1 = \frac{1}{RC}$ rad/s
 $= \omega_p / Q_p$

[7] $\omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$

$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$ rad/s

Note For Midband


$\omega_1 = \omega_p - BW/2$

$\omega_2 = \omega_p + BW/2$

Example

Example

Consider the circuit shown in Figure

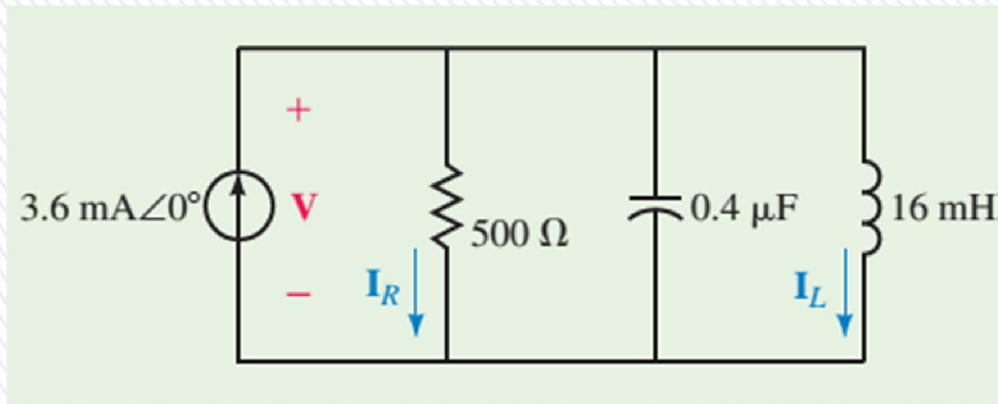

- Determine the resonant frequencies, ω_p (rad/s) and f_p (Hz) of the tank circuit.
- Find the Q of the circuit at resonance.
- Calculate the voltage across the circuit at resonance.
- Solve for currents through the inductor and the resistor at resonance.
- Determine the bandwidth of the circuit in both radians per second and hertz.
- Sketch the voltage response of the circuit, showing the voltage at the half-power frequencies.
- Sketch the selectivity curve of the circuit showing P (watts) versus ω (rad/s).

Solution

a.
$$\omega_p = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(16 \text{ mH})(0.4 \text{ }\mu\text{F})}} = 12.5 \text{ krad/s}$$

$$f_p = \frac{\omega}{2\pi} = \frac{12.5 \text{ krad/s}}{2\pi} = 1989 \text{ Hz}$$

b.
$$Q_p = \frac{R_p}{\omega L} = \frac{500 \text{ }\Omega}{(12.5 \text{ krad/s})(16 \text{ mH})} = \frac{500 \text{ }\Omega}{200 \text{ }\Omega} = 2.5$$

c. At resonance, $V_C = V_L = V_R$, and so

$$\mathbf{V} = \mathbf{IR} = (3.6 \text{ mA}\angle 0^\circ)(500 \text{ }\Omega\angle 0^\circ) = 1.8 \text{ V}\angle 0^\circ$$

d.
$$\mathbf{I}_L = \frac{\mathbf{V}_L}{\mathbf{Z}_L} = \frac{1.8 \text{ V}\angle 0^\circ}{200 \text{ }\Omega\angle 90^\circ} = 9.0 \text{ mA}\angle -90^\circ$$

$$\mathbf{I}_R = \mathbf{I} = 3.6 \text{ mA}\angle 0^\circ$$

e.
$$\text{BW(rad/s)} = \frac{\omega_p}{Q_p} = \frac{12.5 \text{ krad/s}}{2.5} = 5 \text{ krad/s}$$

$$\text{BW(Hz)} = \frac{\text{BW(rad/s)}}{2\pi} = \frac{5 \text{ krad/s}}{2\pi} = 795.8 \text{ Hz}$$

f. The half-power frequencies are calculated from Equations 21-48 and 21-49 since the Q of the circuit is less than 10.

$$\begin{aligned}\omega_1 &= -\frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \\ &= -\frac{1}{0.0004} + \sqrt{\frac{1}{1.6 \times 10^{-7}} + \frac{1}{6.4 \times 10^{-9}}} \\ &= -2500 + 12\,748 \\ &= 10\,248 \text{ rad/s}\end{aligned}$$

Solution

$$\begin{aligned}\omega_2 &= \frac{1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \\ &= \frac{1}{0.0004} + \sqrt{\frac{1}{1.6 \times 10^{-7}} + \frac{1}{6.4 \times 10^{-9}}} \\ &= 2500 + 12\,748 \\ &= 15\,248 \text{ rad/s}\end{aligned}$$

The resulting voltage response curve is illustrated in Figure 21–32.

g. The power dissipated by the circuit at resonance is

$$P = \frac{V^2}{R} = \frac{(1.8 \text{ V})^2}{500 \Omega} = 6.48 \text{ mW}$$

The selectivity curve is now easily sketched as shown in Figure 21–33.

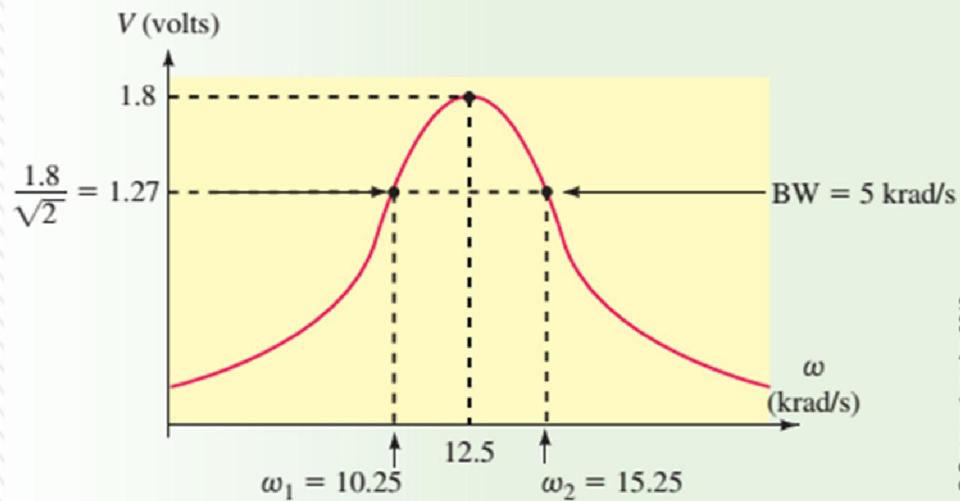


FIGURE 21–32

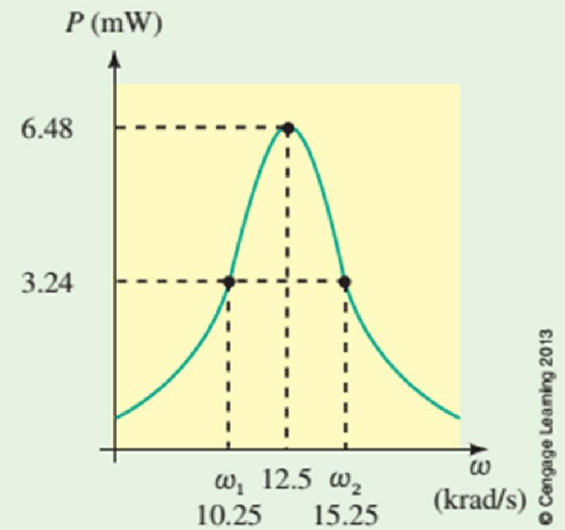


FIGURE 21–33

Thank You

