

**Benha University**  
**Faculty Of Engineering at Shoubra**



**ECE 122**  
**Electrical Circuits (2)(2016/2017)**  
**Lecture (4)**  
**Parallel Resonance (P.2)**

**Prepared By :**

**Dr. Moataz Elsherbini**

[motaz.ali@feng.bu.edu.eg](mailto:motaz.ali@feng.bu.edu.eg)

**Remember**

# Parallel Resonance Circuit

It is usually called tank circuit

## Ideal Circuits

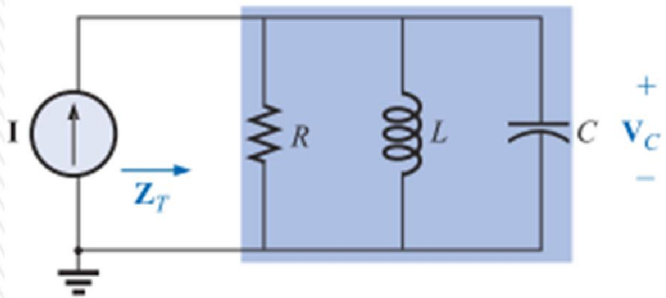


FIG. 20.21

*Ideal parallel resonant network.*

## Practical Circuits


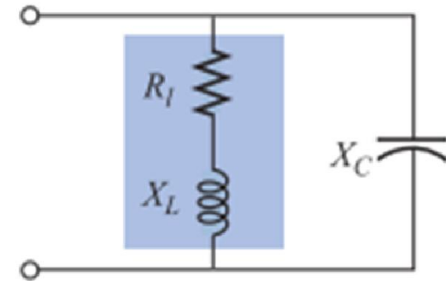


FIG. 20.22

*Practical parallel L-C network.*


## Complex Configuration

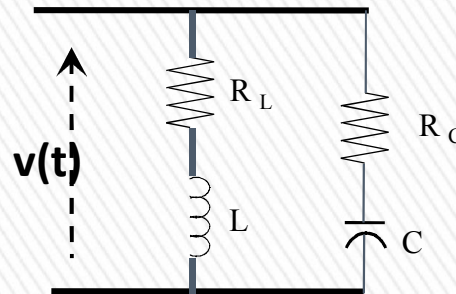

# Practical Parallel Resonance Circuit

## Effect of Winding Resistance on the Parallel Resonant Frequency


- The internal resistance of the coil must be taken into consideration because it is no longer be included in a simple series or parallel combination with the source resistance and any other resistance added for design purposes.
- Even though  $R_L$  is usually relatively small in magnitude compared with other resistance and reactance levels of the network, it does have an important impact on the parallel resonant condition,

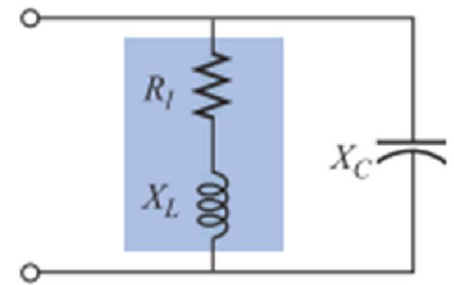

**FIG. 20.22**

*Practical parallel L-C network.*

1. Find a parallel network equivalent to the series R-L branch

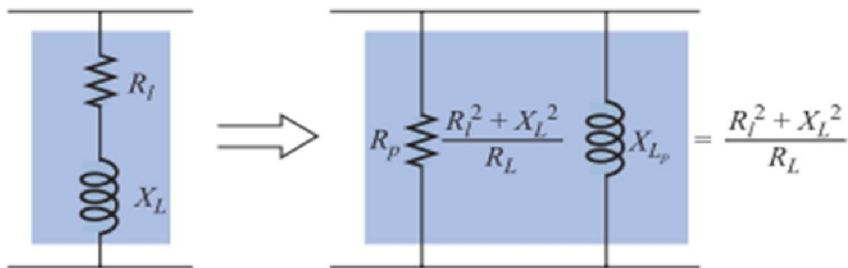

**FIG. 20.23**

*Equivalent parallel network for a series R-L combination.*

$$\mathbf{Z}_{R-L} = R_i + jX_L$$

$$\mathbf{Y}_{R-L} = \frac{1}{\mathbf{Z}_{R-L}} = \frac{1}{R_i + jX_L} = \frac{R_i}{R_i^2 + X_L^2} - j \frac{X_L}{R_i^2 + X_L^2}$$


# Practical Parallel Resonance Circuit

$$\mathbf{Y}_{R-L} = \frac{1}{\frac{R_i^2 + X_L^2}{R_i}} + \frac{1}{j\left(\frac{R_i^2 + X_L^2}{X_L}\right)} = \frac{1}{R_p} + \frac{1}{jX_{Lp}}$$

$$R_p = \frac{R_i^2 + X_L^2}{R_i}$$


$$X_{Lp} = \frac{R_i^2 + X_L^2}{X_L}$$

Redrawing the network

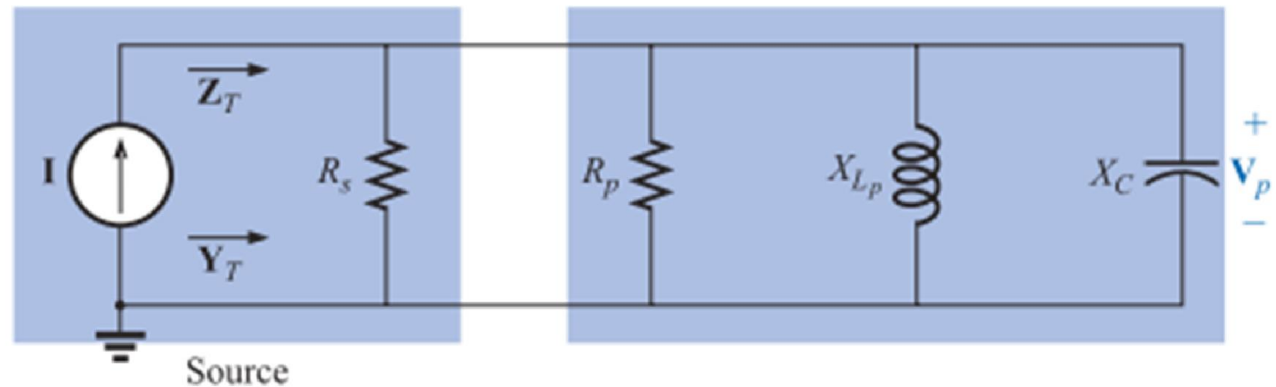

If we define the parallel combination of  $R_s$  and  $R_p$  by the notation

$$R = R_s \parallel R_p$$

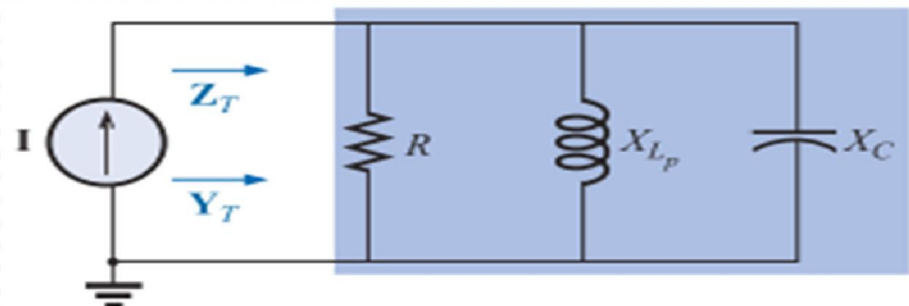

# Practical Parallel Resonance Circuit

$$Y_T = \frac{1}{R} + j\left(\frac{1}{X_C} - \frac{1}{X_{L_p}}\right)$$

$$\frac{1}{X_C} - \frac{1}{X_{L_p}} = 0$$

$$\frac{1}{X_C} = \frac{1}{X_{L_p}}$$

$$X_{L_p} = X_C$$

$$\frac{R_i^2 + X_L^2}{X_L} = X_C$$

The resonant frequency,  $f_p$ , can now be determined as follows:

$$R_i^2 + X_L^2 = X_C X_L = \left(\frac{1}{\omega C}\right)\omega L = \frac{L}{C}$$

$$X_L^2 = \frac{L}{C} - R_i^2$$

$$2\pi f_p L = \sqrt{\frac{L}{C} - R_i^2}$$

$$f_p = \frac{1}{2\pi L} \sqrt{\frac{L}{C} - R_i^2}$$

Multiplying within the square-root sign by  $C/L$  and rearranging produces :

$$f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_i^2 C}{L}}$$

$$f_p = f_s \sqrt{1 - \frac{R_i^2 C}{L}}$$

# Practical Parallel Resonance Circuit

## 1. Maximum impedance

➤ At  $f = f_p$  the input impedance of a parallel resonant circuit will be near its maximum value but not quite its maximum value due to the frequency dependence of  $R_p$ .

➤ The frequency at which maximum impedance will occur is:

$$f_m = f_s \sqrt{1 - \frac{1}{4} \left( \frac{R_s^2 C}{L} \right)}$$

$f_m$  is determined by differentiating the general equation for  $Z_T$  with respect to frequency

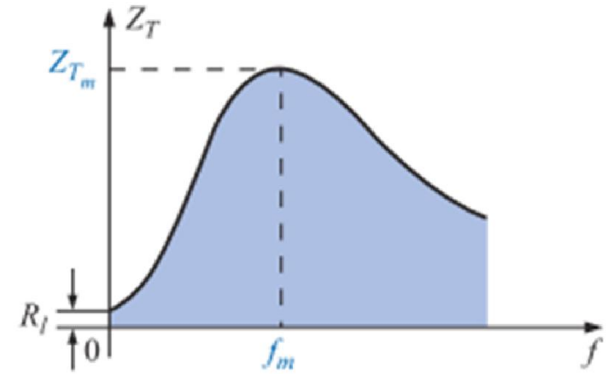


FIG. 20.26

$Z_T$  versus frequency for the parallel resonant circuit.

## 2. Minimum impedance

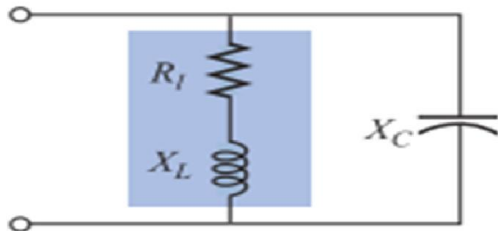


FIG. 20.22

Practical parallel L-C network.

At  $f = 0$  Hz,

$X_C$  is O.C,  $X_L = \text{zero}$

$$Z_T = R_s \parallel R_l \cong R_l.$$

As  $R_s$  is sufficiently large for the current source (ideally infinity)

# Practical Parallel Resonance Circuit


➤ The quality factor of the practical parallel resonant circuit

determined by the ratio of the reactive power to the real power at resonance

$$Q_p = \frac{V_p^2 / X_{L_p}}{V_p^2 / R}$$

$$R = R_s \parallel R_p$$

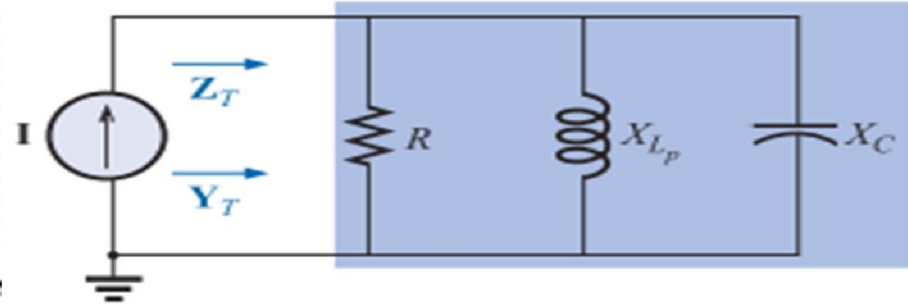$V_p$  is the voltage across the parallel branches.



$$Q_p = \frac{R}{X_{L_p}} = \frac{R_s \parallel R_p}{X_{L_p}}$$

$$Q_p = \frac{R_s \parallel R_p}{X_C}$$

For the ideal current source ( $R_s = \infty \Omega$ )

$$R = R_s \parallel R_p \cong R_p$$

$$Q_p = \frac{R_s \parallel R_p}{X_{L_p}} = \frac{R_p}{X_{L_p}} = \frac{(R_l^2 + X_L^2) / R_l}{(R_l^2 + X_L^2) / X_L}$$

$$Q_p = \frac{X_L}{R_l} = Q_l$$

$$R_s \gg R_p$$


which is simply the quality factor  $Q_l$  of the coil.



# Practical Parallel Resonance Circuit

➤ Bandwidth and Half-Power point ➤

$$BW = f_2 - f_1 = \frac{f_r}{Q_p}$$

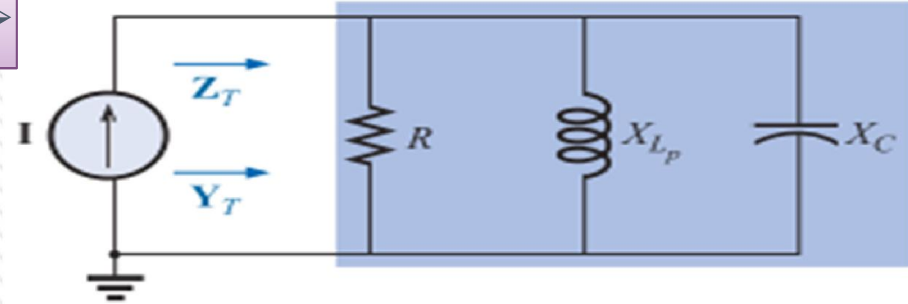

➤ The cutoff frequencies  $f_1$  and  $f_2$  can be determined using the equivalent network shown in the figure:

$$\mathbf{Z} = \frac{1}{\frac{1}{R} + j\left(\omega C - \frac{1}{\omega L}\right)} = 0.707R$$

$$f_1 = \frac{1}{4\pi C} \left[ \frac{1}{R} - \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$


$$f_2 = \frac{1}{4\pi C} \left[ \frac{1}{R} + \sqrt{\frac{1}{R^2} + \frac{4C}{L}} \right]$$

# قوانين المحاضرة

①

# Parallel Resonance


Ideal circuit

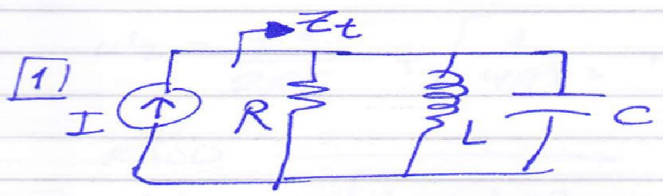

②  $X_L = X_C$  at Resonance  
 $\therefore \omega_p = \frac{1}{\sqrt{LC}}$  rad/s

③  $Y = \frac{1}{Z} = Y_1 + Y_2 + Y_3$   
 $= \frac{1}{R} + j(\omega C - \frac{1}{\omega L})$

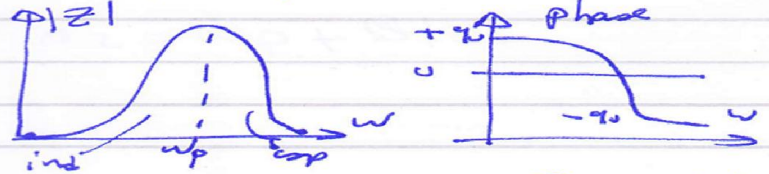
④ at Resonance  $G = \frac{1}{R}$   
 $\rightarrow$  admittance  
 $\rightarrow V, I$  in phase.



⑤  $Q_p = \frac{R}{X_C} = \frac{R}{X_L} = \frac{\omega_p R}{1} = \frac{\omega_p R}{1}$   
 $= R/\omega L = \omega R C$

⑥  $BW = \omega_2 - \omega_1 = \frac{1}{RC}$  rad/s  
 $= \omega_p / Q_p$

Practical circuit

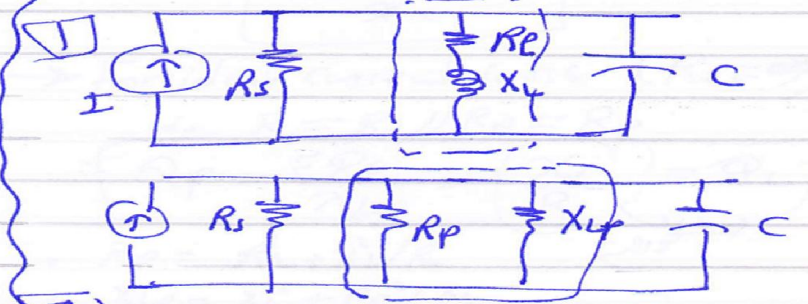

①  $Z = R_s + jX_L \rightarrow Y = \frac{1}{Z} = \frac{1}{R_s + jX_L} = \frac{R_s - jX_L}{R_s^2 + X_L^2}$   
 $R_p = \frac{R_s^2 + X_L^2}{R_s} \rightarrow X_{Lp} = \frac{R_s X_L}{X_L^2}$

②  $R = R_s \parallel R_p$   
 $Y_t = \frac{1}{R} + j(\frac{1}{X_C} - \frac{1}{X_{Lp}})$

③ at Resonance  $\frac{1}{X_C} = \frac{1}{X_{Lp}}$   
 $\therefore f_p = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{R_s^2 C}{L}}$   
 $\rightarrow f_0 = f_s$

④ max impedance freq  $f_m \rightarrow \frac{dZ_t}{df} = 0$

$f_m = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \frac{1}{4} \frac{R_s^2 C}{L}}$

\* Max impedance at  $f = 0$  Hz

$X_L = \infty, X_C = 0$   
 $\therefore Z_t = R_s \parallel R_p = R_e$

$$\boxed{7} \omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ rad/s}$$

$$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}} \text{ rad/s}$$

Also

$$\boxed{8} \omega_1 = \omega_p \sqrt{1 + \left(\frac{1}{2a}\right)^2} - \omega_0/2Q$$

$$\omega_2 = \omega_p \sqrt{1 + \left(\frac{1}{2a}\right)^2} + \omega_0/2Q$$

Note for Midband

$$\omega_1 = \omega_p - B/2$$

$$\omega_2 = \omega_p + B/2$$

$$\boxed{6} Q_p = \frac{R}{X_{Lp}} = \frac{R_s // R_p}{X_{Lp}}$$

$$= \frac{R_s // R_p}{X_L}$$

→ For ideal current source ( $R_s \rightarrow \infty$ )

$$\therefore R = R_s // R_p = R_p$$

$$\therefore Q_p = \frac{R_p}{X_{Lp}} = \left(\frac{X_L}{R_L}\right) = Q_L$$

$$\rightarrow R_p = R_L^2 + X_L^2 / R_L$$

$$\rightarrow X_{Lp} = X_L^2 + R_p^2 / X_L$$

$$\boxed{7} BW = f_r / Q_p = f_r - f_l$$

$$= \omega_p / aQ = \frac{1}{RC} \text{ rad/s}$$

$$\omega_1 = \frac{-1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$

$$\omega_2 = \frac{+1}{2RC} + \sqrt{\frac{1}{4R^2C^2} + \frac{1}{LC}}$$


$$\boxed{8} Z = \frac{1}{\sqrt{2}} R = \frac{1}{\frac{1}{R} + j(\omega C - \frac{1}{\omega L})}$$

# Examples
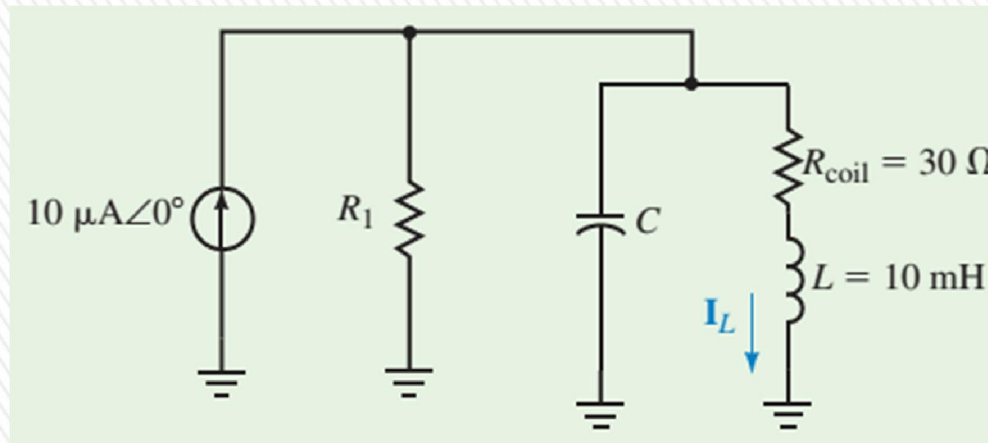
## Example (1)

Determine the values of  $R_1$  and  $C$  for the resonant tank circuit of the Figure so that the given conditions are met.

$L=10\text{ mH}$ ,  $R_{\text{coil}}=30\Omega$ ,  $f_p=58\text{ kHz}$ ,  $BW=1\text{ kHz}$ , Solve for the current,  $I_L$ , through the inductor.



$$Q_P = \frac{f_P}{\text{BW(Hz)}} = \frac{58 \text{ kHz}}{1 \text{ kHz}} = 58$$


$$\omega_P = 2\pi f_P = (2\pi)(58 \text{ kHz}) = 364.4 \text{ krad/s}$$

$$C = \frac{1}{\omega_P^2 L} = \frac{1}{(364.4 \text{ krad/s})^2 (10 \text{ mH})} = 753 \text{ pF}$$

$$\begin{aligned} Q_{\text{coil}} &= \frac{\omega_P L}{R_{\text{coil}}} \\ &= \frac{(364.4 \text{ krad/s})(10 \text{ mH})}{30 \Omega} \\ &= \frac{3.644 \text{ k}\Omega}{30 \Omega} = 121.5 \end{aligned}$$

$$R_P \cong Q_{\text{coil}}^2 R_{\text{coil}} = (121.5)^2 (30 \Omega) = 443 \text{ k}\Omega$$

$$X_{LP} \cong X_L = 3644 \Omega$$

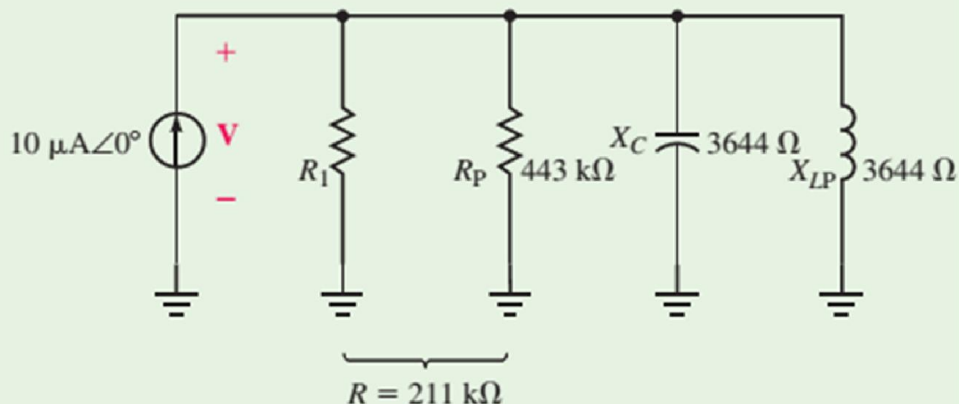

The quality factor  $Q_P$  is used to determine the total resistance of the circuit

$$R = Q_P X_C = (58)(3.644 \text{ k}\Omega) = 211 \text{ k}\Omega$$

But

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_P}$$
$$\frac{1}{R_1} = \frac{1}{R} - \frac{1}{R_P} = \frac{1}{211 \text{ k}\Omega} - \frac{1}{443 \text{ k}\Omega} = 2.47 \mu\text{S}$$

And so

$$R_1 = 405 \text{ k}\Omega$$

The voltage across the circuit is determined to be

$$\mathbf{V} = \mathbf{I}R = (10 \mu\text{A} \angle 0^\circ)(211 \text{ k}\Omega) = 2.11 \text{ V} \angle 0^\circ$$


and the current through the inductor is

$$\mathbf{I}_L = \frac{\mathbf{V}}{R_{\text{coil}} + jX_L}$$
$$= \frac{2.11 \text{ V} \angle 0^\circ}{30 + j3644 \Omega} = \frac{2.11 \text{ V} \angle 0^\circ}{3644 \Omega \angle 89.95^\circ} = 579 \mu\text{A} \angle -89.95^\circ$$


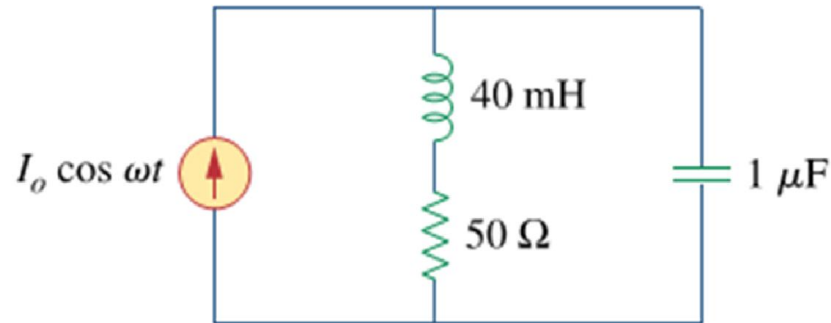
## Example (2)

For the “tank” circuit in Fig., find the resonant frequency



$$Y = \frac{1}{R + j\omega L} + j\omega C = j\omega C + \frac{R - j\omega L}{R^2 + \omega^2 L^2}$$

At resonance,  $\text{Im}(Y) = 0$ , i.e.

$$\omega_0 C - \frac{\omega_0 L}{R^2 + \omega_0^2 L^2} = 0$$

$$R^2 + \omega_0^2 L^2 = \frac{L}{C}$$

$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} = \sqrt{\frac{1}{(40 \times 10^{-3})(1 \times 10^{-6})} - \left(\frac{50}{40 \times 10^{-3}}\right)^2}$$

$$\omega_0 = \underline{\underline{4841 \text{ rad/s}}}$$

**Thank You**

