

**Benha University**  
**Faculty Of Engineering at Shoubra**



**ECE 122**  
**Electrical Circuits (2)(2016/2017)**  
**Lecture (5)**  
**Filters**

**Prepared By :**

**Dr. Moataz Elsherbini**

[motaz.ali@feng.bu.edu.eg](mailto:motaz.ali@feng.bu.edu.eg)

# Filters

2

A **filter** is a circuit that is designed to pass signals with desired frequencies and reject or attenuate others.

- The filter can be treated as a network designed to have frequency selective behavior
- A filter can be used to limit the frequency spectrum of a signal to some specified band of frequencies.
- Filters are the circuits used in radio and TV receivers to allow us to select one desired signal out of a multitude of broadcast signals in the environment

. **Filters** may be classified as either digital or analog.

. **Digital filters** are implemented using a digital computer or special purpose digital hardware.

. **Analog filters** may be classified as either passive or active and are usually implemented with R, L, and C components and operational amplifiers.

# Filters

3

## Background:

- An active filter is one that, along with R, L, and C components, also contains an energy source, such as that derived from an operational amplifier.
- A passive filter is one that contains only R, L, and C components. It is not necessary that all three be present. L is often omitted (on purpose) from passive filter design because of the size and cost of inductors – and they also carry along an R that must be included in the design.



# Passive Analog Filters

4


Background:

Four types of filters - "Ideal"


lowpass



highpass

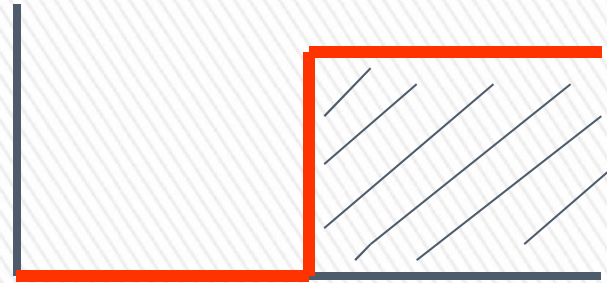

bandpass

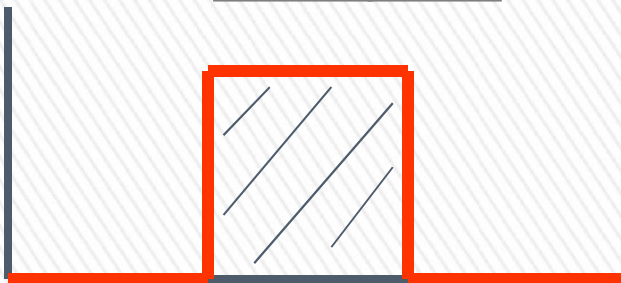

bandstop




# Passive Analog Filters

5


Background:

Realistic Filters:


lowpass

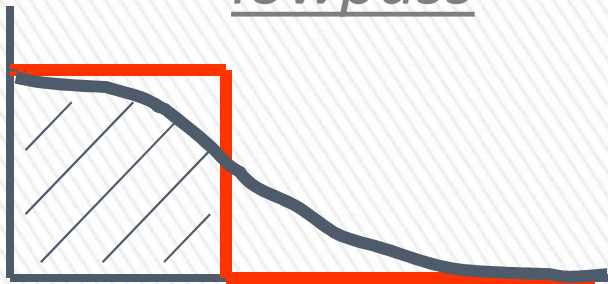


highpass

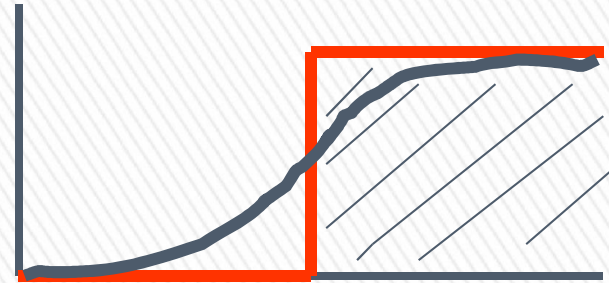

bandpass

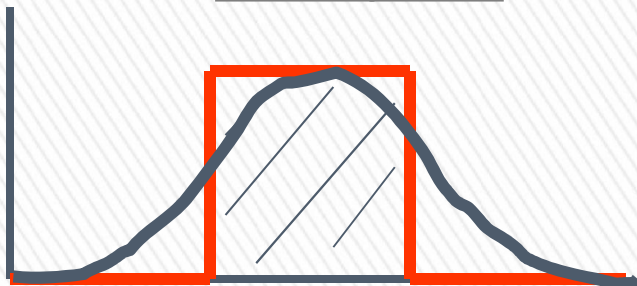

bandstop

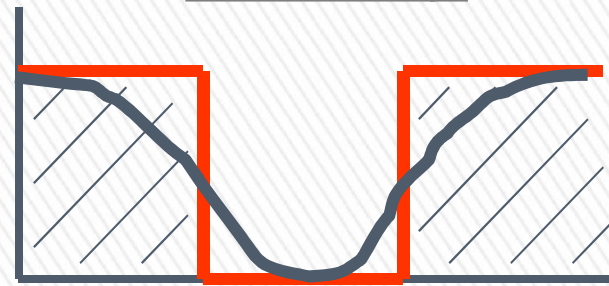



## Filters

Important Table for determining the type of the filter from its Transfer function

Summary of the characteristics of ideal filters.

Type of Filter	$H(0)$	$H(\infty)$	$H(\omega_c)$ or $H(\omega_0)$
Lowpass	1	0	$1/\sqrt{2}$
Highpass	0	1	$1/\sqrt{2}$
Bandpass	0	0	1
Bandstop	1	1	0

## Low Pass Filter




# Passive Analog Filters


8

## Low Pass Filter

Consider the circuit below.

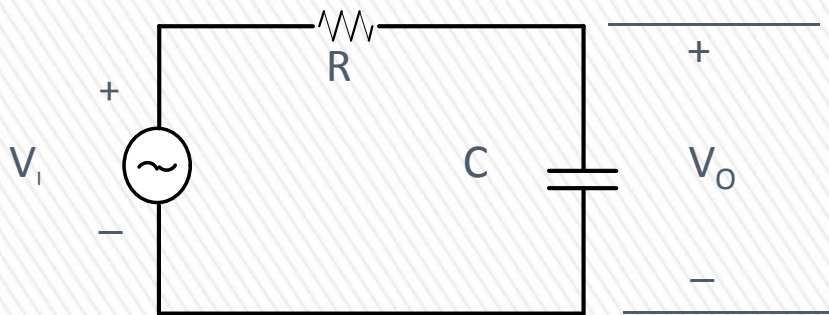

Low pass filter circuit

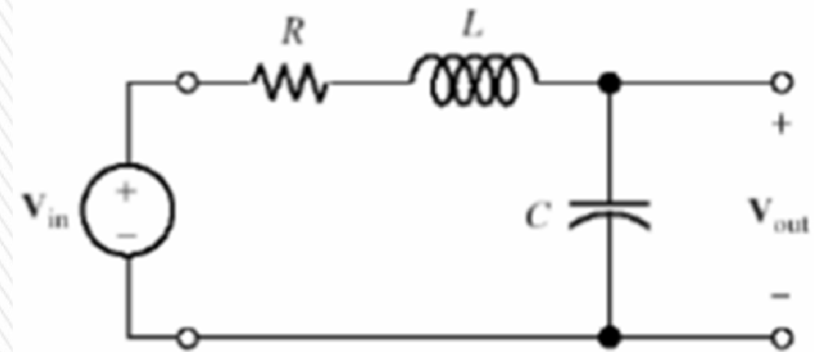

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$


- At low frequency the capacitor is an open circuit ( $V_o = V_{in}$ )
- At high frequency the capacitor is a short and the inductor is open ( $V_o = 0$ )



# Passive Analog Filters


9

## Low Pass Filter

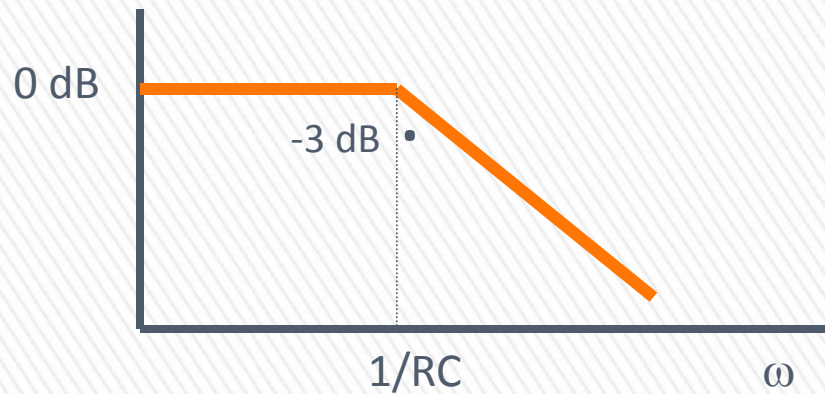

Bode

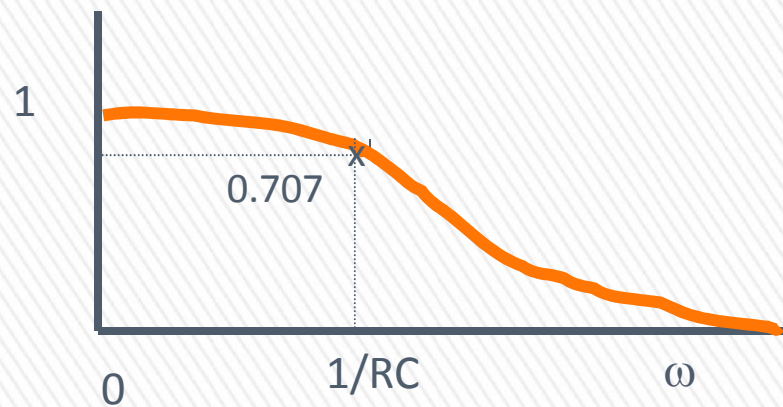Passes low frequencies  
Attenuates high frequencies




Linear Plot

## Example (1)


Show that a series LR circuit is a low-pass filter if the output is taken across the resistor. Calculate the corner frequency  $f_c$  if  $L = 2 \text{ mH}$  and  $R = 10 \text{ k}\Omega$ .

$$V_o = V_i \frac{R}{R + j\omega L}$$

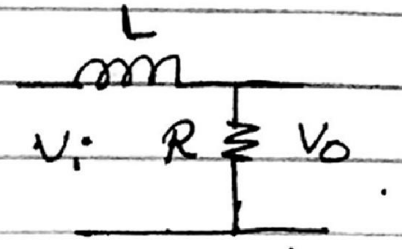

$$\frac{V_o}{V_i} = H(f) = \frac{R}{R + j\omega L}$$
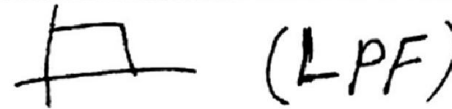
$$\begin{aligned} \text{at } \omega = 0 &\rightarrow H(f) = 1 \\ \omega = \infty &\rightarrow H(f) = 0 \end{aligned}$$



Corner Freq. at  $|H(f)| = \frac{1}{\sqrt{2}} H(0)$

$$H(f) = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega \frac{L}{R}} \quad \neq \frac{1}{\sqrt{2}}$$

$$|H(f)| = \frac{1 \cdot L^0}{\sqrt{1 + (\frac{\omega L}{R})^2} L^0} = \frac{1}{\sqrt{1 + (\frac{\omega L}{R})^2}} = \frac{1}{\sqrt{2}}$$


$$\therefore 1 + \left(\frac{\omega L}{R}\right)^2 = 2 \quad \text{or } \frac{\omega L}{R} = 1 \quad \therefore \omega = \frac{R}{L}$$

$$\therefore 2\pi f = \frac{R}{L} \quad \therefore f = \frac{1}{2\pi} \frac{R}{L} = 796 \text{ kHz}$$


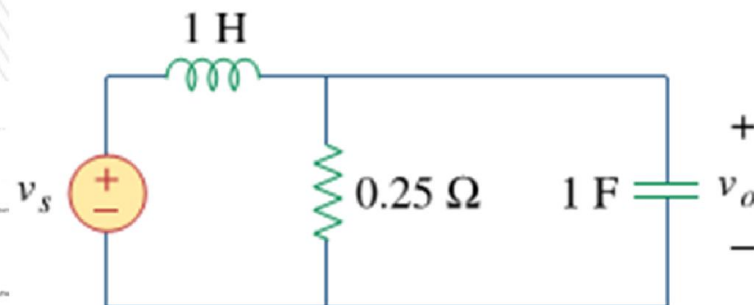
## Example (2)

Find the transfer function  $V_o/V_s$  of the circuit in Figure. Show that the circuit is a low-pass filter.



$$H(f) = \frac{R // X_c}{X_L + R // X_c}$$

$$= \frac{R \left( \frac{1}{j\omega C} \right) / \left( R + \frac{1}{j\omega C} \right)}{j\omega L + \frac{R \left( \frac{1}{j\omega C} \right)}{R + \frac{1}{j\omega C}}}$$

$$= \frac{R \left( \frac{1}{j\omega C} \right)}{\left( R + \frac{1}{j\omega C} \right) (j\omega L) + R \left( \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L) \left( R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L) \left( R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L) \left( R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R + (j\omega C)(j\omega L) \left( R + \frac{1}{j\omega C} \right)}$$

## Example (2)

12

$$= \frac{R}{R - \omega^2 LC \left( R + \frac{1}{j\omega C} \right)}$$

$$= \frac{R}{R - \omega^2 LRC - \frac{1}{j}\omega L} = \frac{R}{R - \omega^2 LRC + j\omega L}$$

at  $\omega = 0 \rightarrow H(f) = 1$

$\omega = \infty \rightarrow H(f) = 0$

$\Rightarrow$  LPF



### Example (3)

Determine the cutoff frequency of the low-pass filter described by

$$H(\omega) = \frac{4}{2 + j\omega 10}$$

Find the gain in dB and phase of  $H(\omega)$  at  $\omega = 2$  rad/s.

∅/ Cutoff freq calculated when  
 $|H(\omega)| = \frac{1}{\sqrt{2}} |H(\omega)|_{\max}$

$$H(0) = \frac{4}{2} = 2 \rightarrow \text{is max}$$

$$H(\infty) = 0$$

∴ ~~is~~ cutoff freq calculated when  $|H(\omega)| = \frac{1}{\sqrt{2}} (2)$ .

$$\text{But } |H(\omega)| = \frac{4 \cancel{L_0}}{\sqrt{2^2 + (10\omega)^2} \cancel{L_0}} = \frac{4^2}{\sqrt{4 + 100\omega^2}} = \frac{2}{\sqrt{2}}$$

### Example (3)

14

$$\text{or } \frac{4}{4+100\omega^2} = \frac{1}{2}$$

or  $\omega^2 = \frac{4}{100}$

$$\text{or } 100\omega^2 + 4 = 8$$
$$\omega = 0.12 \text{ rad/s}$$

$$H(2) = \frac{4}{2+j20} = \frac{2}{1+j10}$$

$$|H(2)| = \frac{2 \angle 0^\circ}{\sqrt{101} \angle \tan^{-1} 10} = \frac{2 \angle 0^\circ}{\sqrt{101} \angle 84.3^\circ}$$

$$\text{Phase } (0 - \tan^{-1} 10) = \underline{\underline{-84.3^\circ}}$$

$$\text{Mag} = \frac{2}{\sqrt{101}} = 0.199$$


$$\text{Mag dB} = 20 \log 0.199 = -14.023 \text{ dB}$$




**High Pass Filter**

# Passive Analog Filters

## High Pass Filter

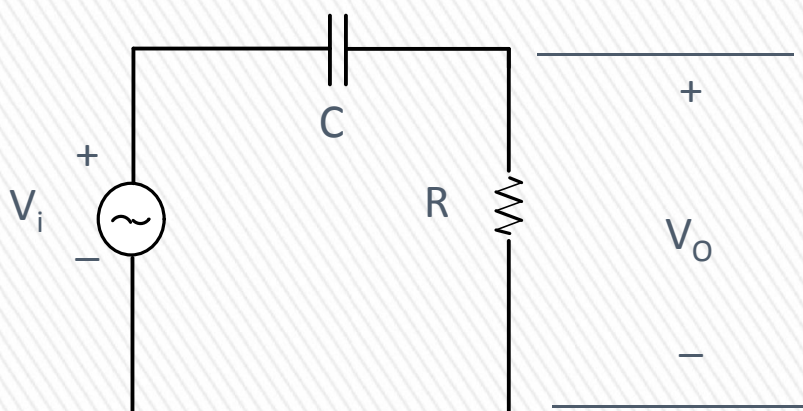

High Pass Filter

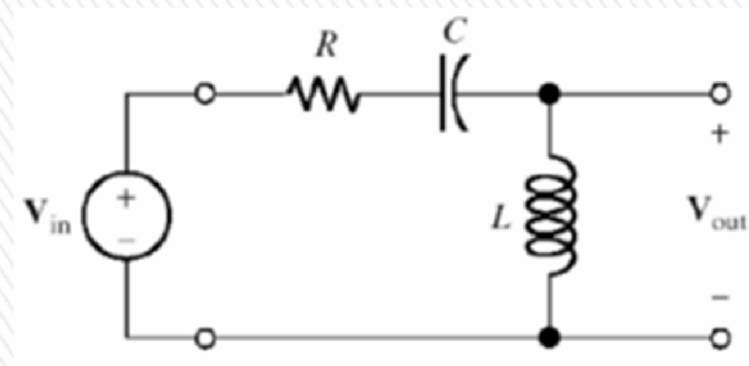

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{R}{R + \frac{1}{j\omega C}} = \frac{j\omega RC}{1 + j\omega RC}$$


- At low frequency the capacitor is an open circuit ( $V_o = 0$ )
- At high frequency the capacitor is a short and the inductor is open ( $V_o = V_{in}$ )



# Passive Analog Filters

## High Pass Filter


Bode

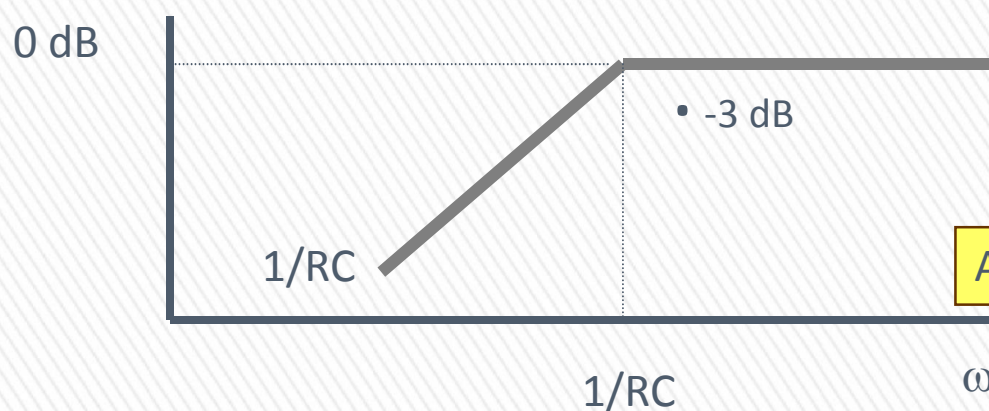

Passes high frequencies

Attenuates low frequencies


Linear

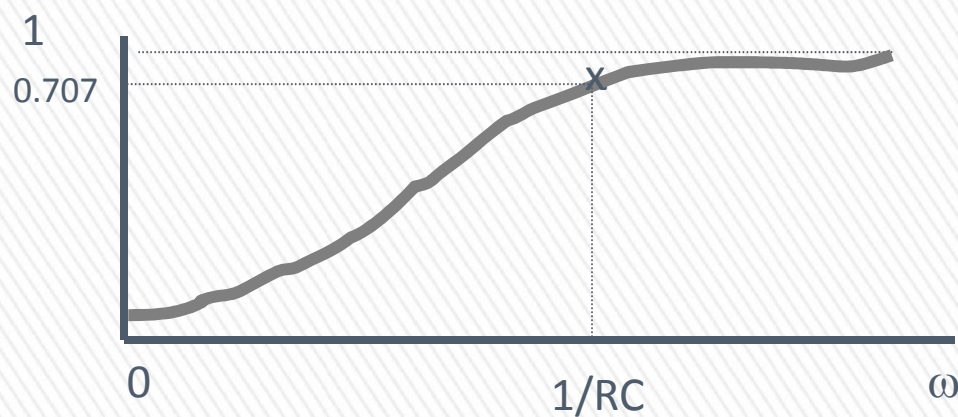
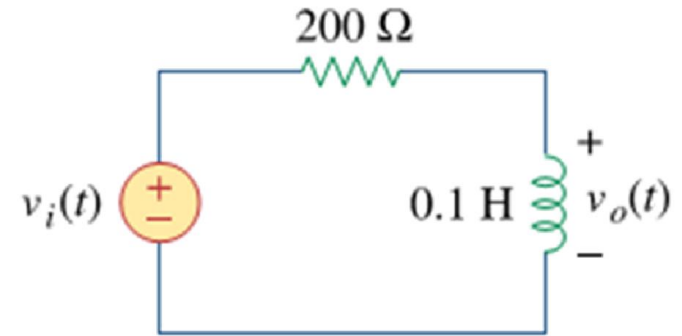
## Example (4)

18

Determine what type of filter in figure . Calculate the corner frequency  $f_c$



80) /  $N_o = N_i \left( \frac{X_L}{R + jX_L} \right)$

$$H(f) = \frac{j\omega L}{R + j\omega L} = \frac{1}{1 + \frac{R}{j\omega L}} \quad \text{at } \omega = 0 \rightarrow H(f) = 0$$

$$\omega = \infty \rightarrow H(f) = 1$$

∴ HPF

$$\rightarrow |H(\omega)| = \frac{1}{\sqrt{2}} \text{ max} = \frac{1}{\sqrt{2}} H(\infty) = \frac{1}{\sqrt{2}}$$

$$= \left| \frac{1}{1 + \frac{R}{j\omega L}} \right| = \left| \frac{1}{1 - j\frac{R}{\omega L}} \right| = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega L}\right)^2}} = \frac{1}{\sqrt{2}}$$

$$\text{or } 1 + \left(\frac{R}{\omega L}\right)^2 = 2 \quad \text{∴ } \left(\frac{R}{\omega L} = 1\right)$$

$$\text{∴ } \omega = \frac{R}{L}, \quad 2\pi f = \frac{R}{L} \rightarrow f = 318.3 \text{ Hz}$$



## Example (5)

19

In a high-pass RL filter with a cutoff frequency of 100 kHz,  $L = 40$  mH. Find  $R$ .

Sol / So it is RL  $\omega = \frac{R}{L} = 2\pi f$   
 $\rightarrow 40\text{mH}$   $\rightarrow 100\text{K}$


$$R = 25.13 \text{ k}\Omega$$

## Band Pass Filter


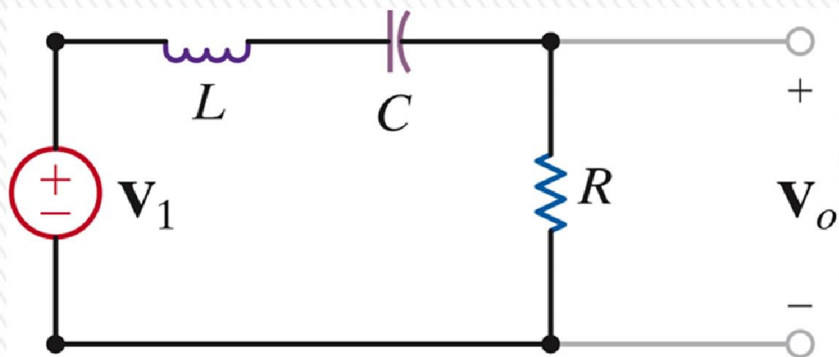
## Simple Passive band-pass filter

The RLC series resonant circuit provides a bandpass filter when the output is taken off the resistor as shown in Fig.



$$H = \frac{V_0}{V_1} = \frac{R}{R + j\left(\omega L - \frac{1}{\omega C}\right)}$$

Transfer Function

$$|H(\omega)| = \frac{\omega RC}{\sqrt{(\omega RC)^2 + (\omega^2 LC - 1)^2}}$$


$$H\left(\omega = \frac{1}{\sqrt{LC}}\right) = 1$$

$$H(\omega=0) = H(\omega=\infty) = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$H(\omega_{LO}) = \frac{1}{\sqrt{2}} = M(\omega_{HI})$$
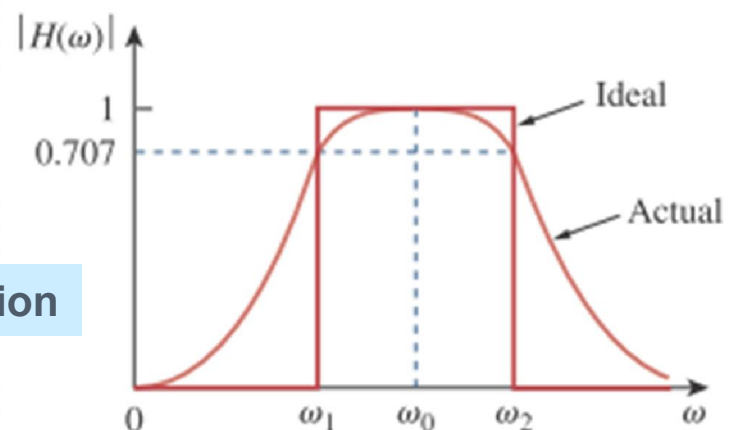
$$BW = \omega_{HI} - \omega_{LO} = \frac{R}{L}$$




$$\omega_1 = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_2 = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$


**Band Stop Filter (reject) ( notch)**



## Simple Passive band-stop filter

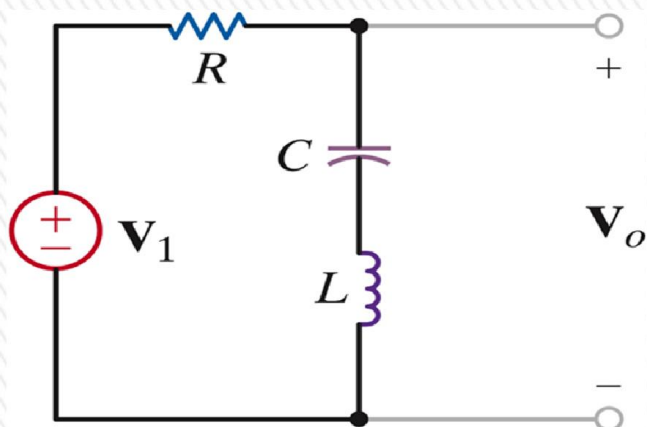

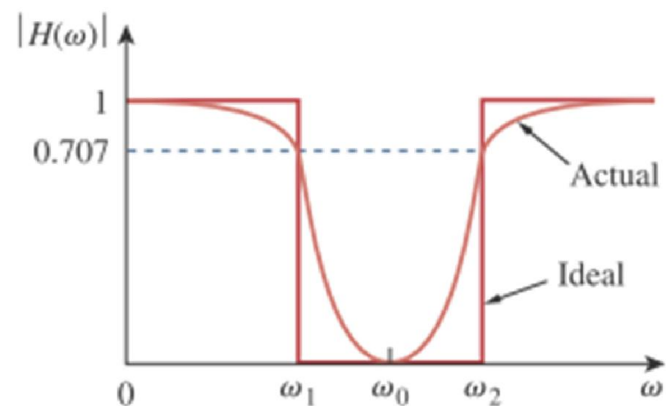- The RLC series resonant circuit provides a band-stop filter when the output is taken off the LC as shown in Fig.
- A filter that prevents a band of frequencies between two designated values
- It is also known as a band-stop, band-reject, or notch filter.



BW = Bandwidth of rejection

$$\mathbf{H(0) = 1, H(\infty) = 1.}$$

$$\mathbf{H(\omega) = \frac{V_o}{V_i} = \frac{j(\omega L - 1/\omega C)}{R + j(\omega L - 1/\omega C)}}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \Rightarrow j\left(\omega_0 L - \frac{1}{\omega_0 C}\right) = 0$$

at  $\omega = 0$  the capacitor acts as open circuit  $\Rightarrow V_0 = V_1$

at  $\omega = \infty$  the inductor acts as open circuit  $\Rightarrow V_0 = V_1$

$\omega_1, \omega_2$  are determined as in the band - pass filter

## Active Filters

**Passive filters have several limitations:**

**1. Cannot generate gains greater than one**

**2. Loading effect makes them difficult to interconnect**


**3. Use of inductance makes them difficult to handle**

**➤ Using operational amplifiers one can design all basic filters, and more, with only resistors and capacitors**




**Remember**


# Filter types Remember

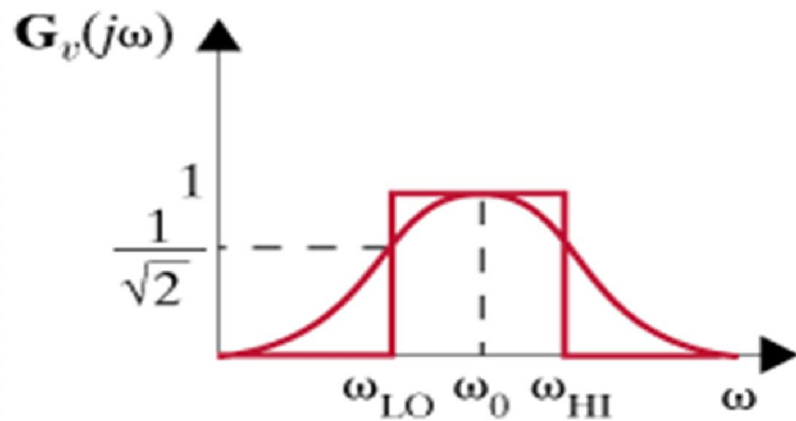


Band-pass filter

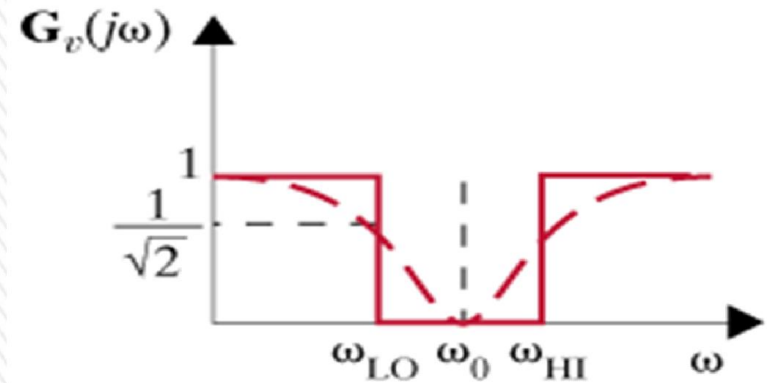

Band-reject filter

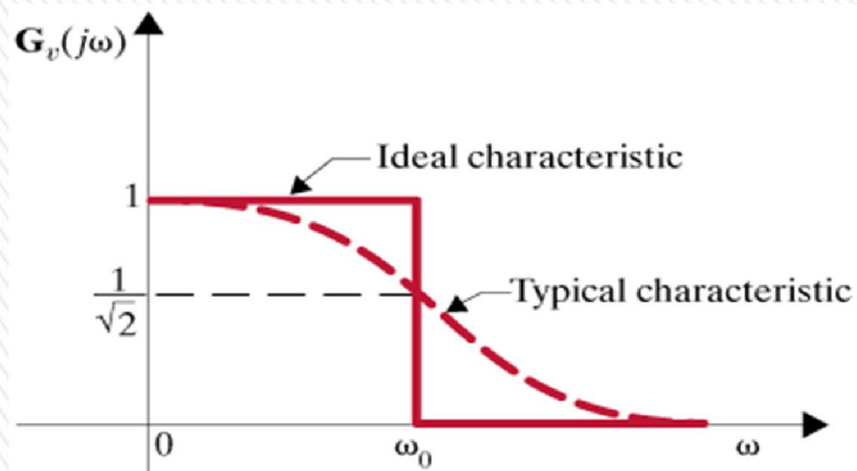

Low-pass filter

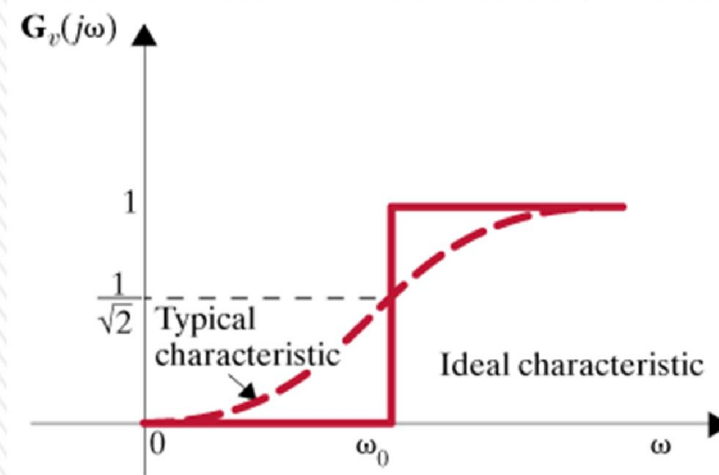

High-pass filter



**Thank You**

