

Midterm

- 1 -

① $f_0 = 90 \text{ MHz}$, $BW = 2 \text{ MHz}$, Series RLC resonance

Sol/08 $BW = \frac{R}{L}$ (rad/sec)

$$\therefore (2 \times 10^6 \times 2\pi) = \frac{R}{L}$$

Let $R = 100 \Omega$ $\therefore L = \frac{100}{2 \times 10^6 \times 2\pi} \cong 7.95 \mu\text{H}$

$\therefore \omega = \frac{1}{\sqrt{LC}} \therefore 2\pi \times 90 \times 10^6 = \frac{1}{\sqrt{7.95 \times 10^{-6} \times C}}$

$\therefore C \cong 0.39 \text{ pF}$

$Q = \frac{f_0}{BW} = \frac{90 \text{ M}}{2 \text{ M}} = 45$

جواب

$Q = \frac{\omega L}{R} = \frac{1}{\omega RC}$

$\omega = 2\pi \times 90 \times 10^6$
 $\therefore 45 = \frac{(2\pi \times 90 \times 10^6) L}{R}$

Let $R = 100$, $L = 7.95 \mu\text{H}$

$45 = \frac{(2\pi \times 90 \times 10^6) \times 100 \times C}{R} \therefore C = 0.39 \text{ pF}$

② ideal parallel Res

$$Q = 45 = \frac{R}{\omega L} = \omega RC$$

$$BW = \frac{1}{RC}$$

بدون

مع

$$BW = \frac{1}{RC} \text{ rad/sec}$$

$$2\pi \times 2 \times 10^6 = \frac{1}{RC}$$

$$Q = \omega RC \text{ at } (R=100)$$

$$45 = (2\pi \times 90 \times 10^6)(100)C = 45$$

$$\therefore C = 0.795 \text{ nF}$$

بدون R في دائرة
Parallel
(في دائرة)


at R=1k C = 79.5 pF

$$Q = \frac{R}{\omega L}$$

$$45 = \frac{100 \text{ (or } 1000)}{(2\pi \times 90 \times 10^6)L}$$

% You select R = 100 ~
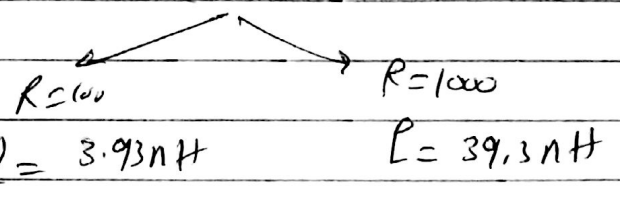
$$C_1 = \frac{1}{2\pi \times 2 \times 10^6 \times 100} = 0.795 \text{ nF}$$



% You select R = 1k

$$C_2 = 79.5 \text{ pF}$$

$$\omega = \frac{1}{TLC_1} = 2\pi \times 90 \times 10^6$$

$$L = 3.93 \text{ nH} \quad R=100$$



% used C2 1k > R

$$L_2 = 39.3 \text{ nH}$$

∴ Q > 10 ∴ $f_1 = f_0 - BW/2 = 90 - \frac{2}{2} = 89 \text{ MHz}$

use Approx. $f_2 = f_0 + BW/2 = 91 \text{ MHz}$

③ BPF using R^sLC^s

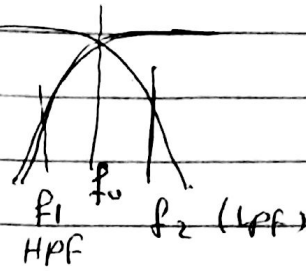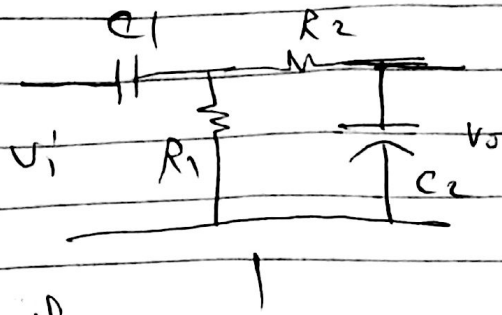

$$f_1 = \frac{1}{2\pi R_1 C_1}$$

$$f_1 = f_0 - BW/2 = 89 \text{ MHz}$$

$$\text{HPF} \Rightarrow 89 \times 10^6 = \frac{1}{2\pi (100) C_1} \quad \text{let } R_1 = 100$$

$$C_1 = 56.1 \text{ pF}$$

$$f_2 = \frac{1}{2\pi R_2 C_2}$$

$$f_2 = f_0 + BW/2 = 91 \text{ MHz}$$

$$91 \text{ MHz} = \frac{1}{2\pi (100) C_2} \quad \text{let } R_2 = 100$$

$$C_2 = 54.9 \text{ pF}$$

④ Q = 55, BW = 2 MHz

$$\therefore Q = f_0 / BW, \quad f_0 = 2 \times 55 \text{ MHz} = 110 \text{ MHz}$$

$$\therefore 270, \quad f_1 = f_0 - BW/2 = 109 \text{ MHz}$$

$$f_2 = f_0 + BW/2 = 111 \text{ MHz}$$

f₀, f₁, f₂ out of range of FM Band

where FM Band is between 88M & 108 MHz

will not receive




- Answer all the following questions
- Illustrate your answers with sketches when necessary.
- The exam consists of One page
- (put your final results in a border)
- Total Mark: 20 Marks
- Examiners: Dr. Moataz Elsherbini

1. It is required to broadcast a shoubra radio station to be detected through your FM radio. Design a suitable series RLC circuit to verify this mission. The station must be heard within bandwidth of 2MHz, while the most purity sound heard at 90MHz. (6 marks)
2. Your close friend in your project team suggested broadcasting the same station by using ideal parallel resonance circuit. Make all necessary modifications to verify the required design at the same resonant frequency and BW, then Calculate the upper and lower cut off frequencies obtained from the new design. (6 marks)
3. Another partner in your project team claimed that he can use passive BPF (using Resistors and Capacitors only) to achieve the same resonant frequency and bandwidth. Provide the necessary help to reach the suitable design. (6 marks)
4. A genius student tries to change the design to obtain Quality factor of 55 at BW of 2MHz. will he success receiving the channel with FM mobile radio?(why?). (2 marks)

The world makes way for the man who knows where he is going

Dr/ Moataz Elsherbini

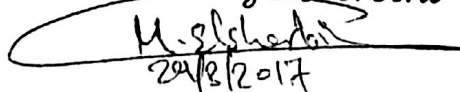
29/3/2017