



Sheet (3 solutions)... Series Resonance

1. A series RLC network has $R=2\text{k}\Omega$, $L=40\text{ mH}$, and $C=1\mu\text{F}$. Calculate the impedance at resonance and at one-fourth, one-half, twice, and four times the resonant frequency.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(40 \times 10^{-3})(1 \times 10^{-6})}} = 5 \text{ krad/s}$$

$$\mathbf{Z(\omega_0) = R = 2 \text{ k}\Omega}$$

$$\mathbf{Z(\omega_0/4) = R + j \left(\frac{\omega_0}{4} L - \frac{4}{\omega_0 C} \right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j \left(\frac{5 \times 10^3}{4} \cdot 40 \times 10^{-3} - \frac{4}{(5 \times 10^3)(1 \times 10^{-6})} \right)}$$

$$\mathbf{Z(\omega_0/4) = 2000 + j(50 - 4000/5)}$$

$$\mathbf{Z(\omega_0/4) = 2 - j0.75 \text{ k}\Omega}$$

$$\mathbf{Z(\omega_0/2) = R + j \left(\frac{\omega_0}{2} L - \frac{2}{\omega_0 C} \right)}$$

$$\mathbf{Z(\omega_0/2) = 2000 + j \left(\frac{(5 \times 10^3)}{2} (40 \times 10^{-3}) - \frac{2}{(5 \times 10^3)(1 \times 10^{-6})} \right)}$$

$$\mathbf{Z(\omega_0/2) = 200 + j(100 - 2000/5)}$$

$$\mathbf{Z(\omega_0/2) = 2 - j0.3 \text{ k}\Omega}$$

$$\mathbf{Z(2\omega_0) = R + j \left(2\omega_0 L - \frac{1}{2\omega_0 C} \right)}$$

$$\mathbf{Z(2\omega_0) = 2000 + j \left((2)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(2)(5 \times 10^3)(1 \times 10^{-6})} \right)}$$

$$\mathbf{Z(2\omega_0) = 2 + j0.3 \text{ k}\Omega}$$


$$\mathbf{Z(4\omega_0) = R + j \left(4\omega_0 L - \frac{1}{4\omega_0 C} \right)}$$

$$\mathbf{Z(4\omega_0) = 2000 + j \left((4)(5 \times 10^3)(40 \times 10^{-3}) - \frac{1}{(4)(5 \times 10^3)(1 \times 10^{-6})} \right)}$$

$$\mathbf{Z(4\omega_0) = 2 + j0.75 \text{ k}\Omega}$$



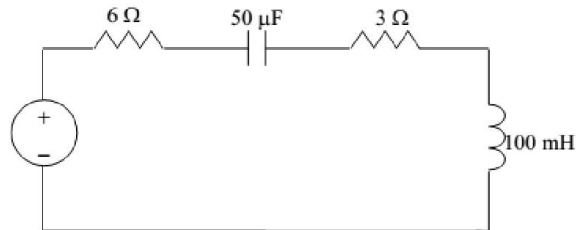2. A coil with resistance 3Ω and inductance 100 mH is connected in series with a capacitor of $50\text{ }\mu\text{F}$, a resistor of 6Ω and a signal generator that gives 110 V rms at all frequencies. Calculate ω_0 , Q , and B at resonance of the resultant series RLC circuit.



$$R = 6 + 3 = 9\ \Omega$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{100 \times 10^{-3} \times 50 \times 10^{-12}}} = 447.21\ \text{krad/s}$$

$$Q = \frac{\omega_0 L}{R} = \frac{447.21 \times 10^3 \times 100 \times 10^{-3}}{9} = 4969$$

$$B = \frac{\omega_0}{Q} = \frac{447.21 \times 10^3}{4969} = 90\ \text{rad/s}$$

3. Design a series RLC circuit with $B=20\text{ rad/s}$ and $\omega_0=1000\text{ rad/s}$. Find the circuit's Q .

Let $R = 10\ \Omega$.

$$L = \frac{R}{B} = \frac{10}{20} = 0.5\ \text{H}$$

$$C = \frac{1}{\omega_0^2 L} = \frac{1}{(1000)^2 (0.5)} = 2\ \mu\text{F}$$

$$Q = \frac{\omega_0}{B} = \frac{1000}{20} = 50$$



Therefore, if $R = 10\ \Omega$ then

$$L = \underline{0.5\ \text{H}}, \quad C = \underline{2\ \mu\text{F}}, \quad Q = \underline{50}$$

Good Luck



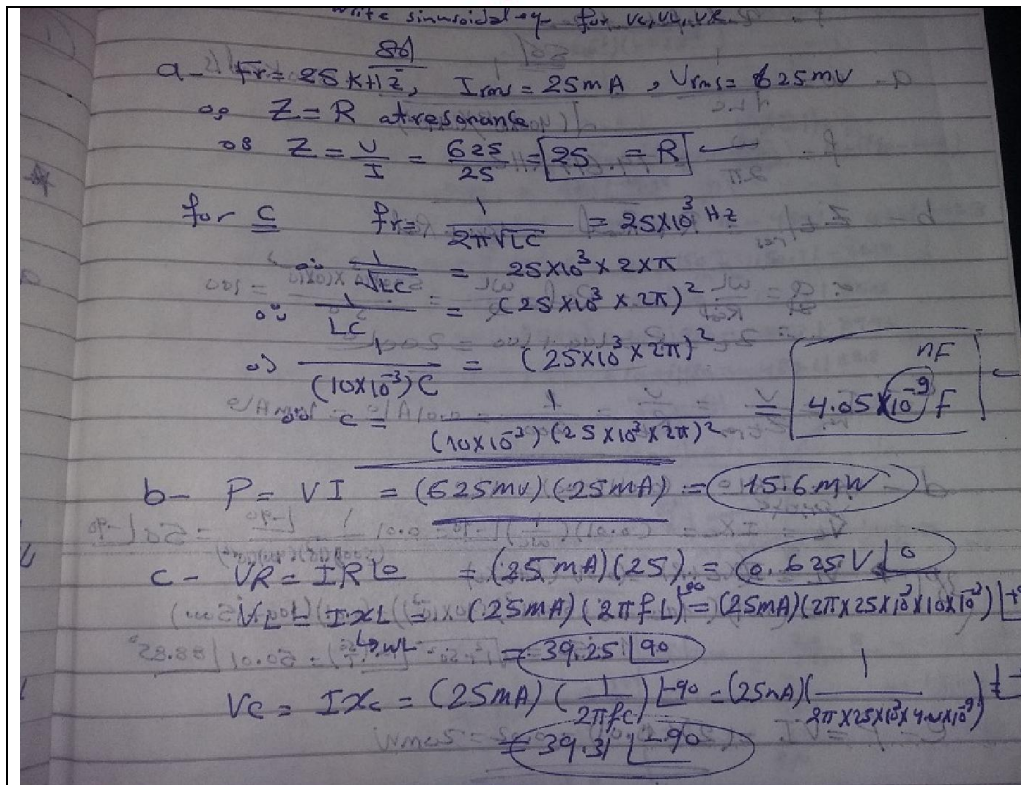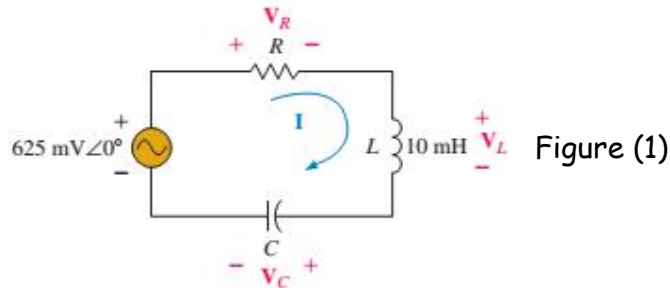4. Consider the circuit of Figure 1
- Determine the values of R and C such that the circuit has a resonant frequency of 25 kHz and an rms current of 25 mA at resonance.
 - Calculate the power dissipated by the circuit at resonance.
 - Determine the phasor voltages, V_C , V_L , and V_R at resonance.



5. Refer to the circuit of Figure 2.
- Determine the resonant frequency expressed as ω (rad/s) and f (Hz).
 - Calculate the total impedance, Z_T , at resonance.
 - Solve for current I at resonance.

Good Luck



- d. Solve for V_R , V_L , and V_C at resonance.
- e. Calculate the power dissipated by the circuit and evaluate the reactive powers, Q_C and Q_L .
- f. Find the quality factor, Q_S , of the circuit.


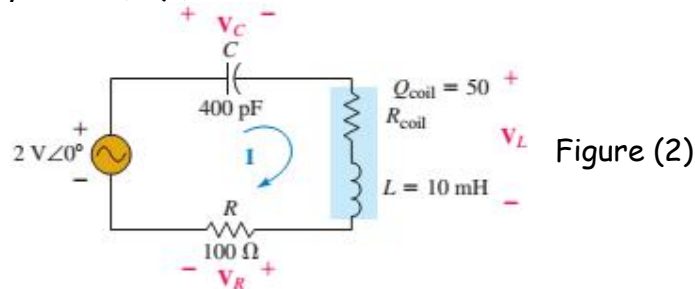


Figure (2)

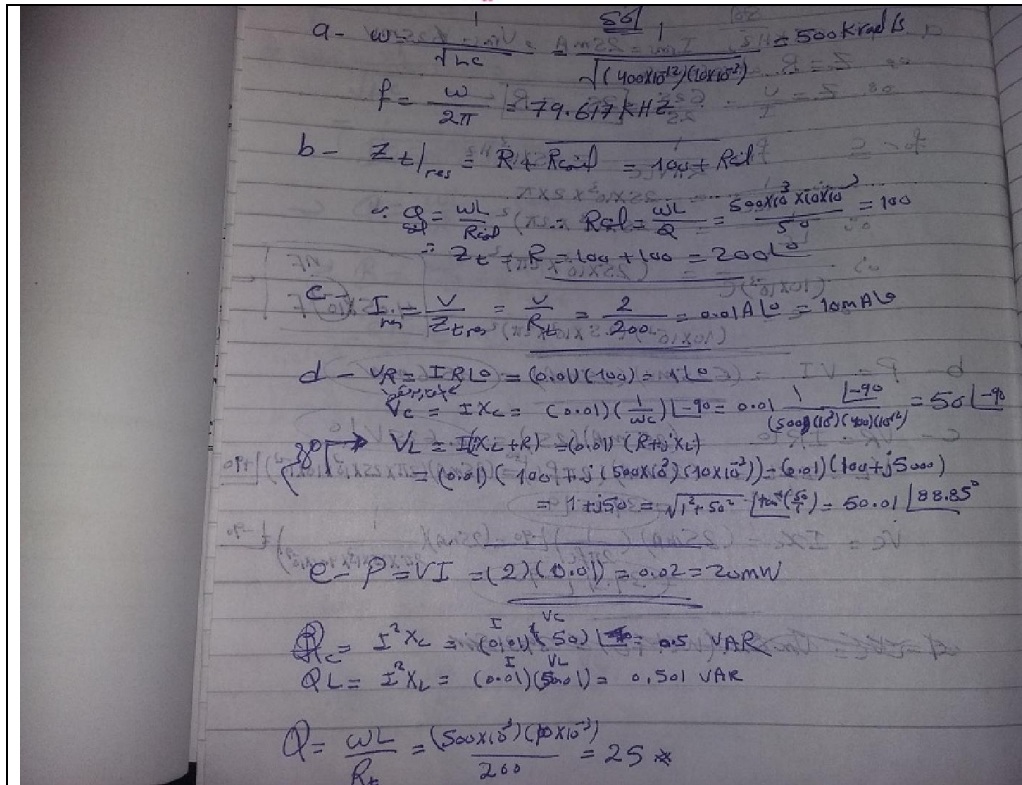

6. Refer to the circuit of Figure 3.
 - a. Find ω_S , Q , and BW (in radians per second).
 - b. Calculate the maximum power dissipated by the circuit.
 - c. From the results obtained in (a) solve for the approximate half-power frequencies, ω_1 and ω_2 .

Good Luck



d. Calculate the actual half-power frequencies, ω_1 and ω_2 , using the component values and the appropriate equations.

