



## Sheet (5)... Passive Filters

1. Show that a series LR circuit is a low-pass filter if the output is taken across the resistor. Calculate the corner frequency  $f_c$  if  $L = 2 \text{ mH}$  and  $R = 10 \text{ k}\Omega$ .

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

$H(0) = 1$  and  $H(\infty) = 0$  showing that this circuit is a lowpass filter.

At the corner frequency,  $|H(\omega_c)| = \frac{1}{\sqrt{2}}$ , i.e.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} \longrightarrow 1 = \frac{\omega_c L}{R} \quad \text{or} \quad \omega_c = \frac{R}{L}$$

Hence,

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3}{2 \times 10^{-3}} = \underline{\underline{796 \text{ kHz}}}$$

2. Find the transfer function  $V_o/V_s$  of the circuit in Figure 1. Show that the circuit is a low-pass filter.

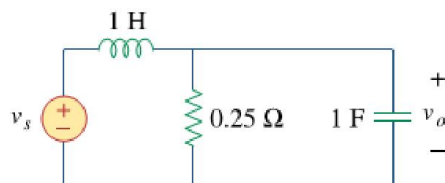


Fig.1



$$\mathbf{H}(\omega) = \frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}}$$

$$\mathbf{H}(\omega) = \frac{\frac{R/j\omega C}{R + 1/j\omega C}}{j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}}$$

$$\mathbf{H}(\omega) = \frac{\mathbf{R}}{\mathbf{R + j\omega L - \omega^2 RLC}}$$

$H(0) = 1$  and  $H(\infty) = 0$  showing that **this circuit is a lowpass filter.**

3. Determine the cutoff frequency of the low-pass filter described by

$$\mathbf{H}(\omega) = \frac{4}{2 + j\omega 10}$$

Find the gain in dB and phase of  $H(\omega)$  at  $\omega = 2$  rad/s.

Hence,

$$\text{At dc, } H(0) = \frac{4}{2} = 2.$$

$$|H(\omega)| = \frac{1}{\sqrt{2}} H(0) = \frac{2}{\sqrt{2}}$$

$$\frac{2}{\sqrt{2}} = \frac{4}{\sqrt{4 + 100\omega_c^2}}$$

$$4 + 100\omega_c^2 = 8 \longrightarrow \omega_c = 0.2$$

$$H(2) = \frac{4}{2 + j20} = \frac{2}{1 + j10}$$

$$|H(2)| = \frac{2}{\sqrt{101}} = 0.199$$

In dB,  $20 \log_{10} |H(2)| = \underline{\underline{-14.023}}$

$$\arg H(2) = -\tan^{-1} 10 = \underline{\underline{-84.3^\circ}}$$

*Good Luck*



4. Determine what type of filter in figure 2. Calculate the corner frequency  $f_c$

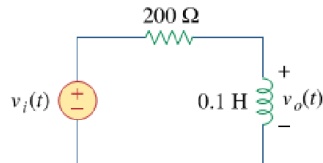


Fig.2

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L}$$

$H(0) = 0$  and  $H(\infty) = 1$  showing that **this circuit is a highpass filter.**

$$H(\omega_c) = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

or  $\omega_c = \frac{R}{L} = 2\pi f_c$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{200}{0.1} = \underline{\underline{318.3 \text{ Hz}}}$$

5. In a high-pass RL filter with a cutoff frequency of 100 kHz,  $L = 40 \text{ mH}$ . Find  $R$ .

$$\omega_c = \frac{R}{L} = 2\pi f_c$$

$$R = 2\pi f_c L = (2\pi)(10^5)(40 \times 10^{-3}) = \underline{\underline{25.13 \text{ k}\Omega}}$$

6. Design a series RLC type band-pass filter with cutoff frequencies of 10 kHz and 11 kHz. Assuming  $C = 80 \text{ pF}$ , find  $R$ ,  $L$ , and  $Q$ .

*Good Luck*



$$\begin{aligned}\omega_1 &= 2\pi f_1 = 20\pi \times 10^3 \\ \omega_2 &= 2\pi f_2 = 22\pi \times 10^3 \\ B &= \omega_2 - \omega_1 = 2\pi \times 10^3 \\ \omega_0 &= \frac{\omega_2 + \omega_1}{2} = 21\pi \times 10^3 \\ Q &= \frac{\omega_0}{B} = \frac{21\pi}{2\pi} = \underline{\underline{10.5}} \\ \omega_0 &= \frac{1}{\sqrt{LC}} \longrightarrow L = \frac{1}{\omega_0^2 C} \\ L &= \frac{1}{(21\pi \times 10^3)^2 (80 \times 10^{-12})} = \underline{\underline{2.872 \text{ H}}} \\ B &= \frac{R}{L} \longrightarrow R = BL \\ R &= (2\pi \times 10^3)(2.872) = \underline{\underline{18.045 \text{ k}\Omega}}\end{aligned}$$

7. Determine the range of frequencies that will be passed by a series RLC band-pass filter with  $R= 10\Omega$ ,  $L= 25\text{mH}$ , and  $C= 0.4 \mu\text{F}$ . Find the quality factor.

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(25 \times 10^{-3})(0.4 \times 10^{-6})}} = 10 \text{ krad/s}$$

$$B = \frac{R}{L} = \frac{10}{25 \times 10^{-3}} = 0.4 \text{ krad/s}$$

$$Q = \frac{10}{0.4} = \underline{\underline{25}}$$

$$\omega_1 = \omega_0 - B/2 = 10 - 0.2 = 9.8 \text{ krad/s} \quad \text{or} \quad f_1 = \frac{9.8}{2\pi} = 1.56 \text{ kHz}$$

$$\omega_2 = \omega_0 + B/2 = 10 + 0.2 = 10.2 \text{ krad/s} \quad \text{or} \quad f_2 = \frac{10.2}{2\pi} = 1.62 \text{ kHz}$$

Therefore,

$$\underline{\underline{1.56 \text{ kHz} < f < 1.62 \text{ kHz}}}$$

*Good Luck*



- 
8. The circuit parameters for a series RLC band-stop filter are  $R= 2 \text{ k}\Omega$ ,  $L= 0.1 \text{ H}$ ,  $C= 40 \text{ pF}$ . Calculate:
- (a) The center frequency
  - (b) The half-power frequencies
  - (c) The quality factor.

$$(a) \quad \omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(0.1)(40 \times 10^{-12})}} = \underline{0.5 \times 10^6 \text{ rad/s}}$$

$$(b) \quad B = \frac{R}{L} = \frac{2 \times 10^3}{0.1} = 2 \times 10^4$$

$$Q = \frac{\omega_0}{B} = \frac{0.5 \times 10^6}{2 \times 10^4} = 25$$

As a high Q circuit,

$$\omega_1 = \omega_0 - \frac{B}{2} = 10^4 (50 - 1) = \underline{490 \text{ krad/s}}$$

$$\omega_2 = \omega_0 + \frac{B}{2} = 10^4 (50 + 1) = \underline{510 \text{ krad/s}}$$

(c) As seen in part (b),  $Q = \underline{25}$