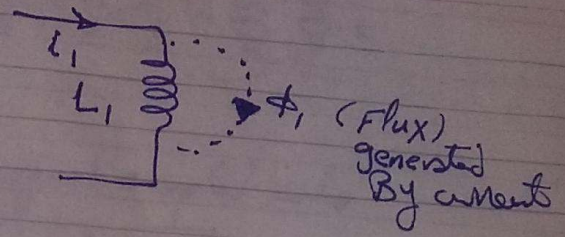


(1)
مفرد القوانین

[1] Self inductance

a) V_{L_1} (induced emf) = $N_1 \frac{d\phi_1}{dt}$
 $= L_1 \frac{di_1}{dt}$




b) $L_1 = N_1 \frac{d\phi_1}{di_1}$

For linear sy $L_1 = N_1 \phi_1 / i_1$
 For sinusoidal $V_{L_1} = L_1 \frac{di_1}{dt} = j\omega L_1 i_1$

[2] Mutual inductance

a- $M = K \sqrt{L_1 L_2}$ Henry

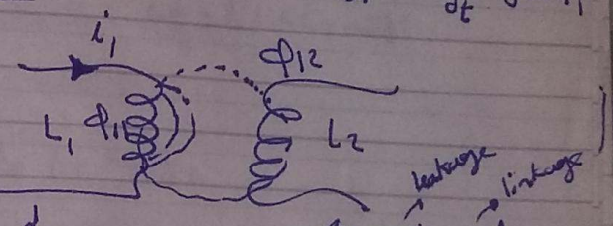where b- $M = \frac{N_1 \phi_{21}}{di_2} = \frac{N_2 \phi_{12}}{di_1}$



$\phi_1 = \phi_{11} + \phi_{12}$
 $\phi_2 = \phi_{22} + \phi_{21}$

c- $K = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{21}}{\phi_2} = \text{coupling coeff} \leq 1$

d- ~~$M = K \sqrt{L_1 L_2}$~~

depends
 → space bet coils
 → μ of medium bet
 → orientation of axis

[3] self inductance Parameters

$L = \frac{N^2 \mu A}{\text{length of coil}}$ (henery)
 N: no. of turns
 A: area


$M = \mu_0 \mu_r$
 $\mu_r \rightarrow$ permeability of free space $4\pi \times 10^{-7}$
 \rightarrow prod of inverse

(2)

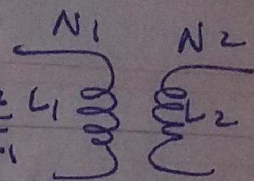3) Transformer

→ Turns Ratio =


$$\frac{N_1}{N_2} = \frac{N_p}{N_s} = \frac{V_1}{V_2} = \frac{I_2}{I_1}$$



$$\rightarrow \frac{N_1}{N_2} = \sqrt{\frac{L_1}{L_2}}$$


Magnetically coupled coils

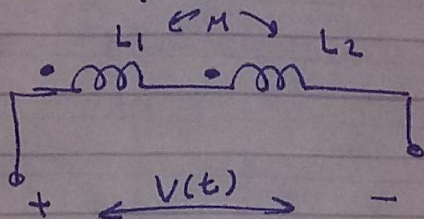[4] Sign of M (series/parallel) ... dot convention



$$L_{eq} = L_1 + L_2 + 2M$$


في اتجاه واحد

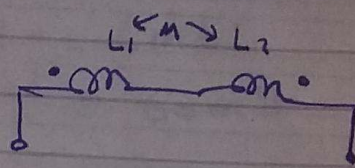


$$L_{eq} = L_1 + L_2 - 2M$$

Note $L_{T1} > L_{T2}$

Parallel

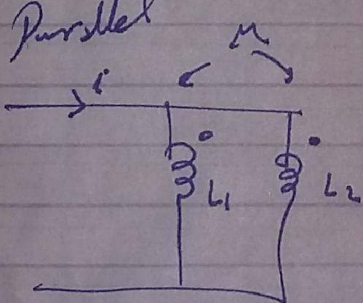

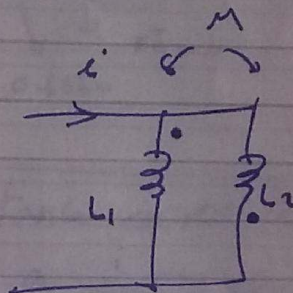
$$L_{T1} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M}$$



$$L_{T2} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$


$L_{T1} > L_{T2}$

series

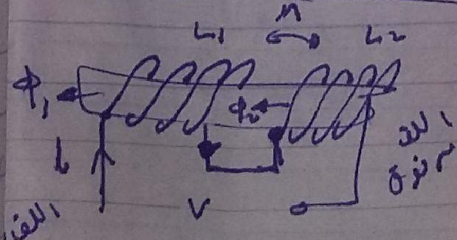

$$L_{eq} = L_1 + L_2 + 2M$$

سلسلة

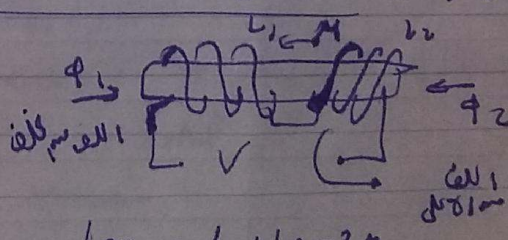

$$L_{eq} = L_1 + L_2 - 2M$$

(3)

Sheet (6)

1) one coil of magnetically coupled pair has current 5A
 Φ_{11}, Φ_{12} are 0.2 mwb, 0.4 mwb respectively
 if $N_1 = 500, N_2 = 1500$, Find L_1, L_2, M, K ?

Sol

$$\rightarrow \Phi_1 = \Phi_{11} + \Phi_{12} = 0.2 + 0.4 = 0.6 \text{ mwb}$$

$$\rightarrow L_1 = \frac{N_1 \Phi_1}{I_1} = \frac{500(0.6)}{5} = 60 \text{ mH}$$

$$\rightarrow K = \frac{\Phi_{12}}{\Phi_1} = \frac{0.4}{0.6} = 0.6667$$

$$\rightarrow M = \frac{N_2 \Phi_{12}}{I_1} = \frac{1500(0.4)}{5} = 120 \text{ mH}$$

$$\rightarrow K = \frac{M}{\sqrt{L_1 L_2}} \quad \text{or} \quad M = K \sqrt{L_1 L_2}$$


\swarrow 120 mH \searrow 60 mH
 0.6667

$$\text{so } L_2 = 540 \text{ mH}$$

2) find the equivalent inductance across terminals a, b!

$$L_{eq} = L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13}$$

$$= 6 - 2 - 2 + 2 = 4 \text{ H}$$

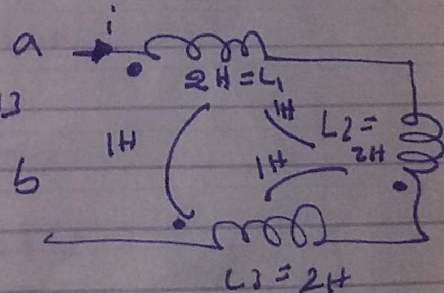

Wp

$$V = (j\omega L_1 i - j\omega M_{12} i - j\omega M_{13} i) +$$

$$(j\omega L_2 i - j\omega M_{12} i + j\omega M_{23} i) +$$

$$(j\omega L_3 i + j\omega M_{23} i - j\omega M_{13} i) = j\omega [L_1 + L_2 - 2M_{12} -$$

$$2M_{13} + 2M_{23}] = j\omega L_{total}$$


4

Loop 1
 طرقتی
 2-80

$$= j\omega L_1 i_1 + (i_1 - i_2) j\omega L_2 + j\omega M i_2$$

$$= i_1 (j\omega L_1 + j\omega L_2) + i_2 (j\omega M - j\omega L_2)$$

→ ①

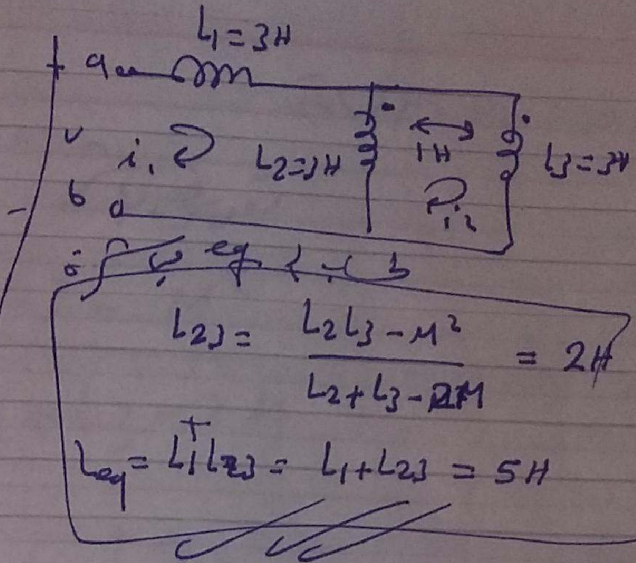

Loop 2

$$0 = [j\omega L_3 i_2 - j\omega M i_1] + (i_2 - i_1) j\omega L_2 - j\omega M (i_2 - i_1)$$

$$0 = i_1 [j\omega M - j\omega L_2] + i_2 [j\omega L_3 - j\omega M + j\omega L_2 - j\omega M]$$

→ ②

$$\Delta = \begin{bmatrix} j\omega(L_1 + L_2) & j\omega(M - L_2) \\ j\omega(M - L_2) & j\omega(L_2 + L_3 - 2M) \end{bmatrix}$$

$$\Delta_1 = \begin{bmatrix} v & j\omega(M - L_2) \\ 0 & j\omega(L_2 + L_3 - 2M) \end{bmatrix}, I_1 = \frac{\Delta_1}{\Delta}$$

$$\Delta_2 = \begin{bmatrix} j\omega(L_1 + L_2) & v \\ j\omega(M - L_2) & 0 \end{bmatrix}, I_2 = \frac{\Delta_2}{\Delta}$$

Z₂ = Δ₂/Δ

Note $Z_{in} = Z_{ab} = \frac{\Delta}{\Delta_{11}} \rightarrow$ الفرائد لى الفرائد

$$Z_{in} = \frac{(j\omega)^2 \cdot 20}{j\omega(4)} = j\omega(5)$$

$L_{total} = 5H$

5


صدا ذلالت م ل بقه

تقریر

$$L_{23} = \frac{L_2 L_3 - M^2}{L_2 + L_3 - 2M} = 2H$$

$$L_{eq} = L_1 + L_{23} = 5H$$

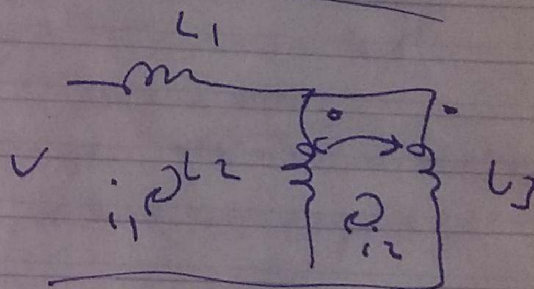① $\psi = i_1 (X_{L1} + X_{L2}) - i_2 X_{L2} + i_2 X_M$




② $0 = i_2 (X_{L2} + X_{L3}) + i_1 X_M - i_1 X_{L2}$

$$0 = i_2 (X_{L2} + X_{L3}) - (i_2 - i_1) j\omega M + (i_2 - i_1) X_{L2} - j\omega M i_2$$

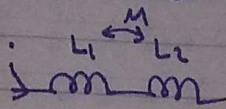(3)

3] Calc. mutual inductance of 2 coils of self inductance 100mH and 200mH are connected in series to yield a total inductance of 146mH.



Sol.

$$L_{eq} = L_1 + L_2 \pm 2M$$

$$146m = 100m + 200m \pm 2M$$

$$\therefore \pm 2M = (146 - 300)m \Rightarrow \pm M = \pm 77mH$$

$$\text{or } \pm 2M = 0 \Rightarrow M = -77mH \text{ or } M = 77mH$$


M - ve

U.P.E.D

$$L_1 + L_2 > 146mH \Rightarrow \text{in series or in series}$$

4] 3 similar coil wound on along common core, The voltage of mutual inductance between each set of coil is +ve, The self inductance of each coil is 0.2H. The effective inductance of first 2 coils is 0.6H, and of all 3 in series is 1H. (When terminals of first coil is interchanged, the effective inductance of 3 coils in series become 0.5H) determine self inductance of each set of coil.

Sol.

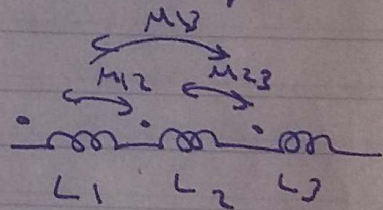

$$\rightarrow L_1 = L_2 = L_3 = L = 0.2H$$

$$\rightarrow L_{12} = 0.6H, L_{total} = 1H$$

$$\rightarrow L_{12} = L_1 + L_2 + 2M_{12} = 0.6$$


$$\therefore M_{12} = 0.1H$$

$$\rightarrow M_{12} = K_{12} \sqrt{L_1 L_2} = K_{12} \sqrt{0.2 \times 0.2} = K_{12} \times 0.2 \therefore K_{12} = 0.5$$

$$\rightarrow L_{total} = L_1 + L_2 + L_3 + 2M_{12} + 2M_{23} + 2M_{13}$$

$$1 = 3 \times 0.2 + 2 \times 0.1 + 2M_{23} + 2M_{13} \therefore M_{13} + M_{23} = 0.1$$

When coil 1 is shorted

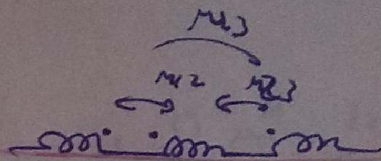

$\therefore M_{12}, M_{13} \rightarrow -ve$

$L_{T_{new}} = 0.5$

$$0.5 = L_1 + L_2 + L_3 - 2M_{12} + 2M_{23} - 2M_{13}$$

$$0.6 = 0.6 - 0.2 + 2M_{23} - 2M_{13}$$

$\therefore M_{23} - M_{13} = 0.05 \rightarrow 2$

Solve 1, 2


$$\therefore M_{13} = 0.025 = k_{13} \sqrt{L_1 L_3} \rightarrow k_{13} = 0.125$$

$$M_{23} = 0.075 = k_{23} \sqrt{L_2 L_3} \rightarrow k_{23} = 0.275$$


Find V_1, V_2, V_3

$$\begin{aligned} \rightarrow V_1 &= L_1 \frac{dI_1}{dt} + M_{12} \frac{dI_2}{dt} \\ &= 10 \times 2 + 2 \times 5 = 36V \end{aligned}$$
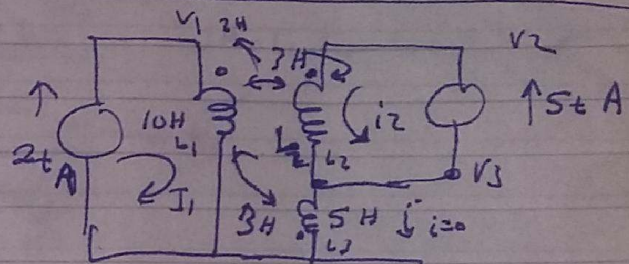
$$\rightarrow V_3 = M_{13} \frac{dI_1}{dt} + L_3 \frac{dI_3}{dt} = 3 \times 2 = 6V$$



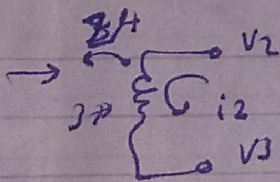($I_3=0$)
 كلفه صفر
 لانه كونه متعلقه بالثابت
 دعاته
 لانه $I_3=0$




$$V_2 - V_3 = L_2 \frac{di_2}{dt} + M_{21} \frac{di_1}{dt}$$

$$V_2 - V_3 = 3 \times 5 + 2 \times 2 = 19V$$

$$V_2 = V_3 + 19 = 25V$$

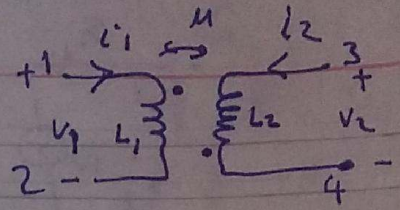5) → $L_2 = 2H$, The inductance at 1,2 is $3H$
 when terminals 3, 4 opened
 → And $1H$ when shorted,
 Determine self of coupled \odot^+ .



$$1- \quad v_{12} = L_1 \frac{di_1}{dt} - M_{12} \frac{di_2}{dt}$$

$$2- \quad v_{34} = L_2 \frac{di_2}{dt} - M_{21} \frac{di_1}{dt}$$

for 3, 4 (o.c) → $i_2 = 0 \quad \therefore \frac{di_2}{dt} = 0$

$$\therefore v_1 = L_1 \frac{di_1}{dt} = j\omega L_1 i_1 = jX_L \cdot i_1$$

$$L_1 = 3H$$

$\therefore v_1$ دالة i_1 بس $3H = L_1$

for 3, 4 s.c $v_2 = 0$ only

$$0 = L_2 \frac{di_2}{dt} - M \frac{di_1}{dt}$$

$$L_2 \frac{di_2}{dt} = M \frac{di_1}{dt}$$

$$\therefore \frac{di_2}{dt} = \frac{M}{L_2} \frac{di_1}{dt}$$

$$\therefore v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt} = L_1 \frac{di_1}{dt} - \frac{M^2}{L_2} \frac{di_1}{dt} = \left(L_1 - \frac{M^2}{L_2} \right) \frac{di_1}{dt}$$

$$L_{eq} = L_1 - \frac{M^2}{L_2} = 1H$$

$$\therefore 3 - \frac{M^2}{2} = 1$$


$$\therefore M = 2H$$

$$M = K \sqrt{L_1 L_2}$$

$$\therefore K = 0.816$$

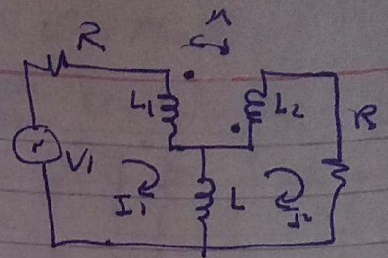7) ratio $I_1/I_2 = ?$ Using $\left\{ \begin{array}{l} \text{direct coupled} \\ \text{conductively coupled} \end{array} \right.$ sol.


$$1) V_1 = I_1 (R + j\omega(L_1 + L_2)) + j\omega M I_2$$



$$V_1 = I_1 (R + j\omega(L_1 + L_2)) + j\omega(M - L) I_2$$

Conductively coupled equivalent
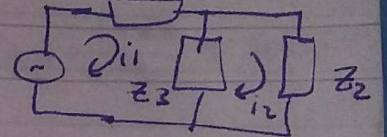
$$2) 0 = I_2 (R + j\omega(L_1 + L_2)) + j\omega(M - L) I_1$$



$$\Delta = \begin{vmatrix} R + j\omega(L_1 + L_2) & j\omega(M - L) \\ j\omega(M - L) & R + j\omega(L_1 + L_2) \end{vmatrix} = V_1 [R + j\omega(L_1 + L_2)]$$

$$V = (Z_1 + Z_3) I_1 - Z_3 I_2 \rightarrow 3$$

$$0 = -Z_3 I_1 + (Z_2 + Z_3) I_2 \rightarrow 4$$

$$\Delta_1 = \begin{vmatrix} V_1 & j\omega(M - L) \\ 0 & R + j\omega(L_1 + L_2) \end{vmatrix} = V_1 [R + j\omega(L_1 + L_2)]$$

capture 3, 4 by 1, 2

$$\Rightarrow Z_1 + Z_3 = R + j\omega(L_1 + L_2) \rightarrow 5$$

$$-Z_3 = j\omega(M - L)$$

$$\Delta_2 = \begin{vmatrix} R + j\omega(L_1 + L_2) & V_1 \\ j\omega(M - L) & 0 \end{vmatrix} = -V_1 (j\omega(M - L)) = V_1 (j\omega(L - M))$$

$$\text{or } Z_3 = j\omega(L - M) \rightarrow 6$$


$$\therefore Z_1 = R + j\omega(L_1 + M) \rightarrow 7$$

$$I_1 = \Delta_1 / \Delta \quad I_2 = \Delta_2 / \Delta$$

$$Z_2 = R + j\omega(L_2 + L) - j\omega(L - M)$$

$$I_1 / I_2 = \Delta_1 / \Delta_2 = \frac{R + j\omega(L_1 + L_2)}{j\omega(L - M)}$$
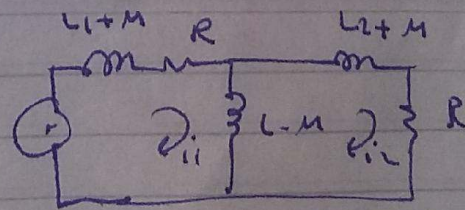
$$\therefore Z_2 = R + j\omega(L_2 + M) \rightarrow 8$$



الماتر المتكافئة