



Sheet (7)... Transient circuits

1. A series RL circuit with $R = 50$ ohms and $L = 10$ H has a constant voltage $V = 100$ v applied at $t = 0$ by the closing of a switch. Find
 - (a) the equations for i , V_R and V_L ,
 - (b) The current at $t = 0.5$ seconds, (c) The time at which $V_R = V_L$.
 - (d) Find the equations for P_R and P_L .
2. In the series circuit shown in Fig.1 the switch is closed on position 1 at $t = 0$, thereby applying the 100 volt source to the RL branch, and at $t = 500$ μ sec the switch is moved to position 2. Obtain the equations for the current in both intervals and sketch the transient.

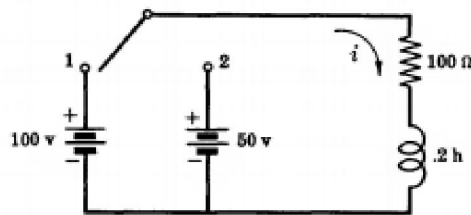


Fig.1

3. A series RL circuit with $R = 50$ ohms and $L = 0.2$ H has a sinusoidal voltage source $v = 150 \sin(500t + \phi)$ applied at a time when $\phi = 0$. Find the complete current.
4. A series RC circuit with $R = 5000$ ohms and $C = 20$ μ f has a constant voltage $V = 100$ v applied at $t = 0$ and the capacitor has no initial charge. Find the equations of i , V_R and V_C .
5. In the RC circuit of Fig. 3 the switch is closed on position 1 at $t=0$ and after 1 TC is moved to position 2. Find the complete current transient.

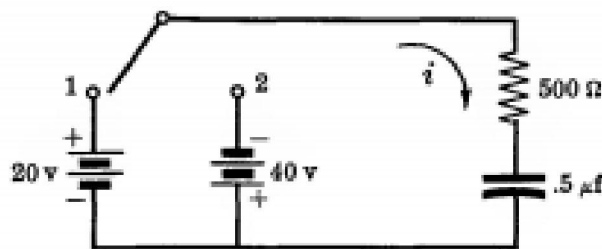


Fig.3



6. In the two-mesh network shown in Fig.4 the switch is closed at $t = 0$. Find the transient mesh currents i_1 and i_2 shown in the diagram, and the transient capacitor voltage V_c .

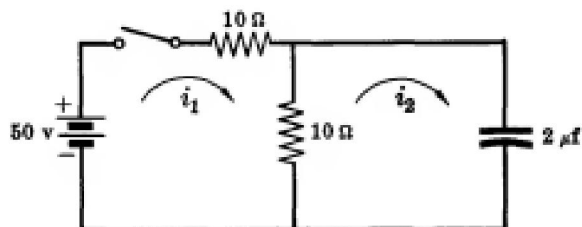


Fig.4

7. A series RC circuit with $R = 100$ ohms and $C = 25 \mu f$ has a sinusoidal voltage source $v = 250 \sin (500t + \varnothing)$ applied at a time when $\varnothing = 0^\circ$. Find the current, assuming there is no initial charge on the capacitor.
8. A series RLC circuit with $R = 3000$ ohms, $L = 10$ h and $C = 200 \mu f$ has a constant voltage $V = 50$ volts applied at $t = 0$. Find the current transient and the maximum value of the current if the capacitor has no initial charge.

Good Luck