

1)




Lec (08) Counters

in a loop je inise to 1 se his koo registers de
ex 1 → 2 → 3 → 4 → 1 , 1 → 3 → 5 → 7 → 1 , etc..

Synchronous Counter) Synchronous counter (Ripple)

ep k ck (ep) F-F) idp - (Synchronous) - 1
ex k, FF n ck n k FF jo ep Ripple = (Asynchronous) - c

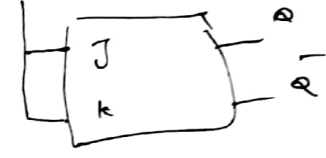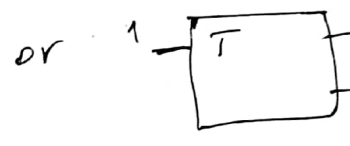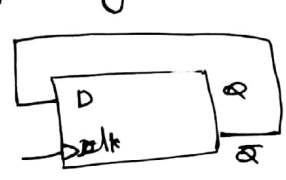[T] A Synchronous (Ripple counter) .. using (toggle; complement Theory)





Complement; Toggle de nste k binary counter) are)
(-ve edge) n, n, n, n FF n ck n n n FF k ep



Ex = Counter → 7 (UP counter) = 3 bit counter (ABC)

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Using T-FF

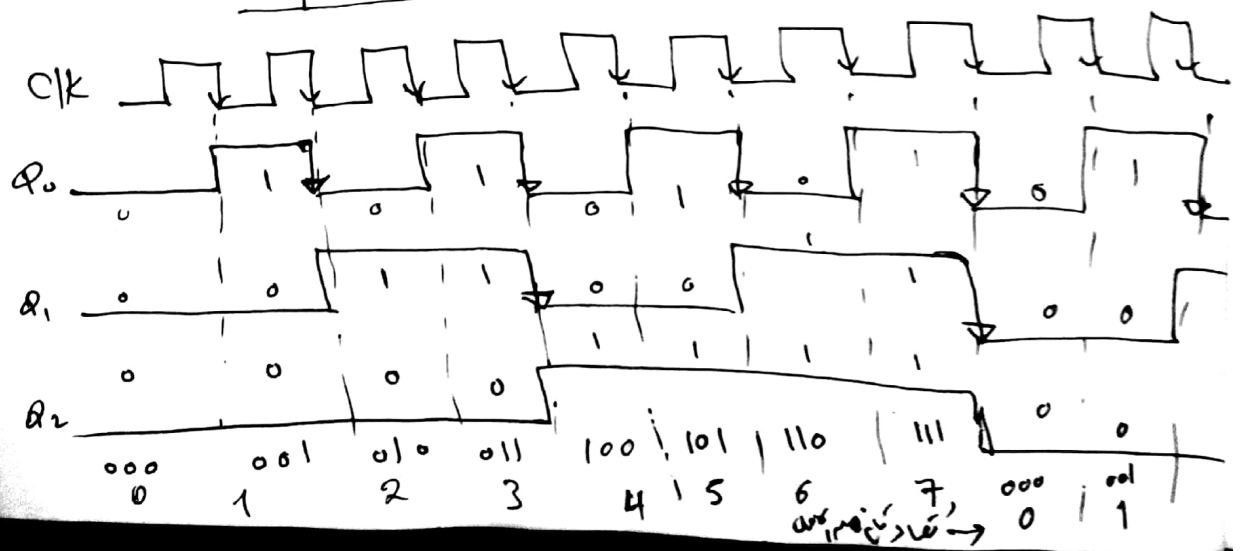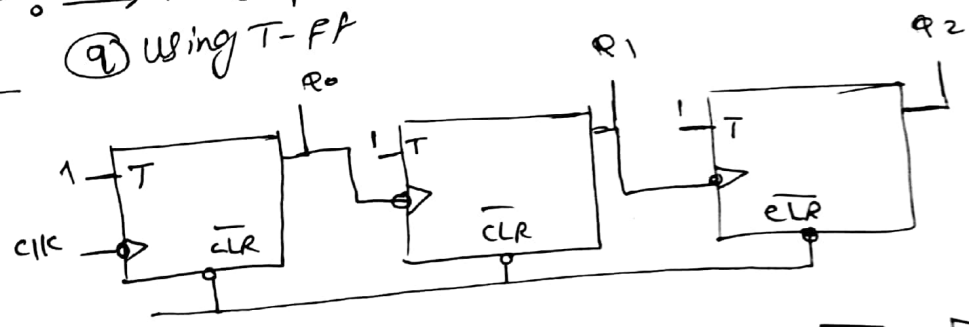


3-bit Counter D-flip flop

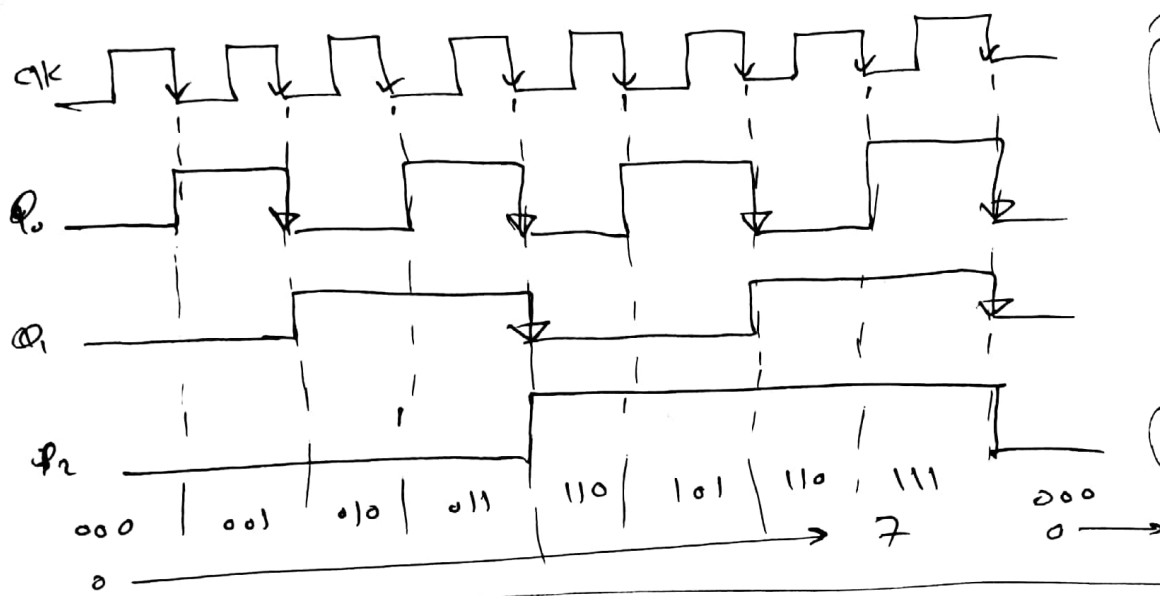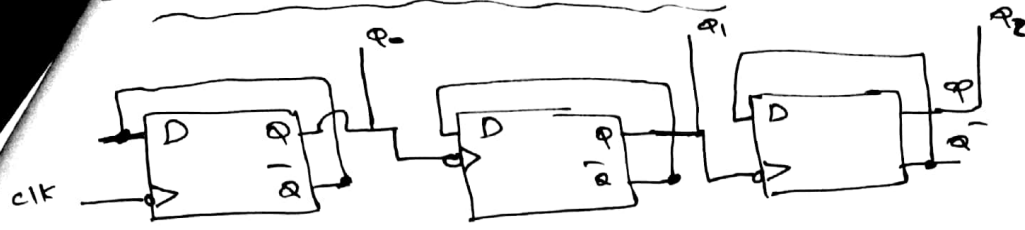


دفعه اولی، دیندره و بعد از آن
 در هر دو بار یک بار تغییر می دهد
 در هر چهار بار یک بار تغییر می دهد

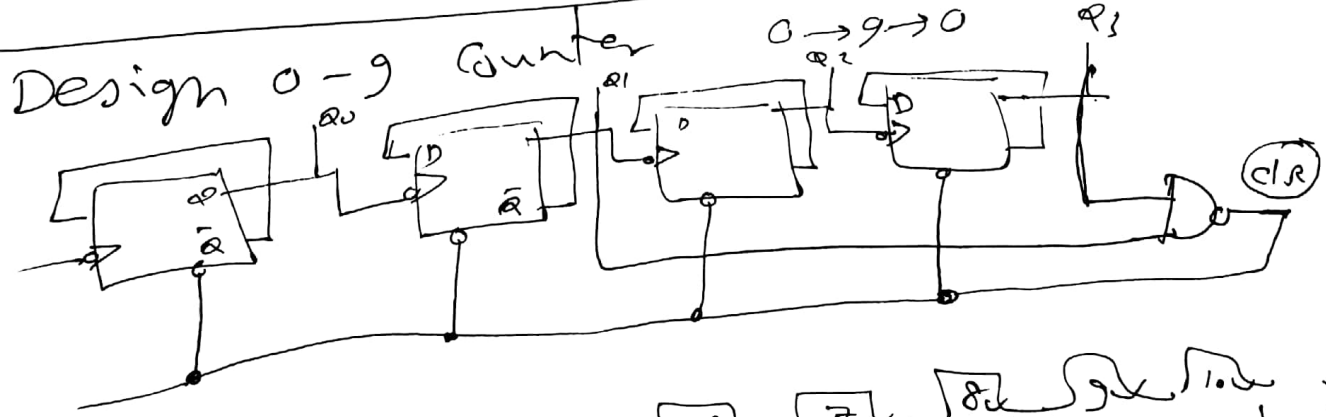لو عازم مداره 0 تا 9 است 4 flip flop که هر یکی 15 بیت
 در هر دو بار یک بار تغییر می دهد و در هر چهار بار یک بار تغییر می دهد



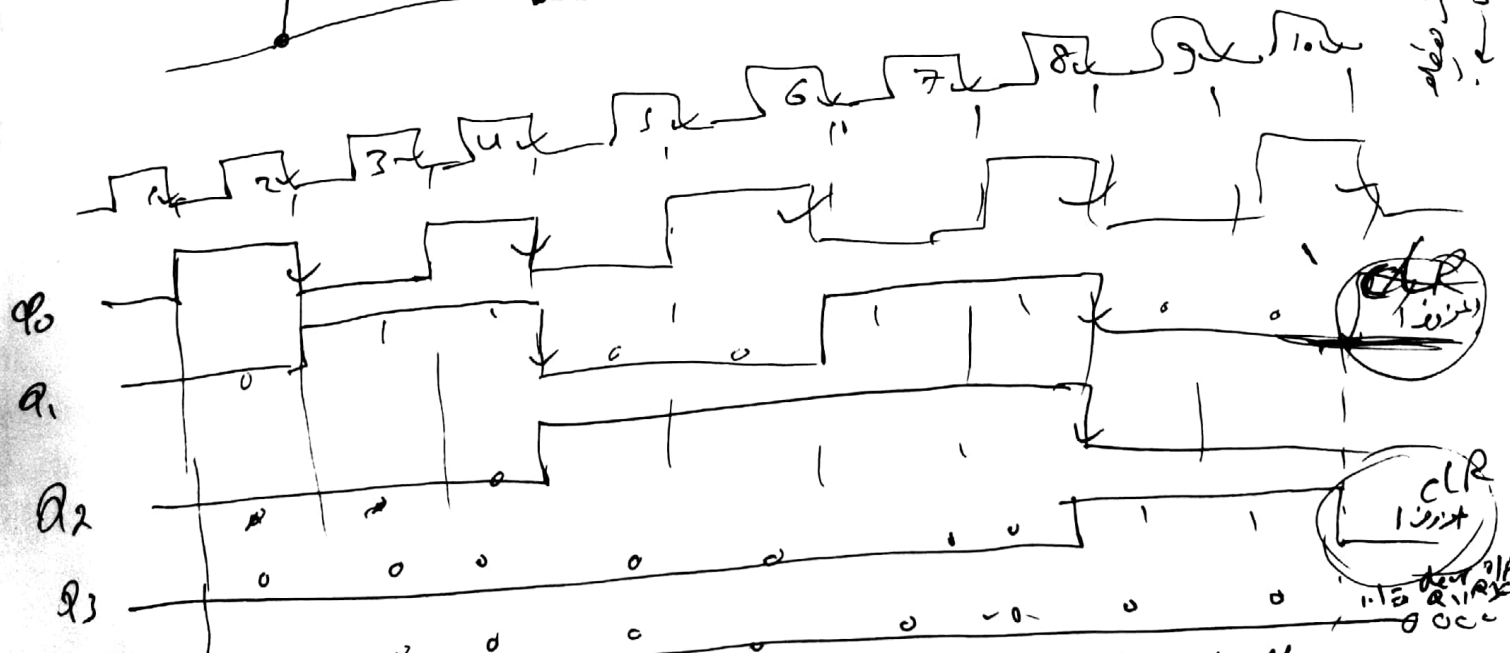
در هر دو بار یک بار تغییر می دهد
 در هر چهار بار یک بار تغییر می دهد



به ترتیب اولی، دیندره و بعد از آن
 در هر دو بار یک بار تغییر می دهد و در هر چهار بار یک بار تغییر می دهد

Analyze 2- Synchronous Counter

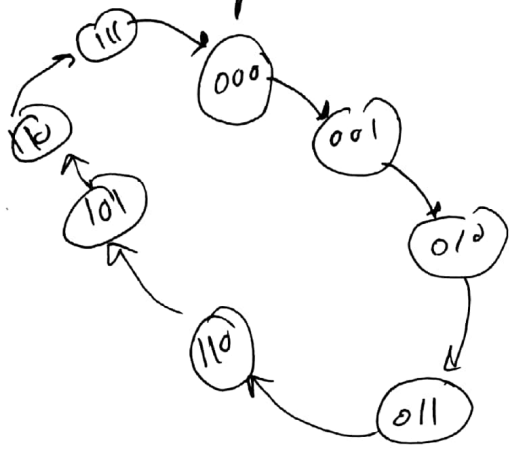Design 3 bit binary counter using T flip flop




Present state	Next state	F.F. input
$Q_2 Q_1 Q_0$	$Q_2^+ Q_1^+ Q_0^+$	$T_{A_2} T_{A_1} T_{A_0}$
0 0 0	0 0 1	0 0 1
0 0 1	0 1 0	0 1 0
0 1 0	0 1 1	0 0 1
0 1 1	1 0 0	1 1 1
1 0 0	1 0 1	0 1 0
1 0 1	1 1 0	0 0 1
1 1 0	1 1 1	1 1 1
1 1 1	0 0 0	1 1 1

$$T_{A_2} = Q_0 Q_1 \bar{Q}_2 + Q_0 Q_1 Q_2$$

$$= Q_0 Q_1 (Q_2 + \bar{Q}_2) = Q_0 Q_1$$

$$T_{A_0} = 1$$


$$T_{A_1} = Q_0$$

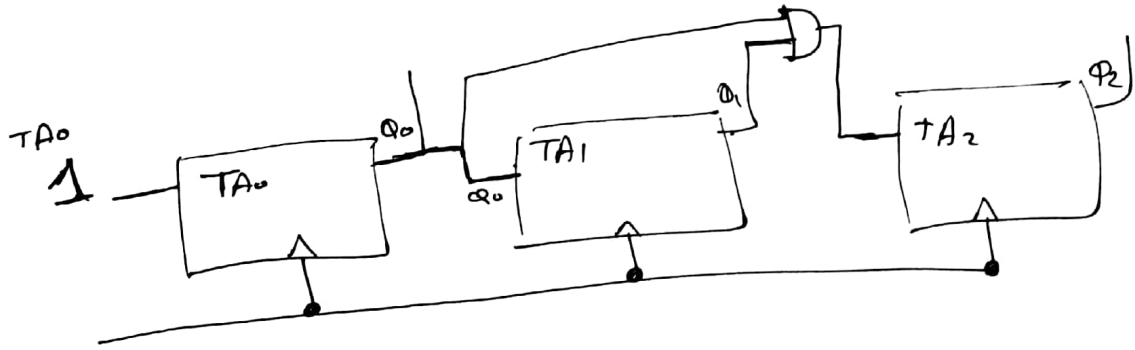

EX Counter with non binary sequence using JK

000 → 001 → 010 → 100 → 101 → 110 → 000

There is un used state (011) (3) *موجود*

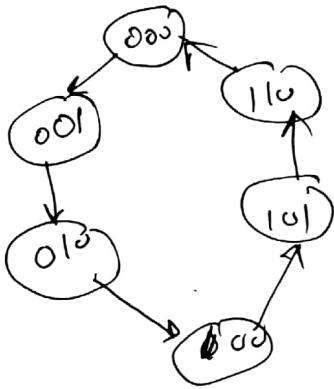

$J_A = 0$
 $K_A = 1$
 $J_B = 0$
 $K_B = 1$

Present state	Next state	F.F inputs		
A B C	A' B' C'	J _A K _A	J _B K _B	J _C K _C
000	001	0 X	0 X	1 X
001	010	0 X	1 X	X 1
010	100	1 X	X 1	0 X
100	101	X 0	0 X	1 X
101	110	X 0	1 X	X 1
110	000	X 1	X 1	0 X

$J_C = 0$
 $K_C = 1$
 Remember excitation table of JK

$J_A = 0, K_A = 1 \Rightarrow$ no change
 $J_A = 0, K_A = 0 \Rightarrow$ Reset
 $\therefore J_A = 0, K_A = X$

Q	Q _{next}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Q	Q _{next}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

for T

Q	Q _{next}	T
0	0	0
0	1	1
1	0	1
1	1	0

for D

Q	Q _{next}	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q_2 \rightarrow Q_1$
 $Q_1 \rightarrow Q_0$
 $Q_0 \rightarrow R$

$\phi_0 = C$
 $\phi_1 = B$
 $\phi_2 = C$

$$J_A = B$$

$$K_A = B$$

$$J_B = \phi_0 + \phi_0 \phi_2 \phi_1 = \phi_0 (\phi_2 \phi_1 + 1)$$

$$K_B = 1$$

$$J_C = \phi_1 \phi_2 + \phi_0 \phi_1 \phi_2$$


$$K_C = 1$$

$$J_C = \phi_0 \phi_1 \phi_2 + \phi_0 \phi_1 \phi_2 = \phi_0 \phi_1 (\phi_2 + \phi_2)$$

$$= \phi_0 \phi_1$$

$$= \phi_0 + \phi_1 = \phi_1$$

$\phi_0 = C$

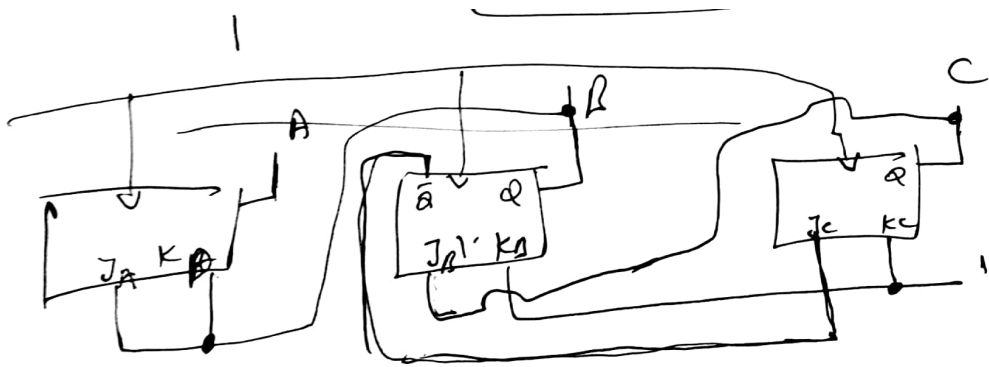


6

3) Analysis of clocked sequential \odot

steps

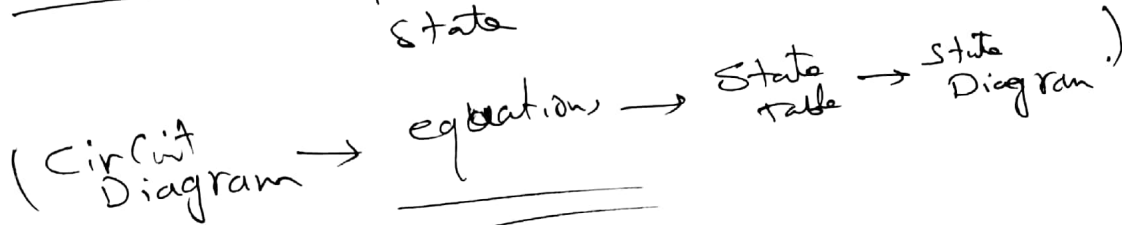
- 1) Determine no. of Flip Flops
- 2) " " " inputs
- 3) " The input eqⁿ for ff (state / transition eqⁿ)
- 4) Draw transition table
Excitation
- 5) Draw State transition Diagram (STD)

* State eqⁿ \Rightarrow specifies the next state as fⁿ of Present state



* state table

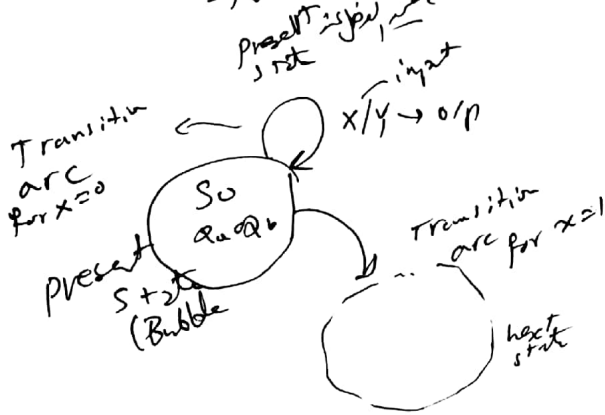
Present state \rightarrow input \rightarrow next state \rightarrow o/p



the behaviour

ex(1)

Analysis of following sequential circuit

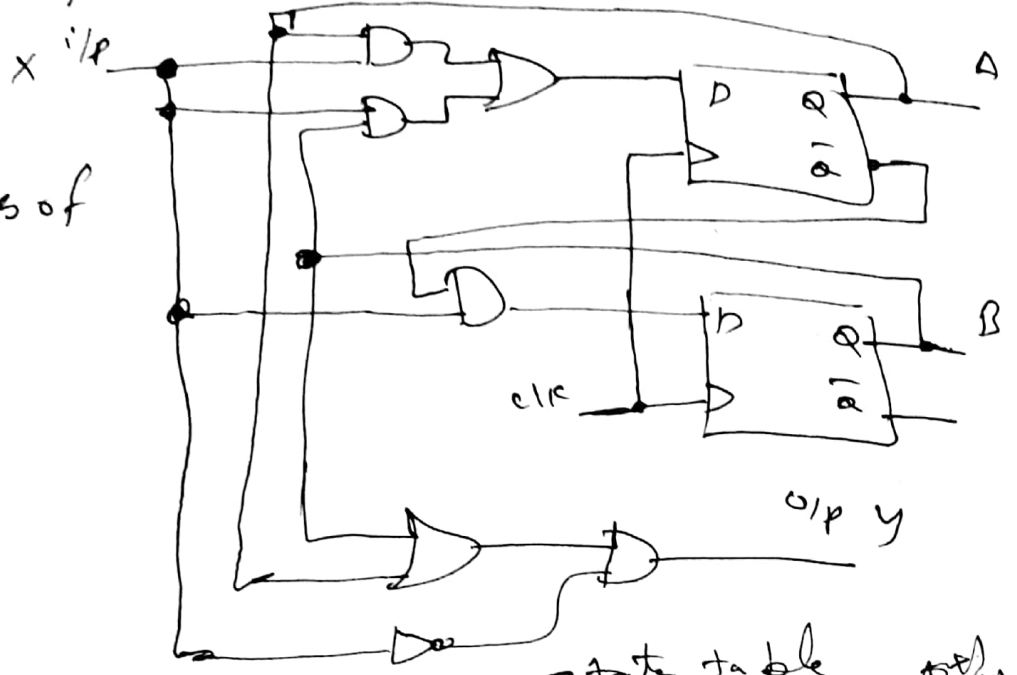

the state = values of all f.f

Example

- AB = 00
- AB = 01
- AB = 10
- AB = 11

1- State eqⁿ

$$A_{next} = D_A = (A \cdot x + x \cdot B)$$

$$B_{next} = D_B = \bar{A} \cdot x$$

$$y_{next} = \bar{x} \cdot (A + B)$$

state table

Present		input	next		o/p
A	B	X	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


Simplified

we can simplify table

Present		X=0		X=1		o/p	
A	B	A	B	A	B	y=0	y=1
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

o/p


③ State Diagram

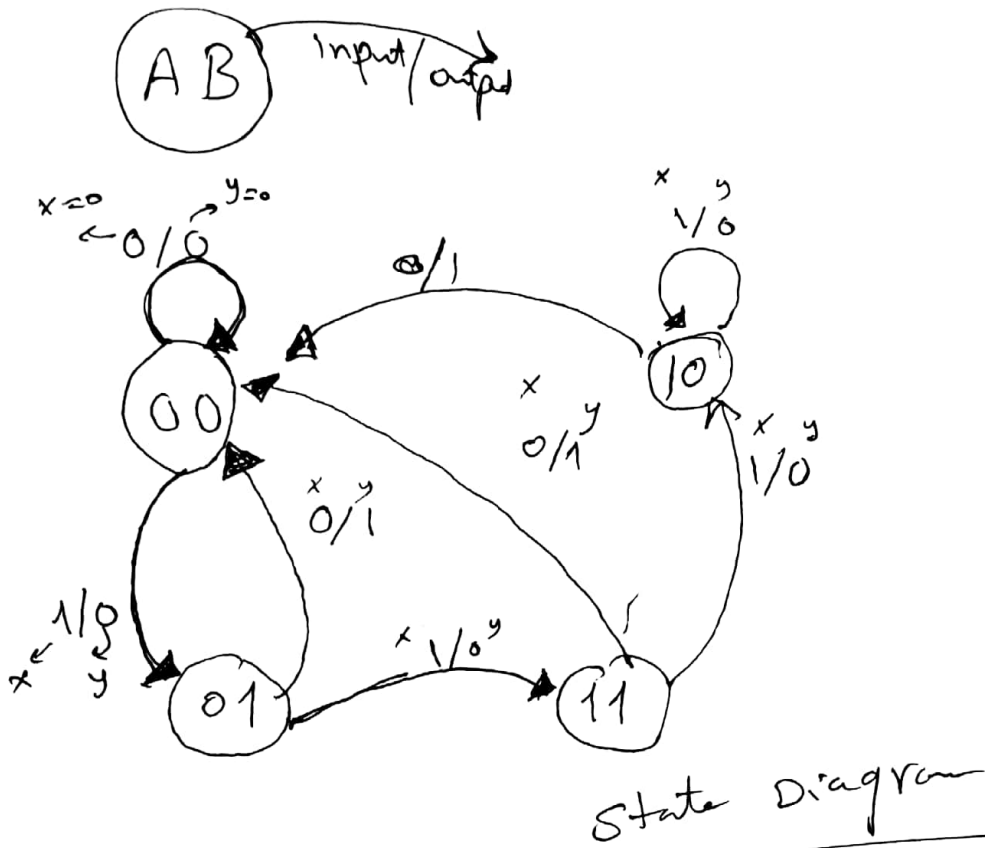

State Diagram


9

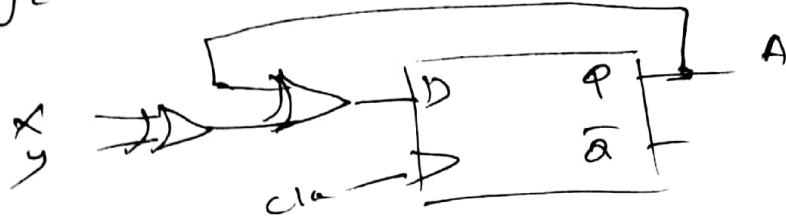Ex(2) Analyze the behaviour of the following circuit?



$$A_{next} = A \oplus (x \oplus y)$$

Present A	i/p		next A
	x	y	
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

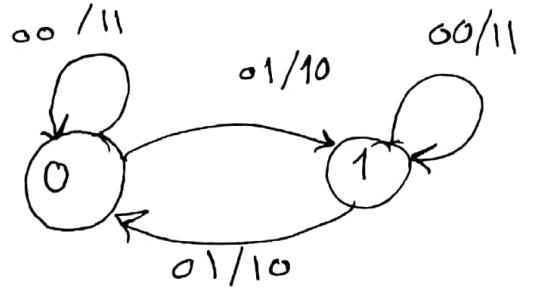

Present	i/p	Next state	o/p (if applicable)

EX 3


10

$$J_A = B$$

$$K_A = B\bar{X}$$

$$J_B = \bar{X}$$

$$K_B = A \oplus X$$

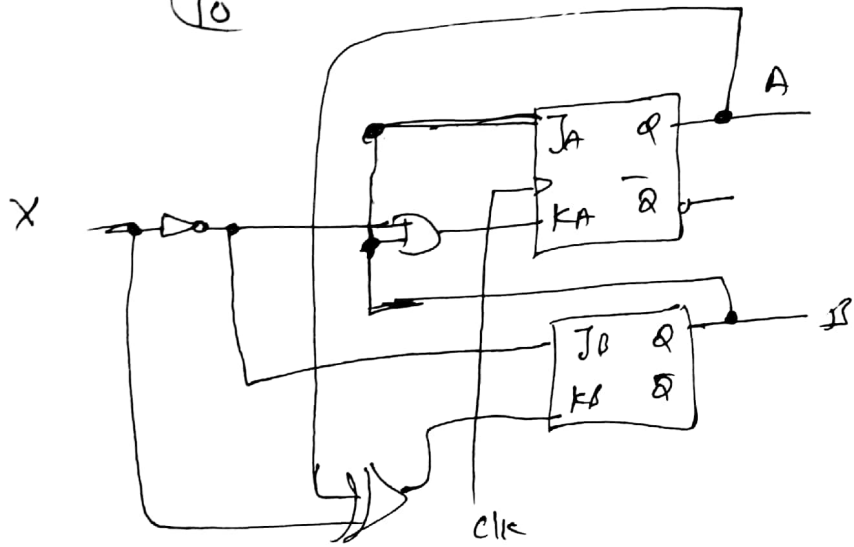


Present		i/p	Next		FF inputs			
A	B	X	A	B	J _A	K _A	J _B	K _B
0	0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0	1
0	1	0	1	1	1	1	1	0
0	1	1	1	0	1	0	0	1
1	0	0	0	0	0	0	0	0
1	0	1	0	1	1	1	1	1
1	1	0	1	1	1	0	0	1
1	1	1	1	0	1	0	0	1

$$A_{next} = \bar{J}_A \bar{Q}_A + \bar{K}_A Q_A$$


$$B_{next} = \bar{J}_B \bar{Q}_B + \bar{K}_B Q_B$$

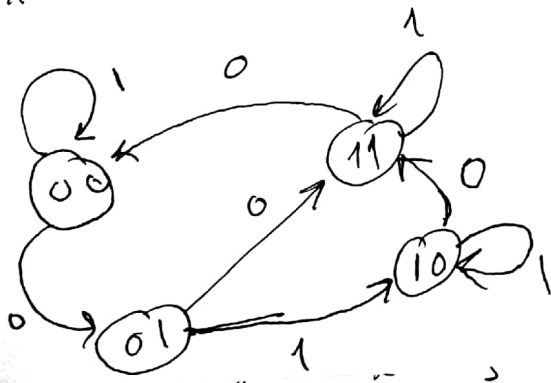$\bar{J}_A = B_{next}$
 $\bar{K}_A = A_{next}$
 $\bar{J}_B = \bar{X}$
 $\bar{K}_B = A_{next}$



no change: 00 to 00, 11 to 11, 10 to 10
 0 = (not present) A next
 0 = A next

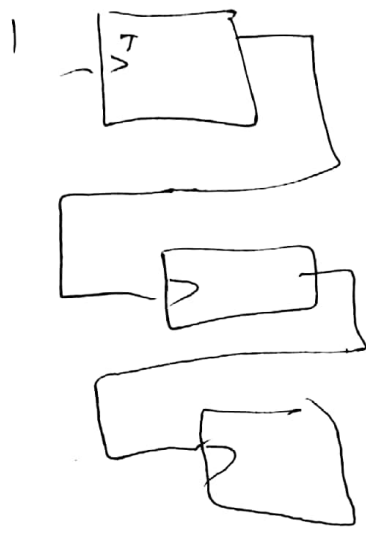Down Counter (1) use +ve edge + Q
 (or) \bar{Q} + (ne) edge



\bar{Q} (clk) \rightarrow +ve edge
 \bar{Q} (clk) \rightarrow +ve edge
 \bar{Q} (clk) \rightarrow +ve edge
 (Q) flip flop

0	1	2	3	4	5	6	7
000	001	010	011	100	101	110	111