



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ELC301
Electronic Engineering

Lecture #4
Transistors


Instructor:
Dr. Moataz Elsherbini

Bipolar Junction Transistor


Agenda

- BJT Structure
- Basic Operation
- Transistor as an Amplifier
- Transistor as a Switch
- DC & AC Analysis

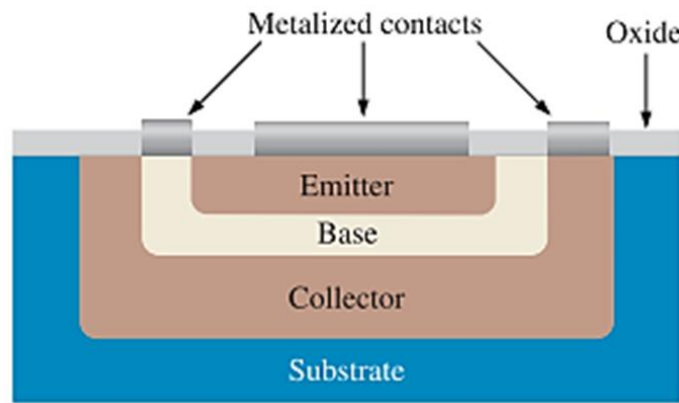
BIPOLAR JUNCTION TRANSISTOR (BJT) STRUCTURE



(a) Basic epitaxial planar structure

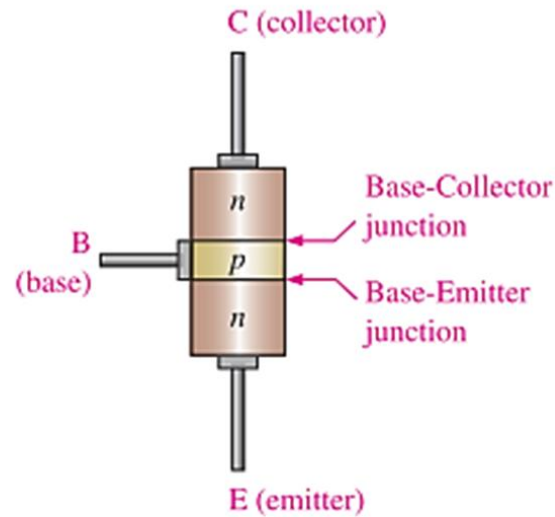


(b) npn

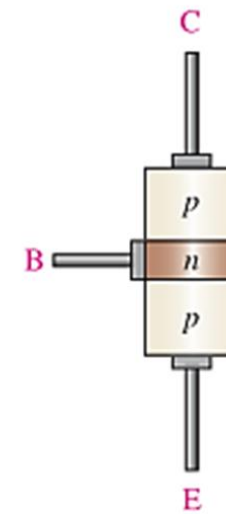


(c) pnp

BJT symbol

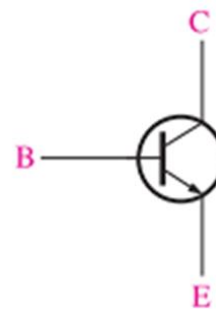



(a) npn

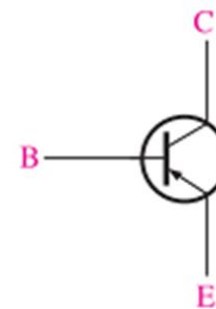



(b) pnp

Transistor Packages


General Purpose

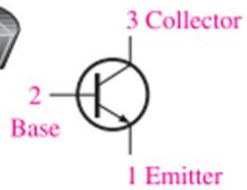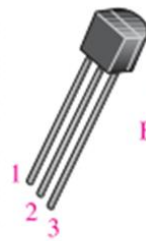

(a) TO-92

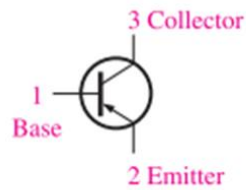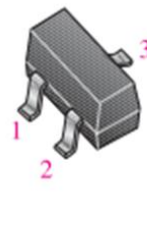


(b) SOT-23


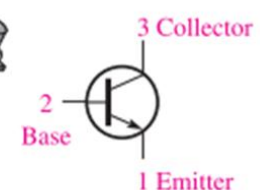


(c) TO-18. Emitter is closest to tab.



Multiple Transistor Package

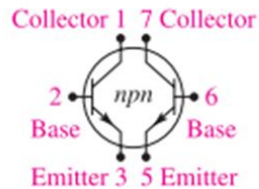

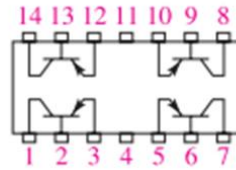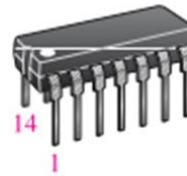(a) Dual metal can. Emitters are closest to tab.




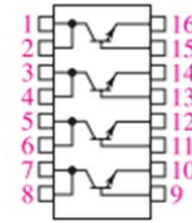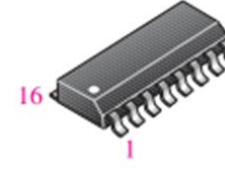(b) Quad dual in-line (DIP) and quad flat-pack. Dot indicates pin 1.




(c) Quad small outline (SO) package for surface-mount technology


Power Transistors

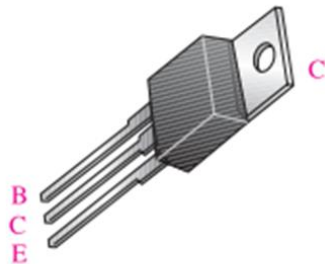


(a) TO-220

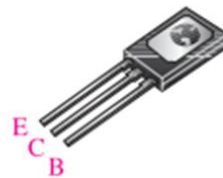

(b) TO-225

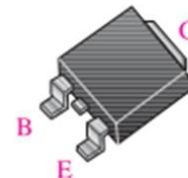


(c) D-Pack

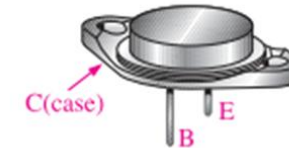

(d) TO-3


Basic Operation

- **Biasing & Operation**

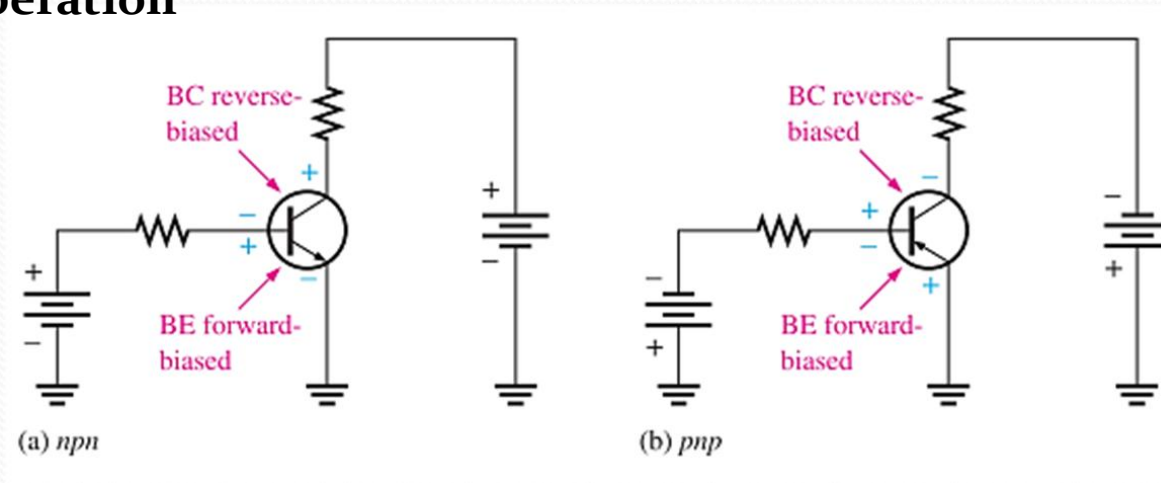

- **Transistor Currents**


$$I_E = I_C + I_B$$

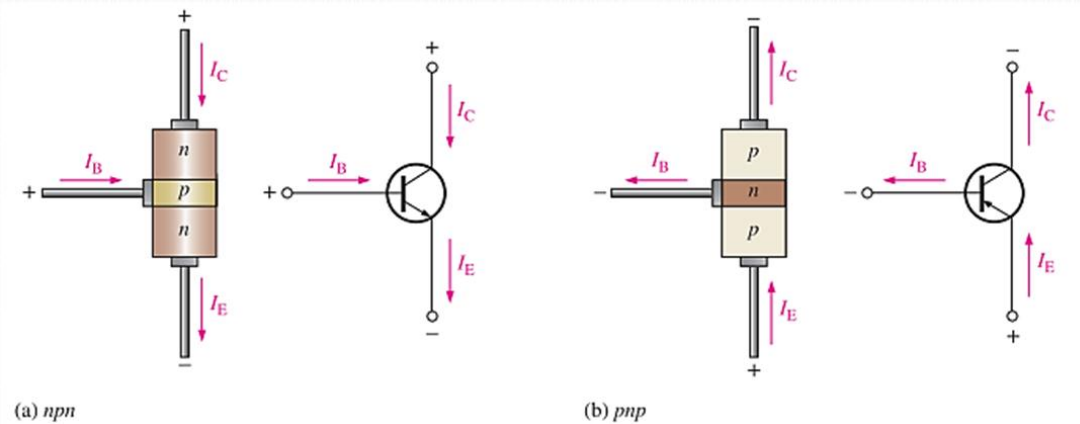

BJT Configurations

Configuration	Input	Output	gain
Common Emitter	Base	Collector	-ve gain
Common Base	Emitter	Collector	+ve gain
Common Collector	Base	Emitter	Unity gain

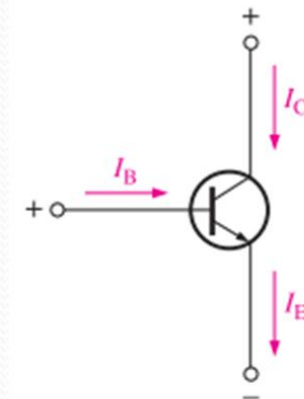- Base terminal can't be output
- Collector terminal can't be input



BJT Parameters

$$\beta_{DC} = \frac{I_C}{I_B}$$

- The dc current gain of a transistor is the ratio of the dc collector current (I_C) to the dc base current (I_B) and is designated dc **beta** (β_{DC}).

$$h_{FE} = \beta_{DC}$$

- Typical values of β_{DC} range from less than 20 to 200 or higher.
- β_{DC} is usually designated as an equivalent hybrid (h) parameter, h_{FE} , on transistor datasheets.

$$\alpha_{DC} = \frac{I_C}{I_E}$$

- The ratio of the dc collector current (I_C) to the dc emitter current (I_E) is the dc alpha (α_{DC}).

Transistor DC Model

I_B : dc base current


I_E : dc emitter current

I_C : dc collector current

V_{BE} : dc voltage at base with respect to emitter

V_{CB} : dc voltage at collector with respect to base

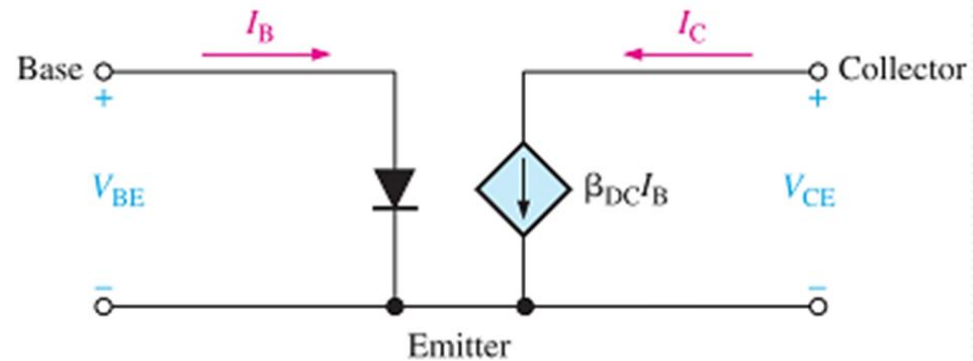V_{CE} : dc voltage at collector with respect to emitter




$$V_{BE} \cong 0.7 \text{ V}$$

$$V_{R_B} = V_{BB} - V_{BE}$$

$$V_{R_B} = I_B R_B$$

$$I_B R_B = V_{BB} - V_{BE}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

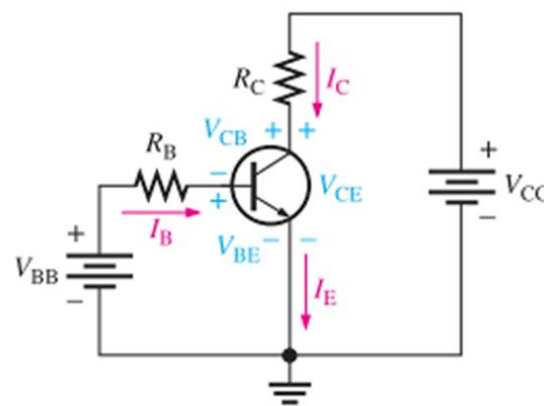

$$V_{CE} = V_{CC} - V_{R_C}$$

$$V_{R_C} = I_C R_C$$

$$I_C = \beta I_B$$




$$V_{CE} = V_{CC} - I_C R_C$$

$$V_{CB} = V_{CE} - V_{BE}$$


Collector characteristic curves

Operation Regions

- Active
- Cut-off
- Saturation

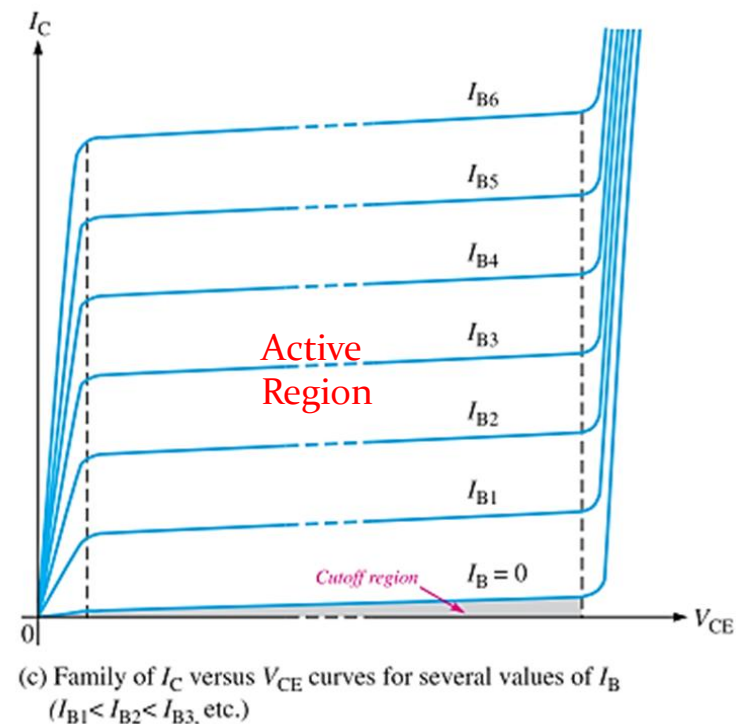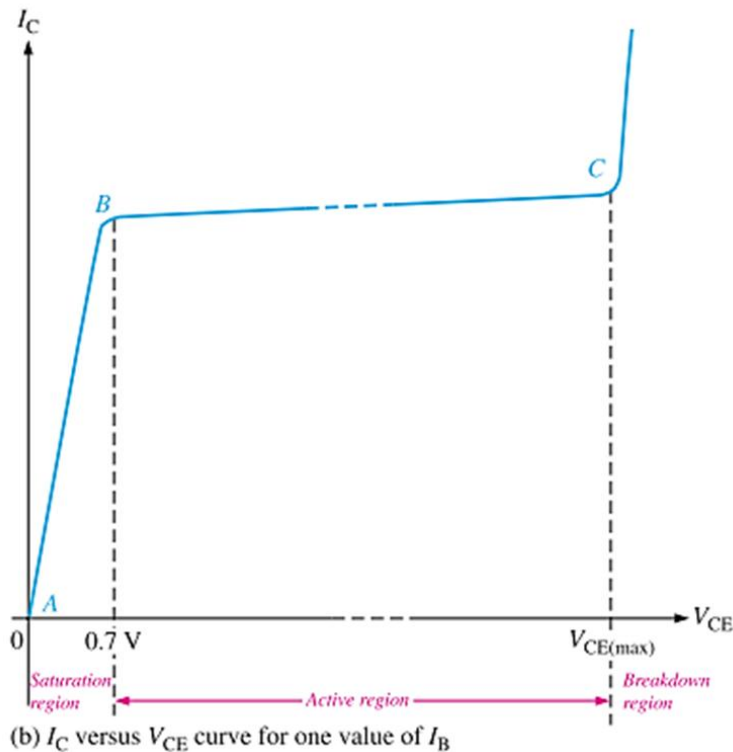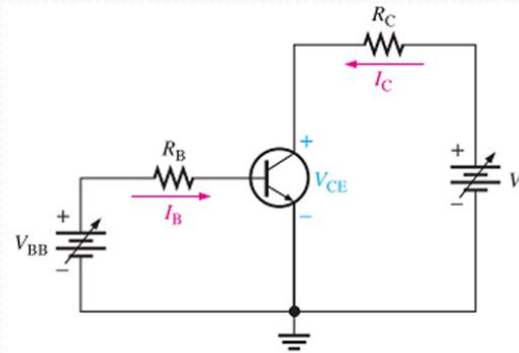

BJT as an Amplifier


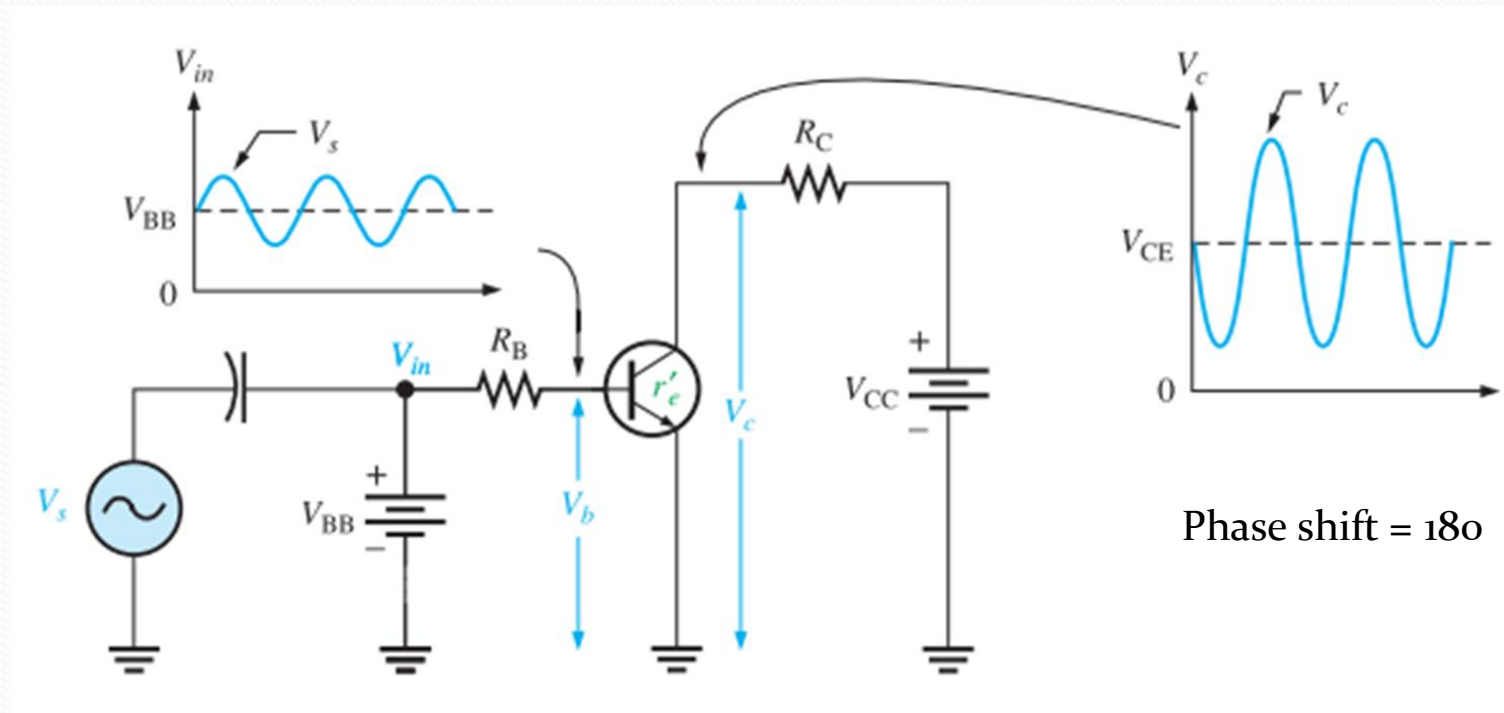


Voltage gain magnitude: $A_v \cong \frac{R_C}{r'_e}$

$$r_e = 26 \text{ mV} / I_E$$

$$I_E = I_C + I_B$$


BJT as a Switch

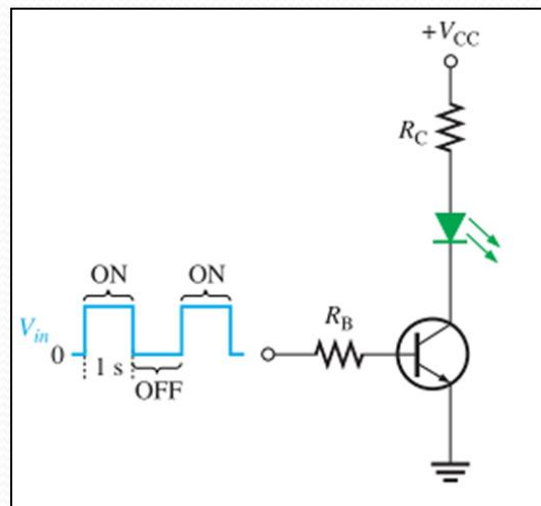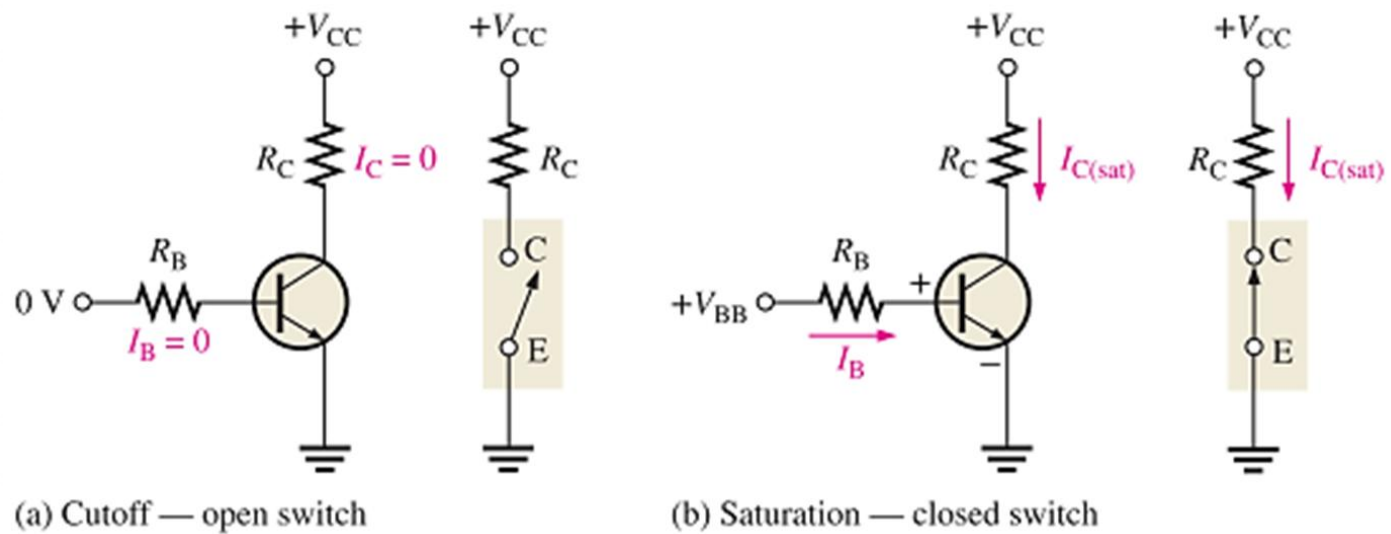



Transistor Bias Circuit

VOLTAGE-DIVIDER BIAS

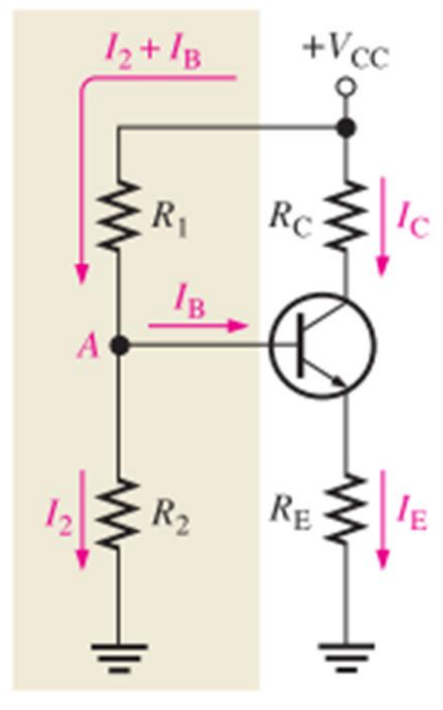

$$V_B \cong \left(\frac{R_2}{R_1 + R_2} \right) V_{CC}$$

$$V_E = V_B - V_{BE}$$

$$I_C \cong I_E = \frac{V_E}{R_E}$$

$$V_C = V_{CC} - I_C R_C$$

$$V_{CE} = V_C - V_E$$



C.E. AC Analysis

- **DC Analysis:**

Capacitors \rightarrow Open Circuit
(See before)

- **AC Analysis:**

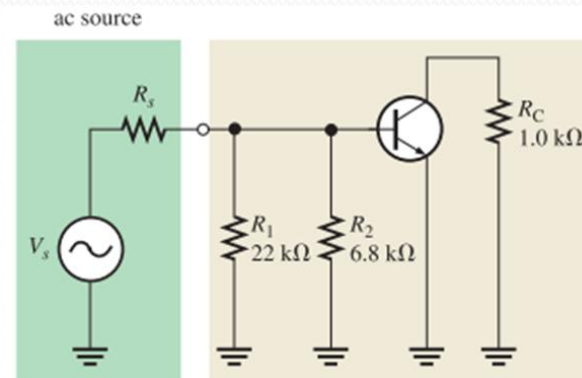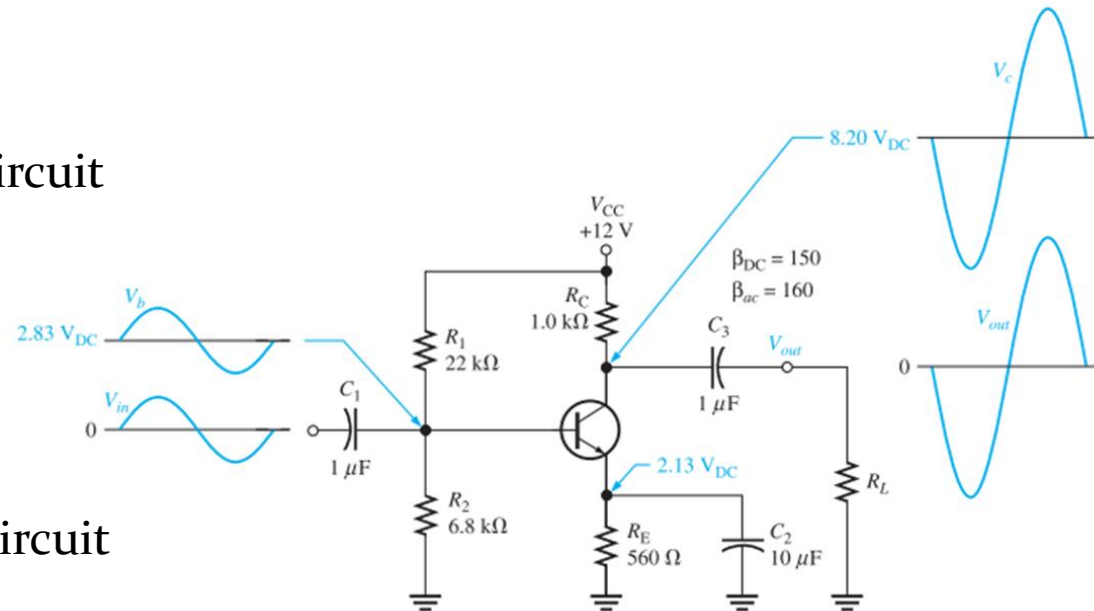Capacitors \rightarrow short Circuit
DC supply \rightarrow ground



AC r-parameter Model

Input resistance

$$R_{in(base)} = \beta_{ac} r'_e$$

Output resistance

$$R_{out} \cong R_C$$

Voltage gain


$$A_v = \frac{R_C}{r'_e}$$

Current gain

$$A_i = \frac{I_c}{I_b} = -A_v \frac{Z_{in}}{R_C}$$

Power gain

$$A_p = A'_v A_i$$

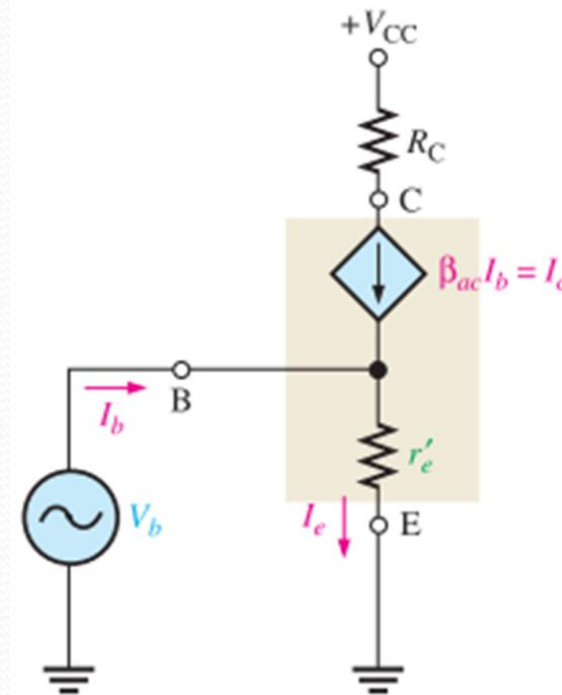


Multistage Amplifier


$$A'_v = A_{v1}A_{v2}A_{v3} \dots A_{vn}$$

$$A_{v(\text{dB})} = 20 \log A_v$$
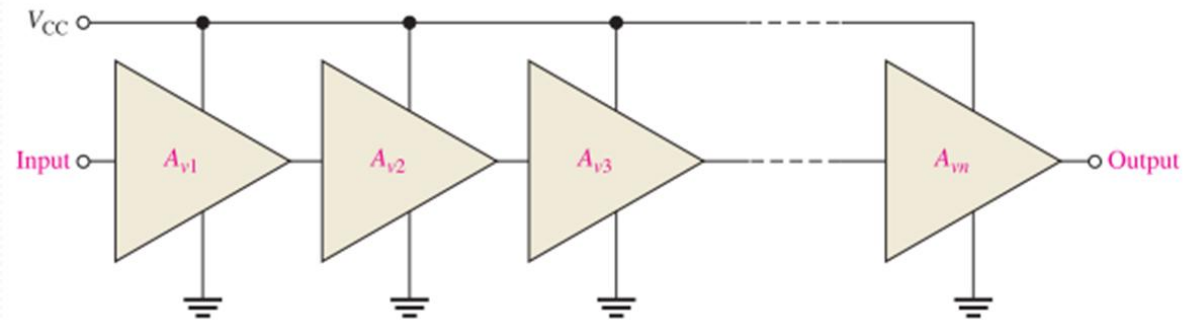
$$A'_{v(\text{dB})} = A_{v1(\text{dB})} + A_{v2(\text{dB})} + \dots + A_{vn(\text{dB})}$$



- A two-stage common-emitter amplifier.

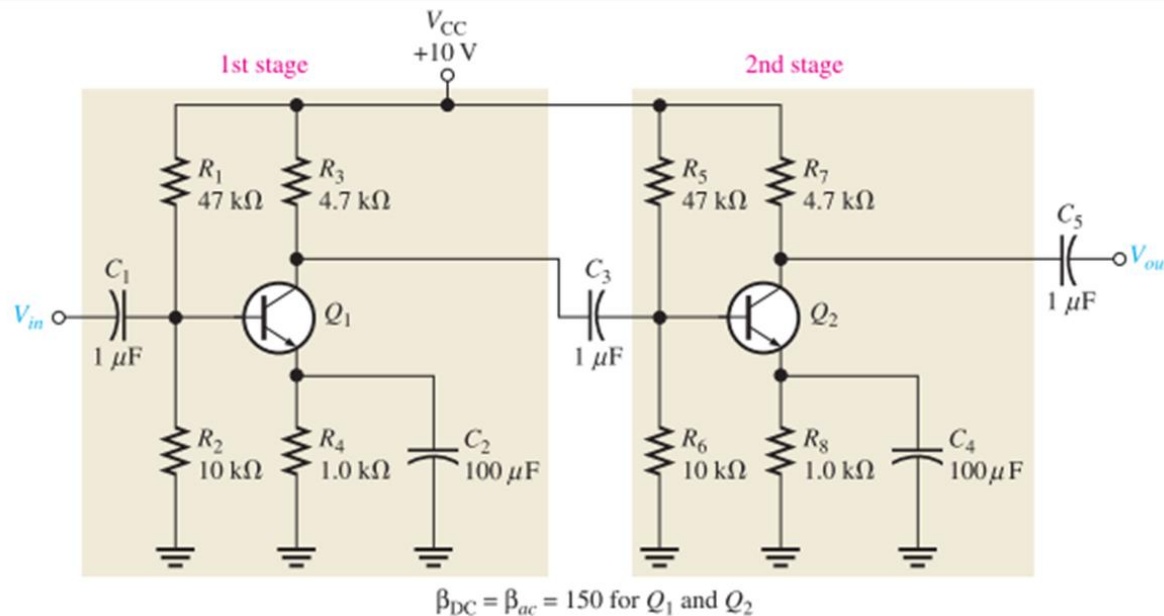

Project

Audio amplifier

TDA 7052
1uF capacitor
Speaker 4 -32 ohm
Audio jack (AUX) mono
Battery 9V
Wires
board

