



BENHA UNIVERSITY
FACULTY OF ENGINEERING AT SHOUBRA

ELC301
Electronic Engineering


Lecture #5
Logic Gates

Instructor:

Dr. Moataz Elsherbini


Logic Gates


Agenda

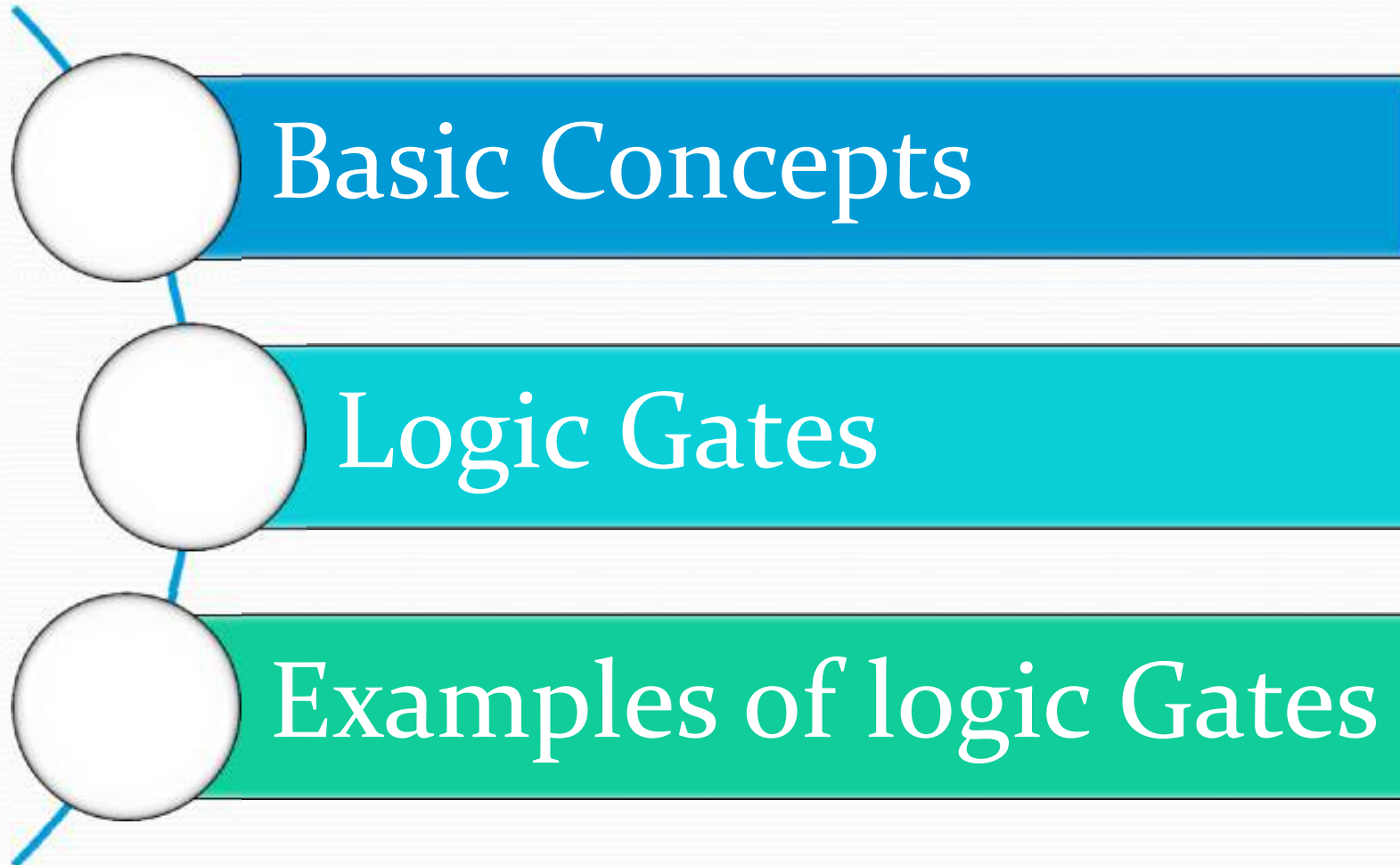- 
- Basic Concepts
 - Logic Gates
 - Examples of logic Gates

- **Digital electronic circuits**, are electronics that represent signals by **discrete** bands of analog **levels**, rather than by continuous ranges (as used in analogue electronics).
- In most cases the number of **states** is **two**.
- They are represented by **two voltage bands**: one near a reference value (typically termed as "**ground**" or zero volts), and the other a value near the **supply** voltage.
- These correspond to the "false" ("**0**") and "true" ("**1**") values of the **Boolean** domain, respectively, yielding **binary** code.

Boolean Algebra	Boolean Logic	Voltage State
Logic "1"	True (T)	High (H)
Logic "0"	False (F)	Low (L)

- 
- A digital circuit is often constructed from small electronic circuits called **logic gates** that can be used to create combinational logic.
 - Each logic gate represents a **function of boolean logic**.
 - A logic gate is an arrangement of electrically controlled switches, better known as **transistors**.
 - Logic gates often use the **fewest number of transistors** in order to reduce their size, power consumption and cost, and increase their reliability.
 - **Integrated circuits** are the **least expensive** way to make logic gates in large volumes. Integrated circuits are usually designed by engineers using electronic design automation software

- 
- Binary variables take on one of two values.
 - Logical operators operate on binary values and binary variables.
 - Basic logical operators are the logic functions AND, OR and NOT.
 - Logic gates implement logic functions.
 - Boolean Algebra: a useful mathematical system for specifying and transforming logic functions.
 - We study Boolean algebra as a foundation for designing and analyzing digital systems!

Binary Variables

- Recall that the two binary values have different names:
 - True/False
 - On/Off
 - Yes/No
 - 1/0
- We use 1 and 0 to denote the two values.
- Variable identifier examples:
 - A, B, y, z, or X_1 for now
 - RESET, START_IT, or ADD₁ later

Logical Operations

- The three basic logical operations are:
 - AND
 - OR
 - NOT
- AND is denoted by a dot (\cdot).
- OR is denoted by a plus ($+$).
- NOT is denoted by an over bar ($\bar{\quad}$), a single quote mark ($'$) after.

Notation Examples

- Examples:
 - $Y=A.B$ is read “Y is equal to A AND B.”
 - $z = x+y$ is read “z is equal to x OR y.”
 - $X = \bar{A}$ is read “X is equal to NOT A.”
- Note: The statement:
 - $1 + 1 = 2$ (read “one plus one equals two”)is not the same as
 - $1 + 1 = 1$ (read “1 or 1 equals 1”).

Operator Definitions

- Operations are defined on the values "0" and "1" for each operator:

AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

NOT

$$\bar{0} = 1$$

$$\bar{1} = 0$$

Buffer

$$0 = 0$$

$$1 = 1$$

Logic Function Implementation

- **Using Switches**

- **Inputs:**

- logic 1 is switch closed
 - logic 0 is switch open


- **Outputs:**

- logic 1 is light on
 - logic 0 is light off.


- **NOT input:**

- logic 1 is switch open
 - logic 0 is switch closed


Switches in parallel => OR

 

Switches in series => AND

 


Normally-closed switch => NOT

 


NOT Gate -- Inverter

If A is NOT true, then Q is true

- The Logic NOT Gate Truth Table

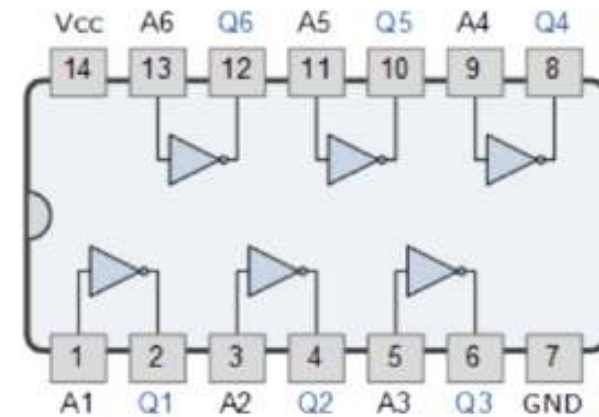

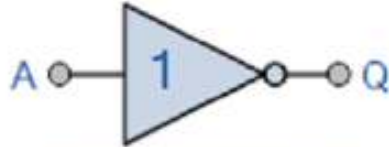
Symbol	Truth Table	
 Inverter or NOT Gate	A	Q
	0	1
	1	0
Boolean Expression $Q = \text{not } A$ or \bar{A}	Read as inverse of A gives Q	

OR Gate


If either A or B is true, then Q is true

- 2-input Transistor OR Gate
- The 2-input Logic OR Gate

B	A	OUT
0	0	0
0	1	1
1	0	1
1	1	1

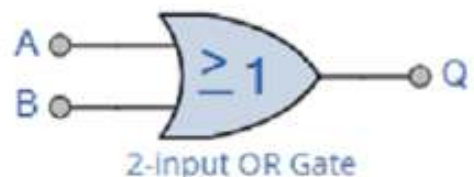
Symbol	Truth Table		
 <p>2-input OR Gate</p>	B	A	Q
	0	0	0
	0	1	1
	1	0	1
	1	1	1
Boolean Expression $Q = A+B$	Read as A OR B gives Q		


The 3-input Logic OR Gate

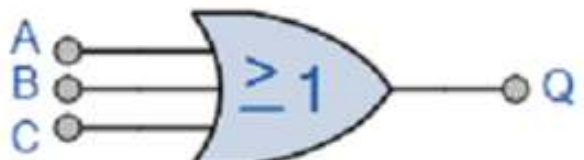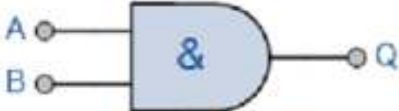Symbol	Truth Table			
 <p>3-Input OR Gate</p>	C	B	A	Q
	0	0	0	0
	0	0	1	1
	0	1	0	1
	0	1	1	1
	1	0	0	1
	1	0	1	1
	1	1	0	1
	1	1	1	1
Boolean Expression $Q = A+B+C$	Read as A OR B OR C gives Q			


AND Gate

If both A and B are true, then Q is true


Symbol	Truth Table		
 <p>2-input AND Gate</p>	B	A	Q
	0	0	0
	0	1	0
	1	0	0
	1	1	1
Boolean Expression $Q = A.B$	Read as A AND B gives Q		

Symbol	Truth Table			
 <p>3-input AND Gate</p>	C	B	A	Q
	0	0	0	0
	0	0	1	0
	0	1	0	0
	0	1	1	0
	1	0	0	0
	1	0	1	0
	1	1	0	0
	1	1	1	1
	Boolean Expression $Q = A.B.C$	Read as A AND B AND C gives Q		


NOR Gate

 

2-input "OR" gate plus a "NOT" gate

 

NAND Gate

 


2-input "AND" gate plus a "NOT" gate




NOR & NAND Universal Gate

 
- Any gate can be constructed using them.




OR gate

 


AND gate

 


NOT gate

 

AND gate

 

OR gate

 

NOT gate

Example of a Logic Function

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- Logical expression form

$$F = AB + BC + AC$$

