




BENHA UNIVERSITY  
FACULTY OF ENGINEERING AT SHOUBRA

ELC301  
Electronic Engineering

Lecture #6  
Operational Amplifiers


**Instructor:**  
**Dr. Moataz Elsherbini**

# Operational Amplifiers & Applications

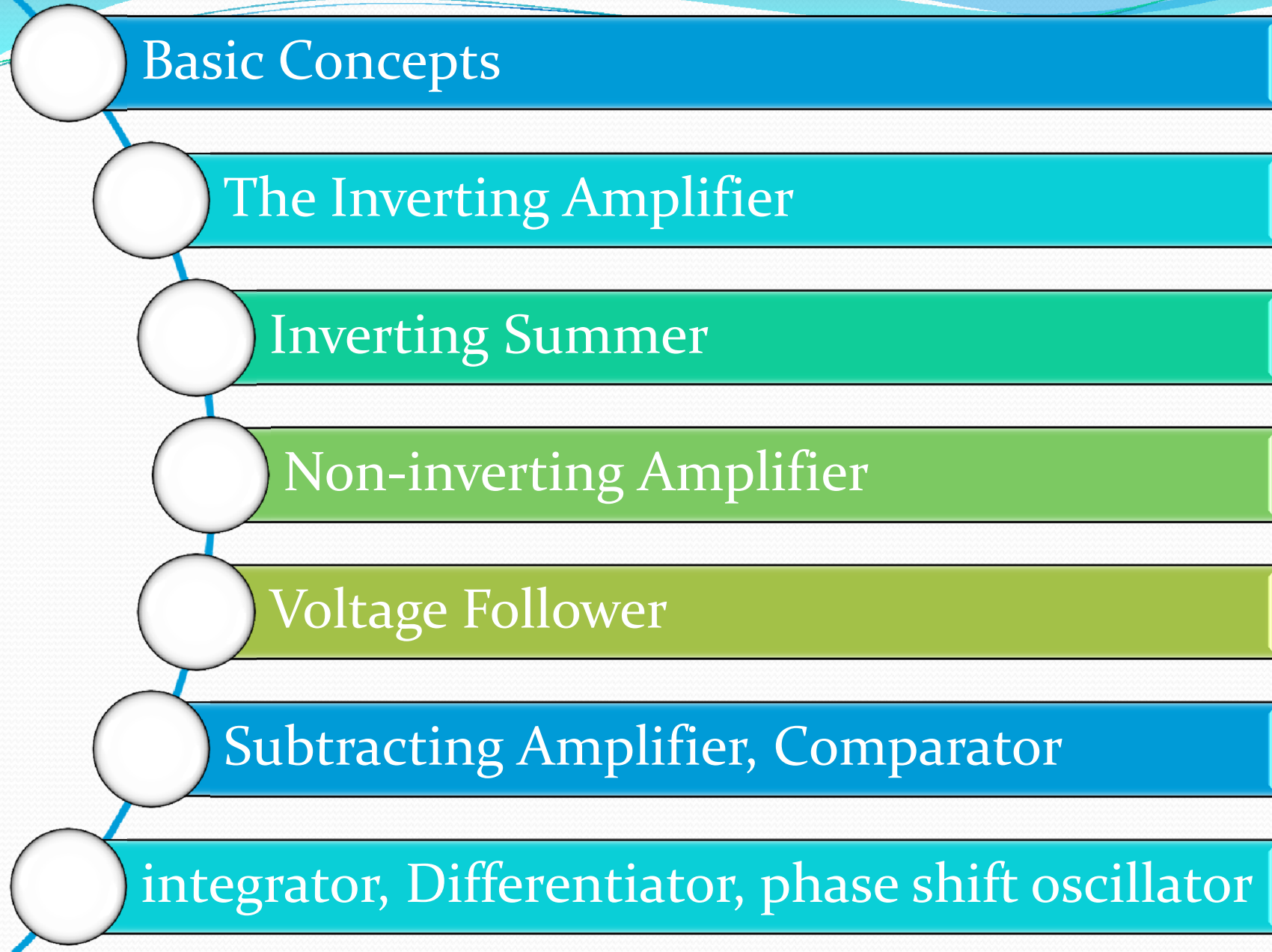

# Op Amp


## Symbol

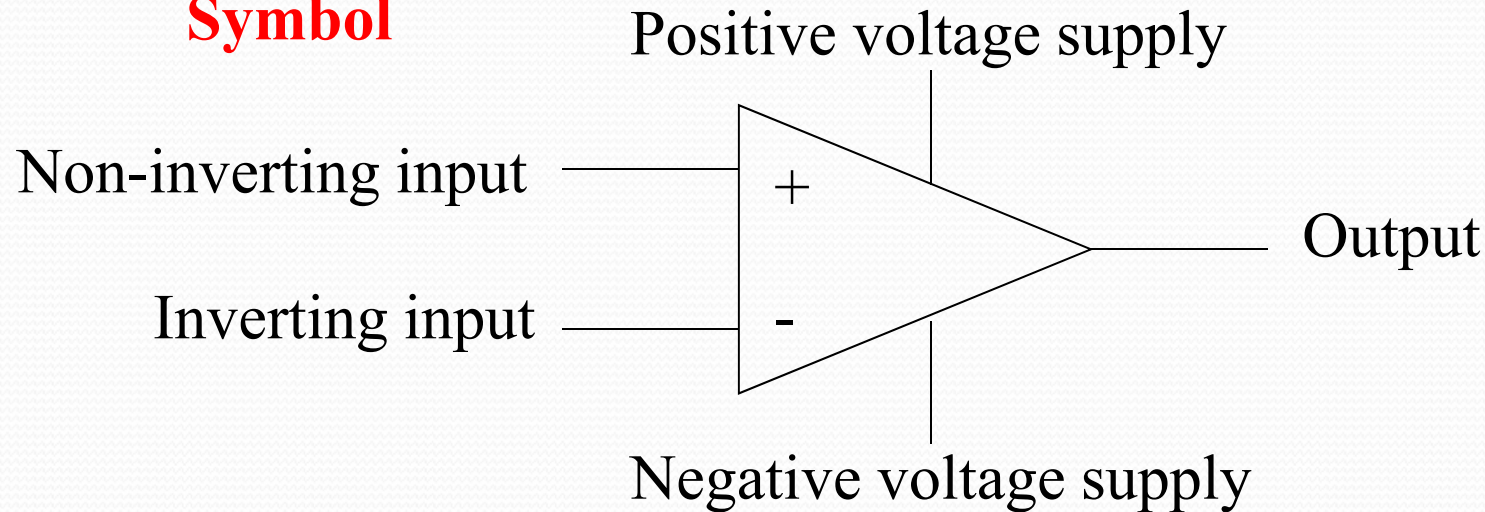


- At a minimum, op amps have 3 terminals: 2 input and 1 output.
- An op amp also requires dc power to operate. Often, the op amp requires both positive and negative voltage supplies ( $V_+$  and  $V_-$ ).

# Op Amp

## Symbol

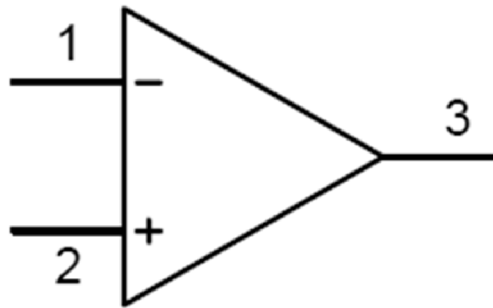

op amp symbol  
(we will use most often)

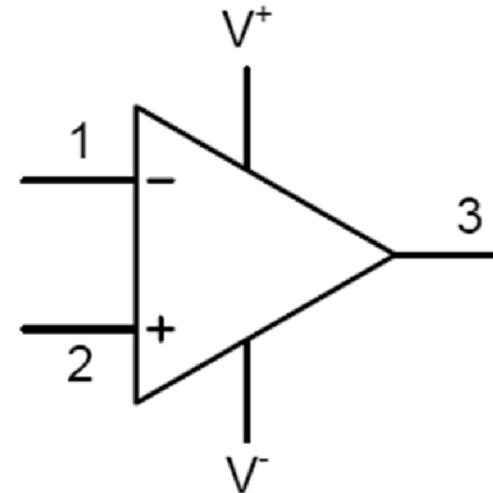

op amp symbol  
with power supply connections

- One of the input terminals (1) is called an inverting input terminal denoted by ‘-’
- The other input terminal (2) is called a non-inverting input terminal denoted by ‘+’



# Op Amp Applications

# 1-The Inverting Amplifier

- Feedback reduces the gain of op-amp
- The positive input is grounded.

$$V^+ = 0$$


$$V^+ = V^-$$

$$i_s = i_2$$


$$\frac{V_s - V^-}{R_1} = \frac{V^- - V_o}{R_2}$$

$$\frac{V_s}{R_1} = \frac{-V_o}{R_2}$$

$$\frac{V_o}{V_s} = \frac{-R_2}{R_1}$$

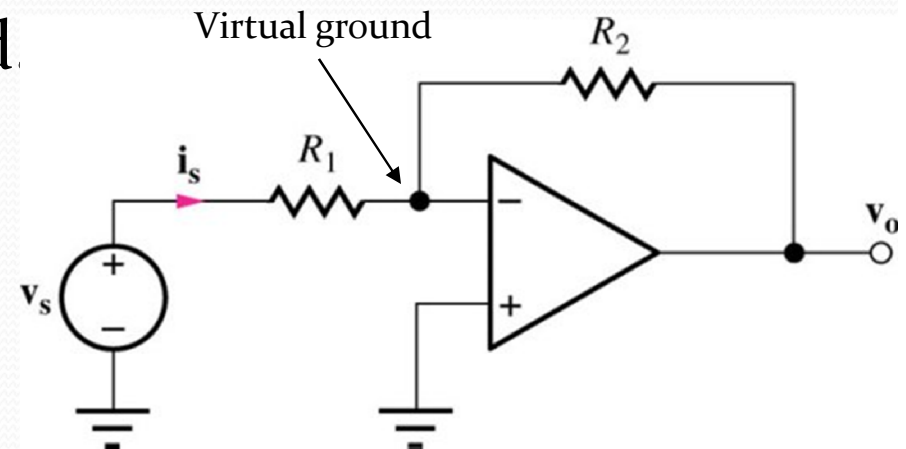

## 2-Inverting Summer

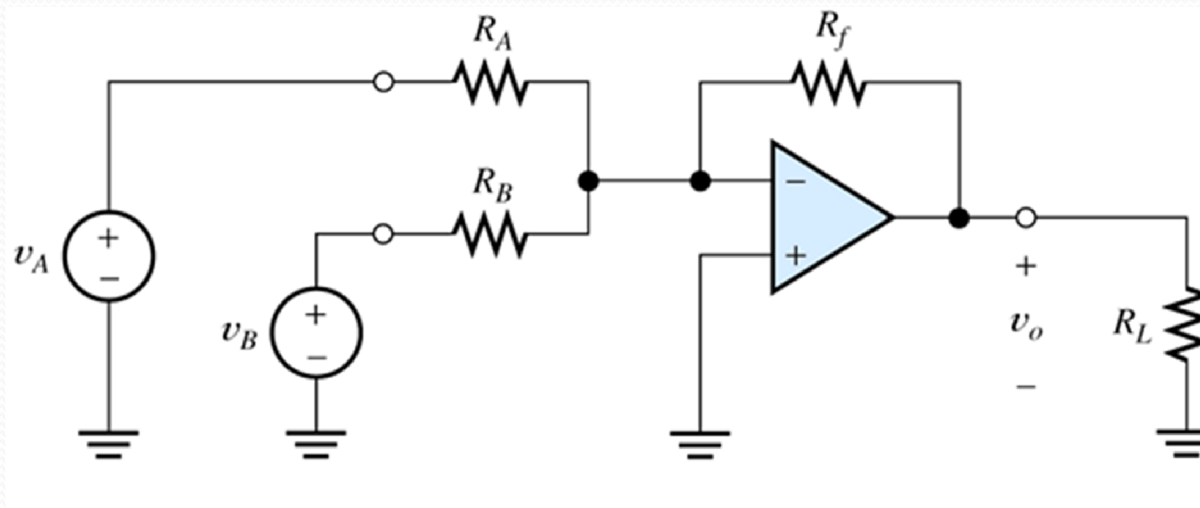

$$V_o = -\left(\frac{R_f}{R_A} V_A + \frac{R_f}{R_B} V_B\right)$$



# 3-Non-inverting Amplifier

$$V^- = v_i$$

$$V^+ = V^- = v_i$$


$$i_1 = i_2$$

$$\frac{0 - V^+}{R_1} = \frac{V^+ - V_o}{R_2}$$

$$v_i \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{V_o}{R_2}$$

$$\frac{V_o}{v_i} = R_2 \left( \frac{1}{R_1} + \frac{1}{R_2} \right)$$
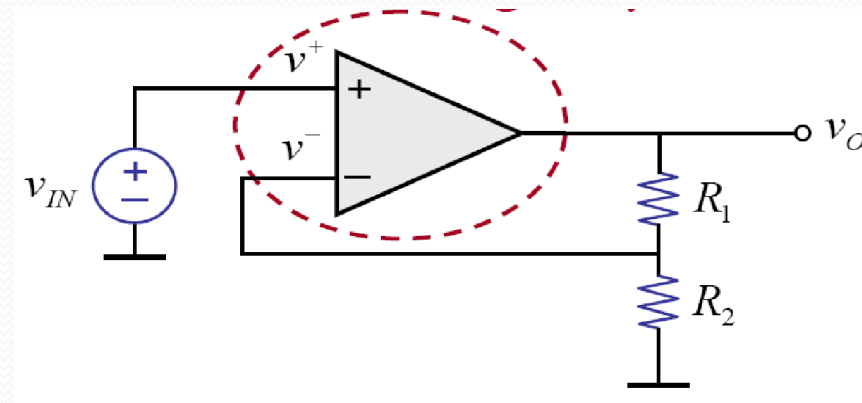
$$\frac{V_o}{v_i} = \left( 1 + \frac{R_2}{R_1} \right)$$



# 4- Unity Follower (Voltage Follower)

$$V^+ = v_i$$

$$V^+ = V^- = v_i$$

$$V^- = v_o$$

$$v_o = v_i$$



voltage gain = 1

$$V^- = v_i$$


$$V^+ = V^- = v_i$$

$$V^+ = v_o$$

$$v_o = v_i$$

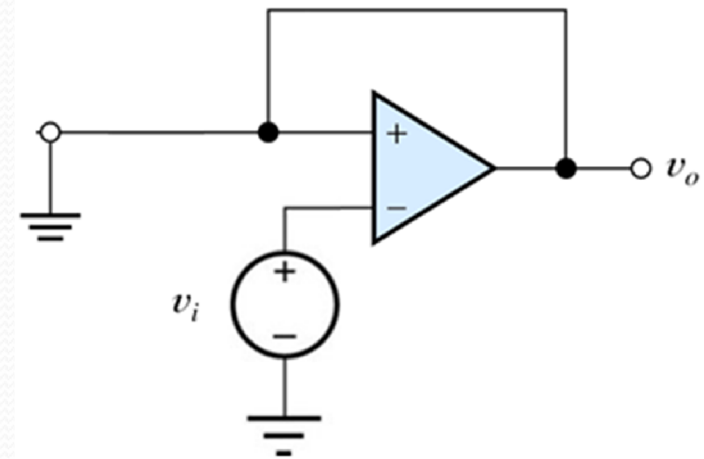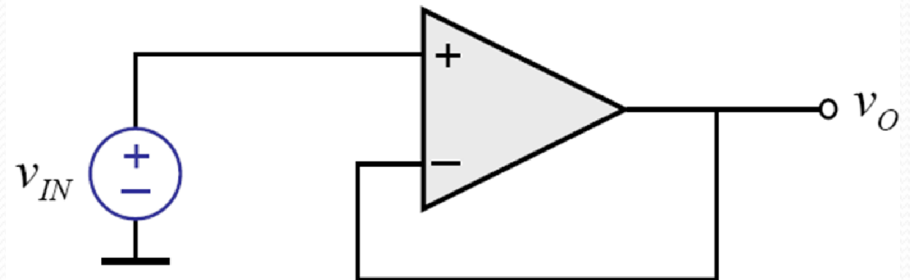
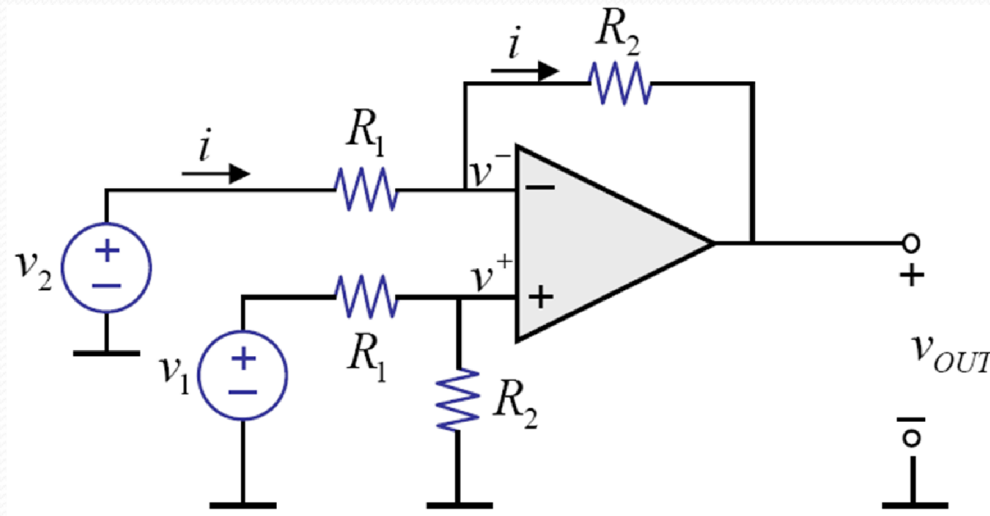
# 5- Differential (Subtracting) Amplifier




$$v_{out} = \frac{R_2}{R_1} (v_1 - v_2)$$

If  $R_2 = R_1$

$$v_{out} = (v_1 - v_2)$$

# 6- Comparator

- Without feedback connection

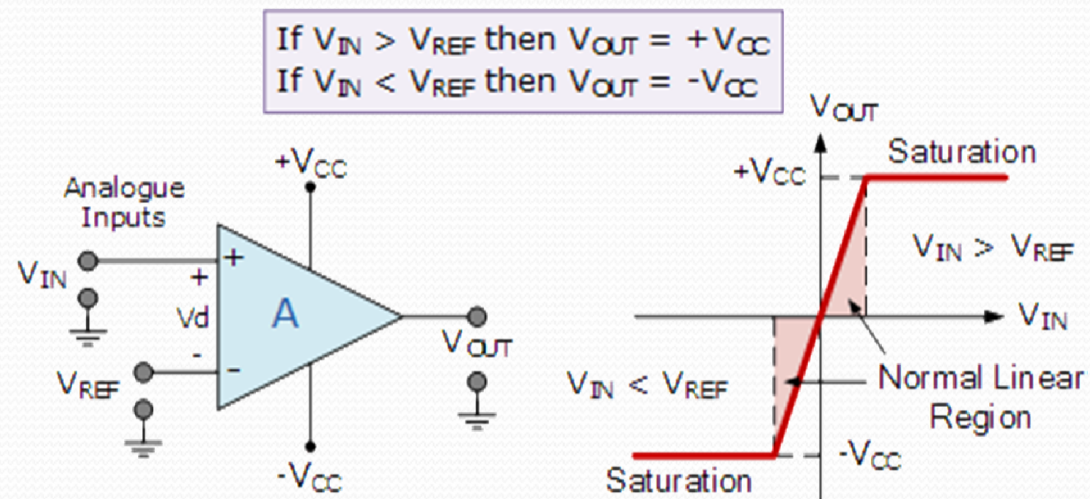


- if*

$$V_{IN} > V_{REF} \quad \text{Then } V_o = +V_{CC}$$


$$V_{IN} < V_{REF} \quad \text{Then } V_o = -V_{CC}$$

# 7- Integrator Amplifier

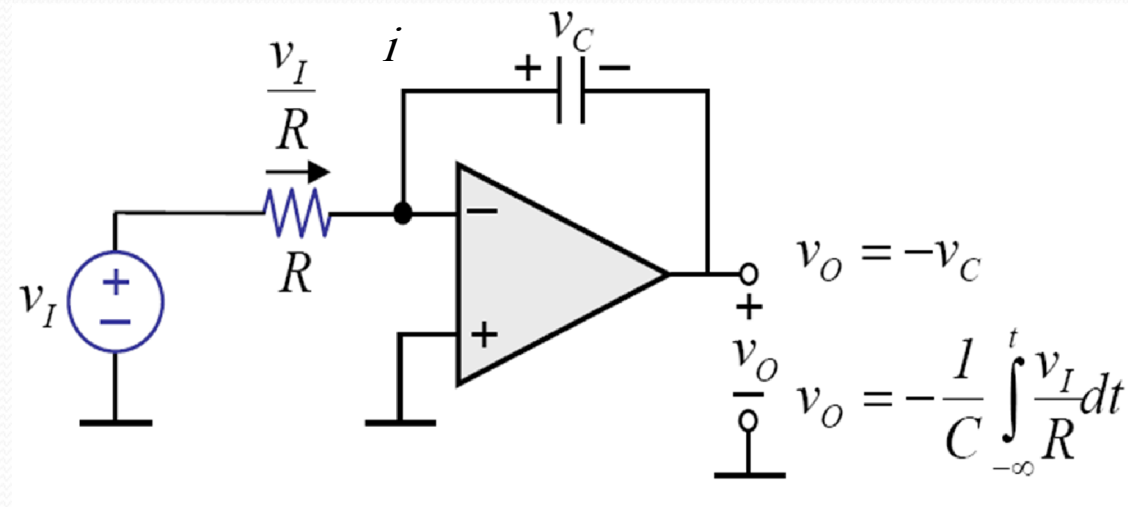


$$V_o = -\frac{1}{RC} \int v_I dt$$

# 8- Differentiator Amplifier

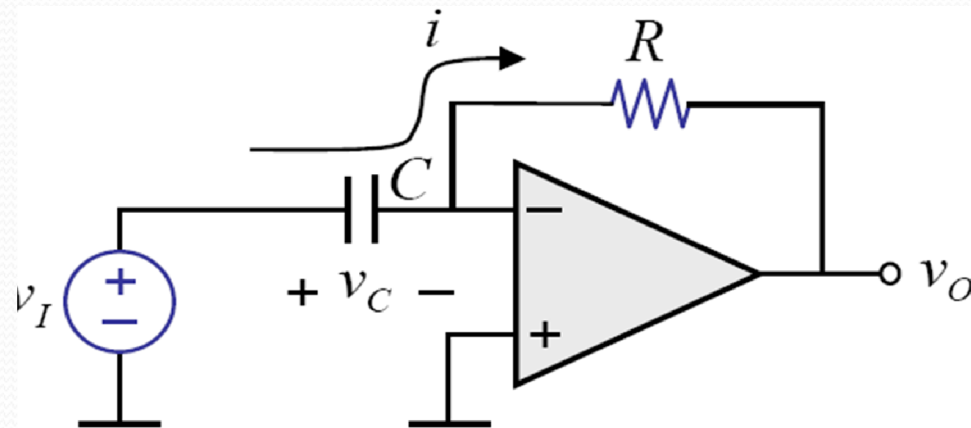

$$V_o = -RC \frac{d}{dt} v_I$$

# 9- The Phase-Shift Oscillator

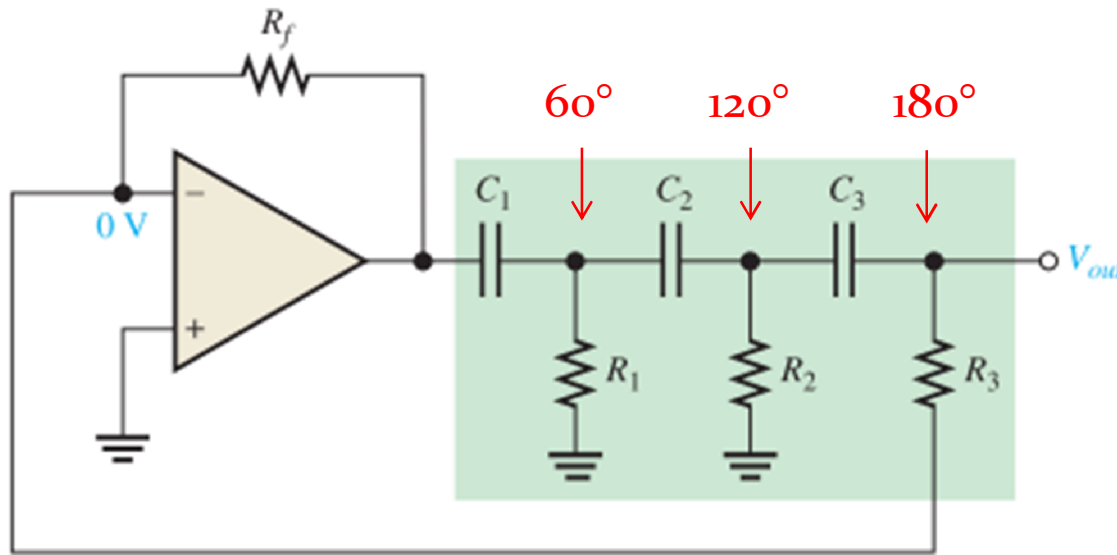

$$B = \frac{1}{29} \quad \text{where } B = R_3/R_f.$$

$$R_1 = R_2 = R_3 = R \text{ and } C_1 = C_2 = C_3 = C. \quad f_r = \frac{1}{2\pi\sqrt{6RC}}$$