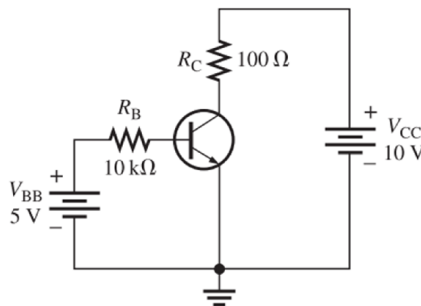



Electronic Engineering

Sheet # 4: Transistors


- 1- Determine I_B , I_C , I_E , V_{BE} , V_{CE} , and V_{CB} in the below circuit. The transistor has a $\beta_{DC} = 150$.



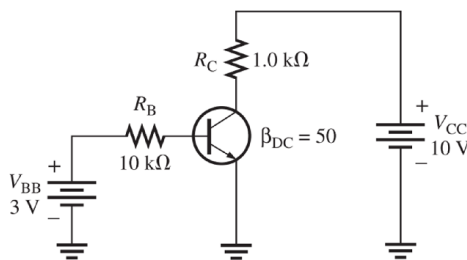- 2- Determine whether or not the transistor in the below figure is in saturation. Assume $V_{CE(sat)} = 0.2 \text{ V}$.




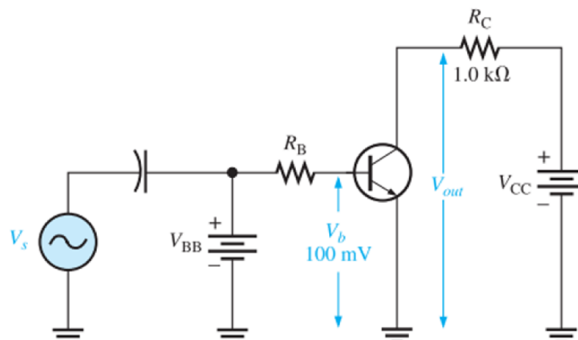- 3- Determine the voltage gain and the ac output voltage in the below figure if $r_{e'} = 50 \text{ ohm}$. Sketch the output voltage waveform.




- 4- For the transistor circuit in the below figure:
a. what is V_{CE} when $V_{IN} = 0 \text{ V}$?

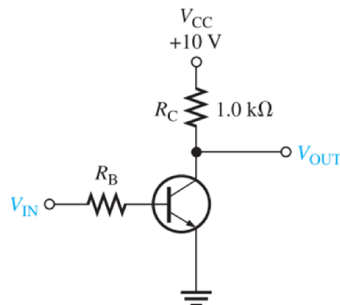
- b. What minimum value of I_B is required to saturate this transistor if β_{DC} is 200? Neglect $V_{CE(sat)}$.
- c. Calculate the maximum value of R_B when $V_{IN} = 5\text{ V}$.



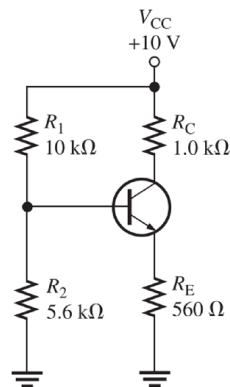- 5- Determine V_{CE} and I_C in the stiff voltage-divider biased transistor circuit in the below figure if $\beta_{DC} = 100$.



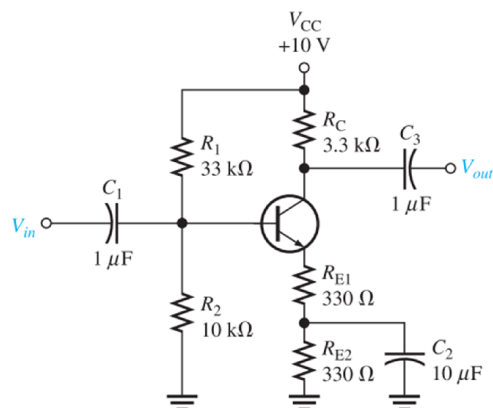- 6- Determine the voltage gain of the swamped amplifier in the below figure. Assume that the bypass capacitor has a negligible reactance for the frequency at which the amplifier is operated. Assume $r_{e'} = 20\text{ ohm}$.



7- A certain cascaded amplifier arrangement has the following voltage gains:
 $A_{v1}=10$, $A_{v2} = 15$, and $A_{v3} = 20$. What is the overall voltage gain? Also express each gain in decibels (dB) and determine the total voltage gain in dB.