

1

المناظرة الأخيرة

1- series RLC (Time Domain)

2- Some examples using Laplace (F-Domain)

Example (1) Series RLC, $R=3000\Omega$, $L=10H$, $C=200\mu F$, connected with DC battery 50v, through "S" switch, closed at $t=0$, with no initial charge.

Solution

using KVL

$$50 = Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

تفاضل (طابقه لو جود تفاضل)

$$0 = R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{1}{C} i$$

$$0 = R \frac{di}{dt} + \frac{d^2i}{dt^2} + \frac{1}{LC} i$$

$$\Rightarrow (D^2 + \frac{R}{L}D + \frac{1}{LC}) i = 0 \rightarrow \text{M.A.S. } -\frac{R}{2L} \pm \sqrt{(\frac{R}{2L})^2 - (\frac{1}{LC})}$$

$$\Rightarrow (D^2 + 300D + 500) i = 0$$

$-298.3 = m_1$ ← $-1.67 = m_2$ ← $\text{ملاصه كذا في المعادلة}$

حسب قيم الجذور m_1, m_2 $\left(\text{وقتها حرجها} \right)$

real & Unequal
(overdamped)
 $(\frac{R}{2L})^2 > \frac{1}{LC}$

$$i = K_1 e^{m_1 t} + K_2 e^{m_2 t}$$

real, equal
critical damping
 $(\frac{R}{2L})^2 = \frac{1}{LC}$

$$i = e^{mt} (C_1 + C_2 t)$$

Complex
Underdamping
 $(\frac{R}{2L})^2 < \frac{1}{LC}$

$$i = e^{-\alpha t} [A_1 \cos \omega t + A_2 \sin \omega t]$$

where

$$\alpha = \frac{R}{2L}$$

ترجع للمعادن

$$m_1 = -298.3 \quad m_2 = -1.67$$

$$i_1 = C_1 e^{-298.3t} + C_2 e^{-1.67t}$$

(1) to find constants

at $t=0$ $i_1=0$ (المعيار الحثي)

$$0 = C_1 + C_2 \rightarrow \textcircled{1}$$

في نفس الوقت نفوض $t=0$ $i=0$ المعيار الحثي قبل التفاعل

(2) نفاضل المعادله (i)

$$\therefore \frac{di}{dt} = -298.3 C_1 e^{-298.3t} + (-1.67) C_2 e^{-1.67t} \rightarrow \textcircled{2}$$

(3) نضع المعادله الاصله قبل التفاعل KVL ونفوضه $t=0$

$$50 = 3000 i + 10 \frac{di}{dt} + \frac{1}{200 \times 10^{-6}} \int i dt$$

$$\therefore 5 = \frac{di}{dt} \rightarrow \textcircled{3}$$

ترجع نفوضه $t=0$ $i=0$ ونفوضه $t=0$ $i=0$

$$5 = -298.3 C_1 e^0 + (-1.67) C_2 e^0$$

$$\textcircled{4} \Rightarrow 5 = -298.3 C_1 - 1.67 C_2$$

$$-0.0168 = C_1 \quad \text{نحل (4) لـ (1) نحصل}$$

$$0.168 = C_2$$

$$\therefore i_1 = 0.0168 e^{-1.67t} - 0.0168 e^{-298.3t}$$

Max Current at $\frac{di}{dt} = 0$

$$\frac{di}{dt} = 0 = (-1.67)(0.0168) e^{-1.67t} - 0.0168 e^{-298.3t}$$

$0.0175 = t$

[2] Laplace

طريقة تستخدم لتحويل المعادلات للدوائر بصورة متفاضلة إلى
 صورة S Domain (Freq.) من خلال تحويل متوازي


[1]
$$i(t) \xrightarrow{\text{تحويل}} I(s)$$

في بقاوه
$$V(t) \xrightarrow{\text{تحويل}} V(s)$$

[2]
$$i(t) \xrightarrow{\text{تحويل}} sI(s) - I(0)$$

في ملف coil
$$V(t) \xrightarrow{\text{تحويل}} V(s) = sLI(s) - LI(0)$$

$$= L \frac{di}{dt} = L(sI(s) - I(0))$$

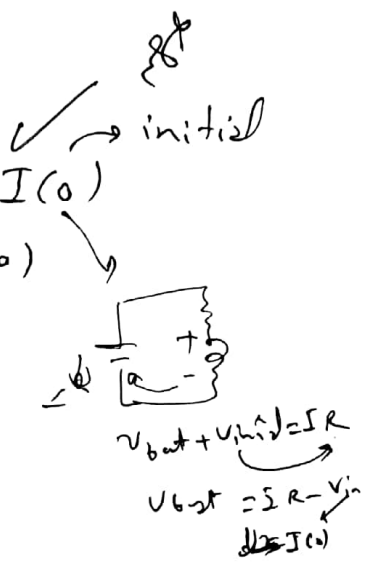

[3]
$$V(t) = \frac{1}{C} \int i dt + V_{\text{initial}}$$

في مكثف capacitor
$$V(s) = \frac{1}{CS} I(s) + \frac{V(0)}{s}$$

مع صفة (كبدون)
$$\text{منه في البداية}$$


- ① $\frac{A}{s} \rightarrow A$
- ② $\frac{A}{s^2} = At$
- ③ $\frac{1}{s+a} = e^{-at}$
- ④ $\frac{1}{(s+a)^2} \rightarrow te^{-at}$
- ⑤ $\frac{\omega}{s^2 + \omega^2} \rightarrow \sin(\omega t)$

- ⑥ $\frac{s}{s^2 + \omega^2} = \cos \omega t$
- ⑦ $\frac{di}{dt} = sI(s) - I(0)$
- ⑧ $\int i dt = \frac{I(s)}{CS} + \frac{V(0)}{s}$

(4)

EX(2) Solve $i(t)$ using Laplace for source $V = 50V$

$$50 = 10i + 0.2 \frac{di}{dt}$$

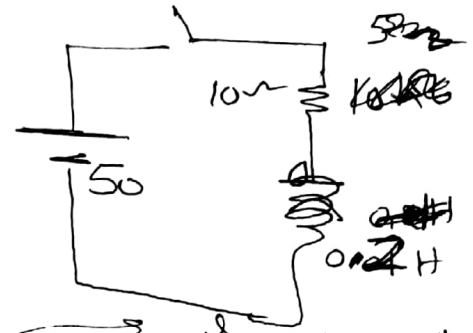

Take Laplace

$$\frac{50}{s} = 10I(s) + 0.2(sI(s) - I(0))$$

at $t=0 \rightarrow i=0$

initial value of current is zero (المعرفة بكونها صفر في البداية)
 مادام مقادير التيارات (مقادير التيارات في البداية)
 (مقادير التيارات في البداية)
 (مقادير التيارات في البداية)

$$\therefore \frac{50}{s} = 10I(s) + 0.2sI(s) = I(s)(10 + 0.2s)$$

$$\therefore I(s) = \frac{50}{s(10 + 0.2s)} = \frac{A}{s} + \frac{B}{10 + 0.2s}$$

$$I(s) = \frac{A(10 + 0.2s) + Bs}{s(10 + 0.2s)} = \frac{10A + s(B + 0.2A)}{s(10 + 0.2s)}$$

$$\therefore 50 = 10A + s(B + 0.2A)$$

$$\therefore 50 = 10A \Rightarrow A = 5$$

$$B + 0.2A = 0 \Rightarrow B = -0.2A = -1$$

$$\therefore I(s) = \frac{5}{s} - \frac{1}{10 + 0.2s} = \frac{5}{s} - \frac{5}{s + 50}$$

فيما يخص 0.2 (مقادير التيارات في البداية)

$$\therefore I(t) = 5 - 5e^{-50t} = 5(1 - e^{-50t})$$

EX(2) 9.5

RL + AC

if supply was $(50 e^{-100t}) \rightarrow AC$

$$50 e^{-100t} = 10 i + 0.2 \frac{di}{dt}$$

$$\frac{50}{s+100} = 10 I(s) + 0.2 (s I(s) - I(0))$$
$$= I(s) [10 + 0.2s]$$

$$I(s) = \frac{50}{(s+100)(10+0.2s)} = \frac{50}{(s+100)(s+50)}$$

$$I(s) = \frac{A}{s+100} + \frac{B}{s+50} = \frac{250}{(s+100)(s+50)}$$

$$\therefore A(s+50) + B(s+100) = 250$$

$$\therefore s(A+B) = 0$$

$$\therefore A = -B$$

$$50A + 100B = 250$$

$$\therefore 50B = 250$$

$$\therefore \begin{cases} B = 5 \\ A = -5 \end{cases}$$


$$\therefore I(s) = \frac{-5}{s+100} + \frac{5}{s+50}$$

$$\therefore i(t) = -5e^{-100t} + 5e^{-50t}$$

7(3)

RC + DC

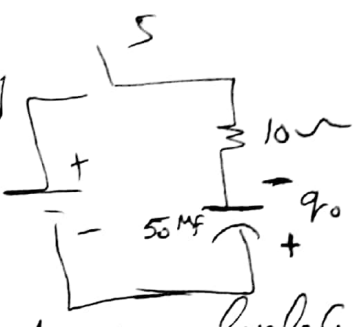in RC series circuit, capacitor is initially charged with $Q = 2500 \mu C$, at $t = 0$ switch closed, a constant supply $100V$ applied to the circuit, Find the current using Laplace.



main

Sol.

$$100 = 10i + \frac{1}{C} \int i dt = 10i + \frac{1}{50 \times 10^{-6}} \int i dt$$

take Laplace

$$\frac{100}{s} = 10 I(s) + \left[\frac{I(s)}{Cs} - \frac{V_{initial}}{s} \right] \rightarrow \frac{Q}{C}$$

المعروف للعرضة ايجابية $V_{initial}$: V_{supply} في $t=0$ ، $V_{initial} = 0$ ، $V_{supply} = 100$.

MF

$$\frac{100}{s} = 10 I(s) + \left[\frac{I(s)}{50 \times 10^{-6} s} \right] - \frac{2500 \times 10^{-6}}{50 \times 10^{-6} s}$$

$$\therefore I(s) = \frac{150}{10s + 2 \times 10^4} = \frac{15}{s + 2 \times 10^3}$$

$$\therefore \mathcal{L}^{-1}(I(s)) = I(t) e^{-2 \times 10^3 t}$$

$$\therefore I(t) = 15 e^{-2 \times 10^3 t}$$



Pin